

# EE109: Introduction to Embedded Systems

## Spring 2021 - Final Exam

### 5/8/21, 2PM – 3:40PM + 20 min to upload

[Complete all the information in the box below.]

**<No Need to Fill this out due to Gradescope>**

Name: \_\_\_\_\_

Student ID: \_\_\_\_\_

Email: \_\_\_\_\_@usc.edu

**Lecture section (Circle One):**

Redekopp	Redekopp	Weber	Qian
9:30 a.m.	11 a.m.	12:30 p.m.	2 p.m.

**Calculators ARE allowed.**

Page	Ques.	Your score	Max score	Recommended Time
			0	0 min.
	1		8	8 min.
	2		12	10 min.
	3		10	12 min.
	4		12	13 min.
	5		10	15 min.
	6		10	12 min.
	7		12	15 min.
	8		8	15 min.
	<b>Total</b>		82	100 min.
		Scan/Upload		20 min.

1. **Multiple Choice / Short answer (8 pts.):** Answer the questions below.

1.1 An \_\_\_\_\_ (**ASIC / FPGA**) cannot be reconfigured and is fixed once fabricated.

1.2 A state machine with 4 flip-flops can implement a state machine with a maximum of \_\_\_\_\_ (**2 / 4 / 8 / 16**) states.

1.3 **True / False** \_\_\_\_ Caching breaks logic into multiple stages to overlap their execution.

1.4 Having completed the labs of EE 109, a student should know NOT to:

- a.) Use volatile variables in an ISR
- b.) Use 'float' and 'double' types if it can be avoided
- c.) Use global variables in embedded programs
- d.) Use nested if statements to implement a state machine

1.5 To ensure devices correctly interpret the **timing** of bits sent over an asynchronous RS-232 connection, both devices must use a common

- a.) Ground signal
- b.) Baud rate
- c.) Prescaler

1.6 An edge-triggered D flip-flop can be built from how many level-sensitive D-Latches?


- a.) 1
- b.) 2
- c.) A D flip-flop cannot be built from level-sensitive D-Latches

1.7 A low-resistance ( $R=0$ ) pathway between two points with a voltage difference is referred to as a(n) \_\_\_\_\_ (**short / open / high-impedance**) circuit.

1.8 To make a signal a digital output on the Arduino, set the appropriate bit of the \_\_\_\_\_ (general name of the) register to a \_\_\_\_\_ ( 1 / 0 ).

- a.) DDR / 0
- b.) PORT / 0
- c.) DDR / 1
- d.) PORT / 1

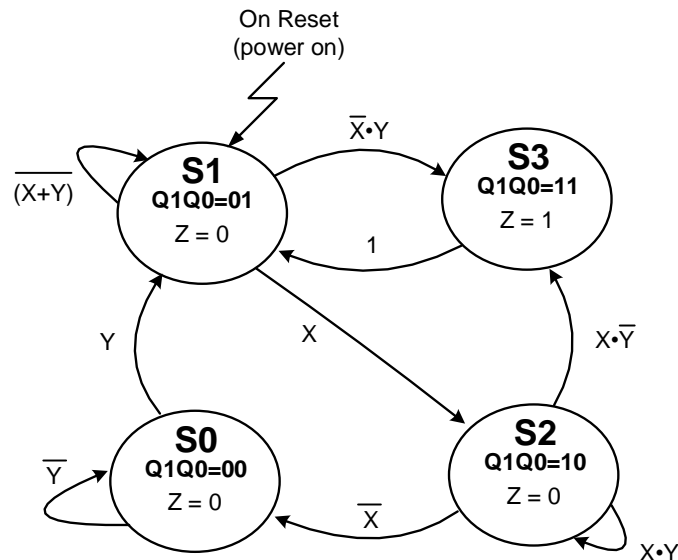2. **State Machines I (12 pts.):** Consider the completed state diagram shown below to answer the questions below.




- a.) Complete the state transition table by filling in the next state columns and the output column in the table below.

Current State		Next State				Output
		$X Y = 0 0$ State*	$X Y = 0 1$ State*	$X Y = 1 0$ State*	$X Y = 1 1$ State*	
State	Q1 Q0					Z
S0	0 0	S__	S__	S__	S__	__
S1	0 1	S__	S__	S__	S__	__
S2	1 0	S__	S__	S__	S__	__
S3	1 1	S__	S__	S__	S__	__

- b.) To implement the reset condition, what should be connected to the following flip flop inputs?


- i.) The **SET of the Q0 flip-flop** should be connected to:
- RESET
  - $\sim$ RESET
  - 0 (GND)
  - 1 (Vdd)
- ii.) The **CLR of the Q0 flip-flop** should be connected to:
- RESET
  - $\sim$ RESET
  - 0 (GND)
  - 1 (Vdd)
- iii.) The **SET of the Q1 flip-flop** should be connected to:
- RESET
  - $\sim$ RESET
  - 0 (GND)
  - 1 (Vdd)
- iv.) The **CLR of the Q1 flip-flop** should be connected to:
- RESET
  - $\sim$ RESET
  - 0 (GND)
  - 1 (Vdd)

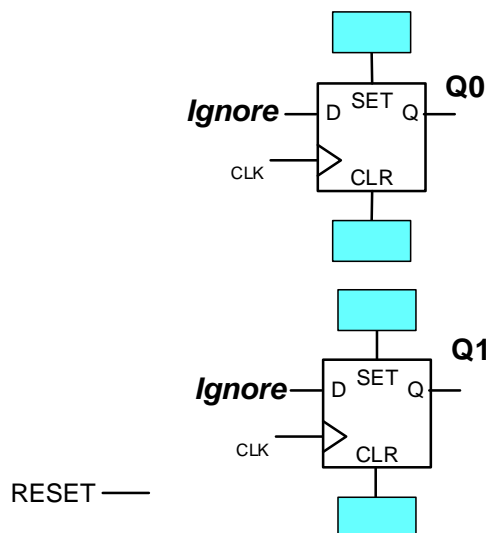

3. **State Machines II (10 pts).** You are given a state machine with 1 flip-flop, **Q**, and two inputs: **J** and **K** and two states: S0 and S1 whose desired behavior is shown in the table below. Answer the following questions.

Current State		Next State								Output
State	Q	J K = 0 0		J K = 0 1		J K = 1 0		J K = 1 1		Z
		State*	Q*	State*	Q*	State*	Q*	State*	Q*	
S0	0	S0	0	S0	0	S1	1	S0	0	1
S1	1	S0	0	S0	0	S1	1	S1	1	0

- a.) Use the state table above to complete the corresponding state diagram (**fill in/draw all the correct state transitions** and be sure to label them correctly based on the table). For each transition you must arrive at a minimal SOP expression (i.e. combine multiple transitions to the same state to form a single, minimal SOP expression for the transition condition). **Fill in the Z output values** for each state.

 


- b.) Find a **minimal, POS** equation for D (input to the **single** flip-flop, Q) and a **minimal equation** (SOP or POS) for Z. **Show your work below** (to get full credit) and put your final answer in the blanks below.

D (minimal **POS**) = \_\_\_\_\_

Z = \_\_\_\_\_

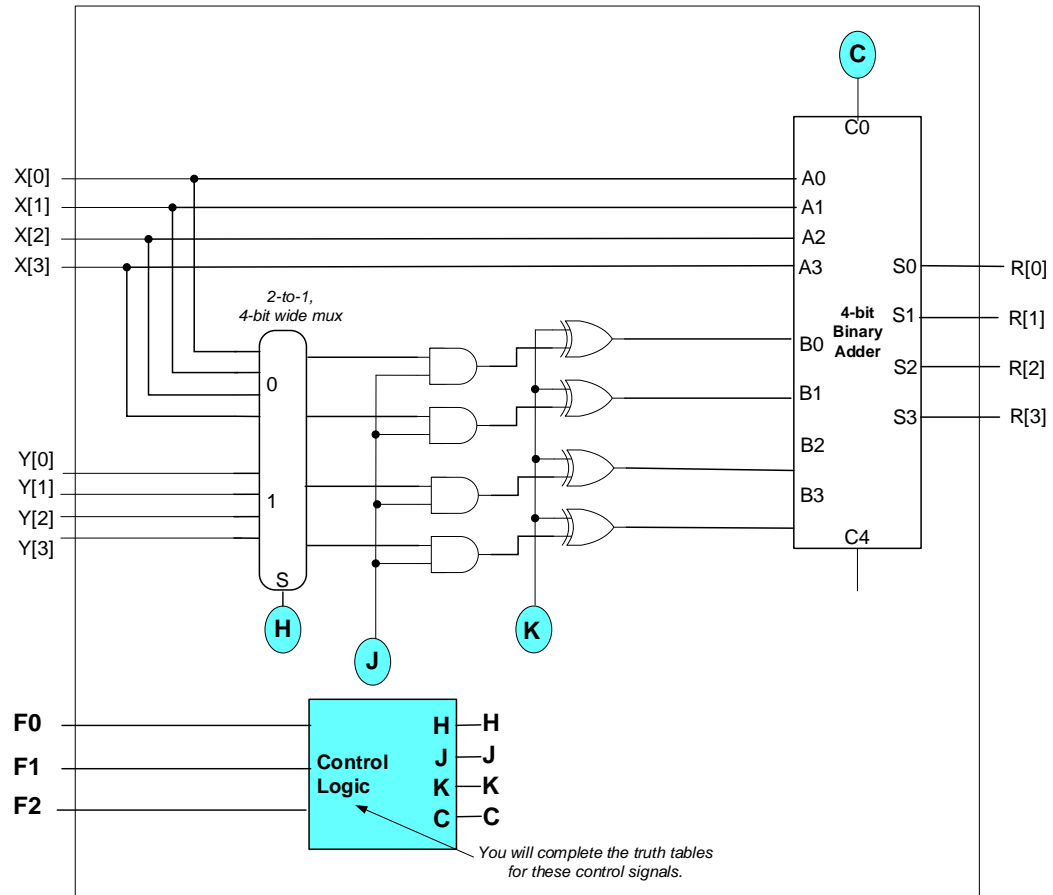4. **Datapath Design I (10 pts.):** Consider the datapath below with the accompanying table showing the correspondence of the function select bits **F[2:0]** to the **resulting arithmetic operation performed to produce the output R[3:0]**. **Complete the table** for the control signals: H, J, K, C to achieve the desired operations. Finally, find the logic for (only) the signals, **H** and **K**. All input and output numbers are 2's complement numbers. Do not worry about overflow.



Complete the table for the values of H, J, K, and C. Use d for don't care where appropriate.

F2	F1	F0	H	J	K	C	Desired Arithmetic Operation (resulting output for R[3:0])
0	x	x					$X[3:0] + 1$
1	0	0					$X[3:0] - 1$
1	0	1					$X[3:0] - Y[3:0]$
1	1	0					$X[3:0] + Y[3:0]$
1	1	1					$2 * X[3:0]$

What is the minimal SOP logic for H : \_\_\_\_\_

What is the minimal SOP logic for K : \_\_\_\_\_

5. **Adder Design (10 pts.):** You are given a **3-bit unsigned** number,  $W[2:0]$ , and three **single bit** unsigned inputs:  $X$ ,  $Y$ , and  $Z$ . Design a circuit that generates a **2's complement system** output  $F = W - X - Y - Z$ .

- a. **Complete the statement to make it true:**



The output values for  $F$  can range from \_\_\_\_\_ decimal to \_\_\_\_\_ decimal.

- b. **Complete the statement to make it true:**

To represent the range of  $F$  you found above requires \_\_\_\_\_ (how many) bits.

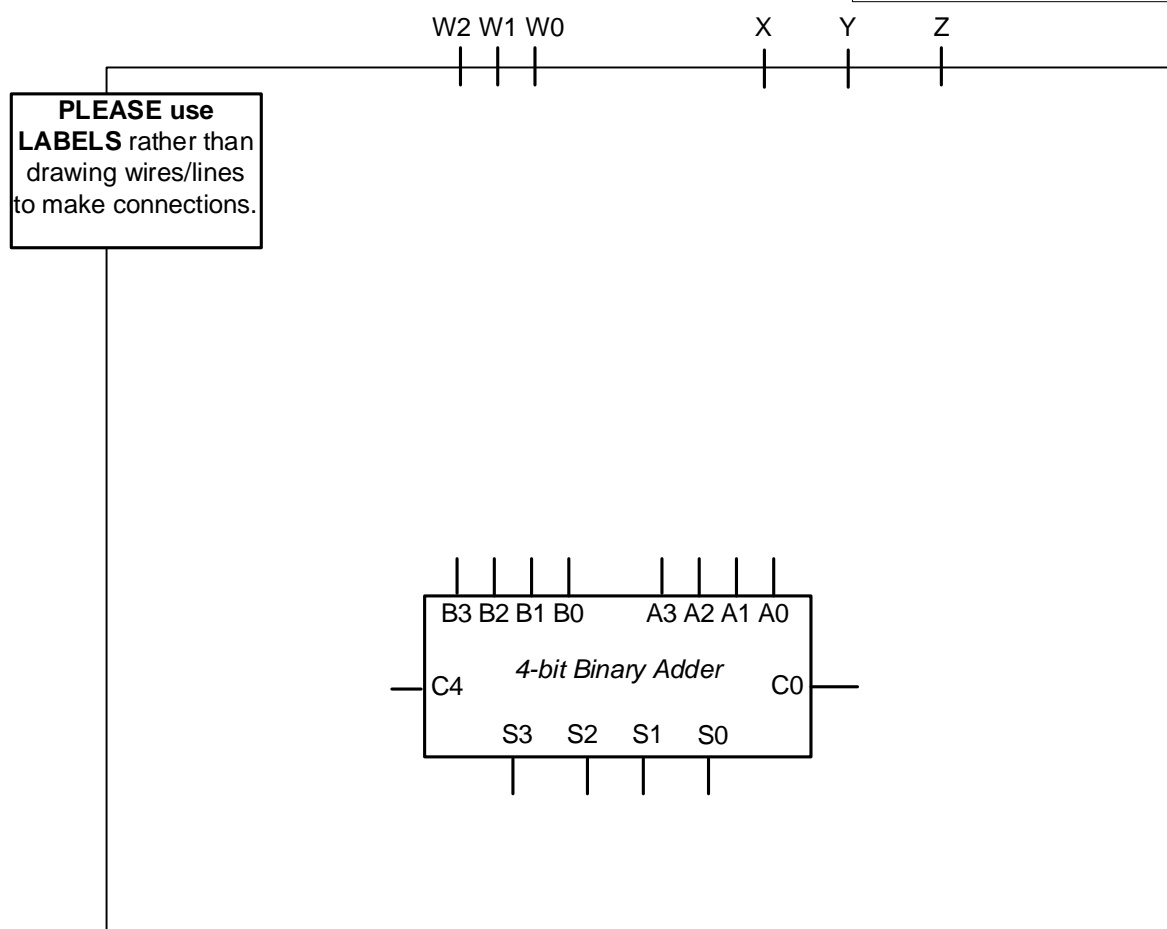 
- c. **Design** the circuit to generate the appropriate number of outputs for  $F$  using a single 4-bit adder and a **minimal number** of full and half adders along with simple AND, OR, NOT gates. [Hint:  $W - X - Y - Z = W - (X + Y + Z)$  ]

*Feel free to add/use a minimal number of additional full and half adders such as these*




*Show and clearly label the appropriate number of  $F$  output bits here ( $F_0$  should be the LSB)*

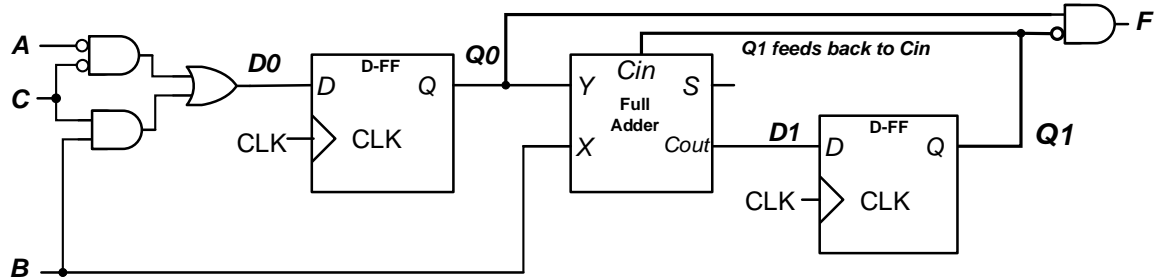6. **FPGAs/Memories Design (10 pts.):** Consider the circuit shown below. Show how to implement the design using the two 3-input, 2-output CLBs below by determining the contents of the 8x2 memory and the mux selects. If necessary, place a **dash ('-')** in any memory cell (bit place) that is a don't care.





 *Circuit to be implemented using the CLB's below*



 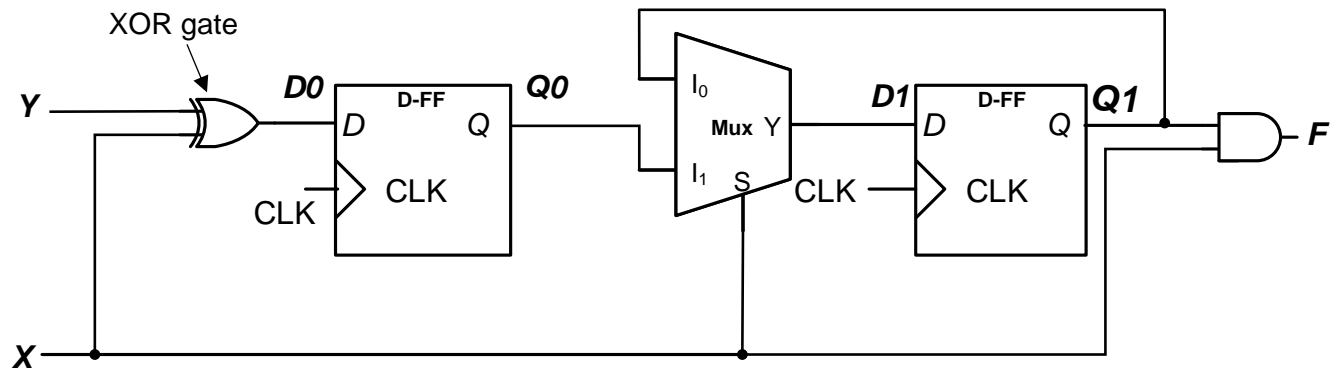
7. **Sequential Logic (12 pts.):** Complete the waveform diagram below for D0, Q0, D1, Q1 and F. Assume the D flip-flops shown below are **positive-edge triggered**. **Q0 starts at 1 and Q1 starts at 0.** (You can determine the **starting** value of D0, D1, and F from the given information.)

Hint: You can find the waveforms for D0 and Q0 using only the left half of the circuit and then use those results to find D1, Q1, and F.





 8. **Interrupts and Arduino Coding (8 pts.)** Your Arduino needs to output the two periodic signals shown below (which only show a few cycles of the desired pattern which continue indefinitely) on Port D, bit 2 (PD2) and Port D, bit 3 (PD3). The signal on PD2 has a period of 30ms and duty cycle of 33.3% (high for 10ms, low for 20ms). The signal on 3 has a period of 40ms and duty cycle of 50% (high for 20ms, low for 20ms).



You must use the 16-bit TIMER1 to produce both signals. **You may not use any delay functions to produce the output.** Determine the prescaler and counter modulus value (max count) to store in the OCR1A register, and write the ISR (TIMER1\_COMPA\_vect) that will generate the desired signals. If multiple pairs of prescaler and modulus values will work, use ones that give the more accurate timing. **Note:** The Arduino system clock is 16MHz. (note: 1 millisecond (ms) =  $10^{-3}$  seconds, 1 microsecond ( $\mu$ s) =  $10^{-6}$  seconds)

**Complete your answers in the linked sp21-fi-isr.c file and then upload the completed file to Gradescope. The contents are reproduced below.**

```
// Indicate what prescaler you choose by deleting the options you don't
// want then write your chosen OCR value below.
// ----- FILL IN THE 2 LINES BELOW -----
// Prescaler: 1 / 8 / 64 / 256 / 1024
// OCR1A: _____

// Assume the outputs have been initialized and set to output a '1', the
// TIMER1 is initialized correctly with the values you chose above, and
// that interrupts have been enabled so that the ISR below is called each time
// TIMER1 reaches your OCR1A value.
// ----- COMPLETE THE CODE BELOW -----
// declare any needed global variables here
```

```
ISR(TIMER1_COMPA_vect)
{ // show ISR code here..NO delay functions are allowed (losing all credit)

}
}
```

**Intentionally blank for scratch work. You may detach it but please turn it in with your exam:**

Name: \_\_\_\_\_ Section time: \_\_\_\_\_

***Single-Variable Theorems***

(T1)	$X + 0 = X$	(T1')	$X \cdot 1 = X$	(Identities)
(T2)	$X + 1 = 1$	(T2')	$X \cdot 0 = 0$	(Null elements)
(T3)	$X + X = X$	(T3')	$X \cdot X = X$	(Idempotency)
(T4)	$(X')' = X$			(Involution)
(T5)	$X + X' = 1$	(T5')	$X \cdot X' = 0$	(Complement)

***Two- and Three-Variable Theorems***

(T6)	$X + Y = Y + X$	(T6')	$X \cdot Y = Y \cdot X$	(Commutativity)
(T7)	$(X + Y) + Z = X + (Y + Z)$	(T7')	$(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$	(Associativity)
(T8)	$X \cdot (Y + Z) = X \cdot Y + X \cdot Z$	(T8')	$X + (Y \cdot Z) = (X + Y) \cdot (X + Z)$	(Distributivity)
(T9)	$X + X \cdot Y = X$	(T9')	$X \cdot (X + Y) = X$	(Covering)
(T10)	$X \cdot Y + X \cdot Y' = X$	(T10')	$(X + Y) \cdot (X + Y') = X$	(Combining)
(T11)	$X \cdot Y + X' \cdot Z + Y \cdot Z =$ $X \cdot Y + X' \cdot Z$	(T11')	$(X + Y) \cdot (X' + Z) \cdot (Y + Z) =$ $(X + Y) \cdot (X' + Z)$	(Consensus)

***DeMorgan's Theorem***

$(X \cdot Y)' = X' + Y'$	$(X + Y)' = X' \cdot Y'$	(DeMorgan's)
--------------------------	--------------------------	--------------