

EE109: Introduction to Embedded Systems

Spring 2023 - Midterm Exam

3/7/23, 7PM – 8:40PM

[Complete all the information in the box below.]

Name: _____

Student ID: _____

Email: _____@usc.edu

Lecture section (Circle One):

Redekopp	Redekopp	Weber	Puvvada
9:30 a.m.	11 a.m.	12:30 p.m.	2 p.m.

Ques.	Your score	Max score	Recommended Time
-		-	0 min.
1		6.5	6 min.
2		2	2 min.
3		4.5	5 min.
4		7	10 min.
5		8	10 min.
6		12	15 min.
7		10	15 min.
8		8	12 min.
9		17	25 min.
Total		75	

All work MUST be on these EXAM PAGES. No Scratch work will be graded or viewed.

1. (6.5 pts) Number Systems


1.1. Convert **153** decimal to an 8-bit unsigned binary number: _____

1.2. Convert **1000111011101.110** binary to hexadecimal: _____

1.3. Using a **6-bit code** to represent colors would allow for how many unique colors to be represented: _____

 2. (2 pts.) Mux Behavior

The circuit to the right can be equivalently replaced with a single 2-input logic gate (e.g. **NAND, OR, XOR...**) with inputs: {X,Y} and output F. Identify that gate:



Equivalent gate type: _____

3. (4.5 pts.) Decoder Behavior

Consider the three circuits below. Indicate which ones form a valid 1-to-2 decoder **with** enable. Hint: Use your knowledge of a decoder but apply DeMorgan's theorem to manipulate the circuits and verify if they do indeed implement a **valid** 1-to-2 decoder. (Circle the correct option for each circuit).

Valid / Invalid	Valid / Invalid	Valid / Invalid

4. (7 pts.) Analog Circuits


Consider the resistive circuit to the right and answer the following questions.

4.1. When SW1 and SW2 **open**, what is **V1**? _____ V

4.2. When SW1 is **open** and SW2 **closed**, what is the **equivalent resistance** of all the resistors? _____ ohms

4.3. When SW1 AND SW2 are **closed**, what is the **equivalent resistance** of ALL the resistors and what is **the current, i1**,?

_____ ohms $i1 =$ _____ A

 

5. (8 pts.) Logic Simplification

Billy Bruin arrived at what he believes is a **minimal, POS equation** for a function, F, that he desired to implement. The equation he found was:

$$F(w, x, y, z) = (w + x + \bar{y} + z)(\bar{x} + z)(\bar{w} + z)$$

To prove or disprove that Billy Bruin's equation truly is a minimal, POS implementation, **construct a Karnaugh map in the area below** using the equation above to fill in the values. Then **group** and **translate** to show the minimal, **POS** equation yielded by your Karnaugh Map and show your answer in the blank below to see if it agrees with the equation Billy found.

5.1. Construct, group and translate a Karnaugh map for the given equation in the space below.


5.2. Minimal POS equation for F that you found:

F = _____

 6. (12 pts.) Logic Function Design

Consider a circuit which takes as input a **1-bit** value **A**, and a **3-bit unsigned** input **B[2:0]** (i.e. B2,B1,B0). The output of the circuit should be an **unsigned** value, **Z** given by the description below. Then use the K-maps to find the specified minimal expressions.

if (A is 0) then Z = B[2:0] else if (A is 1 and B[2:0] < 3) then Z = 2*B[2:0] + 1 else Z = B[2:0] - 3



Note: If you consider the above description, a negative result is NOT possible.

Ex. 1: if A = 1 and B = 010 (2 decimal) then because A is 1 and $B < 3$, $Z = 2*2 + 1 = 5$ dec.

Ex. 2: if A = 1 and B = 110 (6 decimal) then because A is 1 and $B \nless 3$, $Z = 6 - 3 = 3$ dec.

6.1. What is the minimum number of output bits needed for Z? _____

6.2. Complete the truth table for this circuit showing the Z output bits .

6.3. Use the Karnaugh maps to find the minimal **SOP expression for Z0** and minimal **POS expression for Z1**. You do not have to implement any other bits of Z.

A	B2	B1	B0	Z1	Z0
0	0	0	0		0
0	0	0	1		1
0	0	1	0		0
0	0	1	1		1
0	1	0	0		0
0	1	0	1		1
0	1	1	0		0
0	1	1	1		1
1	0	0	0		1
1	0	0	1		1
1	0	1	0		1
1	0	1	1		0
1	1	0	0		1
1	1	0	1		0
1	1	1	0		1
1	1	1	1		0

		A B2				
		00	01	11	10	
B1B0	00	0	4	12	8	Kmap for Z0,SOP
	01	1	5	13	9	
	11	3	7	15	11	
	10	2	6	14	10	

		A B2				
		00	01	11	10	
B1B0	00	0	4	12	8	Kmap for Z1,POS
	01	1	5	13	9	
	11	3	7	15	11	
	10	2	6	14	10	

Fill in the minimal **SOP** expression for Z0.


Z0 **minimal,SOP** = _____

Fill in the minimal **POS** expression for Z1.

Z1 **minimal,POS** = _____

8. (8 pts.) **Tree Muxes.** – Suppose you are given **8 data inputs: A-H** that correspond to the select combinations shown in the table below. Now suppose we **ONLY** want to design a **5-to-1 mux** to select and pass a **subset of 5 of the 8 input using the select bits MS2, MS1, MS0**. Billy Bruin's initial attempt to design the 5-to-1 mux is shown. However, Billy was unsure what to connect to some of the inputs and, instead, used placeholder variables: **x1-x4**. Assuming Billy's design follows the specification of input / select combinations in the table below and **can output 5 UNIQUE** inputs from the set A-H, help Billy by answering the following questions.

MS2	MS1	MS0	Y
0	0	0	A
0	0	1	B
0	1	0	C
0	1	1	D
1	0	0	E
1	0	1	F
1	1	0	G
1	1	1	H

 

- 8.1. Whenever **MS1** is **0**, the select bit that will pass/connect to S0 input of the 4-to-1 mux is (circle the correct answer):

MS2 / MS0

- 8.2. What input(s) (or subset of inputs if many are possible), **A-H**, could correctly be connected to the input labelled **x1** (circle all that are possible):

x1: **A B C D E F G H**


- 8.3. What inputs (from the options **A-H, MS2, MS1, and MS0**) **MUST** be connected to **x2, x3, and x4**.

x2=_____ x3=_____ x4=_____

- 8.4. Because of where Billy has connected **C** and **H** to inputs 2 and 3 of the 4-to-1 mux, which **two** inputs listed below cannot be connected anywhere. Or said differently, which **two** inputs could never be selected and passed to the output of the mux.

(Circle two): **A B D E F G**

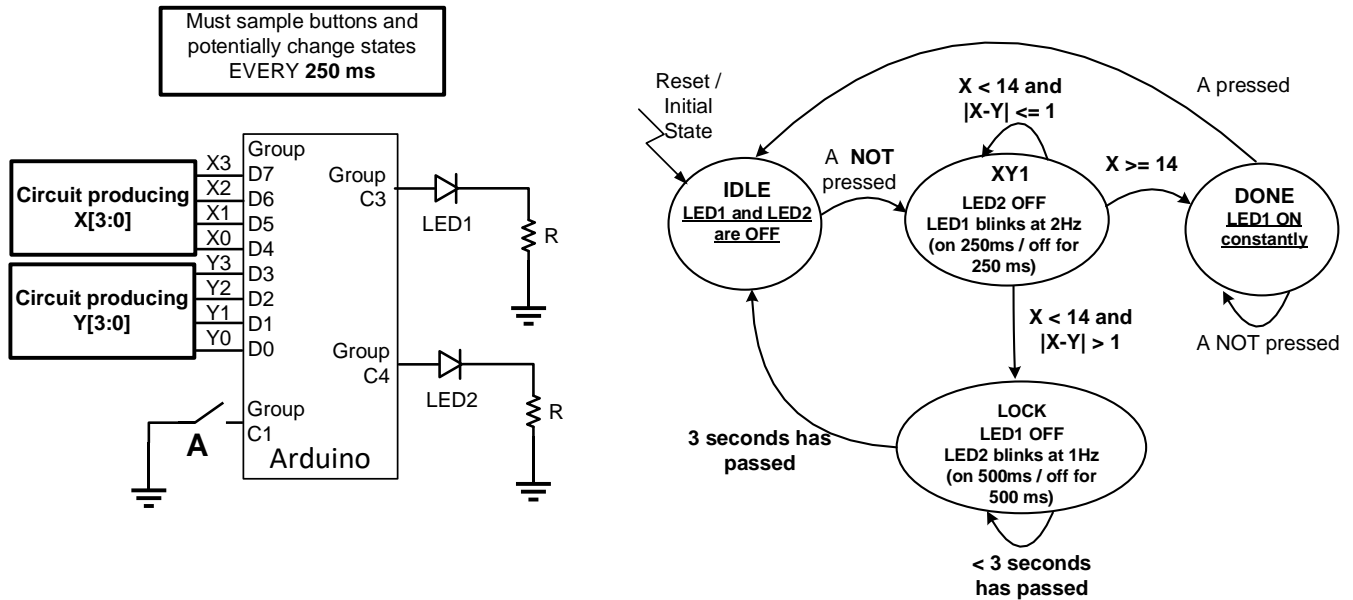9. (17 pts) **State Machines** - Complete the implementation of Arduino code (on this and the following page) to implement the following behavior which will require the use of state. Two circuits produce 4-bit unsigned numbers: $X[3:0]$ and $Y[3:0]$ and are connected to group **D** as shown below. A button: **A** (on group **C**, bit **1**) is connected as shown below. Two LEDs are connected: **LED1** is connected to group **C**, bit **3** and **LED2** to group **C**, bit **4**. The state should transition based on the values of the 4-bit numbers X and Y as well as the button A as shown in the state diagram below. The buttons **MUST** be sampled (and state updated) **every 250 ms**. The LEDs should be off, blink, or be on as described in the state diagram.



- You should NOT add any other delay statements (delay_ms()) to the code.
- You may not change the structure or values of the code provided in the skeleton.
- You need not worry about debouncing.

Assume the following #includes and declarations should you want to use them.

```

1 #include <avr/io.h>
2 #include <util/delay.h> // allows for _delay_ms() function
3 #include <stdlib.h> // allows abs() - absolute value
4
5 const int A = 1; LED1 = 3, LED2 = 4;
6 enum {IDLE, XY1, DONE, LOCK};
7

```

```

8 int main() {
9     char state = IDLE, cnt; // state variable and 3 sec. count
10    /* Other necessary initialization code */
...
11    while(1) { // this is the only loop allowed
12        _delay_ms(250); /* this is the ONLY delay statement allowed */
13        char a = ( _____ & _____ ); // sample the A button input
14
15        // combined next state and output logic
16        if( state == IDLE ) {
17            _____; // appropriate output action
18            if( _____ ) { state = XY1; }
19        }
20        else if (state == XY1) {
21            unsigned char inp = PIND;
22            // extract 4-bits of x and y as separate numbers that can be compared
23            char y = (inp & 0x_____);
24            char x = _____;
25            if(x >= 14){
26                state = DONE;
27            }
28            else if(abs(x-y) > 1){
29                state = LOCK;
30                cnt = ____;
31            }
32            else {
33                PORTC ___ = (1 << LED1); // Enter operator to flip/toggle LED1
34            }
35        }
36        else if(state == DONE) {
37            _____;
38            if( _____ ) { state = IDLE; }
39        }
40        else {
41            PORTC _____; // Clear the appropriate LED
42            cnt++;
43            if( (cnt % _____) == _____ )
44                { PORTC ___ = (1 << LED2); } // Enter operator to flip/toggle LED2
45            if(cnt == _____){
46                state = IDLE;
47            }
48        }
49    } /* end while */
50    return 0;
51 } /* end main */

```