

Unit 14

State Machine Design

Outcomes

- I can create a state diagram to solve a sequential problem
- I can implement a working state machine given a state diagram


STATE MACHINES OVERVIEW

State Machines

- (Finite) state machines or (FSMs) provide the “brains” or control for electronic and electro-mechanical systems
- We've implemented state machines in software, now let's see how we can build them in hardware
- We use the state to help us know which step of an algorithm we are currently at
- **Goal is to generate output values at _____**
 - **When you need time dependent outputs, you can use an FSM**
- FSMs require _____ and _____ logic elements
 - Sequential Logic to remember what step (state) we're in
 - Encodes everything that has happened in the past
 - Combinational Logic to produce outputs and find what state to go to next
 - Generates outputs based on what state we're in and the input values

State Machine Example

 - Design a sequence detector to check for the combination "101"
- Input, X, provides 1-bit per clock
- Check the sequence of X for "101" in successive clocks
- If "101" detected, output Z=1 (Z=0 all other times)



Another State Diagram Example

- "101" Sequence Detector should output F=1 when the sequence 101 is found in consecutive order




State Diagram for "101" Sequence Detector

See the end of this slide set for more detailed solutions and explanations.


Correct Specification of State Diagrams

 - For HW especially, it is critical that **exactly one transition from a state may be true at a time**
 - We can't go _____ at once and if we don't tell it explicitly where to go next, it may go to any random state
 - If you want to stay in a state, include an explicit _____ arrow
 - On the 2nd example if you want to stay in Q1, include a loopback labeled X=0



Correct Specification of State Diagrams 2

 - **Exactly one transition from a state may be true at a time**
 - Make sure the conditions you associate with the arrows coming out of a state are _____ (< 2 true) but all inclusive (> 0 true)




ALWAYS double check your transitions to ensure they are mutually exclusive.

State Machines


- The HW for a state machines can be broken into 3 sections of logic
 - State Memory (SM)
 - Just FF's to remember the _____
 - _____ Logic (NSL)
 - Combo logic to determine the next state
 - Essentially implements the transition conditions
 - _____ Logic (OFL)
 - Combo logic to produce the outputs

State Machine

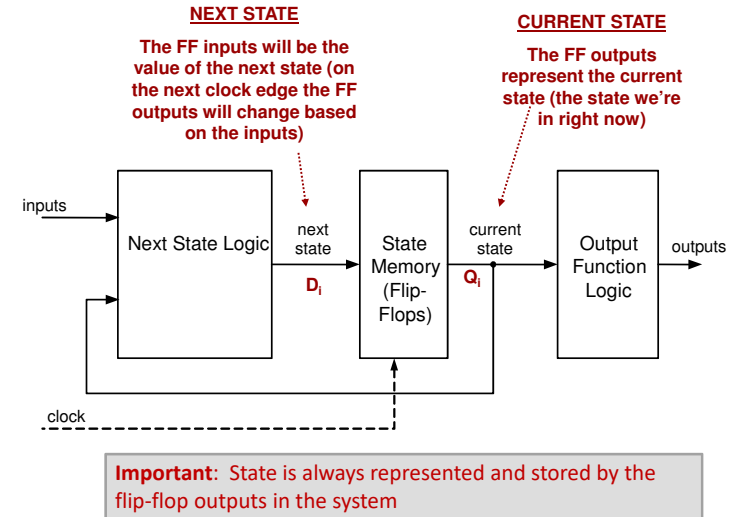

State Machines

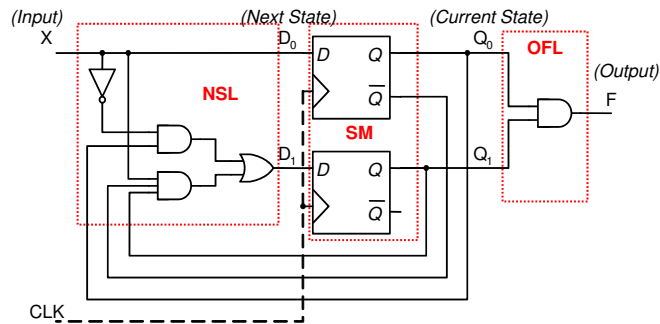- Below is a circuit implementing a state machine, notice how it breaks into the 3 sections




STATE MACHINE DESIGN

State Diagram vs. State Machine

State Diagrams

 1. States
2. Transition Conditions
3. Outputs


State Machines require sequential logic to remember the current state (w/ just combo logic we could only look at the current value of X, but now we can take 4 separate actions when X=0)



State Diagram for "101" Sequence Detector

State Machine

 1. State Memory => FF's
 - n-FF's => 2ⁿ states
2. Next State Logic (NSL)
 - combinational logic
 - logic for FF inputs
3. Output Function Logic (OFL)
 - MOORE: f(state)
 - MEALY: f(state + inputs)



State Machine Design

- State machine design involves taking a problem description and coming up with a state diagram and then designing a circuit to implement that operation



State Machine Design


- Coming up with a state diagram is non-trivial
- Requires creative solutions
- Designing the circuit from the state diagram is done according to a simple set of steps
- To come up w/ a state diagram to solve a problem
 - Write out an algorithm or _____ to solve the problem
 - Each step in your algorithm will usually be _____ in your state diagram
 - Ask yourself what past inputs need to be _____ and that will usually lead to a state representation

EXAMPLE 1

Alternating Detector


- Given bits coming in from a sensor, design a system that outputs true if the previous 2 input bits alternate (are the same) or false if the same bit value is detected in that past two clock cycles

 – What do you need to remember? The _____ bits.



Alternating Detector

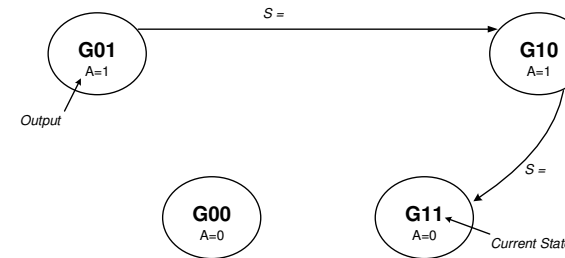- Design a state machine to check if sensor produces two 0's in a row (i.e. 2 consecutive spaces) or two 1's in a row (i.e. 2 consecutive teeth)




- G10 = Last cycle we got 1, two cycles ago we got 0
- G01 = Last cycle we got 0, two cycles ago we got 1
- G11 = Got 2 consecutive 1's
- G00 = Got 2 consecutive 0's

6 Steps of State Machine Design

- State Diagram
- Transition/Output Table
- State Assignment
 - Determine the # of FF's required
 - Assign binary codes to replace symbolic names
- Excitation Table (Rename Q* to D)
- K-Maps for NSL and OFL
 - One K-Map for every FF input
 - One K-Map for every output of OFL
- Draw out the circuit

Transition Output Table

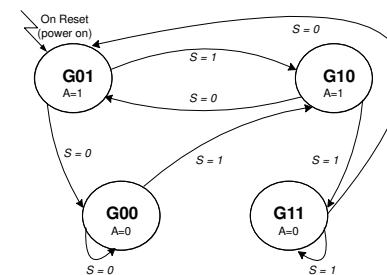
- Convert state diagram to transition/output table
 - Show Next State & Output as a function of Current State and Input



Current State	Input (S)	Next State	Output (A)
G01	0		1
G01	1		1
G11	0		0
G11	1		0
G00	0		0
G00	1		0
G10	0		1
G10	1		1

Transition Output Table

 - Now assign binary codes to represent states



State Assignment Mapping


State	Q ₁	Q ₀
G01	0	0
G11	0	1
G00	1	0
G10	1	1

Current State		Input S	Next State		Output A
Q ₁	Q ₀		Q ₁ *	Q ₀ *	
0	0	0	1	0	1
0	0	1	1	1	1
0	1	0	0	0	0
0	1	1	0	1	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	1	0	1	1

Transition Output Table

- Convert state diagram to transition/output table


Current State			Next State						Output A
			S = 0			S = 1			
State	Q ₁	Q ₀	State			State			
G01	0	0	G00	1	0	G10	1	1	1
G11	0	1	G01	0	0	G11	0	1	0
G10	1	1	G01	0	0	G11	0	1	1
G00	1	0	G00	1	0	G10	1	1	0

 

Here we have redrawn the 8 row table from the previous slide into 4 rows & 2 columns. We've also separated the output A since it doesn't depend on S but only Q₁ and Q₀


Excitation Table

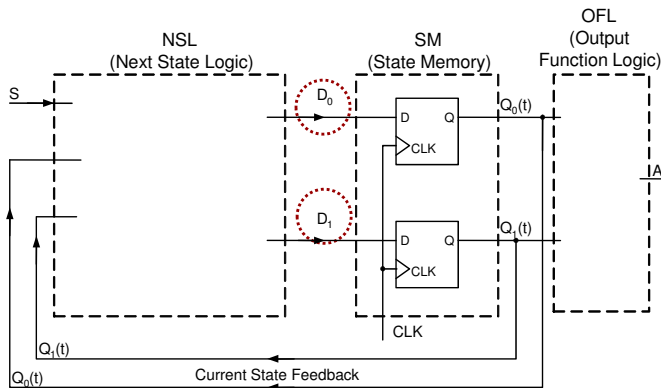- The goal is to produce logic for the inputs to the FF's (D₁, D₀)...these are the excitation equations



Excitation Table

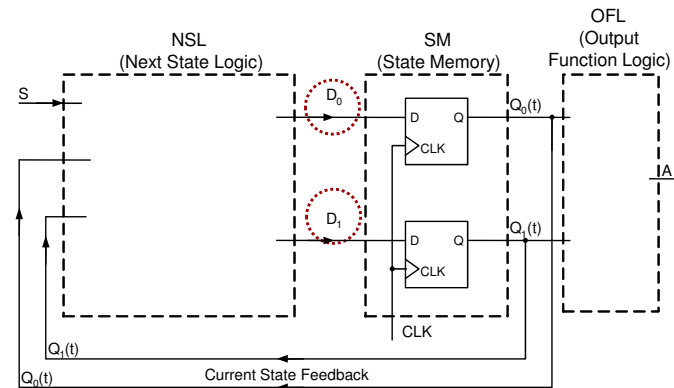- Using your transition table you know what you want Q* to be, but how can you make that happen?
- For D-FF's Q* will be whatever _____



Excitation Table

- In a D-FF Q^* will be whatever D is, so if we know what we want Q^* to be just make sure that's what the D input is

Current State			Next State						Output
			S = 0			S = 1			
State	Q_1	Q_0	State	D_1	D_0	State	D_1	D_0	A
G01	0	0	G00	1	0	G10	1	1	1
G11	0	1	G01	0	0	G11	0	1	0
G10	1	1	G01	0	0	G11	0	1	1
G00	1	0	G00	1	0	G10	1	1	0

Karnaugh Maps

- Now need to perform K-Maps for D_1 , D_0 , and A

Current State			Next State						Output
			S = 0			S = 1			
State	Q_1	Q_0	State	D_1	D_0	State	D_1	D_0	A
G01	0	0	G00	1	0	G10	1	1	1
G11	0	1	G01	0	0	G11	0	1	0
G10	1	1	G01	0	0	G11	0	1	1
G00	1	0	G00	1	0	G10	1	1	0

		S	
		0	1
Q1Q0	00		
	01		
	11		
	10		

D1 =

Karnaugh Maps

- Now need to perform K-Maps for D_1 , D_0 , and A

Current State			Next State						Output
			S = 0			S = 1			
State	Q_1	Q_0	State	D_1	D_0	State	D_1	D_0	A
G01	0	0	G00	1	0	G10	1	1	1
G11	0	1	G01	0	0	G11	0	1	0
G10	1	1	G01	0	0	G11	0	1	1
G00	1	0	G00	1	0	G10	1	1	0

		S	
		0	1
Q1Q0	00		
	01		
	11		
	10		

D0 =

Karnaugh Maps

- Now need to perform K-Maps for D_1 , D_0 , and A


Current State			Next State						Output
			S = 0			S = 1			
State	Q_1	Q_0	State	D_1	D_0	State	D_1	D_0	A
G01	0	0	G00	1	0	G10	1	1	1
G11	0	1	G01	0	0	G11	0	1	0
G10	1	1	G01	0	0	G11	0	1	1
G00	1	0	G00	1	0	G10	1	1	0

		Q1	
		0	1
Q0	0	1	0
	1	0	1

**A = $Q_1'Q_0' + Q_1Q_0$
= Q_1 XNOR Q_0**


Implementing the Circuit

- Implements the alternating detector

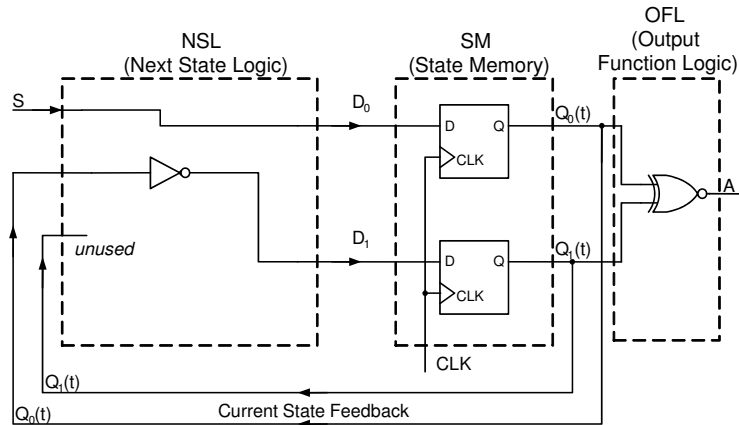


Implementing an Initial State

 - How can we make the machine start in G0 on reset (or power on?)
- Flip-flops by themselves will initialize to a random state (1 or 0) when power is turned on




Implementing an Initial State

 - Use the CLEAR and PRESET inputs on our flip-flops in the state memory
 - When CLEAR is active the FF initializes Q=0
 - When PRESET is active the FF initializes Q=1




Implementing an Initial State

 - We assigned G0 the binary code $Q_1Q_0=00$ so we must initialize our Flip-Flop's to 00




Implementing an Initial State

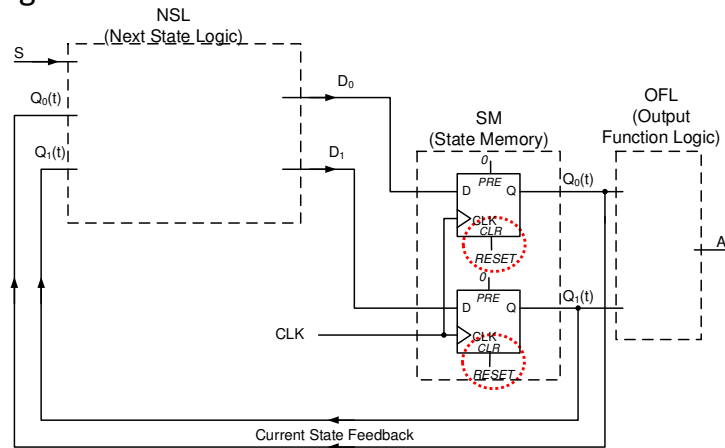- Use the CLR inputs of your FF's along with the RESET signal to initialize them to 0's




Implementing an Initial State

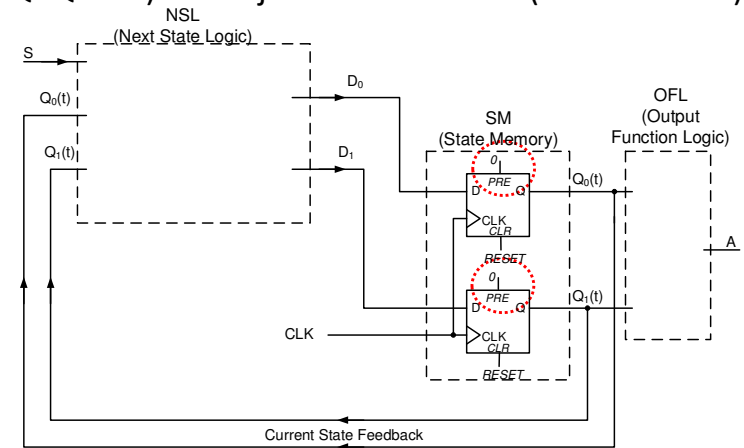- We don't want to initialize our flip-flops to 1's (only $Q_1Q_0=00$) so we just don't use PRE (tie to 'off'='0')



Implementing an Initial State

 - When RESET is activated Q's initialize to 0 and then when it goes back to 1 the Q's look at the D inputs



Alternate State Assignment

- Important Fact:** The codes we assign to our states can have a big impact on the size of the NSL and OFL
- Let us work again with a different set of assignments

State	Q_1	Q_0
G01	0	0
G11	0	1
G10	1	1
G00	1	0


Old Assignments

Current State	Next State				Output		
	S = 0		S = 1				
State	Q_1	Q_0	State		State		A
G01	0	0	G00		G10		1
G10	0	1	G01		G11		1
G00	1	1	G00		G10		0
G11	1	0	G01		G11		0

New Assignments

Alternate State Assignment



Current State			Next State						Output
			S = 0			S = 1			
State	Q ₁	Q ₀	State	Q ₁ *= D1	Q ₀ *= D0	State	Q ₁ *= =D1	Q ₀ *= =D0	A
G01	0	0	G00	1	1	G10	0	1	1
G10	0	1	G01	0	0	G11	1	0	1
G00	1	1	G00	1	1	G10	0	1	0
G11	1	0	G01	0	0	G11	1	0	0

 

  EXAMPLE 2



Traffic Light Controller

- Design the controller for a traffic light at an intersection
 - Main street has a protected turn while small street does not
 - Sensors embedded in the street to detect cars waiting to turn
 - Let $S = \text{_____}$ to check if any car is waiting
 - Simplify and only have Green and Red lights (no yellow)



State Assignment

 
 
- Design of the traffic light controller with main turn arrow
- Represent states with some binary code
 - Codes: 3 States => 2 bit code: 00=SSG, 10=MSG, 11=MTG




K-Maps

- Find logic for each FF input by using K-Maps


Current State	Next State						Output				
	S = 0			S = 1			SSG	MTG	MSG		
State	Q ₁	Q ₀	State	Q ₁ *	Q ₀ *	State	Q ₁ *	Q ₀ *	SSG	MTG	MSG
SS	0	0									
N/A	0	1									
MT	1	1									
MS	1	0									

  


MSG = ____

 


$D_1 = Q_1' + Q_0$

 

$D_0 = S \cdot Q_1'$

 

SSG = ____


 


MTG = ____

  
EXAMPLE 3

Water Pump

- Implement the water pump controller using the High and Low sensors as inputs




Transition Table

 

Current State	Q	Next State							
		HL = 0 0		HL = 0 1		HL = 1 1		HL = 1 0	
Symbol	Q	Sym.	Q*	Sym.	Q*	Sym.	Q*	Sym.	Q*
OFF	0								
ON	1								

 Note: The State Value, Q forms the Pump output (i.e. 1 when we want the pump to be on and 0 otherwise)




D =

 EXAMPLE 4


State Machine Example

- Design a sequence detector to check for the combination "1011"
- Input, X, provides 1-bit per clock
- Check the sequence of X for "1011" in successive clocks
- If "1011" detected, output Z=1 (Z=0 all other times)



State Diagram

 - Be sure to handle overlapping sequences



Transition Output Table

- Translate the state diagram into the transition output table

Current State				Next State								Output
				X = 0				X = 1				
State	Q2	Q1	Q0	State*	Q2*	Q1*	Q0*	State*	Q2*	Q1*	Q0*	Z
Sinit	0	0	0	Sinit	0	0	0	S1	0	1	1	0
S10	0	0	1	Sinit	0	0	0	S101	0	1	0	0
S1	0	1	1	S10	0	0	1	S1	0	1	1	0
S101	0	1	0	S10	0	0	1	S1011	1	1	0	0
S1011	1	1	0	S10	0	0	1	S1	0	1	1	1

Transition Output Table

- Translate the state diagram into the transition output table

Current State				Next State								Output
State	Q2	Q1	Q0	X = 0				X = 1				
State*	D2	D1	D0	State*	D2	D1	D0	State*	D2	D1	D0	Z
Sinit	0	0	0	Sinit	0	0	0	S1	0	1	1	0
S10	0	0	1	Sinit	0	0	0	S101	0	1	0	0
S1	0	1	1	S10	0	0	1	S1	0	1	1	0
S101	0	1	0	S10	0	0	1	S1011	1	1	0	0
S1011	1	1	0	S10	0	0	1	S1	0	1	1	1

NSL & OFL

Current State				Next State								Output
State	Q2	Q1	Q0	X = 0				X = 1				
State*	D2	D1	D0	State*	D2	D1	D0	State*	D2	D1	D0	Z
Sinit	0	0	0	Sinit	0	0	0	S1	0	1	1	0
S10	0	0	1	Sinit	0	0	0	S101	0	1	0	0
S1	0	1	1	S10	0	0	1	S1	0	1	1	0
S101	0	1	0	S10	0	0	1	S1011	1	1	0	0
S1011	1	1	0	S10	0	0	1	S1	0	1	1	1

Q1Q0	Q2=0	Q2=1
00	0	d
01	0	d
11	0	d
10	0	1

$Z = Q2$

Q1Q0	XQ2=00	XQ2=01	XQ2=11	XQ2=10
00	0	d	d	0
01	0	d	d	0
11	0	d	d	0
10	0	0	0	1

$D_2 = X \cdot Q2' \cdot Q1' \cdot Q0'$


Q1Q0	XQ2=00	XQ2=01	XQ2=11	XQ2=10
00	0	d	d	1
01	0	d	d	1
11	0	d	d	1
10	0	0	1	1

$D_1 = X$


Q1Q0	XQ2=00	XQ2=01	XQ2=11	XQ2=10
00	0	d	d	1
01	0	d	d	0
11	1	d	d	1
10	1	1	1	0

$D_0 = Q2 + Q1Q0 + X'Q1 + XQ1'Q0'$

Drawing the Circuit

 


Waveform for 1011 Detector

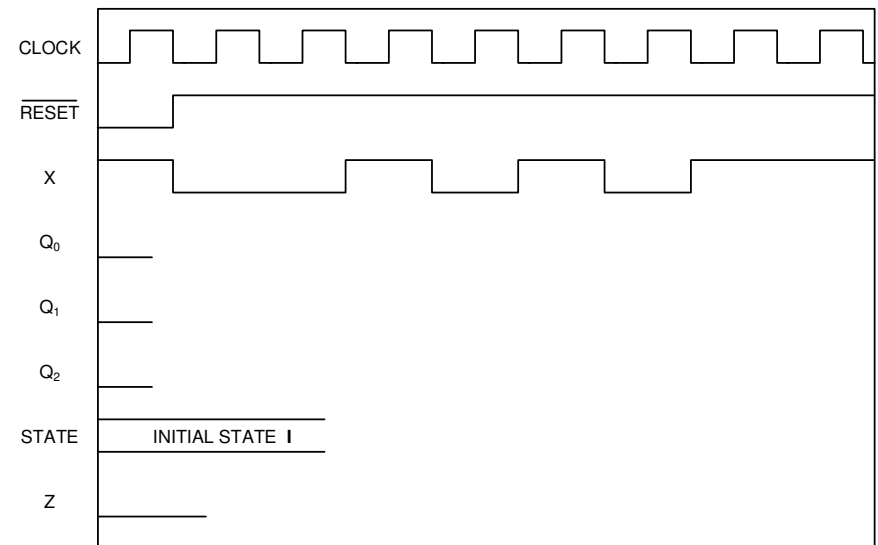

SELECTED SOLUTIONS

Another State Diagram Example

 - “101” Sequence Detector should output F=1 when the sequence 101 is found in consecutive order



Another State Diagram Example

- “101” Sequence Detector should output F=1 when the sequence 101 is found in consecutive order

