



Unit 7

Fundamental Digital Building Blocks: Decoders & Multiplexers

CHECKERS / DECODERS



Gates

  - Gates can have more than 2 inputs but the functions stay the same
 - AND = output = 1 if ALL inputs are 1
 - Outputs 1 for only 1 input combination
 - OR = output = 1 if ANY input is 1
 - Outputs 0 for only 1 input combination





Checkers / Decoders

  - An AND gate only outputs '1' for 1 combination
 - That combination can be changed by adding inverters to the inputs
 - We can think of the AND gate as "checking" or "decoding" a specific combination and outputting a '1' when it matches.





Checkers / Decoders

  - Place inverters at the input of the AND gates such that
 - F produces '1' only for input combination {x,y,z} = {010}
 - G produces '1' only for input combination {x,y,z} = {110}



Checkers / Decoders

 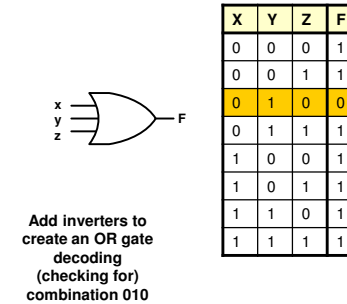- An OR gate only outputs '0' for 1 combination
 - That combination can be changed by adding inverters to the inputs



Decoder Exercise

- Compilers translate software to instructions that tell the processor to ADD, LOAD from Memory, Store to Memory, etc.
- These instructions are binary codes
- The processor must decode the instruction
- Create an AND gate decoder for each instruction type in the table that will produce '1' when that instruction is about to be executed

Instruction Type	6-bit OPCODE OP[5:0]
ADD	001000
LOAD	100011
STORE	101011
BRANCH	000100


ADD

LOAD

STORE


Full Decoders

 - A full decoder is a building block that:
 - Takes in an n-bit binary number as input
 - Decodes that binary number and activates the corresponding output
 - Individual outputs for _____ input combinations




Decoders

 - A decoder is a building block that:
 - Takes a binary number as input
 - Decodes that binary number and activates the corresponding output
 - Put in 6=110, Output 6 activates ('1')
 - Put in 5=101, Output 5 activates ('1')




Decoders

 - A decoder is a building block that:
 - Takes a binary number as input
 - Decodes that binary number and activates the corresponding output
 - Put in 6=110, Output 6 activates ('1')
 - Put in 5=101, Output 5 activates ('1')




Decoder Sizes

 - A decoder w/ an **n-bit input** has **2ⁿ outputs**
 - 1 output for every combination of the n-bit input



2-to-4 Decoder

 


3-to-8 Decoder


Exercise

- Complete the design of a 2-to-4 decoder

X	Y	D0	D1	D2	D3
0	0				
0	1				
1	0				
1	1				


 


Building Decoders

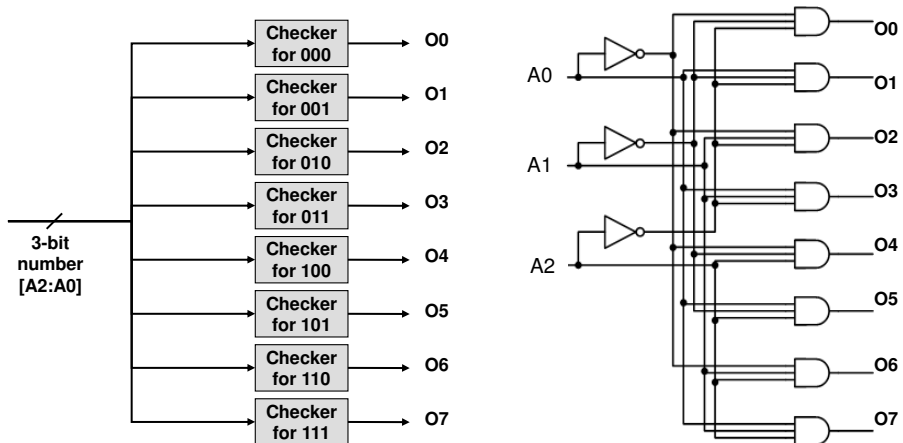

Vending Machine Example

 
 
Assuming the keypad produces a 4-bit numeric output, add logic to produce the release signals for each of the 16 vending items.





Consider any problems with this design.

Enables

  - In a normal decoder exactly one output is active at all times
- It may be undesirable to always have an active output
- We can add an extra input (called an enable) that can independently force all the outputs to their inactive values




Enables

  

Implementing Enables


- Original 2-to-4 decoder

 


E —
When E=0, force all outputs = 0
When E=1, outputs operate as they did originally

Multiplexers

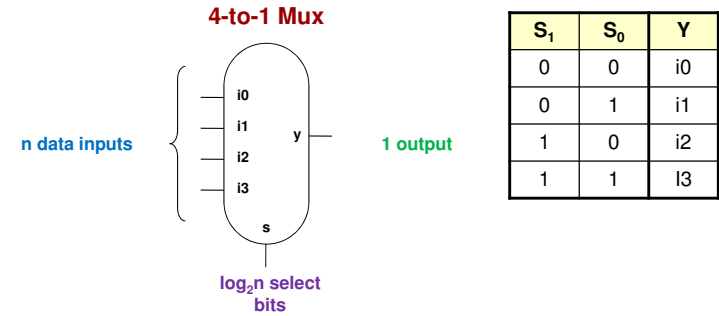
- Multiplexers are one of the most common digital circuits
- Anatomy: n data inputs, $\log_2 n$ select bits, 1 output
- A multiplexer ("mux" for short) selects one data input and passes it to the output



Multiplexers

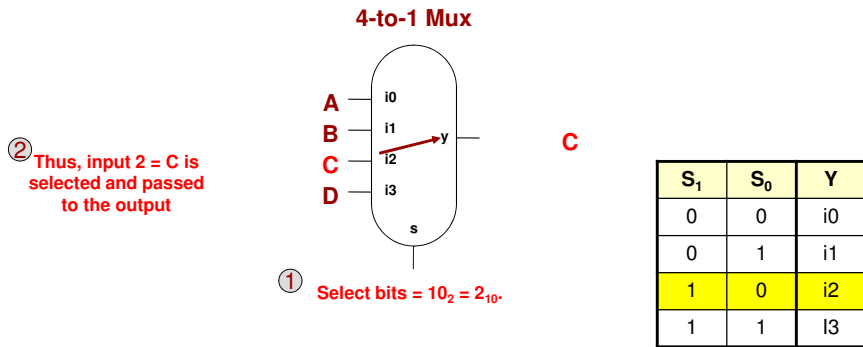


Multiplexers

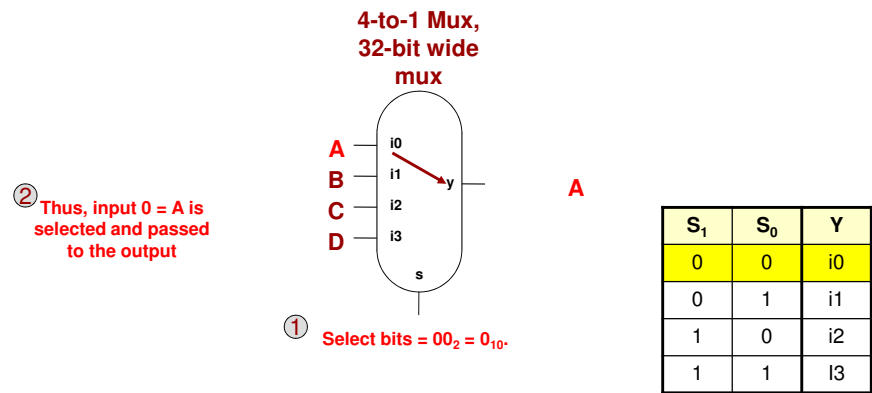

Multiplexers

2-to-1 Mux,
32-bit wide mux

 


② Thus, input 1 = B is selected and passed to the output

S	Y
0	i0
1	i1

① Select bits = $1_2 = 1_{10}$.


Recall Using T1/T2

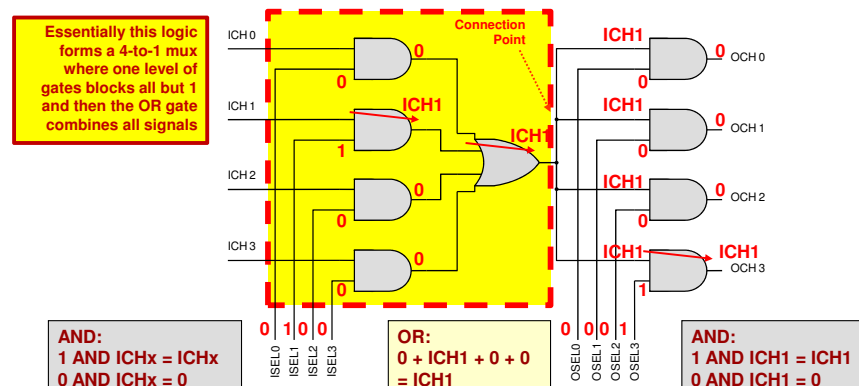- 1st Level of AND gates act as barriers only passing 1 channel
- OR gates combines 3 streams of 0's with the 1 channel that got passed (i.e. ICH1)
- 2nd Level of AND gates passes the channel to only the selected output



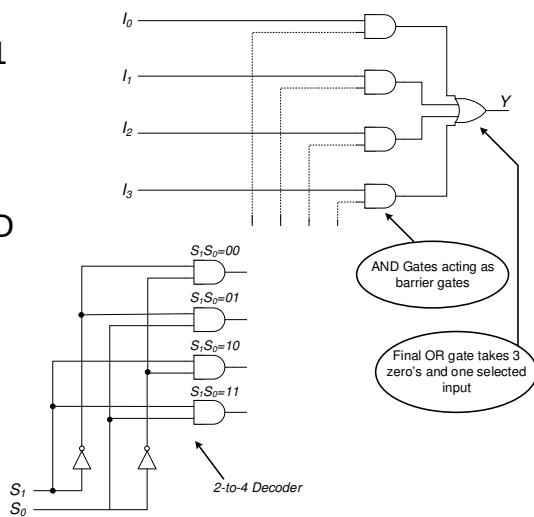
Exercise: Build a 4-to-1 mux

- Complete the 4-to-1 mux to the right by drawing wires between the 2-to-4 decode and the AND gates




Building a Mux

 - To build a mux
 - Decode the select bits and include the corresponding data input.
 - Finally OR all the first level outputs together.




Building a Mux

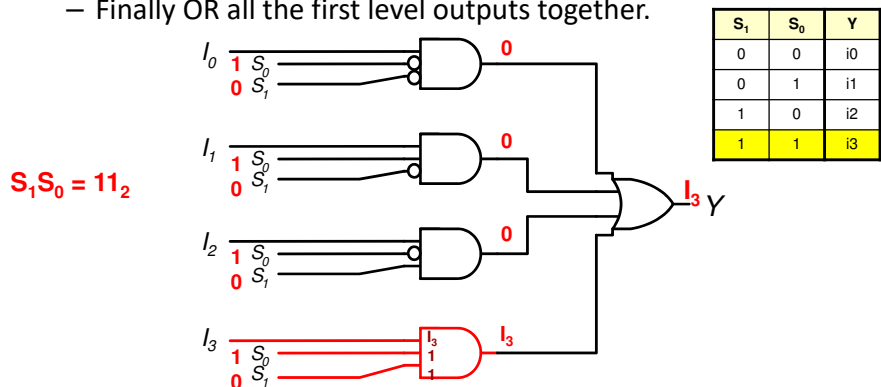- To build a mux
 - Decode the select bits and include the corresponding data input.
 - Finally OR all the first level outputs together.




Building a Mux

 - To build a mux
 - Decode the select bits and include the corresponding data input.
 - Finally OR all the first level outputs together.




Building Wide Muxes

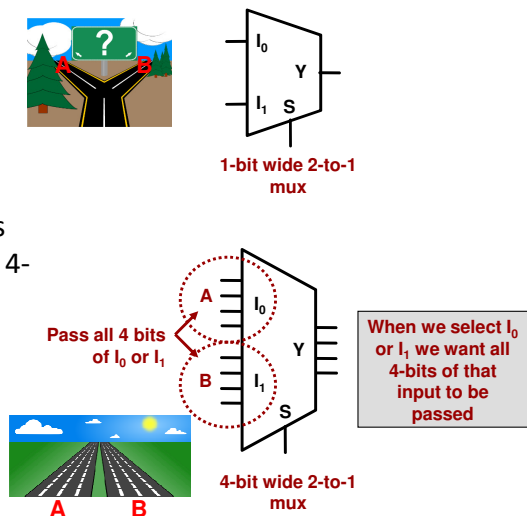- So far muxes only have single bit inputs...
 - I_0 is only 1-bit
 - I_1 is only 1-bit
- What if we still want to select between 2 inputs but now each input is a 4-bit number
- Use a 4-bit wide 2-to-1 mux




Building Wide Muxes

 - Use one mux per _____
 - To build a 4-bit wide 2-to-1 mux, use ___ separate 2-to-1 muxes
- Operation:
 - When $S=0$, all muxes pass their I_0 inputs which means all the A bits get through
 - When $S=1$, all muxes pass their I_1 inputs which means all the B bits get through
- In general, to build an **m-bit wide (i.e. m-lane) n-to-1 mux**, use ___ individual _____ muxes



Multiplexers


4-to-1 Mux,
32-bit wide
mux

 

② Thus, input 0 = A[31:0] is selected and passed to the output

Multiplexers

2-to-1 Mux,
32-bit wide mux

 


② Thus, input 1 = B[31:0] is selected and passed to the output

Exercise


- How many 1-bit wide muxes and of what size would you need to build a **4-to-1, 8-bit** wide mux (i.e. there are 4 numbers: W[7:0], X[7:0], Y[7:0] and Z[7:0] and you must select one)
- How many 1-bit wide muxes and of what size would you need to build a **8-to-1, 2-bit** wide mux?

Building Large Muxes

 - Similar to a tournament of sports teams
 - Many teams enter and then are narrowed down to 1 winner
 - In each round winners play _____




Design an 8-to-1 mux with 2-to-1 Muxes

 

Cascading Muxes

- Use several small muxes to build large ones
- Rules
 1. Arrange the muxes in stages (based on necessary number of inputs in 1st stage)
 2. Outputs of one stage feed to inputs of the next until only 1 final output
 3. All muxes in a stage connect to the same group of select bits
 - Usually, LSB connects to first stage
 - MSB connect to last stage

Building a 4-to-1 Mux

 


Building a 4-to-1 Mux

S ₁	S ₀	Y
0	0	D ₀
0	1	D ₁
1	0	D ₂
1	1	D ₃

Walk through an example:

$$S_1 S_0 = 01$$

 


Building a 4-to-1 Mux

S ₁	S ₀	Y
0	0	D ₀
0	1	D ₁
1	0	D ₂
1	1	D ₃

Walk through an example:

$S_1 S_0 = 01$

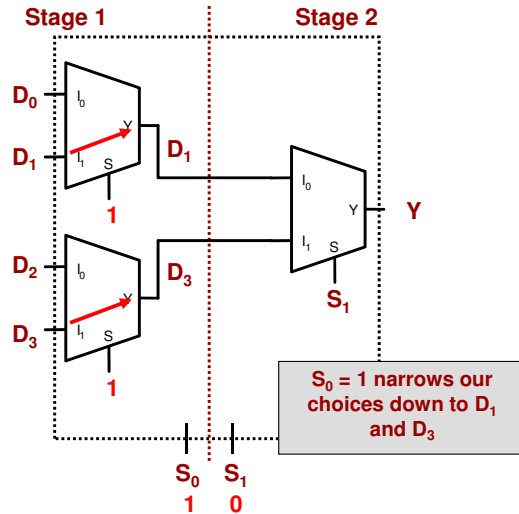


Building a 4-to-1 Mux

S ₁	S ₀	Y
0	0	D ₀
0	1	D ₁
1	0	D ₂
1	1	D ₃

Walk through an example:

$S_1 S_0 = 01$

 

Device vs. System Labels

- When using hierarchy (i.e. building blocks) to design a circuit be sure to show both device and system labels
 - Device Labels: Signal names used inside the block
 - inside to indicate which input/output is which to the outside user
 - System labels: Signal names used outside the block
 - outside signals from the circuit being built
 - Can have the same name as the device label if such a signal name exists at the outside level


Analogy: Formal and Actual parameters in software function calls

- a and b are like device labels and indicate the names used inside a block.
- x and y are like system labels and represent the actual values to be used.

```
int div(int i0, int i1)
{ int t = i0/i1;
  return t; }
int main()
{
  int d0=10, d1=2;
  int s = div(d0,d1);
}
```

Device Labels: Indicate which input/output is which inside the block.

 System Labels: Actual signals from the circuit being built



Exercise

- Sketch how you could build a 16-to-1 mux with 4-to-1 muxes? 8-to-1 and 2-to1 muxes?

Exercise

- Create a 3-to-1 mux using 2-to-1 muxes
 - Inputs: I₀, I₁, I₂ and select bits S₁, S₀
 - Output: Y

S ₁	S ₀	Y
0	0	D ₀
0	1	D ₁
1	0	D ₂

I₀ _


I₁ _

I₂ _

_ Y

Select-bit Ordering

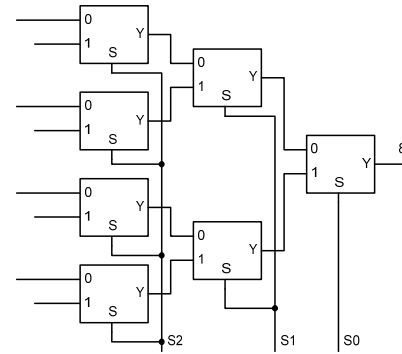- If we connect the select bits as shown to build an 8-to-1 mux, show how to label the inputs (i₀-i₇) so that the correct input is passed based on the binary value of S₂:S₀



Selects			OUT Y
S ₂	S ₁	S ₀	
0	0	0	
1			
0	1	0	
1			
0	0	1	
1			
0	1	1	
1			