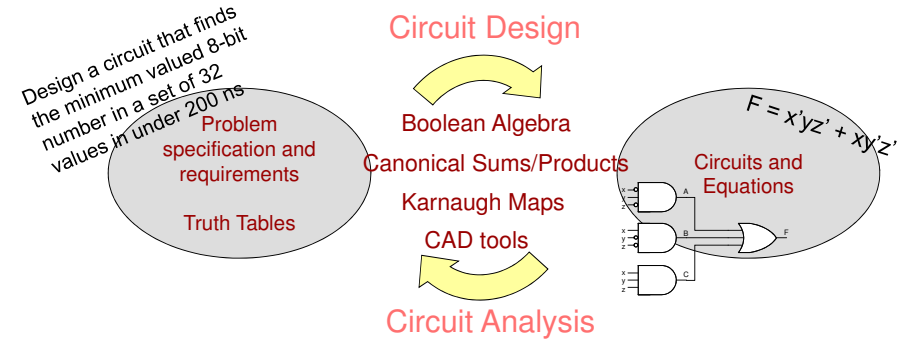


Unit 8

Minterm and Canonical Sums
2- and 3-Variable Boolean Algebra Theorems
DeMorgan's Theorem
Simplification using Boolean Algebra


Circuit Design and Analysis

- There are two basic tasks as a digital design engineer...
 - **Circuit Design/Synthesis:** Take a set of requirements or functional descriptions and arrive at a logic circuit
 - **Circuit Analysis:** Given a logic circuit, find or verify the logic function it implements



Outcomes

 - The goal of this unit is to teach you how you can construct a digital circuit to implement ANY logic function
 - Example: Given a truth table, build a circuit from ANDs and ORs that will implement the function specified by the truth table



SYNTHESIZING LOGIC FUNCTIONS

The Problem

- Given a logic function, how do we arrive at a circuit to implement this combinational function?
- Rather than trying to solve the problem all at once we will do it in two steps:
 - Use gates to convert raw inputs (e.g. x,y,z) to intermediate signals;
 - Convert the intermediate signals to produce the output (e.g. P)

Primes between 0-7

X	Y	Z	P
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

1's Count of Inputs

I3	I2	I1	C1	C0
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Using Decoders to Implement Functions


- Given an any logic function, it can be implemented with the superposition of decoders/checkers

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Using Decoders to Implement Functions

- Given an any logic function, it can be implemented with the superposition of decoders

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 


X	Y	Z	A
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

Using Decoders to Implement Functions

- Given an any logic function, it can be implemented with the superposition of decoders


X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 

X	Y	Z	A	B
0	0	0	0	0
0	0	1	0	0
0	1	0	1	0
0	1	1	0	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	0	0


Using Decoders to Implement Functions

 - Given an any logic function, it can be implemented with the superposition of decoders




Using Decoders to Implement Functions

 - Given an any logic function, it can be implemented with the superposition of decoders




Using Decoders to Implement Functions

 - Given an any logic function, it can be implemented with the superposition of decoders




Using Decoders to Implement Functions

 - Given an any logic function, it can be implemented with the superposition of decoders



Using Decoders to Implement Functions

 - Given an any logic function, it can be implemented with the superposition of decoders




Defining Minterms

- We call an AND gate checking for one combination of a logic function (truth table) a **minterm**
- Write the expression for each minterm of 3 variables: x, y, z

Row #	Minterm Expression	x	y	z	Minterms								
					m_0	m_1	m_2	m_3	m_4	m_5	m_6	m_7	
0	m_0	0	0	0	1	0	0	0	0	0	0	0	0
1	m_1	0	0	1	0	1	0	0	0	0	0	0	0
2	m_2	0	1	0	0	0	1	0	0	0	0	0	0
3	m_3	0	1	1	0	0	0	1	0	0	0	0	0
4	m_4	1	0	0	0	0	0	0	1	0	0	0	0
5	m_5	1	0	1	0	0	0	0	0	1	0	0	0
6	m_6	1	1	0	0	0	0	0	0	0	1	0	0
7	m_7	1	1	1	0	0	0	0	0	0	0	1	0

Checkers / Decoders

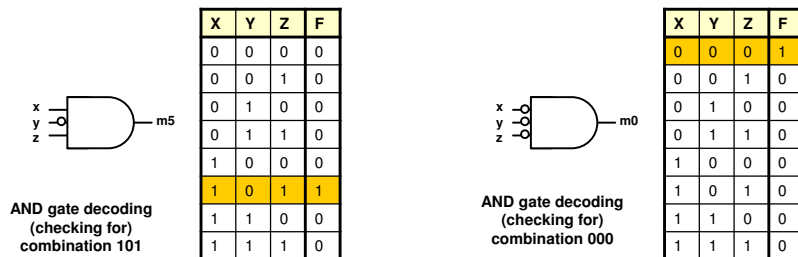- The m_i functions on the previous slide are just AND gate checkers
 - That combination can be changed by adding inverters to the inputs
 - We can think of the AND gate as "checking" or "decoding" a specific combination and outputting a '1' when it matches.



Applying Minterms to Synthesize a Function

- Each numbered minterm checks whether the inputs are equal to the corresponding combination. When the inputs are equal, the minterm will evaluate to 1 and thus the whole function will evaluate to 1.

x	y	z	P
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

$P = m_2 + m_3 + m_5 + m_7$
 $= x'yz' + x'yz + xy'z + xyz$

when $x,y,z = \{0,1,0\} = 2$ then
 $P = 0' \cdot 1 \cdot 0' + 0' \cdot 1 \cdot 0 + 0 \cdot 1' \cdot 0 + 0 \cdot 1 \cdot 0$
 $= 1 + 0 + 0 + 0 = 1$

when $x,y,z = \{1,0,1\} = 5$ then
 $P = 1' \cdot 0 \cdot 1' + 1' \cdot 0 \cdot 1 + 1 \cdot 0' \cdot 1 + 1 \cdot 0 \cdot 1$
 $= 0 + 0 + 1 + 0 = 1$

when $x,y,z = \{0,0,1\} = 1$ then
 $P = 0' \cdot 0 \cdot 1' + 0' \cdot 0 \cdot 1 + 0 \cdot 0' \cdot 1 + 0 \cdot 0 \cdot 1$
 $= 0 + 0 + 0 + 0 = 0$

Definitions

- **Literal:** A single bit _____ or its _____
 - **Good:** x, y', ALARM'
 - **Bad:** (x+y)
- **Product Term:** A _____ literal by itself or an _____'ing (not NAND'ing) of literals
 - **Good:** z, x•y, ALARM•PANIC•ENABLED
 - **BAD:** (x•y)', ALARM•(PANIC+ENABLED)
- **Minterm:** A product term where each input variable of a function appears as exactly one literal
 - $f(x,y,z) =>$
 - x'y'z
 - xyz
 - x'y
 - x+y+z


Minterms

- Consider F(A,B)
- One minterm per combination of the input variables
- Only one minterm can evaluate to 1 at any time

A	B	F	m ₀	m ₁	m ₂	m ₃
A	B	F	A'•B'	A'•B	A•B'	A•B
0	0	0	1	0	0	0
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	0	0	0	0	1

Finding Equations/Circuits

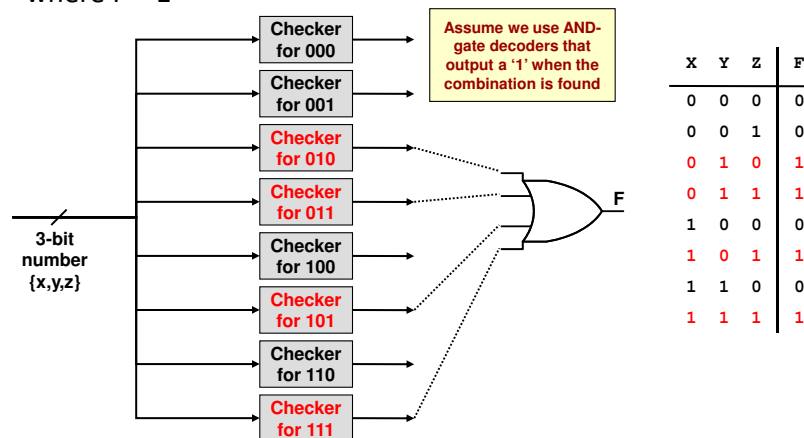- Given a function and checkers (called decoders) for each combination, we just need to OR together the checkers where F = 1



Canonical Sums

- Given a T.T., _____ together all the minterms where F = _____
 - (Σ = SUM or OR of all the minterms)

$$F = m_2 + m_3 + m_5 + m_7$$

$$= (X'Y'Z') + (X'Y'Z) + (XY'Z') + (XYZ)$$

Canonical Sum:

$$F = \sum_{xyz} (2, 3, 5, 7)$$



List the minterms where F is 1.

	X	Y	Z	F
m ₀	0	0	0	0
m ₁	0	0	1	0
m ₂	0	1	0	1
m ₃	0	1	1	1
m ₄	1	0	0	0
m ₅	1	0	1	1
m ₆	1	1	0	0
m ₇	1	1	1	1

Using OR-gate checkers


AN ALTERNATIVE

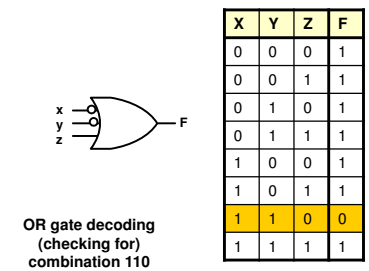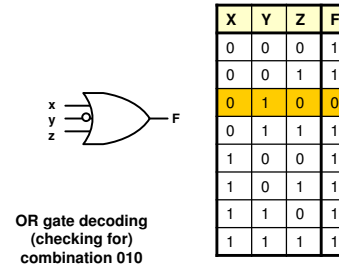- An OR gate only outputs '0' for 1 combination
 - That combination can be changed by adding inverters to the inputs
 - We can think of the OR gate as "checking" or "decoding" a specific combination and outputting a '0' when it matches.



Finding Equations/Circuits

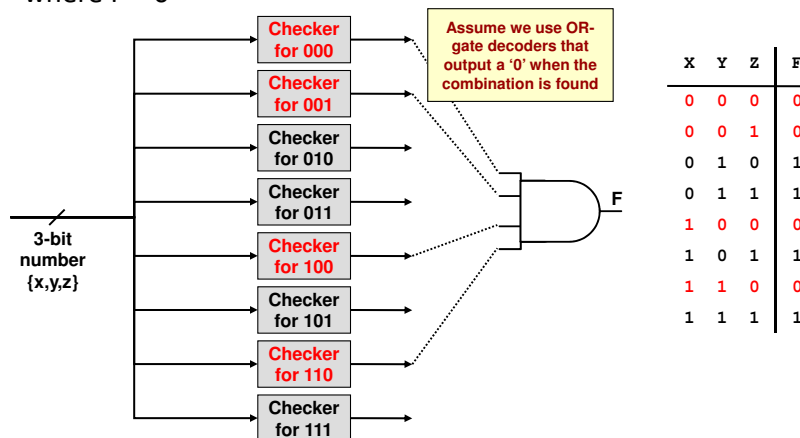- Given a function and checkers (called decoders) for each combination, we just need to AND together the checkers where $F = 0$



Applying Maxterms to Synthesize a Function

- Each output that should produce a '0' can be checked-for with an OR gate
 - We refer to that OR-gate checker as a Maxterm of the function (M_i)
- We then AND together the maxterms

x	y	z	P	use...
0	0	0	0	M_0
0	0	1	0	M_1
0	1	1	1	
1	0	0	0	M_4
1	0	1	1	
1	1	0	0	M_6
1	1	1	1	

$$\begin{aligned}
 P &= M_0 \cdot M_1 \cdot M_4 \cdot M_6 \\
 &= (x+y+z) \cdot (x+y+z') \cdot (x'+y+z) \cdot (x'+y'+z)
 \end{aligned}$$

when $x,y,z = \{0,0,1\} = 1$ then

$$\begin{aligned}
 P &= (0+0+1) \cdot (0+0+1') \cdot (0'+0+1) \cdot (0'+0'+1) \\
 &= 1 \cdot 0 \cdot 1 \cdot 1 = 0
 \end{aligned}$$

when $x,y,z = \{1,1,0\} = 6$ then

$$\begin{aligned}
 P &= (1+1+0) \cdot (1+1+0') \cdot (1'+1+0) \cdot (1'+1'+0) \\
 &= 1 \cdot 1 \cdot 1 \cdot 0 = 0
 \end{aligned}$$

when $x,y,z = \{1,1,1\} = 7$ then

$$\begin{aligned}
 P &= (1+1+1) \cdot (1+1+1') \cdot (1'+1+1) \cdot (1'+1'+1) \\
 &= 1 \cdot 1 \cdot 1 \cdot 1 = 1
 \end{aligned}$$

Canonical Products

- Given a T.T., AND together all the maxterms where F = 0

$$F = M_0 \cdot M_1 \cdot M_4 \cdot M_6$$

$$= (X+Y+Z) \cdot (X+Y+Z') \cdot (X'+Y+Z) \cdot (X'+Y'+Z)$$





Canonical Product:

$$F = \prod_{xyz} (0, 1, 4, 6)$$

List the maxterms where F is 0.

	X	Y	Z	F
M ₀	0	0	0	0
M ₁	0	0	1	0
M ₂	0	1	0	1
M ₃	0	1	1	1
M ₄	1	0	0	0
M ₅	1	0	1	1
M ₆	1	1	0	0
M ₇	1	1	1	1

Definitions



- Literal:** A single bit variable or its inverse
 - Good: x, y', ALARM'
- Sum Term:** A single literal by itself or an OR'ing (not NOR'ing) of literals
 - Good: z, x'+y, ALARM+PANIC+ENABLED
 - BAD: (x+y)', ALARM*(PANIC+ENABLED)
- Maxterm:** A sum term where each input variable of a function appears as exactly one literal
 - f(x,y,z) =>
 - x'+y'+z 
 - x+y+z 
 - x'y 
 - x*y*z 

You are only responsible for Canonical Sums (not Products)

LOGIC FUNCTION NOTATION

Boolean Algebra Terminology

- SOP () Form:** An SOP expression is a logical sum (OR) of product terms
 - Correct Examples: [x'y'z + w + a'b*c], [w + x'z*y + y'z]
 - Incorrect Examples: [x'y*z + w*(a+b)], [x*y + (y'z)']
- POS () Form:** A POS expression is a logical product (AND) of sum terms.
 - Correct Examples: [(x+y+z) * (w'+z) * (a)], [z'*(x+y)*(w'+y)]
 - Incorrect Examples: [x' + y*(x+w)], [(x+y)*(x+z)']
- SOP equations yield _____ circuits with AND gates in the 1st level with OR gates in the 2nd (aka AND-OR circuits)
- POS equations yield _____ circuits with OR gates in the 1st level with AND gates in the 2nd (aka OR-AND circuits)

  

Check Yourself

Expression	SOP / POS / Both / Neither
$w \cdot x \cdot (y \cdot z)' + xy'z + w$	
$xy + xz + (w'y)z$	
$(w+y'+z)(w+x)$	
$(w+y)x(w'+z)$	
$w'y + w'y + xy'$	
$w+x+y$	

Canonical Sums & Products

- **Canonical Sum:** An ____ expression where all the product terms are ____ (i.e. have each literal in each product term)
- **Canonical Product:** A ____ expression where all the sum terms are ____ (i.e. each literal in each sum term)

Canonical Sum:

$$F = \sum_{xyz} (2, 3, 5, 7)$$

$$F = m_2 + m_3 + m_5 + m_7 = (X'Y'Z') + (X'Y'Z) + (XY'Z') + (XYZ)$$

Canonical Product:


$$F = \prod_{xyz} (0, 1, 4, 6)$$

$$F = M_0 \cdot M_1 \cdot M_4 \cdot M_6 = (X+Y+Z) \cdot (X+Y+Z') \cdot (X'+Y+Z) \cdot (X'+Y'+Z)$$

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Logic Functions

 - A logic function maps input combinations to an output value ('1' or '0')
- 3 possible representations of a function
 - Equation
 - Schematic
 - Truth Table
- Can convert between representations
- Truth table is only unique representation*



* Canonical Sums/Products (minterm/maxterm) representation provides a standard equation/schematic form that is unique per function

Unique Representations

- Canonical => Same functions will have same representations
- Truth Tables along with Canonical Sums and Products specify a function *uniquely*
- Equations/circuit schematics are NOT inherently canonical

x	y	z	P
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Canonical Sum

$$P = \sum_{x,y,z} (2,3,5,7)$$

ON-Set of P (minterms)

Yields SOP equation, AND-OR circuit

Canonical Product

$$P = \prod_{x,y,z} (0,1,4,6)$$

OFF-Set of P (maxterms)

Yields POS equation, OR-AND circuit

2 & 3 Variable Theorems

T6	$X+Y = Y+X$	T6'	$X \cdot Y = Y \cdot X$	Commutativity
T7	$(X+Y)+Z = X+(Y+Z)$	T7'	$(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$	Associativity
T8	$XY+XZ = X(Y+Z)$	T8'	$(X+Y)(X+Z) = X+YZ$	Distribution & Factoring
T9	$X + XY = X$	T9'	$X(X+Y) = X$	Covering
T10	$XY + XY' = X$	T10'	$(X+Y)(X+Y') = X$	Combining
T11	$XY + X'Z + YZ = XY + X'Z$	T11'	$(X+Y)(X'+Z)(Y+Z) = (X+Y)(X'+Z)$	Consensus
DM	$(X+Y)' = X' \cdot Y'$	DM'	$(X \cdot Y)' = X' + Y'$	DeMorgan's

Proofs Through Other Theorems

T8	$XY+XZ = X(Y+Z)$	T8'	$(X+Y)(X+Z) = X+YZ$
T9	$X + XY = X$	T9'	$X(X+Y) = X$
T10	$XY + XY' = X$	T10'	$(X+Y)(X+Y') = X$
T11	$XY + XZ + YZ = XY + X'Z$	T11'	$(X+Y)(X'+Z)(Y+Z) = (X+Y)(X'+Z)$

- Prove T9: $X + XY = X$
-
-
-
- Prove T10: $XY + XY' = X$
-
-
-
- Prove T10': $(X+Y)(X+Y')=X$
-
-
-

OR


DeMorgan's Theorem

- Inverting output of an AND gate = inverting the inputs of an OR gate
- Inverting output of an OR gate = inverting the inputs of an AND gate

A function's inverse is equivalent to inverting all the inputs and changing AND to OR and vice versa

A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0


$\overline{A \cdot B}$

 

A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

$\overline{A+B}$

 

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

Analogy: Turning a gate "inside-out" (like your socks).

DeMorgan's Theorem

$$F = \overline{\overline{X+Y} + \overline{Z}} \cdot (Y+W)$$

Use DeMorgan's theorem to simplify "move" inversions (either to break-up "big bars" or join "small bars")

$$F = \overline{\overline{X+Y} + \overline{Z}} \cdot (Y+W)$$

$$F = \overline{\overline{X+Y}} \cdot \overline{\overline{Z}} \cdot (Y+W)$$

$$F =$$

$$F =$$

Generalized DeMorgan's Theorem

$$F'(X_1, \dots, X_n, +, \cdot) = F(X_1', \dots, X_n', \cdot, +)$$

To find F' , swap AND's and OR's and complement each literal. However, you must maintain the original order of operations.

Note: This parentheses doesn't matter (we are just OR'ing X', Y, and the following subexpression)

$$F = (\bar{X} + Y) + \bar{Z} \cdot (Y + W)$$

$$F = \bar{X} + Y + (\bar{Z} \cdot (Y + W))$$


Fully parenthesized to show original order of ops.

$$\bar{F} = X \cdot \bar{Y} \cdot (Z + (\bar{Y} \cdot \bar{W}))$$

AND's & OR's swapped
Each literal is inverted


DeMorgan's Theorem Example

 - Cancel as many bubbles as you can using DeMorgan's theorem.




AND-OR / NAND-NAND

 - Canonical Sums yield
 - AND-OR Implementation
 - NAND-NAND Implementation





OR-AND / NOR-NOR

 - Canonical Products yield
 - OR-AND Implementation
 - NOR-NOR Implementation



  
Example: Automobile Buzzer

- Convert each implementation to use either just NOR or just NAND gates + inverters



Convert to NAND-NAND

 - Convert the 2-to-1 mux below to use just NAND or NOR gates?



Logic Synthesis

- Describe the function
 - Usually with a truth table
- Find the sum of minterm (or product of maxterm) expression
 - In this class, you're only responsible for the sum of minterm approach
- Use Boolean Algebra (T8-T11) to find a simplified expression

Synthesize/Simplify Exercise 1

- Synthesize this function
 - First generate the canonical sum
 - Then use theorems to simplify

T8	$XY + XZ = X(Y+Z)$	T8'	$(X+Y)(X+Z) = X+YZ$
T9	$X + XY = X$	T9'	$X(X+Y) = X$
T10	$XY + XY' = X$	T10'	$(X+Y)(X+Y') = X$
T11	$XY + X'Z + YZ = XY + X'Z$	T11'	$(X+Y)(X'+Z)(Y+Z) = (X+Y)(X'+Z)$

Primes between 0-7

X	Y	Z	P
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Synthesize/Simplify Exercise 2

- Synthesize each output separately
 - First generate the canonical sum
 - Then use theorems to simplify

T8	$XY + XZ = X(Y + Z)$	T8'	$(X + Y)(X + Z) = X + YZ$
T9	$X + XY = X$	T9'	$X(X + Y) = X$
T10	$XY + XY' = X$	T10'	$(X + Y)(X + Y') = X$
T11	$XY + XZ + YZ = XY + XZ$	T11'	$(X + Y)(X' + Z)(Y + Z) = (X + Y)(X' + Z)$

I3	I2	I1	M1	M0
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	0
1	0	0	1	1
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

Encode the highest input ID (ie. 3, 2, or 1) that is ON (=1)

Synthesize/Simplify Exercise 3 (Optional)

- Synthesize each output separately
 - First generate the canonical sum
 - Then use theorems to simplify

T8	$XY + XZ = X(Y + Z)$	T8'	$(X + Y)(X + Z) = X + YZ$
T9	$X + XY = X$	T9'	$X(X + Y) = X$
T10	$XY + XY' = X$	T10'	$(X + Y)(X + Y') = X$
T11	$XY + XZ + YZ = XY + XZ$	T11'	$(X + Y)(X' + Z)(Y + Z) = (X + Y)(X' + Z)$

1's Count of Inputs

I3	I2	I1	C1	C0
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1