

2. Practice Problem Solutions

The following are solutions to the set of practice problems presented separately. Use these only after attempting the problems on your own.

HW2 - Number Systems and Conversions

1.

a. 1110110.010111_2
 $= 1*2^6 + 1*2^5 + 1*2^4 + 1*2^2 + 1*2^1 + 1*2^{-2} + 1*2^{-4} + 1*2^{-5} + 1*2^{-6}$
 $= 118.359375_{10}$
 $= 001 | 110 | 110.010 | 111_2 = 166.27_8$
 $= 0111 | 0110.0101 | 1100_2 = 76.5C_{16}$

b. $15B.35_{16}$
 $= 1*16^2 + 5*16^1 + 11*16^0 + 3*16^{-1} + 5*16^{-2} = 347.20703125_{10}$
 $= 0001 | 0101 | 1011.0011 | 0101_2$
 $= 101 | 011 | 011.001 | 101 | 010_2 = 533.152_8$

2. Use the "Making Change" method

a. Start by listing the powers of 2 and then find the coefficients of the number by starting with the largest powers and working toward lower powers determining which ones sum to the desired value.

0	1	1	1	0	0	1	1	0	1	1	.	1	0	1
1024	512	256	128	64	32	16	8	4	2	1		.5	.25	.125

$$(923.625)_{10} = (1110011011.101)_2$$

3.

a. 4530.152_8
 $= 100 101 011 000.001 101 01_2$
 $= 1001 | 0101 | 1000.0011 | 0101_2 = 958.35_{16}$

4.

a. $DABB.AD00_{16}$
 $= 1101 1010 1011 1011.1010 1101_2$
 $= 001 | 101 | 101 | 010 | 111 | 011.101 | 011 | 010_2 = 155273.532_8$

b. $BAD.A_{16} = 11*16^2 + 10*16^1 + 13*16^0 + 10*16^{-1} = 2989.625_{10}$

5. Use the "Making Change" method: Start by listing the powers of 5 and then find the coefficients of the number by starting with the largest powers and working toward lower powers determining which ones sum to the desired value

a.

0	3	2	0	3	3	.	3	1
3125	625	125	25	5	1		.2	.04

$$(2143.64)_{10} = (32033.31)_5$$

HW3 - Boolean Algebra, Logic Functions, and Canonical Representation, 2-Level Implementations

1. **Probably the easiest method is perfect induction (i.e. a truth table)**
 $F = X + X' = 1$

X	X'	F
0	1	1
1	0	1

2.

a.

$$\begin{aligned}
 F &= WXYZ \cdot (WXYZ' + WX'YZ + W'XYZ + WXY'Z) \\
 &= WWXXYYZZ' \cdot WWXX'YYZZ + W'WXXYYZZ + \\
 &\quad WWXXYY'ZZ \qquad \qquad \qquad T8 \\
 &= WXYZZ' + WXX'YZ + WW'XYZ + WXY'Z \qquad T3' \\
 &= 0 + 0 + 0 + 0 + 0 \qquad T5' \\
 &= 0 \qquad \qquad \qquad A4'
 \end{aligned}$$

b.

$$\begin{aligned}
 F &= AB + ABC'D + ABDE' + ABC'E + C'D \\
 &= AB \cdot (1 + C'D + DE' + C'E) + C'D \qquad T8 \\
 &= AB \cdot (1 + DE' + C'E) + C'D \qquad T6 \\
 &= AB \cdot (1) + C'D \qquad T2 \\
 &= AB + C'D \qquad T1'
 \end{aligned}$$

3.

a. $F = X'Y + X'Y'Z'$

XYZ	X'	X' • Y	Y'	Z'	X' • Y' • Z'	F
000	1	0	1	1	1	1
001	1	0	1	0	0	0
010	1	1	0	1	0	1
011	1	1	0	0	0	1
100	0	0	1	1	0	0
101	0	0	1	0	0	0
110	0	0	0	1	0	0
111	0	0	0	0	0	0

b. $F = W' + X' \cdot (Y' + Z)$

WXYZ	W'	Y'	Y'+Z	X'	$X' \cdot (Y'+Z)$	F
0000	1	1	1	1	1	1
0001	1	1	1	1	1	1
0010	1	0	0	1	0	1
0011	1	0	1	1	1	1
0100	1	1	1	0	0	1
0101	1	1	1	0	0	1
0110	1	0	0	0	0	1
0111	1	0	1	0	0	1
1000	0	1	1	1	1	1
1001	0	1	1	1	1	1
1010	0	0	0	1	0	0
1011	0	0	1	1	1	1
1100	0	1	1	0	0	0
1101	0	1	1	0	0	0
1110	0	0	0	0	0	0
1111	0	0	1	0	0	0

c. $F = (A' + B' + CD) \cdot (B + C' + D')$

ABCD	A'	B'	CD	$A' + B' + CD$	C'	D'	$B + C' + D'$	F
0000	1	1	0	1	1	1	1	1
0001	1	1	0	1	1	0	1	1
0010	1	1	0	1	0	1	1	1
0011	1	1	1	1	0	0	0	0
0100	1	0	0	1	1	1	1	1
0101	1	0	0	1	1	0	1	1
0110	1	0	0	1	0	1	1	1
0111	1	0	1	1	0	0	1	1
1000	0	1	0	1	1	1	1	1
1001	0	1	0	1	1	0	1	1
1010	0	1	0	1	0	1	1	1
1011	0	1	1	1	0	0	0	0
1100	0	0	0	0	1	1	1	0
1101	0	0	0	0	1	0	1	0
1110	0	0	0	0	0	1	1	0
1111	0	0	1	1	0	0	1	1

d.

$$\begin{aligned}
 F &= (((A' + B)' + C')' + D)' \\
 &= ((A' + B)' + C') \cdot D' && \text{DEMORGANS} \\
 &= (A \cdot B' + C') \cdot D' && \text{DEMORGANS} \\
 &= AB'D' + C'D' && \text{T8}
 \end{aligned}$$

ABCD	B'	D'	A•B'•D'	C'	C'•D'	F
0000	1	1	0	1	1	1
0001	1	0	0	1	0	0
0010	1	1	0	0	0	0
0011	1	0	0	0	0	0
0100	0	1	0	1	1	1
0101	0	0	0	1	0	0
0110	0	1	0	0	0	0
0111	0	0	0	0	0	0
1000	1	1	1	1	1	1
1001	1	0	0	1	0	0
1010	1	1	1	0	0	1
1011	1	0	0	0	0	0
1100	0	1	0	1	1	1
1101	0	0	0	1	0	0
1110	0	1	0	0	0	0
1111	0	0	0	0	0	0

4.

a.

$$\begin{aligned}
 F &= \Sigma_{XYZ} (0,2,3) \\
 &= m_0 + m_2 + m_3 \\
 &= X'Y'Z' + X'YZ' + X'YZ \\
 &= \Pi_{XYZ} (1,4,5,6,7) \\
 &= M_1 \cdot M_4 \cdot M_5 \cdot M_6 \cdot M_7 \\
 &= (X+Y+Z') \cdot (X'+Y+Z) \cdot (X'+Y+Z') \cdot (X'+Y'+Z) \cdot (X'+Y'+Z')
 \end{aligned}$$

b.

$$\begin{aligned}
 F &= \Pi_{ABC} (1,2,4,6) \\
 &= M_1 \cdot M_2 \cdot M_4 \cdot M_6 \\
 &= (A + B + C') \cdot (A + B' + C) \cdot (A' + B + C) \cdot (A' + B' + C) \\
 &= \Sigma_{A,B,C} (0,3,5,7) \\
 &= m_0 + m_3 + m_5 + m_7 \\
 &= A'B'C' + A'BC + AB'C + ABC
 \end{aligned}$$

c.

$$\begin{aligned}
 F &= \Sigma_{ABCD}(1,2,5,7) \\
 &= m_1 + m_2 + m_5 + m_7 \\
 &= A'B'C'D + A'B'CD' + A'BC'D + A'BCD \\
 &= \Pi_{ABCD}(0,3,4,6,8,9,10,11,12,13,14,15) \\
 &= M_0 \cdot M_3 \cdot M_4 \cdot M_6 \cdot M_8 \cdot M_9 \cdot M_{10} \cdot M_{11} \cdot M_{12} \cdot M_{13} \cdot M_{14} \cdot M_{15} \\
 &= (A + B + C + D) \cdot (A + B + C' + D') \cdot (A + B' + C + D) \\
 &\quad \cdot (A + B' + C' + D) \cdot (A' + B + C + D) \cdot (A' + B + C + D') \\
 &\quad \cdot (A' + B + C' + D) \cdot (A' + B + C' + D') \cdot (A' + B' + C + D) \\
 &\quad \cdot (A' + B' + C + D') \cdot (A' + B' + C' + D) \cdot (A' + B' + C' + D')
 \end{aligned}$$

d.

$$\begin{aligned}
 F &= X' + YZ' + YZ = X' + YZ' && T3 \\
 &= X'(Y + Y')(Z + Z') + (X + X')(YZ') && T1'/T5 \\
 &= X'Y'Z' + X'YZ' + X'YZ + XYZ' + X'YZ' && T8 \\
 &= m_0 + m_1 + m_2 + m_3 + m_6 \\
 &= \Sigma_{XYZ}(0,1,2,3,6)
 \end{aligned}$$


$$\begin{aligned}
 &= \Pi_{X,Y,Z}(4,5,7) \\
 &= M_4 \cdot M_5 \cdot M_7 \\
 &= (X' + Y + Z) \cdot (X' + Y + Z') \cdot (X' + Y' + Z')
 \end{aligned}$$

e.

$$\begin{aligned}
 F &= A'B + B'C + AC' \\
 &= (A'BC + A'BC') + (AB'C + A'B'C) + (ABC' + AB'C') && T10 \\
 &= m_3 + m_2 + m_5 + m_1 + m_6 + m_4 \\
 &= \Sigma_{ABC}(1,2,3,4,5,6)
 \end{aligned}$$

$$\begin{aligned}
 &= \Pi_{ABC}(0,7) \\
 &= M_0 \cdot M_7 \\
 &= (A + B + C) \cdot (A' + B' + C')
 \end{aligned}$$

5.

 

6. **One possible solution:**

$$\begin{aligned}
 &XY + X'Z + YZ \\
 &XY + X'Z + YZ \cdot 1 && T1' \\
 &XY + X'Z + YZ \cdot (X + X') && T5 \\
 &XY + X'Z + XYZ + X'ZY && T8 \\
 &(XY + XYZ) + (X'Z + X'ZY) && T6 \\
 &XY + X'Z && T9
 \end{aligned}$$

7.

a.

$$\begin{aligned}
 F &= X'Z' + (Y(X'+Z))' \\
 &= X'Z' + Y' + (X'+Z)' && \text{DEMORGANS} \\
 &= X'Z' + Y' + XZ' && \text{DEMORGANS} \\
 &= (X' + X) \cdot Z' + Y' && T8 \\
 &= 1 \cdot Z' + Y' && T5 \\
 \text{POS} &= Z' + Y' && T1'
 \end{aligned}$$

b.

$$\begin{aligned}
 G &= XY + Y'Z' \\
 &= (XY + Y')(XY + Z') && T8' \\
 &= (X + Y')(Y + Y')(X + Z')(Y + Z') && T8' \\
 &= (X + Y')(X + Z')(Y + Z') && T3' \\
 &= (X + Y')(Y + Z') && T11' \\
 \text{POS} &= (X + Y') \cdot (Y + Z')
 \end{aligned}$$

c.

$$\begin{aligned}
 H &= AB \cdot (CD)' + A + D \\
 &= (AB \cdot (C' + D')) + A + D && \text{DEMORGANS} \\
 &= (AB + A + D) \cdot (C' + D' + A + D) && T8' \\
 &= (A(B+1) + D) \cdot (1) \\
 &= (A + D) \cdot 1 && T1' \\
 \text{POS} &= A + D
 \end{aligned}$$

8.

$$\begin{aligned}
 Z &= AB + (C' + A'B')' + A'(AB + AC'D') \\
 &= AB + (C' + A'B')' + A'AB + A'AC'D' && T8 \\
 &= AB + C \cdot (A+B) + 0 + 0 && \text{DEMORGANS, T5'} \\
 \text{SOP} &= AB + AC + BC && T8
 \end{aligned}$$

9.

$$\begin{aligned}
 \text{a. } F &= x'y' + xy'z + z' \\
 &\text{Let us simplify first} \\
 &= y'(x' + xz) + z' \\
 &= y'(x'(z + z') + xz) + z' && T1', T5 \\
 &= y'(x'z + x'z' + xz) + z' && T8
 \end{aligned}$$

$$\begin{aligned}
 &= y'(x'z + x'z + x'z' + xz) + z' && \text{T3 (replicate terms)} \\
 &= y'(x'(z+z') + z(x'+x)) + z' && \text{T8} \\
 &= y'(x' + z) + z' && \text{T5, T1'}
 \end{aligned}$$

Now let us convert to POS using T8'

$$\begin{aligned}
 &= (z'+y')(z' + x' + z) && \text{T8'} \\
 &= (z'+y') && \text{T5, T1'}
 \end{aligned}$$

b. $G = (x'+y')(y)(w'+y+z)$


Convert to SOP using T8 (simplifying as we go)

$$\begin{aligned}
 &= (x'y + y'y)(w' + y + z) && \text{T8} \\
 &= x'y(w' + y + z) && \text{T5'/T1} \\
 &= w'x'y + x'y + x'yz && \text{T8} \\
 &= x'y(w' + 1 + z) && \text{T8} \\
 &= x'y && \text{T2 / T1'}
 \end{aligned}$$

HW4 - Circuit Design w/ Karnaugh Maps


1.

 a. $F = \Sigma_{ABCD}(1,2,4,5,9,10,12,13)$




$$F_{SOP} = \overline{C}D + B\overline{C} + \overline{B}C\overline{D}$$

b. $F = \prod_{MNOP}(0,1,2,8,9)$

 

$$F_{SOP} = N + OP + MO$$

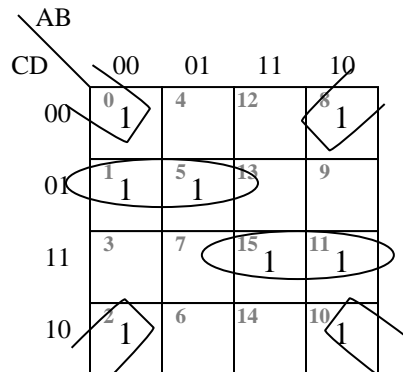c. $F = \Sigma_{ABCD}(0,1,2,5,8,10,11,15)$



$$F_{SOP} = \overline{A}\overline{C}D + A\overline{C}D + \overline{B}\overline{D}$$

d. $F = \prod_{WXYZ} (3,6,7,12,14)$

	WX			
YZ	00	01	11	10
00	0 1	4 1	12 1	8 1
01	1 1	5 1	13 1	9 1
11	3 1	7 1	15 1	11 1
10	2 1	6 1	14 1	10 1

$$F_{SOP} = \overline{W}\overline{Y} + WZ + \overline{X}\overline{Z}$$

2.

a. $F = X'Y' + X'Z' + W'X + XYZ$

	WX			
YZ	00	01	11	10
00	0 1	4 1	12 0	8 1
01	1 1	5 1	13 0	9 1
11	3 0	7 1	15 1	11 0
10	2 1	6 1	14 0	10 1

$$F_{POS} = (W' + X' + Y)(X + Y' + Z')(W' + X' + Z)$$

b. The 4-bit prime numbers are: 2, 3, 5, 7, 11, 13

	AB			
CD	00	01	11	10
00	0 0	4 0	12 0	8 0
01	1 0	5 1	13 1	9 0
11	3 1	7 1	15 1	11 1
10	2 1	6 0	14 0	10 0

$$F_{POS} = (C+D)(B'+D)(A'+D)(A'+B+C)$$

- c. The 4-bit numbers that are not perfect squares or cubes are: 2, 3, 5, 6, 7, 10, 11, 12, 13, 14, 15.

AB \ CD		AB			
		00	01	11	10
CD	00	0 0	4 0	12 1	8 0
	01	1 0	5 1	13 1	9 0
	11	3 1	7 1	15 1	11 1
	10	2 1	6 1	14 1	10 1

$$F_{POS} = (B + C)(A + C + D)$$

- d. The 4-bit numbers divisible by 3 or 5 are: 0, 3, 5, 6, 9, 10, 12, 15

AB \ CD		AB			
		00	01	11	10
CD	00	0 1	4 0	12 1	8 0
	01	1 0	5 1	13 0	9 1
	11	3 1	7 0	15 1	11 0
	10	2 0	6 1	14 0	10 1

$$F_{POS} = (A+B+C+D')(A+B+C'+D)(A+B'+C+D)(A+B'+C'+D')(A'+B+C+D) \cdot (A'+B+C'+D')(A'+B'+C+D')(A'+B'+C'+D)$$

3. The K-Maps are below:


AB \ CD		AB			
		00	01	11	10
CD	00	0	1	1	
	01	1	1	1	1
	11	3	7	15	11
	10	2	6	14	10

$$F_{SOP} = \overline{C}D + \overline{B}C + \overline{B}C\overline{D}$$


		AB			
		00	01	11	10
CD	00	0			0
	01	1	5	13	9
	11	3	7	15	11
	10	2	6	14	10

$$F_{POS} = (\bar{C} + \bar{D})(\bar{B} + \bar{C})(B + C + D)$$


a. AND – OR Implementation

 


b. OR - AND Implementation

 

c. NAND - NAND Implementation

 


d. NOR - NOR Implementation

 

4.

 - a. The values with an odd number of 1s are: 1, 2, 4, 7, 8, 11, 13, 14. The Don't Care numbers are: 0, 4, 5, 8, 10, 12, and 15.




$$SOP = A'C' + BD + AC + B'D'$$

- b. $F = B'C'D' + BCD' + ABC'D$, $d = A'BC'D + A'B'CD'$

$$F = (A+A')B'C'D' + (A+A')BCD' + ABC'D$$

$$= AB'C'D' + A'B'C'D' + ABCD' + A'BCD' + ABC'D$$

$$d = A'BC'D + A'B'CD'$$

 

$$F_{SOP} = B'C'D' + BC'D + BCD'$$

5.

a. $F = A'C + ACE + CAB' + B'A'DE + A'D'E'$

BC DE		00	01	11	10
		00	01	11	10
00	1	1	1	1	1
01	1	1	1	0	
11	1	1	1	0	
10	0	1	1	0	

A=0

BC DE		00	01	11	10
		00	01	11	10
00	0	1	0	0	
01	0	1	1	0	
11	0	1	1	0	
10	0	1	0	0	

A=1

$$F_{SOP} = A'C + A'D'E' + A'B'DE + B'C + CE$$


b. $F = (AB + A'B')(C'D' + CD)$
 $= ABC'D' + A'B'C'D' + ABCD + A'B'CD$

• K-Map:

AB CD		00	01	11	10
		00	01	11	10
00	1		1		
01					
11	1		1		
10					


$$F_{SOP} = ABC'D' + A'B'C'D' + ABCD + A'B'CD$$

- NAND – NAND Implementation

 


c. $F = A'B'C'D' + A'B'CD' + A'BC'D' + A'BC'D + AB'CD'$

- K-Map:

 


$$F_{SOP} = A'C'D' + A'BC' + B'CD'$$

- NAND – NAND Implementation

 


d. The numbers are: 2, 3, 4, 5, 10, 12, 13, 14, 15.

- K-Map:

 

$$\text{SOP} = AB + BC' + A'B'C + ACD'$$



- NAND – NAND Implementation

 

6.

a. $F = A'C + ACE + CAB' + B'A'DE + A'D'E'$


• K-Map:

  

$$F_{POS} = (A' + C')(A' + B' + E)(B' + C + E')(C + D + E')(C + D' + E)$$


b. $F = (AB + A'B')(C'D' + CD)$

• K-Map:

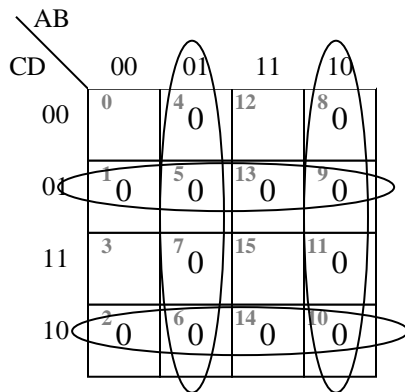


$$F_{POS} = (A + B')(A' + B)(C + D')(C' + D)$$

NOR – NOR Implementation

 


c. $F = A'B'C'D' + A'B'CD' + A'BC'D' + A'BC'D + AB'CD'$

- K-Map:

 


$$F_{\text{pos}} = (B + D')(B' + C')(A' + C)$$

- NOR – NOR Implementation:

 


d. The numbers are: 2, 3, 4, 5, 10, 12, 13, 14, 15.

- K-Map:

 


$$\text{POS} = (B + C)(A + B' + C')(A' + B + D')$$

- NOR – NOR Implementation:

 

7. A and B are both 2-bit signed numbers. They range from -2 to +1. Thus $F = A + B$ is ranging from -4 to +2. We need 3 bits to represent the signed number F.

- a. The block diagram is below:

 


b. The truth table is below:


A1	A0	B1	B0	F2	F1	F0
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	1	1	0
0	0	1	1	1	1	1
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	1	1	1
0	1	1	1	0	0	0
1	0	0	0	1	1	0
1	0	0	1	1	1	1
1	0	1	0	1	0	0
1	0	1	1	1	0	1
1	1	0	0	1	1	1
1	1	0	1	0	0	0
1	1	1	0	1	0	1
1	1	1	1	1	1	0

c.

K-Map of output “F₂”

 

K-Map of output “F₁”

 

$$F2_{SOP} = A_1A_0' + B_1B_0' + A_1B_1 + A_1B_0' + A_0'B_1$$

$$F1_{SOP} = A_1B_1'B_0' + A_1A_0'B_1' + A_1'A_0'B_1 + A_1'B_1B_0' + A_1'A_0B_1'B_0 + A_1A_0B_1B_0$$


K-Map of output “F₀”

A ₁ A ₀		B ₁ B ₀			
		00	01	11	10
00	0	4 1	12 1	8	
	1	5	13	9 1	
01	1	5	13	9 1	
	3 1	7	15	11 1	
11	3 1	7	15	11 1	
	2	6 1	14 1	10	
10	2	6 1	14 1	10	

$$F_{0SOP} = A_0B_0' + A_0'B_0$$

d. AND-OR implementation


Implementation of F₂

 


Implementation of F₁

The implementation consists of four 3-input AND gates, two 4-input AND gates and one 6-input OR gate.

Implementation of F₀

 


NAND – NAND Implementation

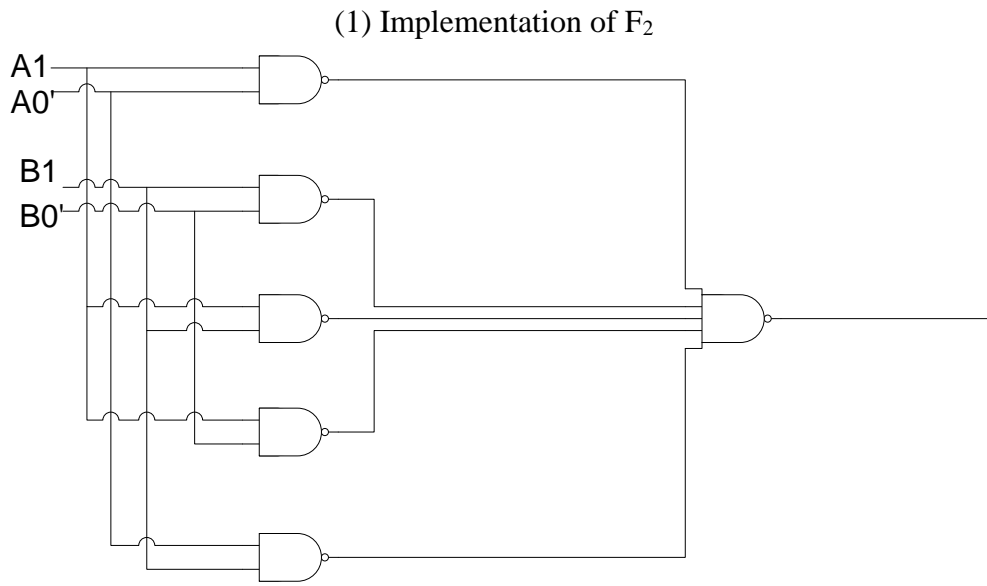

(2) Implementation of F_1


The implementation consists of four 3-input NAND gates, two 4-input NAND gates and one 6-input NAND gate.

(3) Implementation of F_0

 

8. X is a 3-bit unsigned number. It ranges from 0 to 7. Thus $Y = 3X + 1$ is ranging from 1 to 22. We need 5 bits to represent the unsigned number Y.

a. The block diagram is below:

 


b. The truth table is below:

X	X ₂	X ₁	X ₀	Y ₄	Y ₃	Y ₂	Y ₁	Y ₀	Y
0	0	0	0	0	0	0	0	1	1
1	0	0	1	0	0	1	0	0	4
2	0	1	0	0	0	1	1	1	7
3	0	1	1	0	1	0	1	0	10
4	1	0	0	0	1	1	0	1	13
5	1	0	1	1	0	0	0	0	16
6	1	1	0	1	0	0	1	1	19
7	1	1	1	1	0	1	1	0	22


c.

K-Map of output “Y₄”

 


$$Y_{4POS} = X_2(X_1 + X_0)$$

K-Map of output “Y₃”

 


$$Y_{3POS} = (X_2 + X_1)(X_1' + X_0)(X_2' + X_0')$$

K-Map of output “Y₂”

 


$$Y_{2POS} = (X_2 + X_1 + X_0)(X_2 + X_1' + X_0')(X_2' + X_1' + X_0)(X_2' + X_1 + X_0')$$

K-Map of output “Y₁”

 

$Y_{1POS} = X_1$

K-Map of output “Y₀”

 


$Y_{0POS} = X_0'$


d.

- OR – AND Implementation


Implementation of Y₄

 

Implementation of Y₃

 

Implementation of Y_2

 

Implementation of Y_1 (straight wire connection)



Implementation of Y_0 (straight wire connection)




- NOR – NOR Implementation

Convert all gates in the above implementations to NOR gates. For Y_1 and Y_0 just use wires.

e. This will not be covered at this point of the class since we have not yet discussed adders. Ignore this question.

9. X is a 3-bit signed number. It ranges from -4 to +3.
Thus, $Z = X^2 + 2X + 1 = (X + 1)^2$ is ranging from 0 to +16. We need 6 bits to represent signed number Z.

a. The block diagram is below:

 


b. The truth table is below:

X	X ₂	X ₁	X ₀	Z ₅	Z ₄	Z ₃	Z ₂	Z ₁	Z ₀	Z
+0	0	0	0	0	0	0	0	0	1	+1
+1	0	0	1	0	0	0	1	0	0	+4
+2	0	1	0	0	0	1	0	0	1	+9
+3	0	1	1	0	1	0	0	0	0	+16
-1	1	1	1	0	0	0	0	0	0	+0
-2	1	1	0	0	0	0	0	0	0	+1
-3	1	0	1	0	0	0	0	0	0	+4
-4	1	0	0	0	0	1	0	0	1	+9

c.


No K-Map needed for Z₅. “Z₅” = 0

K-Map of output “Z₄”

 

$$Z_{4SOP} = X_2'X_1X_0$$

K-Map of output “Z₃”

 

$$Z_{3SOP} = X_2'X_1X_0' + X_2X_1'X_0'$$

K-Map of output “Z₂”

		X_2X_1			
		X_0	00	01	11
0	0	0	2	6	4
	1	1	3	7	5

$$Z_{2SOP} = X_2'X_1'X_0$$


K-Map of output “Z₀”

		X_2X_1			
		X_0	00	01	11
0	0	1	1	6	1
	1	1	3	7	5

$$Z_{0SOP} = X_2'X_0' + X_1'X_0'$$

Note: Z₁ = 0 (constant)

 10. Design a 1-bit comparator that takes in a bit X and a bit Y and outputs $X < Y$, $X > Y$, $X = Y$. Use a single 2-to-4 decoder and 1 single OR gate.



Consider the truth table of each of these simple functions. We can implement each as a sum of minterms. And since a decoder implements the minterms of the input variables, we can arrive at the circuit above.

X	Y	$X < Y$	$X > Y$	$X == Y$
0	0	0	0	1
0	1	1	0	0
1	0	0	1	0
1	1	0	0	1

5. Consider the following decimal numbers +21, +55, +121, -32, -99, -128
- What are the corresponding 8-bit signed-magnitude representation?.
 - What are the corresponding 8-bit 2's complement representation?.
 - Which of the above numbers can be represented in 6-bit signed-magnitude, 6-bit 1's complement, 6-bit 2's complement representations, explain ?

	21	55	121	-32	-99	-128
A	16+4+1=21 00010101	00110111	01111001	10100000	11100011	NA
B	00010101	00110111	01111001	1110000	10011101	10000000
C	Y,Y,Y 010101 in all cases	N,N,N	N,N,N	N,N,Y 100000 in 2's comp	N,N,N	N,N,N

6. What are the corresponding decimal representations for the following binary numbers: 01011011 , 11010010, if

- The binary numbers are in 8-bit signed-magnitude format?
- The binary numbers are in 8-bit 2's complement format?

	01011011	11010010
a)	64+16+8+2+1=91	-(64+16+2)=-82
b)	64+16+8+2+1=91	-128+64+16+2=-46

7. Perform the following addition problems for the following 2's complement numbers. State whether overflow does or does not occur for each problem. Justify your answer for why overflow does or does not occur. Check your work by converting each number to decimal.

a	$\begin{array}{r} 1010\ 0111 \\ +1110\ 0100 \\ \hline \pm 1000\ 1011 \end{array}$	b	$\begin{array}{r} 1001\ 0110 \\ +1011\ 0011 \\ \hline \pm 0100\ 1001 \end{array}$	c	$\begin{array}{r} 0101\ 1100 \\ +1011\ 0101 \\ \hline \pm 0001\ 0001 \end{array}$	d	$\begin{array}{r} 0101\ 1101 \\ +0110\ 1001 \\ \hline 1100\ 0110 \end{array}$
	$n+n=n$ $\underline{cin=cout=1}$ No Overflow		$n+n=p$ $\underline{cin=0,cout=1}$ Overflow		$p+n=p$ $\underline{cin=cout=1}$ NoOverflow		$p+p=n$ $\underline{cin=1,cout=0}$ Overflow

8. This is an exercise to help you remember what gates are used to create a full adder. Using a full adder as shown below and no other gates, can you produce the function $Z = A \cdot B$ (Hint: Write out the logical equations for S and Cout and see if you can hook up the inputs to produce Z).

ANSWER:

Cin	X	Y	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$S = X \oplus Y \oplus Cin$$


$$Cout = XY + XCin + YCin$$

We want $Z=XY$, and if we set $Cin=0$ then the formulas of S and Cout becomes as follows:

$$S = X \oplus Y$$

$$Cout = XY$$

Thus, $Cout = Z = XY$

 

9. Using 1 half-adder and a minimal number of 4-bit binary adders, design a circuit to calculate $Y = 25 \cdot X$, where X is a 4-bit inputs.

ANSWER:

If a number is multiplied by a number that is a power of 2, then the number rewritten using the above formula:

$$2^n X = X 0 \dots 0$$

$$Y = 25 \cdot X = 16 \cdot X + 8 \cdot X + X = X0000 + X000 + X$$

Also adding the information that X is a 4-bit number above formula can be re-written


$$X = X_3 X_2 X_1 X_0$$

$$Y = X_3 X_2 X_1 X_0 0000 + X_3 X_2 X_1 X_0 000 + X_3 X_2 X_1 X_0$$

This can be written as addition by 4 bit adders:

					X_3	X_2	X_1	X_0
					X_3	X_2	X_1	X_0
					X_3	X_2	X_1	X_0
+	X_3	X_2	X_1	X_0	0	0	0	0

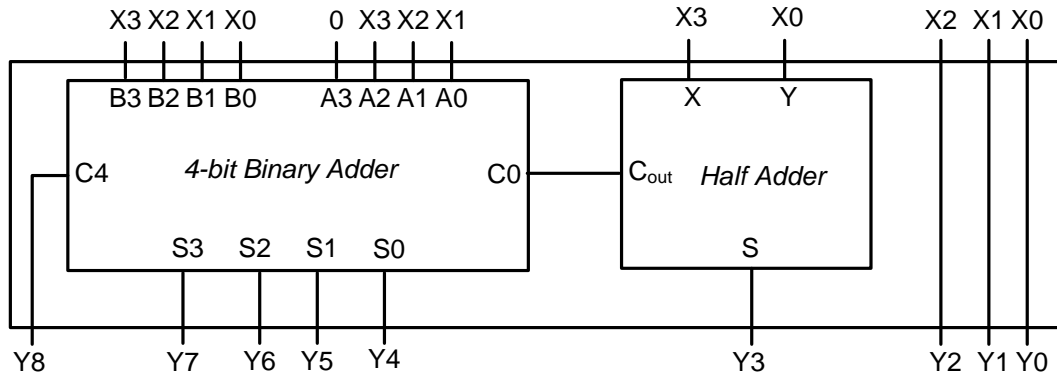Since one row in each addition is all zeros, they can be eliminated and the other two numbers can be added using a 4-bit adder. However, the lower bits require only a single bit adder. The carry from the first addition is transferred to the next one.



10. Using a minimal number of 4-bit adders, design a circuit that implements $Y=20*X+107$, where X is a 3-bit unsigned number.


ANSWER:

$X = X_2X_1X_0$, and thus $20*X = 16*X + 4*X$. These numbers are achieved by inserting zeros at the end. Once we add these three numbers, we see that not all bits require addition. We actually need only a single 4-bit adder and nothing more.

$$\begin{array}{rcccccccc}
 & & & & 1 & & 1 & & 0 & & 1 & & 0 & & 1 & & 1 \\
 & & & & & & & & X_2 & & X_1 & & X_0 & & 0 & & 0 \\
 + & & & & X_2 & & X_1 & & X_0 & & 0 & & 0 & & 0 & & 0 \\
 \hline
 \end{array}$$

Which can be collapsed to the following addition:
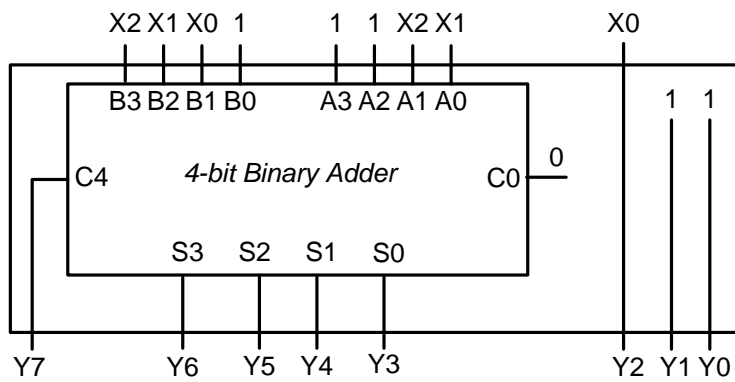
$$\begin{array}{rcccccccc}
 & & & & 1 & & 1 & & X_2 & & X_1 & & X_0 & & 0 & & 0 \\
 + & & & & X_2 & & X_1 & & X_0 & & 1 & & 0 & & 1 & & 1 \\
 \hline
 \end{array}$$



11. Design a minimal circuit using AND/OR/NOT gates to implement the comparison $A > 10$ where A is a 4-bit number.

- Start by writing out the logical algorithm for when $A > 10$ then implement it using gates
- Check that your work is minimal by using a K-Map.

ANSWER:

Let's assume that the number $A = A_3A_2A_1A_0$.

Logical Algorithm: For any number A to be greater than a number B (in this case $10_{10} = 1010_2$), a more significant bit of A must be greater than B . However, in the case of A compared with 1010 , we realize A_3 and A_1 can never be greater than the 1's in those places for 10 . Similarly, A_2 and A_0 can never be less than the 0's in those places. Thus for $A > 10$, there are only 2 cases that need to be checked:

$$A_3 = 1 \text{ and } A_2 > 0 \text{ (i.e. } A_2 = 1)$$

OR

$$A_3=1 \text{ and } A_1 = 1 \text{ and } A_0 > 0 \text{ (i.e. } A_0 = 1).$$


$$\text{Thus } A > 10 = A_3A_2 + A_3A_1A_0.$$

Note that we don't have to check A_2 in the second case because it is DEFINITELY greater than or equal to the 0 in that place of 1010_2 .

A K-Map will also show the same equation $\text{SUM}(11,12,13,14,15)$.


		A_3A_2			
		00	01	11	10
A_1A_0	00	0	4	12 1	8
	01	1	5	13 1	9
	11	3	7	15 1	11 1
	10	2	6	14 1	10

$$A > 10 = A_3A_2 + A_3A_1A_0$$

 

HW 6 – Latches, and Flip-Flops

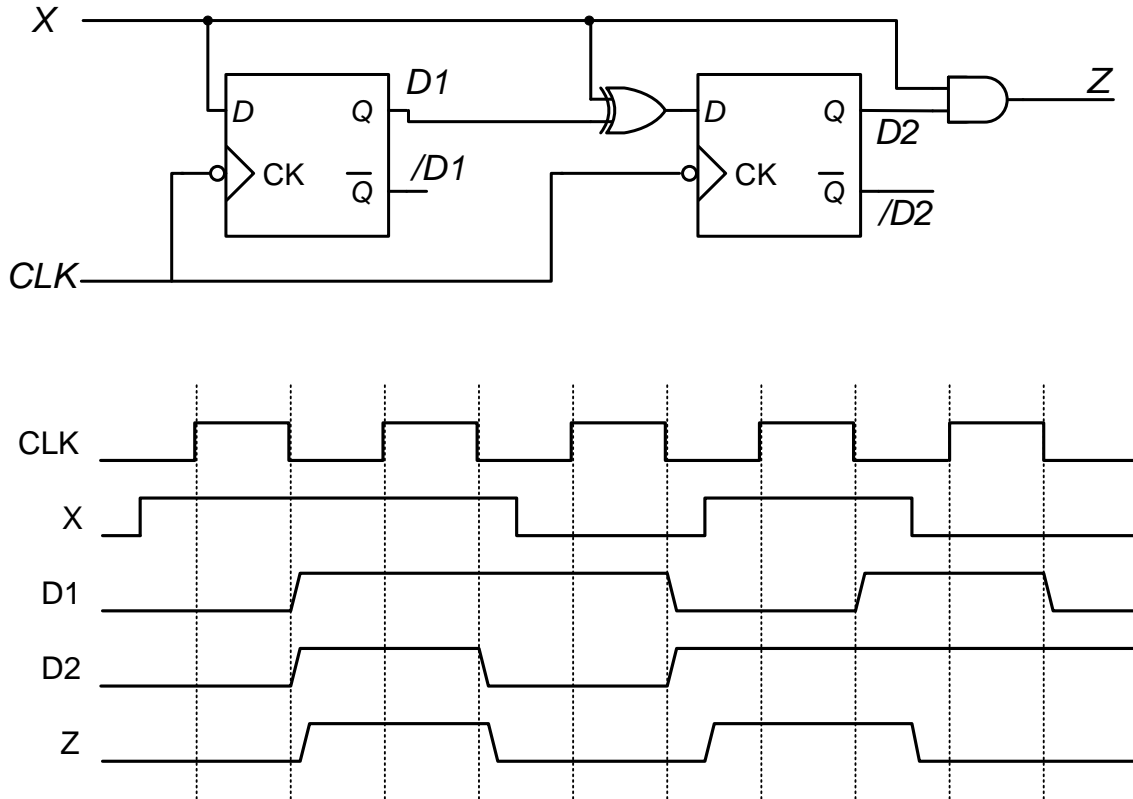- Complete the following waveforms for negative edge-triggered D Flip-Flops.



- We should find the state diagram following the steps in the class notes
 - Convert the diagram to a table.

Current State		Next State								Output
		XY= 00		XY= 01		XY= 10		XY= 11		
Q ₁	Q ₀	Q ₁ *	Q ₀ *	Q ₁ *	Q ₀ *	Q ₁ *	Q ₀ *	Q ₁ *	Q ₀ *	Z
0	0	0	0	0	0	1	0	1	0	0
0	1	0	0	0	0	0	1	0	1	1
1	0	0	0	0	1	0	0	0	1	0
1	1	0	0	0	1	0	1	0	1	0

Convert Q^* to D


Current State		Next State								Output
		XY= 00		XY= 01		XY= 10		XY= 11		
Q_1	Q_0	D1	D0	D1	D0	D1	D0	D1	D0	Z
0	0	0	0	0	0	1	0	1	0	0
0	1	0	0	0	0	0	1	0	1	1
1	0	0	0	0	1	0	0	0	1	0
1	1	0	0	0	1	0	1	0	1	0

b. Perform K-maps to find equations for D1 and D0.

$$D_0 = Q_1 \cdot Y + Q_0 \cdot X$$

$$D_1 = Q_1' \cdot Q_0' \cdot X$$

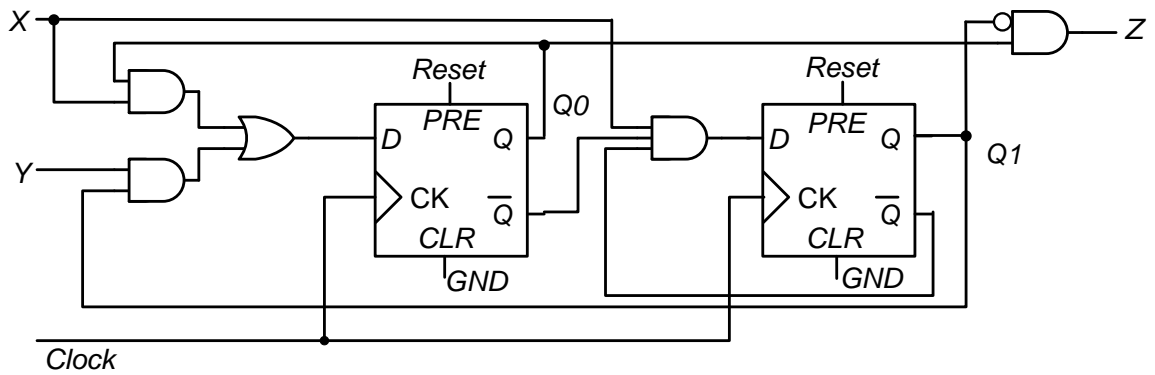c. Draw the circuit and implement the initial state (reset) condition.



3. Because we have 2 states in the state diagram, we use one D flip-flop to implement state memory. We design the combinational logic for the next-state logic and the output function logic by building up the state/transition table.

Current State	Next State / Output				H
	XY = 00	XY = 01	XY = 10	XY = 11	
Symbol/Code	Symbol/Code	Symbol/Code	Symbol/Code	Symbol/Code	
F / 0	F / 0	G / 1	G / 1	G / 1	0
G / 1	F / 0	F / 0	F / 0	G / 1	1
Q0(t)	Q0*	Q0*	Q0*	Q0*	
	D0	D0	D0	D0	

After we get the state/transition table, we build the K-Maps to simplify expressions for D0, and H.

- D₀ K-Map:

XY Q ₀		00	01	11	10
		0	1	1	1
		1	1	1	

$$D_0 = YQ_0' + XQ_0' + XY$$

$$H = Q_0$$

4.

Current State	Next State & Flop-Flop Inputs		Outputs
	Next State	Next State	
	X = 0	X = 1	
Symbol/Code	Symbol/Code	Symbol/Code	Z
A/00	B/01	D/11	0
B/01	C/10	B/01	0
C/10	B/01	A/00	1
D/11	B/01	C/10	0

$Q_1(t), Q_0(t)$ $Q_1^*(t+1), Q_0^*(t+1)$ $Q_1^*(t+1), Q_0^*(t+1)$

After we get the state/transition table, we build the K-Maps to simplify expressions for D1, D0, and Z.

• D1 K-Map:

		X	
		0	1
Q ₁ Q ₀	00	0	1
	01	1	0
	11	0	1
	10	0	0

$$D_1 = X'Q_1'Q_0 + XQ_1'Q_0' + XQ_1Q_0$$

D0 K-Map

		X	
		0	1
Q ₁ Q ₀	00	1	1
	01	0	1
	11	1	0
	10	1	0


$$D_0 = X'Q_1 + X'Q_0' + XQ_1'$$

Z K-Map:

		Q ₁	
		0	1
Q ₀	0	0	1
	1	0	0

$$Z = Q_1Q_0'$$


a. The waveform is below:

 

- 5.
- a. We need 4 states and each of them stores one 2-bit binary number ranging from 00 to 11.

State	S0	S1	S2	S3
Assignment (Q ₁ Q ₀)	00	01	10	11

The state diagram is below:

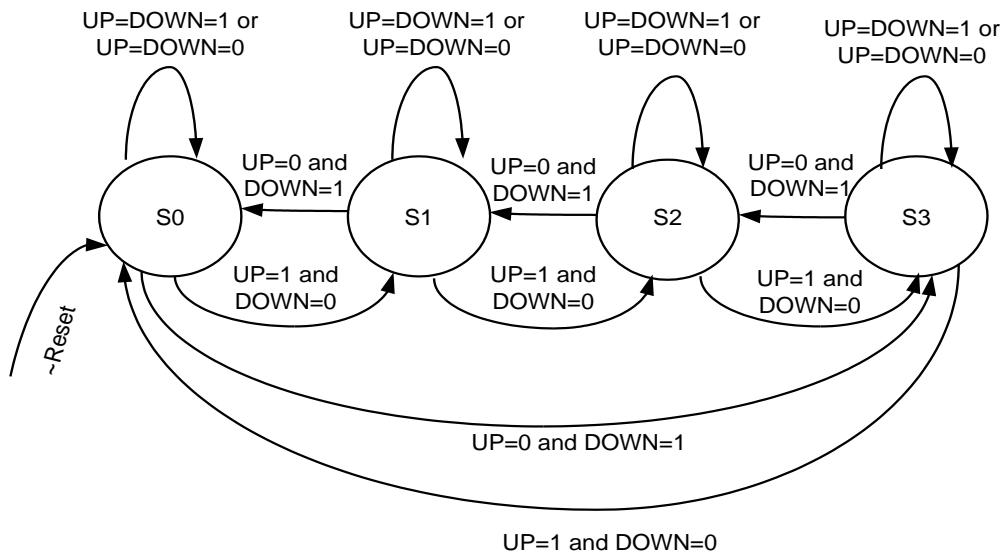

- b. Because we have 4 states in the state diagram, we use two D flip-flops to implement state memory. We design the combinational logic for the next-state logic and the output function logic by building up the state/transition table.

U – UP, D – DOWN

Current State	Next State			
	U·D = 00	U·D = 01	U·D = 10	U·D = 11
Symbol/Code	Symbol/Code	Symbol/Code	Symbol/Code	Symbol/Code
S0/00	S0/00	S3/11	S1/01	S0/00
S1/01	S1/01	S0/00	S2/10	S1/01
S2/10	S2/10	S1/01	S3/11	S2/10
S3/11	S3/11	S2/10	S0/00	S3/11
Q ₁ (t),Q ₀ (t)	Q ₁ (t+1),Q ₀ (t+1) D ₁ ,D ₀	Q ₁ (t+1),Q ₀ (t+1) D ₁ ,D ₀	Q ₁ (t+1),Q ₀ (t+1) D ₁ ,D ₀	Q ₁ (t+1),Q ₀ (t+1) D ₁ ,D ₀

After we get the state/transition table, we build the K-Maps to simplify expressions for D₁, and D₀.

- D₁ K-Map:

		UD			
		00	01	11	10
Q ₁ Q ₀	00	0	4 1	12	8
	01	1	5	13	9 1
	11	6 1	7 1	15 1	11
	10	2 1	6	14 1	10 1


$$D_1 = U' \cdot D' \cdot Q_1 + D \cdot Q_1 \cdot Q_0 + U \cdot Q_1 \cdot Q_0' + U' \cdot DQ_1' \cdot Q_0' + U \cdot D' \cdot Q_1' \cdot Q_0$$

- D₀ K-Map:


		UD			
		00	01	11	10
Q ₁ Q ₀	00	0	4 1	12	8 1
	01	1 1	5	13 1	9
	11	6 1	7	15 1	11
	10	2	6 1	14	10 1

$$D_0 = U' \cdot D' \cdot Q_0 + U \cdot DQ_0 + U' \cdot DQ_0' + U \cdot D' \cdot Q_0'$$


c. The waveform is below:

 

 6. Complete the waveform for the 4-bit counter presented in class.



 7. Complete the waveform for a 4-bit D-Register with Data (Load) Enable and asynchronous reset.




8.1. Unit 7 – Datapath Design

1. Implement a circuit that takes in a 4-bit number $X[3:0]$ and produces a 4-bit value $Z[3:0]$ according to the following function:

if $X < 8$ *then*
 $Z = X + 5;$
else
 $Z = X - 2;$

Using the building blocks below and at most 1 inverter (no other gates), implement this function.

Note: To check $X < 8$, subtract $X - 8$ by taking the 2's complement of 8. The 2's comp. of 8 is $0111 + 1$. Recall, a carry of 0 when subtracting unsigned numbers ($A - B$) indicates overflow which can only occur in unsigned subtraction if the result needed to be negative (i.e. $A < B$). So C_4 will only be 1 if X is not less-than 8. We can invert it to get a signal that is true when $X < 8$. Use those signals to either add 5 (0101) or subtract 2 (add 1110).

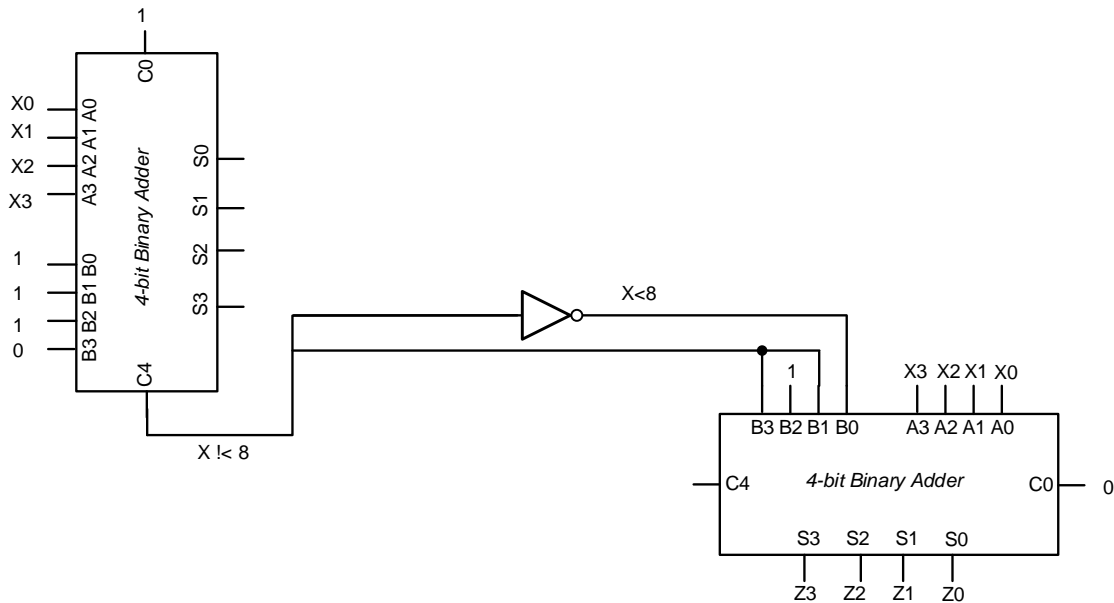


2. Design a circuit that takes in a 4-bit number $X[3:0]$ and outputs a number Y , and performs the operation below. Assume these numbers are unsigned. Use a 4-bit adder and 2-to-1 muxes. Hint: Multiplying by 4 (i.e. 2^2) in binary can be done with no gates just as multiplying by 100 (i.e. 10^2) in decimal can be done simply and easily.

```

if( $X < 0011_2$ )
     $Y = 4X$ 
else
     $Y = X$ 

```

 $4X$ would require 6 outputs and be $X_3 X_2 X_1 X_0 0 0$, thus even if we pass X we need to produce 6 outputs. Recall subtracting $3=0011$ bin. is the same as adding the 2's complement. Next, a carry of 0 when subtracting unsigned numbers ($A-B$) indicates overflow which can only occur in unsigned subtraction if the result needed to be negative (i.e. $A < B$)




3. Design a circuit that takes in two 4-bit numbers, $X[3:0]$ and $Y[3:0]$ along with two function select bits, $FS1$ and $FS0$, and produces an output, $Z[3:0]$, according to the following table:

$FS1, FS0$	Z
0,0	$X+Y$
0,1	$X-Y$
1,0	$Y-X$
1,1	don't care

Use (1) 4-bit adder, 4-bit wide 2-to-1 muxes, and any basic gates you desire.

Approach: Take a 4-bit adder and for each operation listed in the table above identify what should be passed to the A and B inputs of the adder. Then use muxes to perform that function. Design logic for the select bits of the muxes and the carry-in of the adder that use $FS1$ and $FS0$ as input.

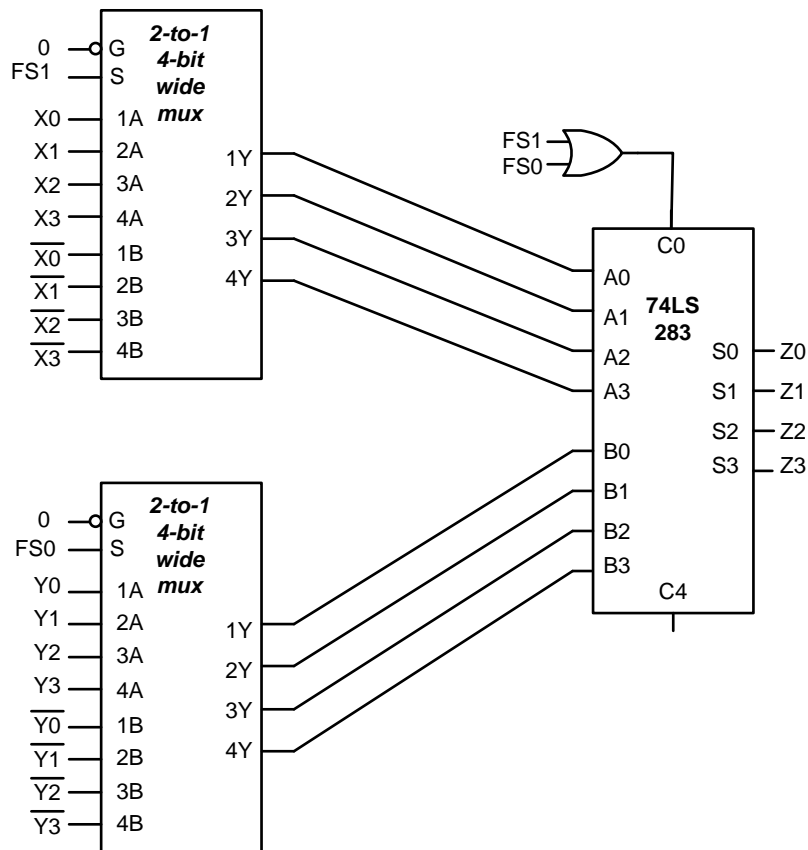Note: In the solution below the A and B inputs of the muxes are like the 0th and 1st inputs of 4 2-to-1 muxes, respectively. Ignore the G input.




4. Design a circuit that takes in two 4-bit **signed magnitude** numbers, $X[3:0]$ and $Y[3:0]$ and produces two 4-bit outputs, $A[3:0]$ and $B[3:0]$ according to the following algorithm:

if $X \geq Y$ *then*
 $A = X$ *and* $B = Y$
else
 $A = Y$ *and* $B = X$


Use a 4-bit adder to subtract and perform the comparison, 4-bit wide 2-to-1 muxes, and basic logic gates. Assume the input $1000 = -0$ will never occur on X or Y .

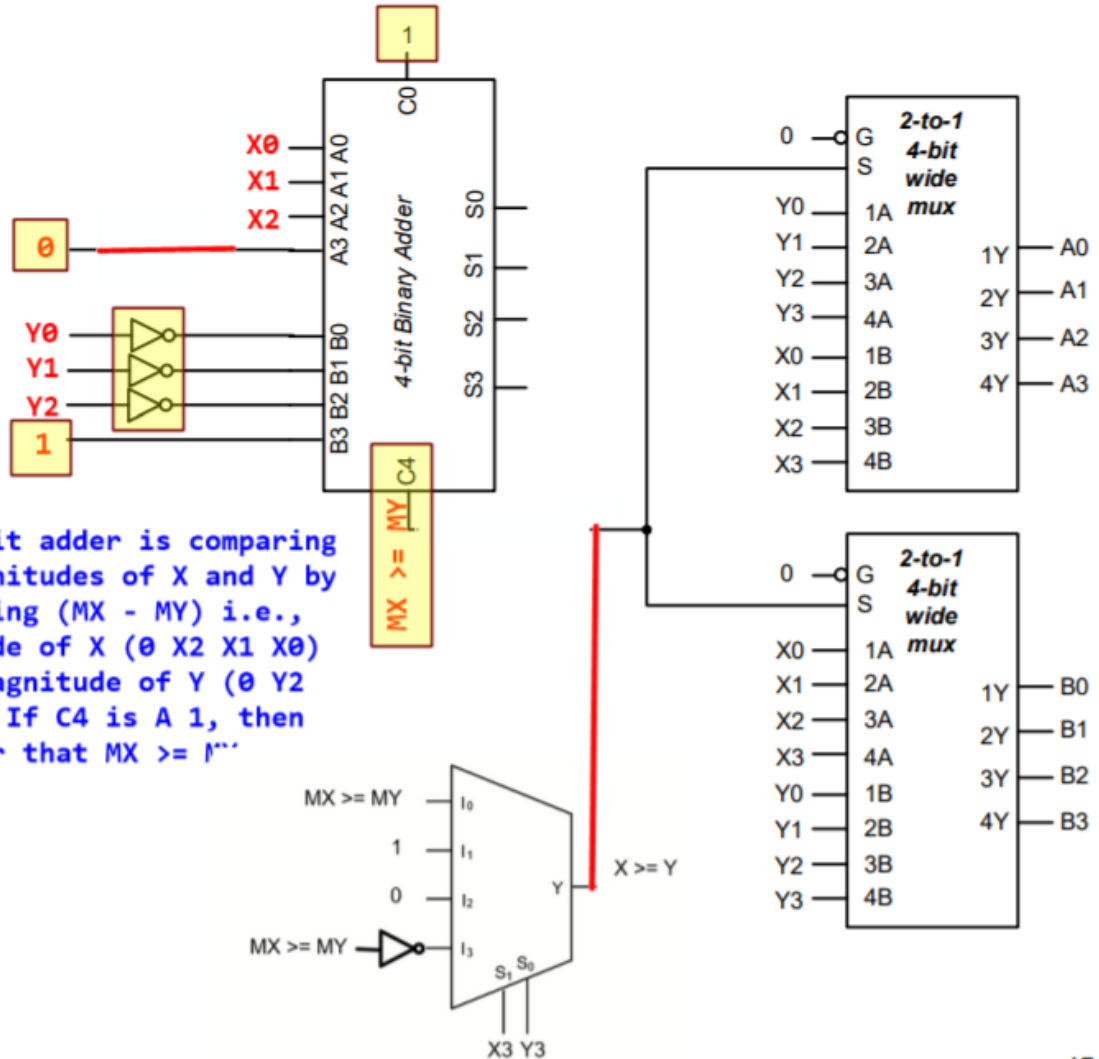Approach: First think about how to compare signed magnitude numbers by using unsigned comparison techniques and how to precondition the inputs to allow the use of unsigned comparison. For example, $1001 = -1$ in signed magnitude and $0100 = +4$ in signed magnitude. So 1001 is really less than 0100 . Use the comparison result to control the selects of the muxes.



 5. Design a circuit that adds two 4-bit, unsigned numbers: $X[3:0]$ and $Y[3:0]$ and outputs either the sum if there is no overflow or 1111 ($=15_{10}$, the maximum unsigned 4-bit number) if there is overflow.

Unsigned overflow is found by looking at C_{out} . You could use a mux to select the sum or 1111 but realize you can just use OR gates for this function.




1. We would like to build an adder whose inputs are in units of pennies and produces sum in nickels and pennies. Essentially, this is a base-5 adder. The 2 inputs of this adder are $A = \{A_2 A_1 A_0\}$ and $B = \{B_2 B_1 B_0\}$. Assume that the maximum input number that A and B can be is 4 pennies. Design an adder to produce the correct nickels/pennies sum, $C = \{ [C_N] ; [C_{P2} C_{P1} C_{P0}] \}$. To implement this design you may assume you can use as many 4-bit adders as you like.

if $X+Y > 4$ dec. then


$$C_N = 1, CP[2:0] = X+Y-5$$

else

$$C_N = 0, CP[2:0] = X+Y$$

 


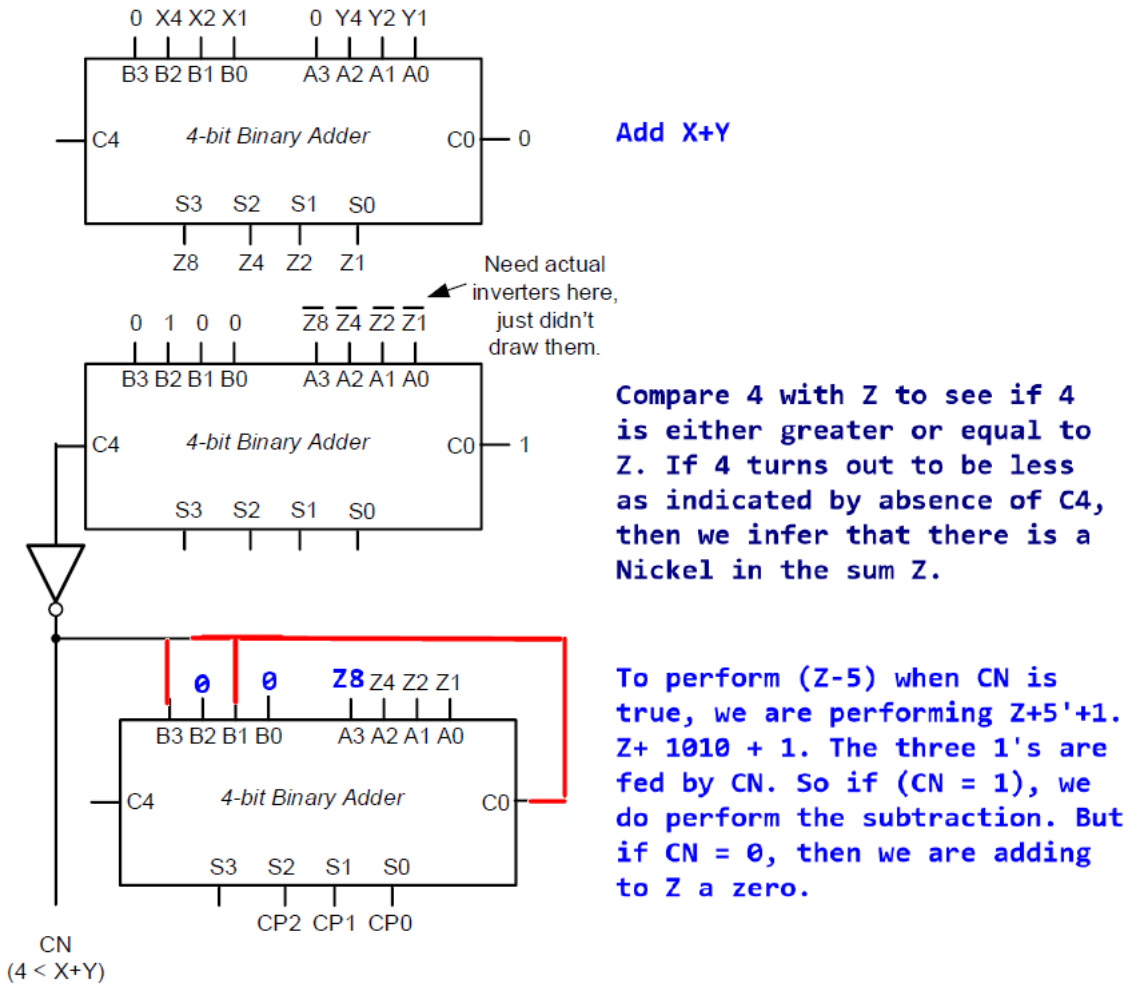*Block diagram for the
nickel/penny adder you
are going to design*



See below for some alternate implementations and simplifications.

Now, noting that the final 4-bit adder really only produces a 3-bit output, we can substitute and use a 3-bit adder in its place...OR...simplify the 4-bit adder shown. Since the 4-bit adder does not utilize the S3 nor C4 output, we can simply and not connect A3, B3 since they will only affect S3 and C4 to arrive at the design below (which uses B0 rather than C0 for the +1 when taking the 2's complement).

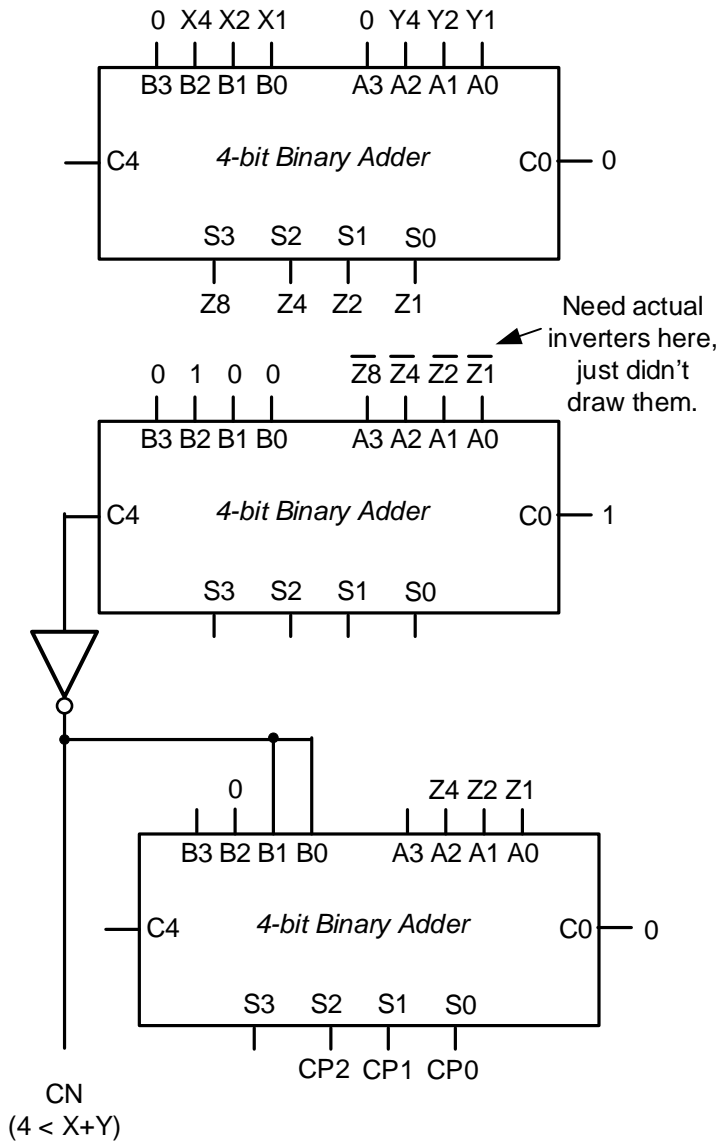

Another approach using a mux rather than a 3rd adder is also shown (and also compares $(X+Y) \geq 5$ rather than $4 < (X+Y)$)

