

EE 109 Homework 1

Name: _____

Due: _____

Score: _____

Neatly show your work to get full credit and clearly show your final answer.

1.) [5 pts.] Use KCL to solve for I_0 .


$$\sum_{i=1}^n I_i(\text{node}) = 0 \rightarrow -3 - 2 + 7 + 6 + I_0 = 0$$

$$\rightarrow I_0 = -8^A$$

Another approach:

$$\sum I_{in}(\text{node}) = \sum I_{out}(\text{node})$$
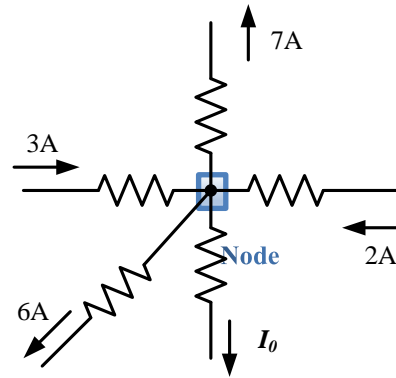
$$\rightarrow 3 + 2 = 7 + 6 + I_0 \rightarrow I_0 = -8^A$$




2.) [8 pts.] Use KVL to solve for V_1 and V_2 .

$$\sum_{i=1}^n v_i(\text{loop}) = 0 \rightarrow$$

$$1) -15 + v_1 + 6 - 2 = 0 \rightarrow v_1 = 11^v$$
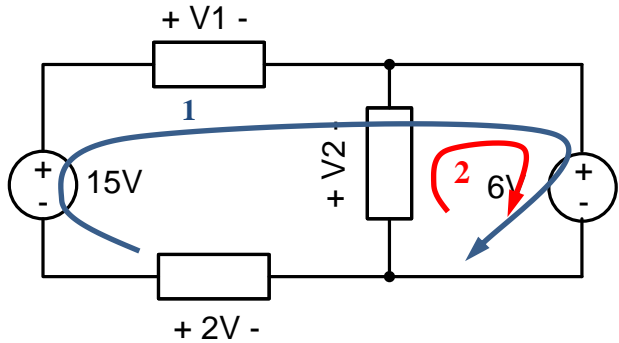
$$2) +v_2 + 6 = 0 \rightarrow v_2 = -6^v$$



3.) [9 pts.] Solve for the currents i_1, i_2, i_3 .

$$\sum_{i=1}^n I_i(@ \text{node } 1) = 0 \rightarrow$$


$$-6 + 5 + i_2 = 0 \rightarrow i_2 = 1^A$$

$$\sum_{i=1}^n I_i(@ \text{node } 2) = 0 \rightarrow$$

$$+6 - 10 - i_1 = 0 \rightarrow i_1 = -4^A$$

$$\sum_{i=1}^n I_i(@ \text{node } 3) = 0 \rightarrow$$
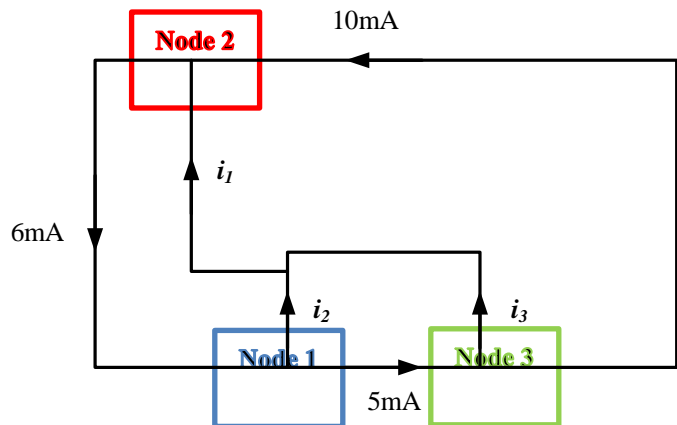
$$-5 + i_3 + 10 = 0 \rightarrow i_3 = -5^A$$




4.) [9 pts.] Solve for the voltages V1, V2, V3

$$\sum_{i=1}^n v_i(\text{loop}) = 0 \rightarrow$$

$$1) -10 + v_1 + 4 = 0 \rightarrow v_1 = 6^v$$

$$2) -3 - 10 + v_1 + v_3 + 5 = 0 \rightarrow v_3 = 2^v$$
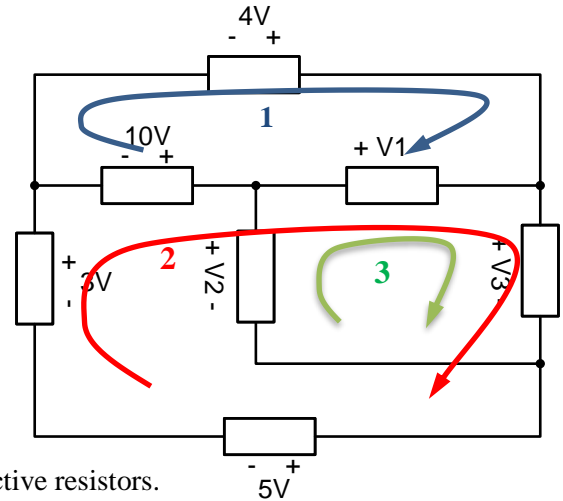
$$3) -v_2 + v_1 + v_3 = 0 \rightarrow v_2 = 8^v$$




5.) [9 pts.] Solve for the voltages V1, V2, V3 across the respective resistors.

$$\sum_{i=1}^n v_i(\text{loop}) = 0 \rightarrow$$

$$1) -v_3 + 9 = 0 \rightarrow v_3 = 9^v$$


$$2) -v_2 + v_3 + 4 = 0 \rightarrow v_2 = 13^v$$
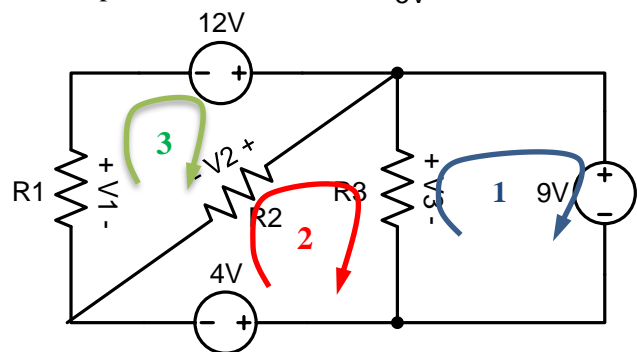
$$3) -v_1 - 12 + v_2 = 0 \rightarrow v_1 = 1^v$$



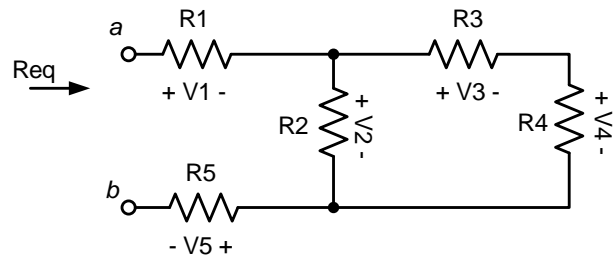
6.) [10 pts.] Reduce the resistor network shown below to a single equivalent resistance. Leave your answer in terms of R1, R2, R4, R5, and R6.

$$\begin{aligned} R_{eq} &= R1 + [R2 \parallel (R3 + R4)] + R5 \\ &= R1 + \frac{R2 \cdot (R3 + R4)}{R2 + R3 + R4} + R5 \\ &= 3 + \frac{4 \cdot (4)}{4 + 2 + 2} + 1 = 6\Omega \end{aligned}$$



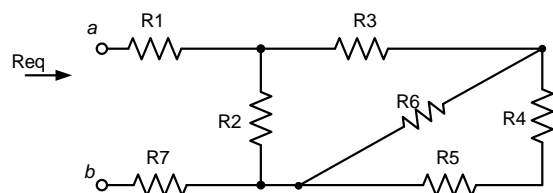7.) [10 pts.] Reduce the resistor network shown below to a single equivalent resistance assuming the following resistor values: R1=5Ω, R2=4Ω, R3=3Ω, R4=1Ω, R5=1Ω, R6=2Ω, R7=7Ω.
Hint: Start by combining R4 and R5 then combine those with R6 and keep going...

$$\begin{aligned} R_{eq} &= R1 + [R2 \parallel (R3 + (R6 \parallel (R4 + R5)))] + R7 \\ R_{eq} &= R1 + [R2 \parallel (R3 + (2 \parallel (2)))] + R7 \\ R_{eq} &= R1 + [R2 \parallel (3 + (1))] + R7 \\ R_{eq} &= R1 + [4 \parallel (4)] + R7 \\ R_{eq} &= R1 + [2] + R7 = 5 + 2 + 7 = 14\Omega \end{aligned}$$



- 8.) [8 pts.] Find an expression for the current i_1 if $R_1=4\Omega$, $R_2=3\Omega$, $R_3=6\Omega$, $R_4=2\Omega$.
Hint: Combine R_2 , R_3 , R_4 into an equivalent resistance which will be in series with R_1 . From here you can use a KVL loop or Ohm's law to solve for i_1 .


$$\sum_{i=1}^n v_i(\text{loop}) = 0 \rightarrow$$

$$-20 + R_1 \cdot i_1 + (R_2 \parallel R_3 \parallel R_4) \cdot i_1 = 0$$

When 3 or more resistors are in parallel you can work with 2 at a time.

$$i_1 = \frac{20}{R_1 + ((R_2 \parallel R_3) \parallel R_4)}$$
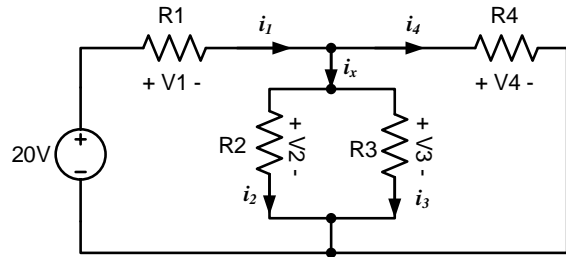
$$i_1 = \frac{20}{4 + ((3 \parallel 6) \parallel 2)} = \frac{20}{4 + \left(\left(\frac{18}{9}\right) \parallel 2\right)} = \frac{20}{4 + \left(\frac{2 * 2}{2 + 2}\right)} = \frac{20}{5} = 4A$$




- 9.) [16 pts.] Use the generalized concept of a voltage divider (review your notes/lecture slides) to find expressions for the voltage V_1 and also V_4 in the circuit below. Your expression should be in terms of V_s and R_1 - R_4 .

$$i_{R1} = i_{R4} = \frac{v(s)}{R_1 + R_2 \parallel R_3 + R_4}$$

$$= \frac{v(s)}{R_1 + \frac{R_2 \cdot R_3}{R_2 + R_3} + R_4}$$

$$V_1 = R_1 \cdot i_{R1} = R_1 \cdot \frac{v(s)}{R_1 + \frac{R_2 \cdot R_3}{R_2 + R_3} + R_4}$$
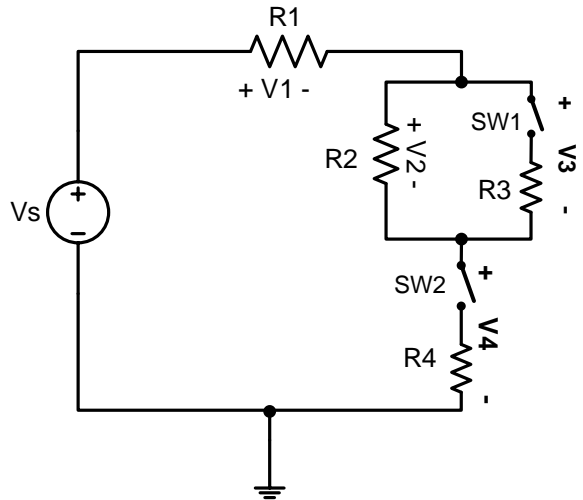
$$V_4 = R_4 \cdot i_{R4} = R_4 \cdot \frac{v(s)}{R_1 + \frac{R_2 \cdot R_3}{R_2 + R_3} + R_4}$$



- 10.) [6 pts.] Look at the circuit from problem 9. If SW_2 is open and SW_1 closed, what would V_4 be (approximately)?

Since SW_2 is in series with R_4 , their resistance can be summed. When a switch is open (not-connected) they can be modeled as an INFINITE resistance. Thus infinity + R_4 = infinity.

$$\begin{aligned}\lim_{R4 \rightarrow \infty} V4 &= \lim_{R4 \rightarrow \infty} R4 \cdot \frac{v(s)}{R1 + \frac{R2 \cdot R3}{R2 + R3} + R4} = \infty \cdot \frac{v(s)}{\left(R1 + \frac{R2 \cdot R3}{R2 + R3} + \infty\right)} \\ &= \infty \cdot \frac{v(s)}{\left(R1 + \frac{R2 \cdot R3}{R2 + R3} + \infty\right)} = \frac{\infty}{\infty} \cdot v(s) = 1 * v(s) = v(s)\end{aligned}$$

11.) [5 pts.] Look at the circuit from problem 9. If SW2 is open and SW1 closed, what would V4 be (approximately)?

Since SW1 is in series with R3, their resistance can be summed. When a switch is open (not-connected) they can be modeled as an INFINITE resistance. Thus infinity + R3 = infinity

$$\begin{aligned}\lim_{R3 \rightarrow \infty} V4 &= \lim_{R3 \rightarrow \infty} R4 \cdot \frac{v(s)}{R1 + \frac{R2 \cdot R3}{R2 + R3} + R4} = R4 \cdot \frac{v(s)}{R1 + \frac{R2 \cdot \infty}{R2 + \infty} + R4} = R4 \cdot \frac{v(s)}{R1 + \frac{R2 \cdot \infty}{\infty} + R4} \\ &= R4 \cdot \frac{v(s)}{R1 + R2 + R4}\end{aligned}$$

Note: This is the appropriate voltage divider equation had R3 been removed altogether. Thus as a resistance becomes large and is in parallel with others, it's as if it's not even there.

12.) [5 pts.] Look at the circuit from problem 9. With SW1 and SW2 closed, if R3 is effectively 0Ω (i.e. replaced by a wire), solve (approximately) for the voltage V4.

$$V4 = R4 \cdot \frac{v(s)}{R1 + \frac{R2 \cdot R3}{R2 + R3} + R4} \rightarrow V4(R3 = 0) = R4 \cdot \frac{v(s)}{R1 + R4}$$

Note: This is the appropriate voltage divider equation had R2 and R3 been removed completely. Thus as a resistor in parallel becomes small it's as if neither resistor is present.