

EE 109 Homework 3 Minterms/Maxterm/K-Maps

Name: _____

Due: See Website

Score: _____

Please post any questions regarding HW problems on Piazza.

HW 3a Blackboard Form – Answer on Blackboard

1. **[BB] (16 pts.)** Derive the truth table for the following functions [One basic approach is to simply plug in each combination and evaluate the expression]. (Note: ' means NOT and unless there is parentheses around an expression the ' only applies to the single variable to its left).
 - a. $F = (A'+B')(C)$
 - b. $G = WX' + XY' + W'$

2. **[BB] (7 pts.)** Implement the following functions

Meaning	Color Bit Combinations		
	C2	C1	C0
Red	0	0	0
Orange	0	0	1
Yellow	0	1	0
Green	0	1	1
Blue	1	0	0
Indigo	1	0	1
Violet	1	1	0
Unused	1	1	1

- a. Build appropriate single gate (+ inverters) checker/decoders that outputs a logic '1' for each of the three primary colors: **Red, Blue, Yellow** (i.e. one decoder to check for each color)

- b. Build an appropriate single gate (+inverters) checker/decoder that outputs a logic '0' for each color: **Green, Blue, Indigo, Violet**.

3. **[BB] (6 pts.)** Given a child's age [0-7 years old], design logic to produce the following outputs: {**Baby, Toddler, Preschool, Kinder, Grade1, Grade2**} which have the following age correspondence/mapping. Use only 1 AND gate (and any number of inverters) per output.

Meaning	Age Combinations		
	A2	A1	A0
Baby	0	0	0
	0	0	1
Toddler	0	1	0
	0	1	1
Preschool	1	0	0
Kindergarten	1	0	1
Grade1	1	1	0
Grade2	1	1	1

4. **[BB] (5 pts.)** Given a 4-bit, unsigned input (A[3:0]) design a logic function, H, using a sum of minterms approach which outputs '1' if the input number is a multiple of 3 (i.e. A[3:0] is in the set {0₁₀, 3₁₀, 6₁₀, ...}). Write out the algebraic (equation using ANDs, ORs, and NOTs) form of the minterm representation for H (do not simplify).
5. **[BB] (5 pts)** Write out the algebraic (equation using ANDs, ORs, and NOTs) form of the sum of minterms representation for G (do not simplify...just keep the minterms as is).
- $$G = \sum_{A,B,C,D} (2,3,6,13,15)$$
6. **[BB] (5 pts.)** Now simplify the result you found from the previous problem to a minimal SOP expression.
7. **[BB] (6 pts.)** Use the theorems of Boolean algebra to find the minimal expression in the indicated form for each of the following logic functions:
- Convert to minimal POS:** $F = X + [(W'Y'Z)(W + (X'(Y+Z)))]$
 - Convert to minimal SOP:**
- $$G = (\overline{w + x + \bar{y}}) + w\bar{x}y + (w\bar{z} + x\bar{y}) \cdot \overline{(x(\bar{w} + z))}$$

HW 3b – Submit on BB

8. **[Practice Only...Do not submit]** Using only 2-input NOR gates (as many as you like for each part), build a circuit that is equivalent to the following circuits. [Hint: Connecting a signal to both inputs of a gate is acceptable.]
- An inverter (Input x and output x')
 - 2-input AND gate (Inputs: x, y and output F = x and y)
 - 2-input OR gate (Inputs: x, y and output F = x or y)
 - Could a, b, and c, be accomplished using only NAND gates: Yes or No?

9. [BB] (50 pts.) Using a Karnaugh map, find both the minimal POS and SOP expression for each of the following functions (both for each).

a. $F = \sum_{ABC} (0,2,4,7)$

b. $G = \prod_{WXYZ} (2,3,7,8,11,12,14,15)$

c. $H(w,x,y,z)$ such that $H = 1$ for input combinations divisible by 2 or 3
($w,x,y,z=0000$ is divisible by 2 and 3).

10. [Practice Only] (0 pts.) Draw the specified implementation schematics.

a. AND-OR implementation for 9a.

b. NOR-NOR implementation for 9b.

c. NAND-NAND implementation for 9c.