


# EE 109 Homework 6

Name: Solutions


Due: \_\_\_\_\_

Score: \_\_\_\_\_

 
1. [BB] Complete the following waveform for a D-Latch with active-high clock (Q responds to D when C=1). Remember latches are level sensitive. To enter your answer online, select which transitions of the clock, C, or the D-input (indicated by a timestamp) will cause Q to toggle (i.e. change from 0 to 1 or 1 to 0). If Q doesn't change do not enter that timestamp as an answer.



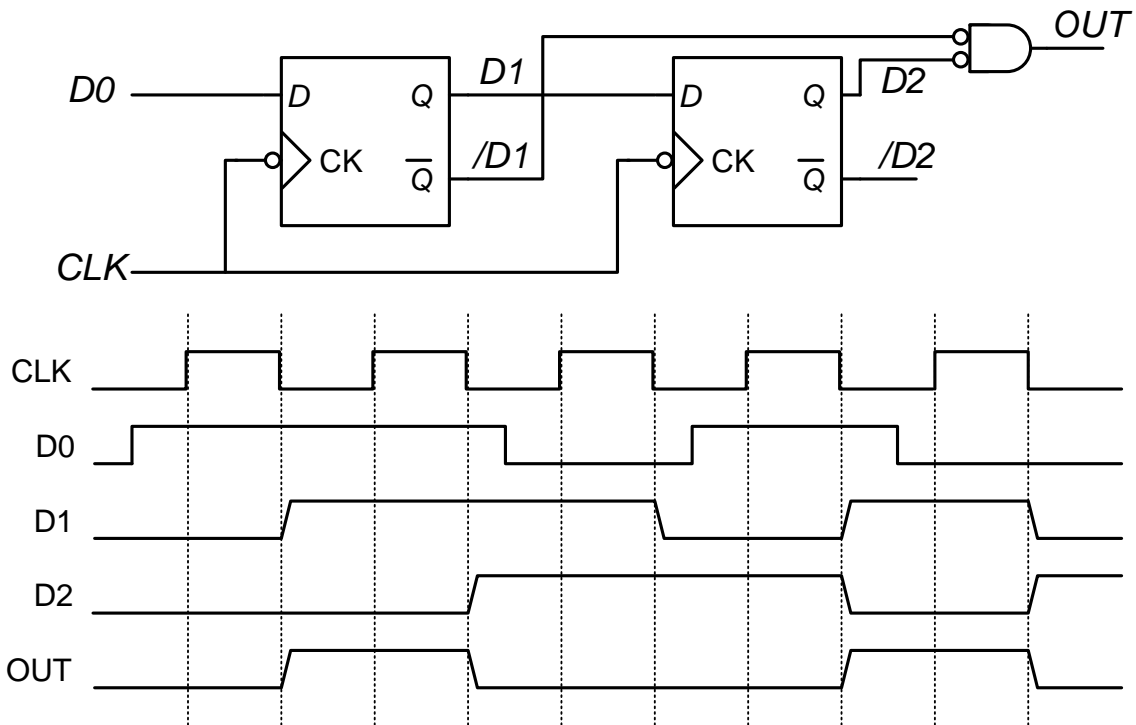2. Complete the waveform for the following design involving two negative edge-triggered D flip-flops. Note: OUT is a combinational logic function of the FF outputs. Note: Combinational logic gates are UNAFFECTED by the clock (only FF's use the clock signal). Thus, a change in the inputs to logic gates causes an immediate change (after a small propagation delay) in the outputs. For D1 and D2 indicate their value during the middle of clock cycles A through F. For OUT indicate which timestamps of D or CLK will cause (either directly or via D1 and D2) OUT to toggle (from 0 to 1 or 1 to 0)



3. The waveform is below:

 

The circuit is checking for 1001 (1 moves to SA, 0 moves to SB, another 0 moves to SC and then X has to be 1 to make F=1)

4.

(a) There is only one D Flip flop, and  $Q_1$  can be 0 or 1. Thus, there are 2 states for this circuit.

(b) The maximum number of transition arrows originating from one state is 8. Because we have A, B and C three external inputs, and there are 8 possible combinations of one 3-bits binary number.

(c) No. Because when A is equal to 1, the input of the D Flip flop is definitely 0. Thus, when the next clock tick comes,  $Q_1$  is equal to 0 and F is 0 too.

5.

Using 1-hot state machine design, we use 1 flip flop per state: QOff, QMon, Q1wr, QAlarm and the corresponding D inputs. The inputs are E=ENTER and C=CORRECT.

### Next State Logic

We can arrive at the next state equations by inspection from the state diagram (looking at each transition pointing TO a state).

$$\begin{aligned} DOff &= Qoff \& (\sim Enter + \sim Correct) + (QMon + Q1wr) \& Enter \& Correct \\ & // \text{ can be } \sim(Enter \& Correct) \end{aligned}$$

$$\begin{aligned} DMon &= Qoff \& Enter \& Correct + QMon \& \sim Enter \\ D1wr &= QMon \& Enter \& \sim Correct + Q1wr \& \sim Enter \\ DAlarm &= QAlarm + Q1wr \& Enter \& \sim Correct \end{aligned}$$


### Output Logic

$$Alarm = QAlarm$$

### Reset Logic

	Initial Value	CLR	SET
QOff	1	GND	RESET
QMon	0	RESET	GND
Q1wr	0	RESET	GND
QAlarm	0	RESET	GND

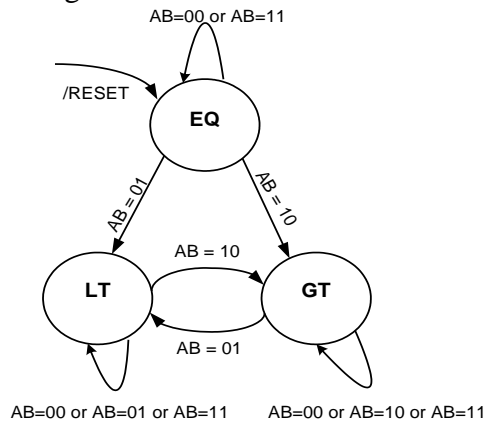6. (a.)  
 (1) First, we build the state diagram.



**Next State Logic**

We can arrive at the next state equations by inspection from the state diagram (looking at each transition pointing TO a state).

$$DEq = QEq \& (\sim A \& \sim B + A \& B)$$

// can be  $QEq \& (A \text{ xnor } B)$

$$DGt = (QEq + QLt)(A \& \sim B) + QGt \& \sim(\sim A \& B)$$

$$DLt = (QEq + QGt)(\sim A \& B) + QLt \& \sim(A \& \sim B)$$

**Output Logic**

$$Eq = QEq$$


$$Lt = QLt$$

$$Gt = QGt$$

**Reset Logic**

	Initial Value	CLR	SET
QEq	1	GND	RESET
QLt	0	RESET	GND
QGt	0	RESET	GND

The waveform is below:

 

7. Complete the waveform for a 4-bit counter with count-enable and data load.

