

Circuits Lab

Equipment and Overview

Mark Redekopp

Solderless BreadBoard/Protoboard

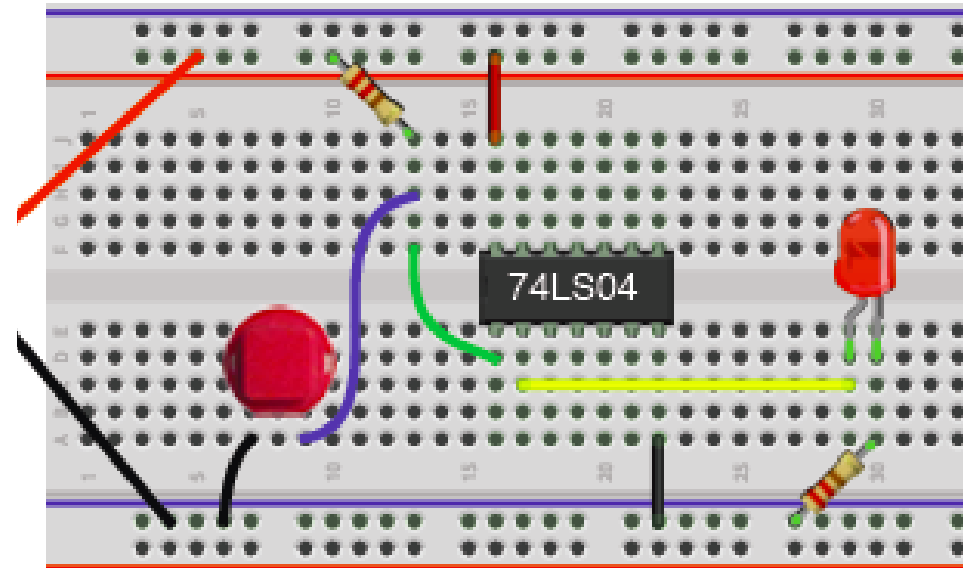
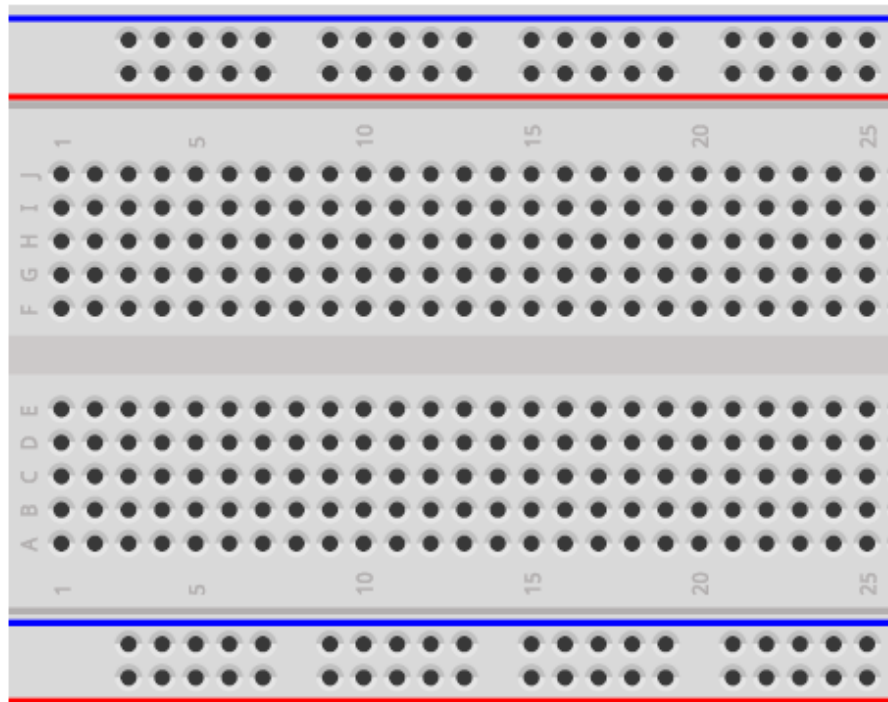


Figure 1: Portion of a breadboard

Solderless BreadBoard/Protoboard

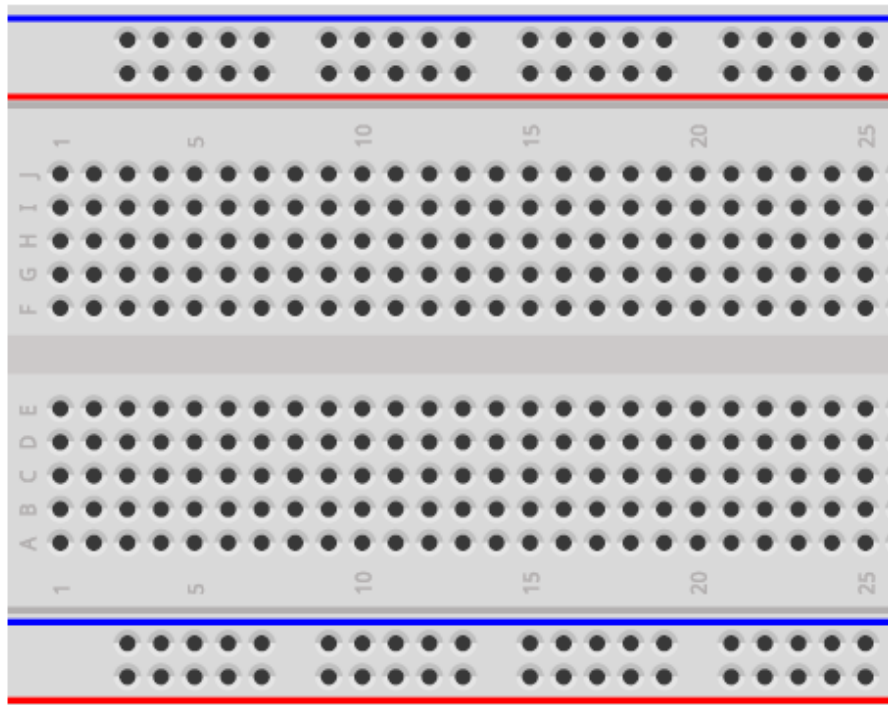
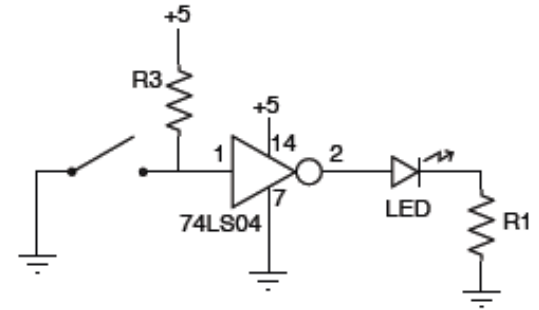


Figure 1: Portion of a breadboard


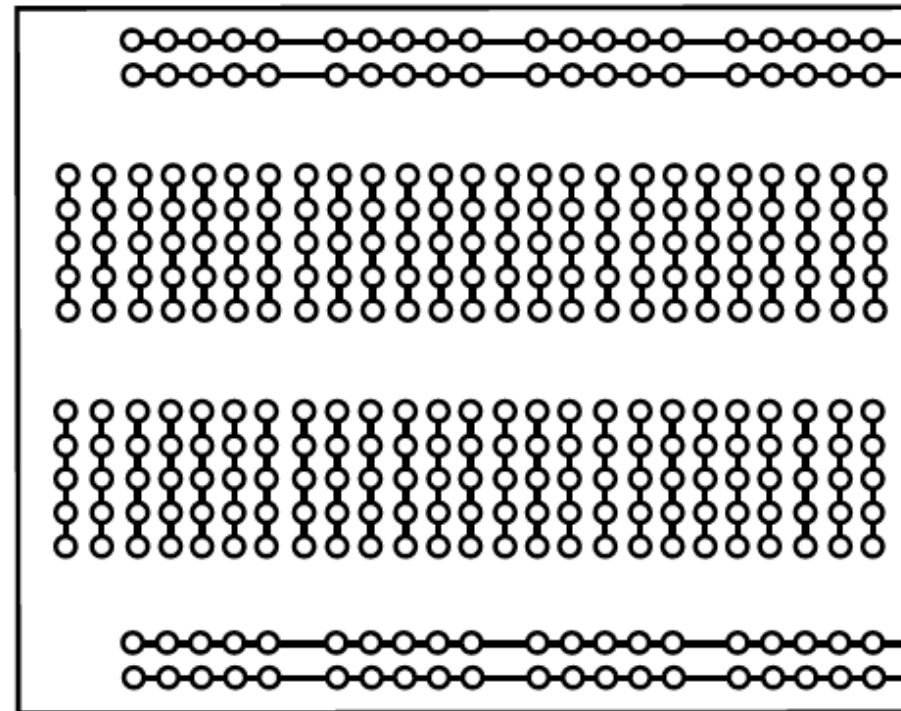


Figure 2: Breadboard holes connection pattern

Power Supply

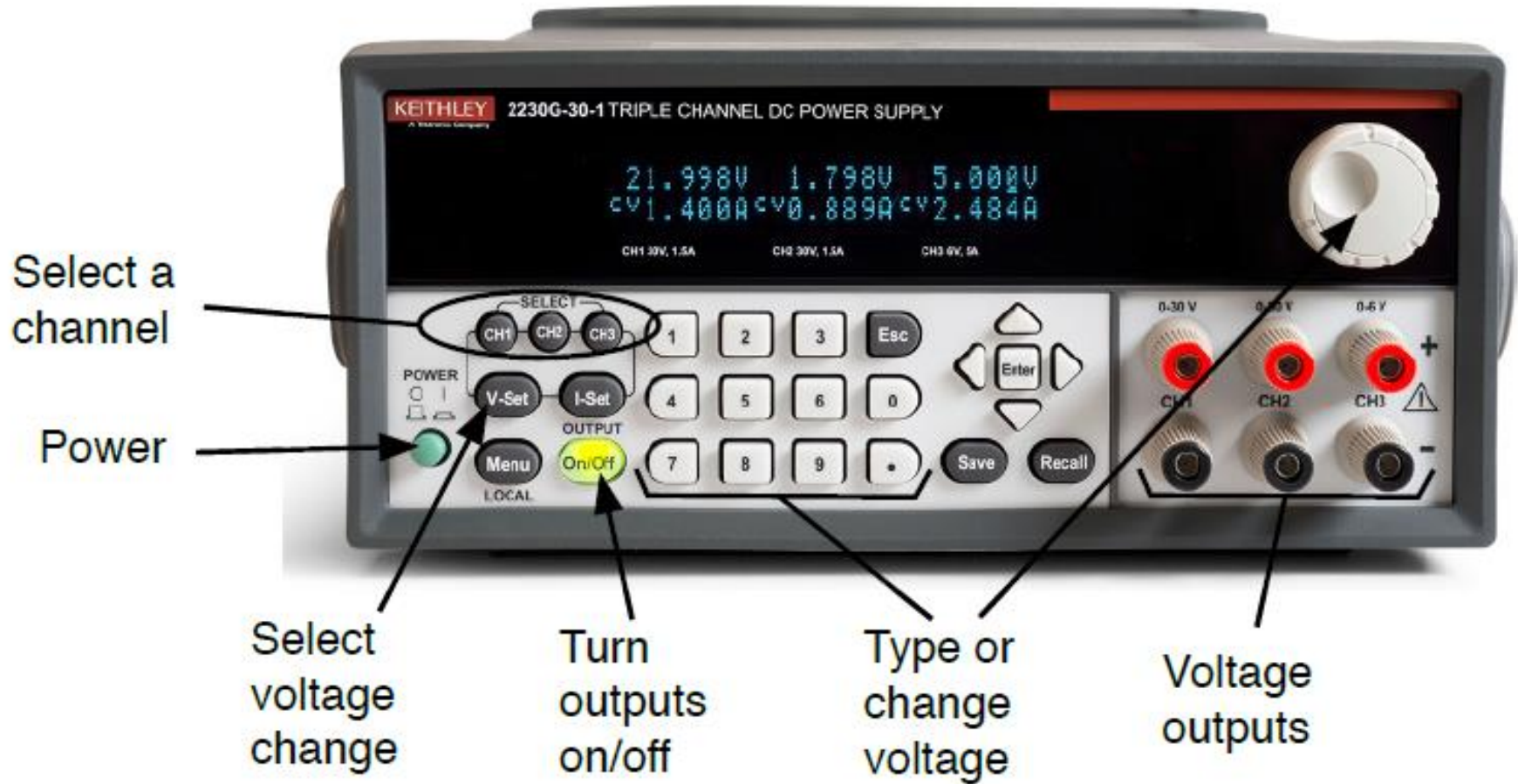

Digital Multimeter

(Measure Voltage, Current, Resistance)



Figure 7: Multimeter

Use these inputs


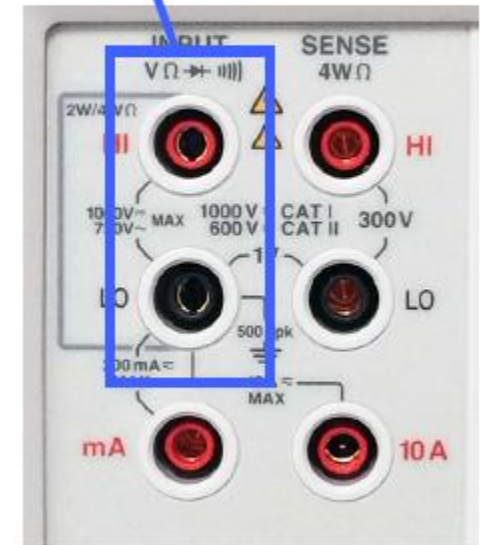


Figure 8: DMM Inputs

Digital Multimeter

(Measure Voltage, Current, Resistance)

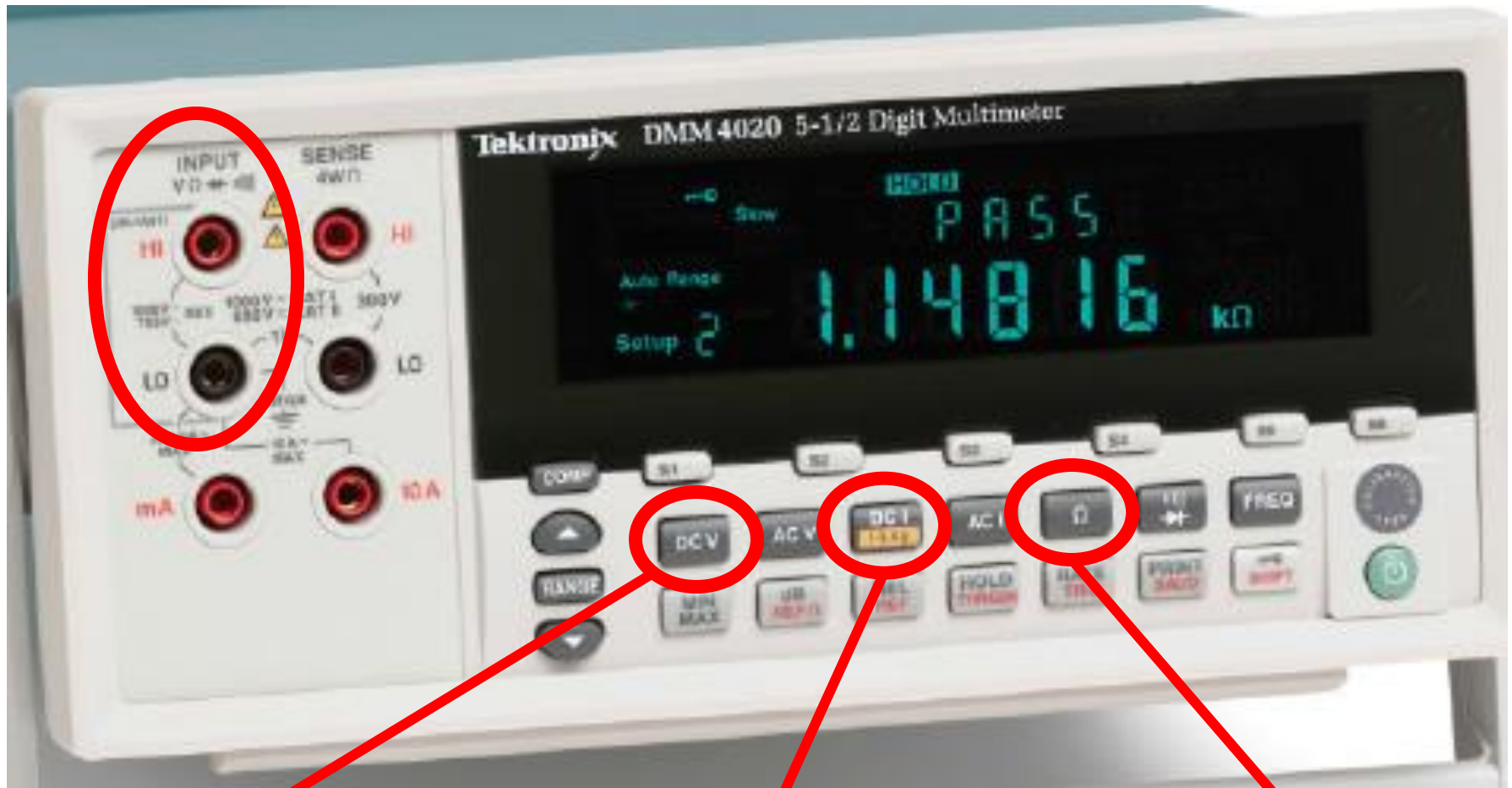

Choose DC V
To measure Voltage

Choose DC I
To measure current

Choose Ω
To measure resistance

Test Leads & Connections



Figure 4: Banana plugs



Figure 5: Test leads with pins on ends

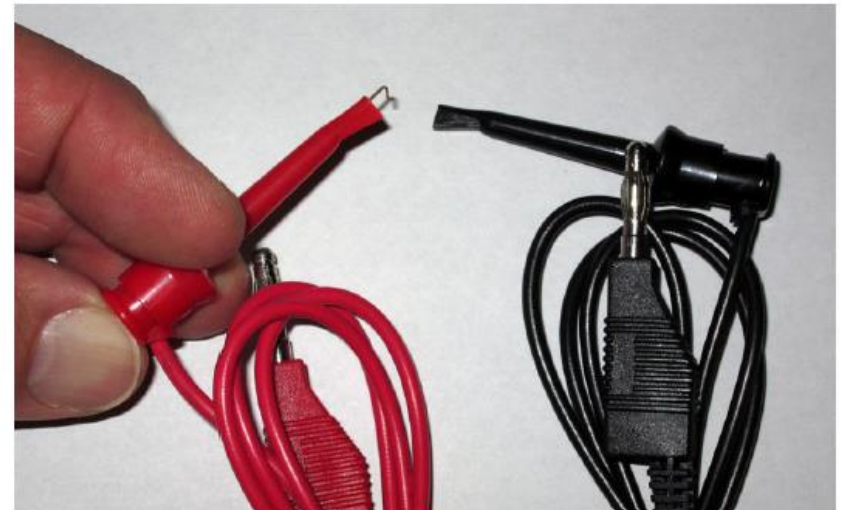



Figure 11: Test clips have a hook at the end that is exposed by pressing on the back of the clip

Banana
 (Meter)
 Banana
 (Meter)



Pin
 (Breadboard)
 Clip
 (Pin of a Device)

Test Leads & Connections

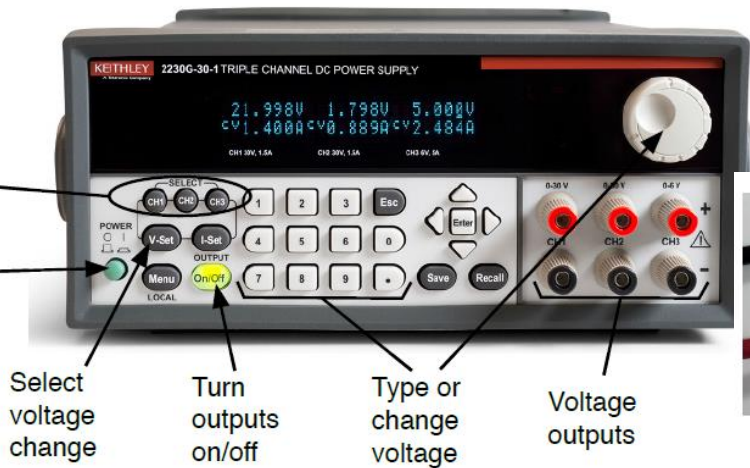

Select voltage change
 Turn outputs on/off
 Type or change voltage
 Voltage outputs

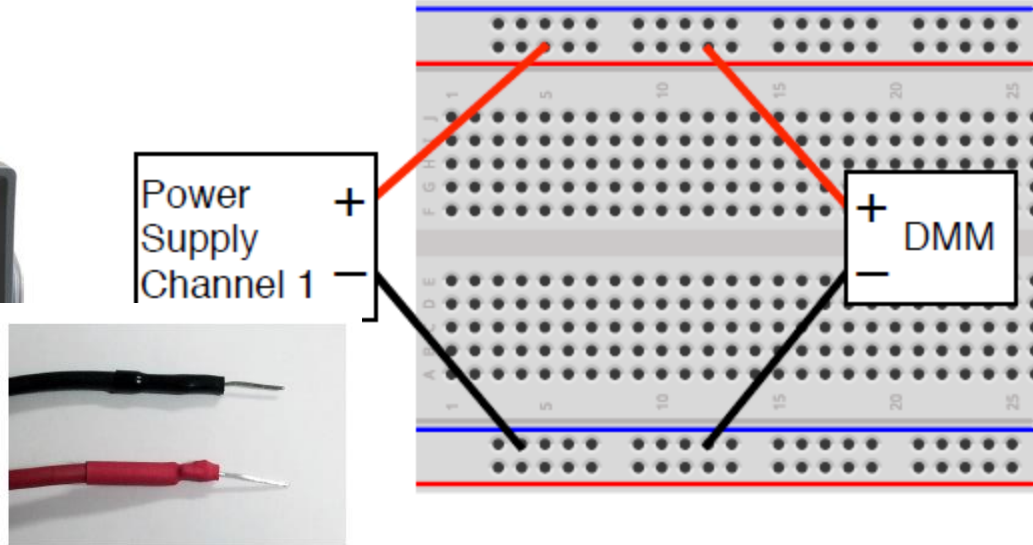


Figure 6: Connecting power supply and DMM to breadboard



Figure 7: Multimeter

Use these inputs

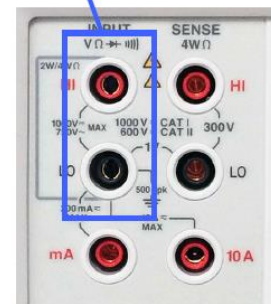


Figure 8: DMM Inputs

Resistors & Their Measurement

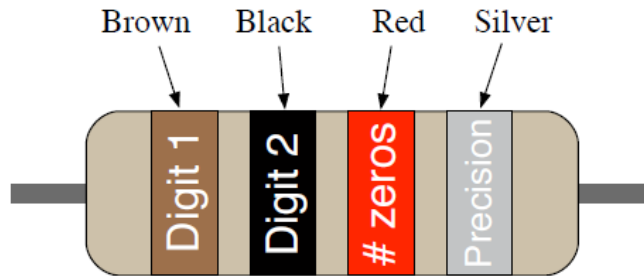


Figure 9: Resistor with color bands. Colors shown are for a 1000Ω, 10% resistor.

| | | |
|--|--------|---|
| | Black | 0 |
| | Brown | 1 |
| | Red | 2 |
| | Orange | 3 |
| | Yellow | 4 |
| | Green | 5 |
| | Blue | 6 |
| | Violet | 7 |
| | Gray | 8 |
| | White | 9 |

Figure 10: Resistor color code

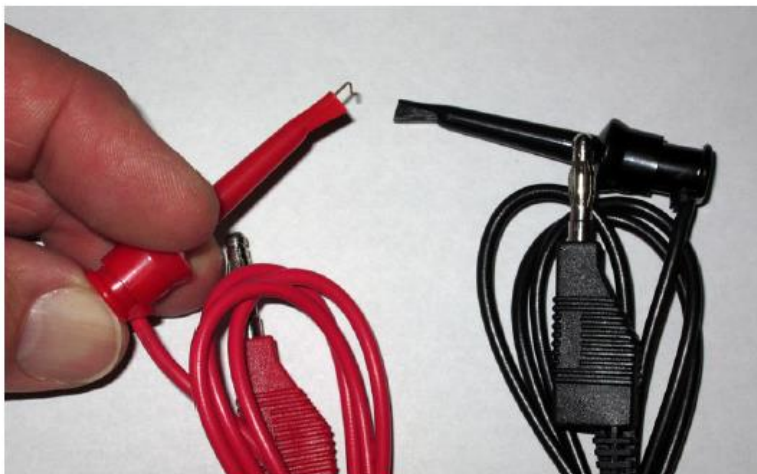


Figure 11: Test clips have a hook at the end that is exposed by pressing on the back of the clip



Figure 12: Attach test clips to resistor leads

Voltage Divider Circuit

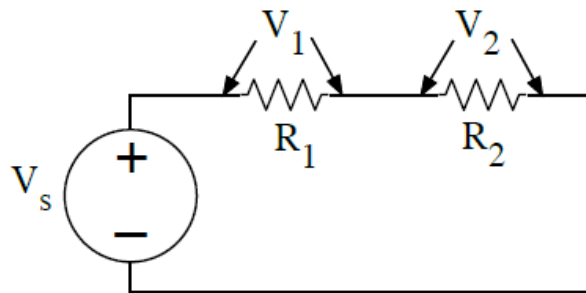


Figure 15: Circuit with resistors in series


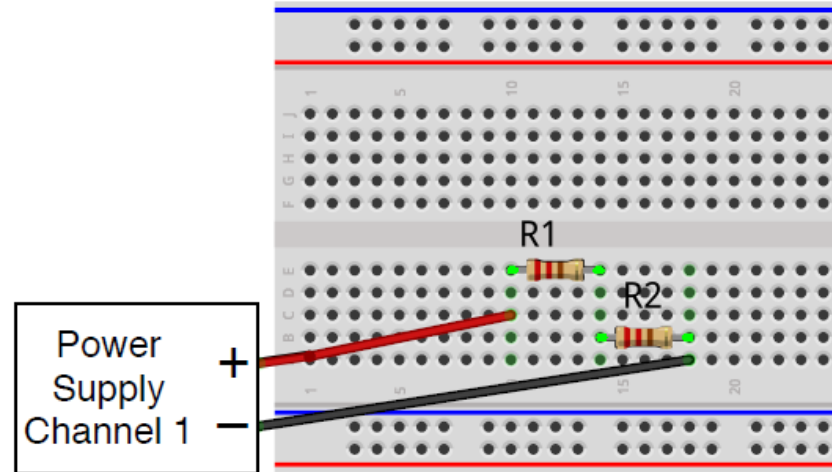
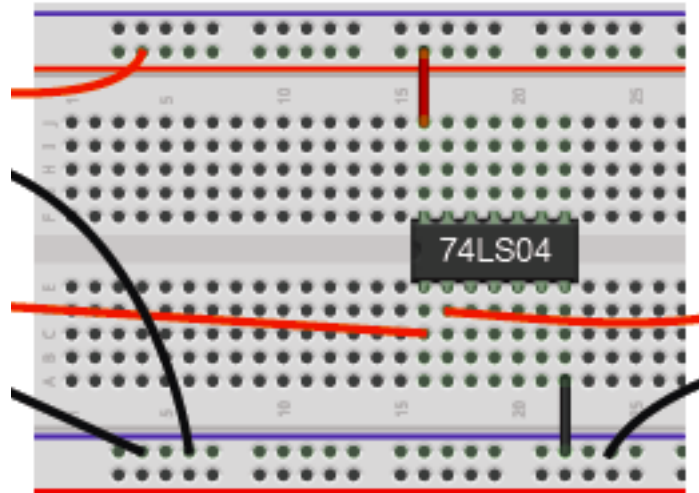


Figure 16: Series resistors on a breadboard

Understanding Chip Connections

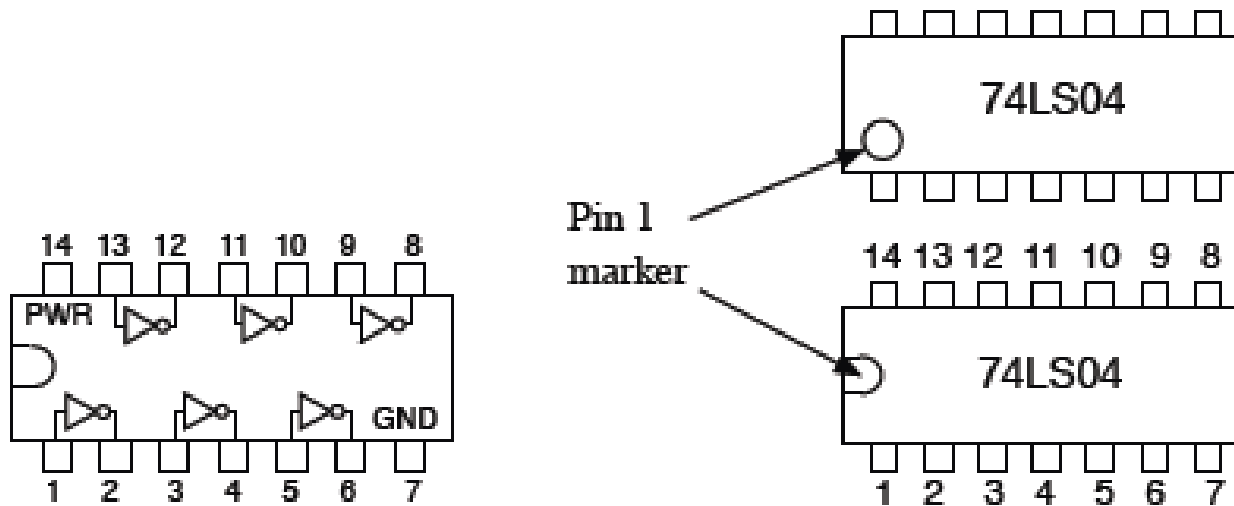


PROCEDURAL NOTES


Buttons



Pushbuttons

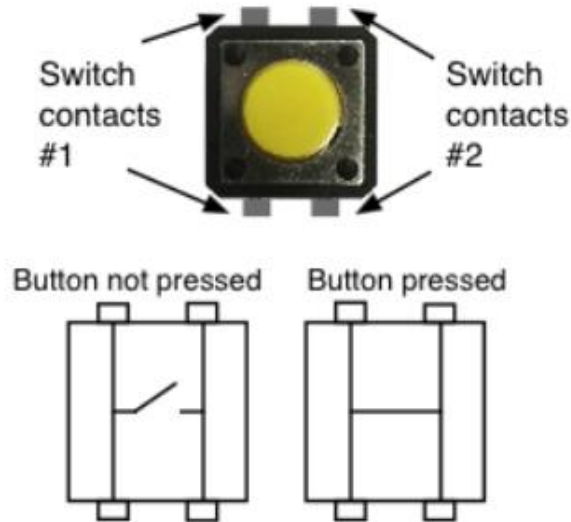


Schematic of buttons

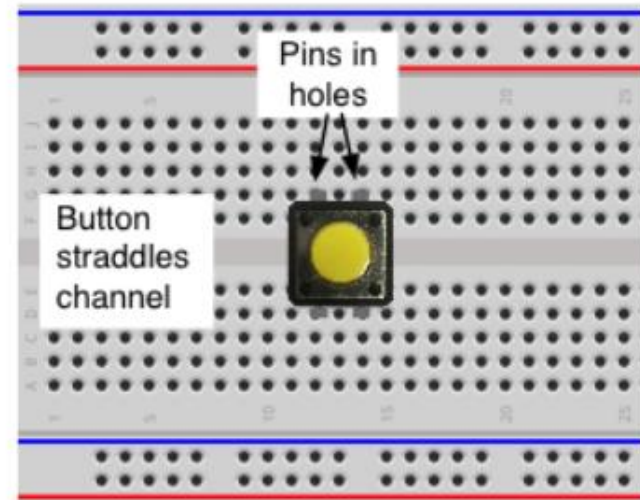


Buttons installed on breadboard


Switch Configurations

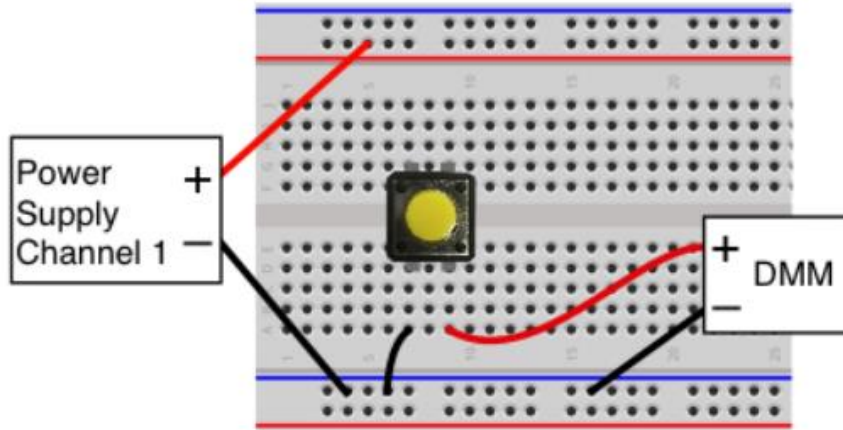


Button with one contact grounded

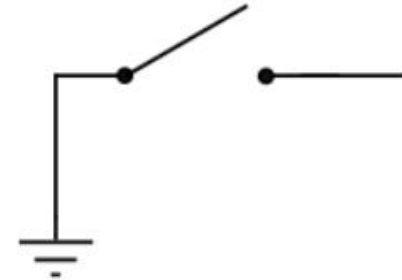

Schematic of circuit

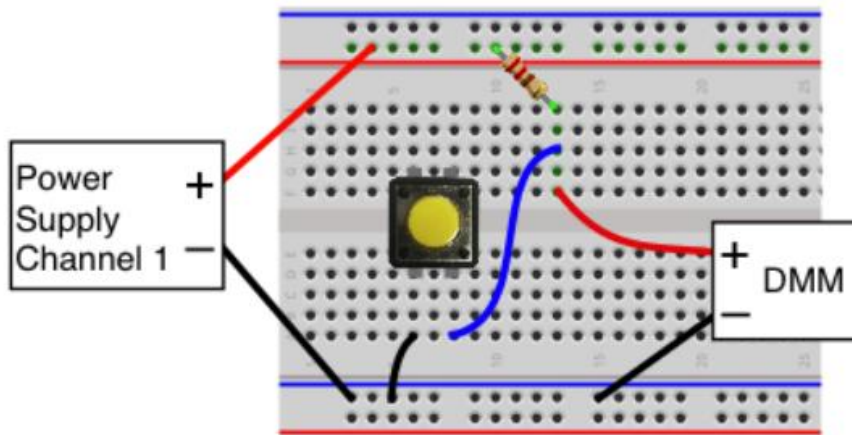


Button with resistor to +5 volts

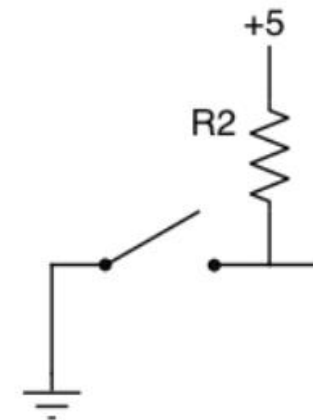


Schematic of circuit


Digital Circuits

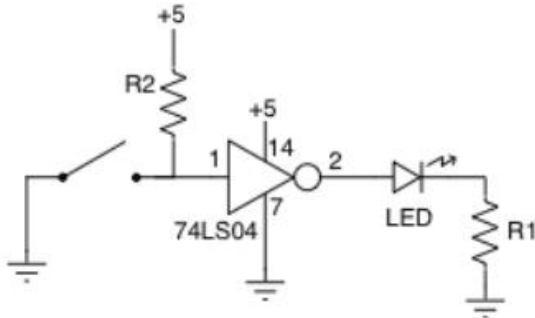

Button, 74LS04 and LED circuit

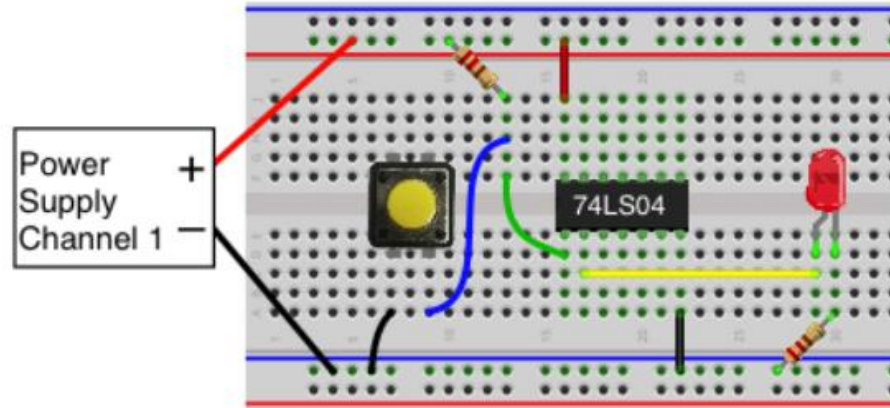

Button, 74LS04 and LED on a breadboard

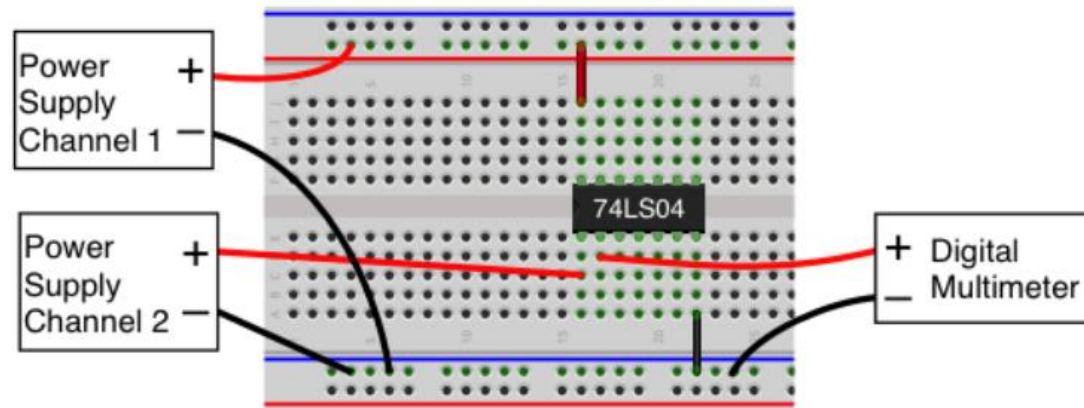

Measuring threshold with DMM

WHEN YOU ARRIVE

When You Arrive...

- We will issue toolkits in plastic boxes
 - These are yours to keep for the semester and then return everything but the Arduino at the end of the semester
 - Put a paper with your name on it somewhere in the box
 - You may take these home so you can work anywhere
- Parts available at the front table in VHE 205
- May work in teams of 2 and a few groups of 3
 - Ensure each member rotates building and using the equipment
 - Each person should submit their own answers