 


Unit 10

Fundamental Digital Building Blocks: Decoders & Multiplexers


Checkers / Decoders

- Recall
 - AND gates output '1' for only a single combination
 - OR gates output '0' for only a single combination
 - Inputs (inverted or non-inverted) determine which combination is checked for
 - We say that gate is "checking for" or "decoding" a specific combination



X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

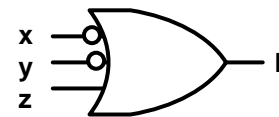AND gate decoding
 (checking for)
 combination 010



X	Y	Z	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

OR gate decoding
 (checking for)
 combination 110


Motivation

- Just like there are patterns and structures that occur commonly in nature, there are several common logic structures that occur over and over again in digital circuits
 - Decoders, Multiplexers, Adders, Registers
- In addition, we design hardware using a **hierarchical** approach
 - We design a **small component** using **basic logic gates** (e.g. a 1-bit mux)
 - We build a **large component** by interconnecting many copies of the **small component** + a few extra gates (e.g. a 32-bit mux)
 - We build **chips** by interconnecting many **large components** (e.g. a router)
 - Each components is truly made out of many gates but the design process is faster and easier by using hierarchy
- Let's look at a few common components
 - We'll start by describing the behavior of the component and then determine what gates are inside

DECODERS

Decoders

 
- A decoder is a building block that:
 - Takes in an n-bit binary number as input
 - Decodes that binary number and activates the corresponding output
 - Individual outputs for ALL 2^n input combinations



Decoders


- A decoder is a building block that:
 - Takes a binary number as input
 - Decodes that binary number and activates the corresponding output
 - Put in 6=110, Output 6 activates ('1')
 - Put in 5=101, Output 5 activates ('1')

X	Y	Z	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

 


Decoder Sizes

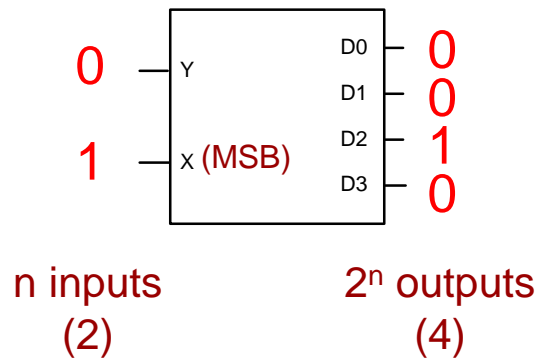- A decoder w/ an **n-bit input** has **2^n outputs**
 - 1 output for every combination of the n-bit input



**2-to-4
Decoder**


 


**3-to-8
Decoder**



Exercise

- Complete the design of a 2-to-4 decoder

X	Y	D0	D1	D2	D3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

  


Building Decoders

 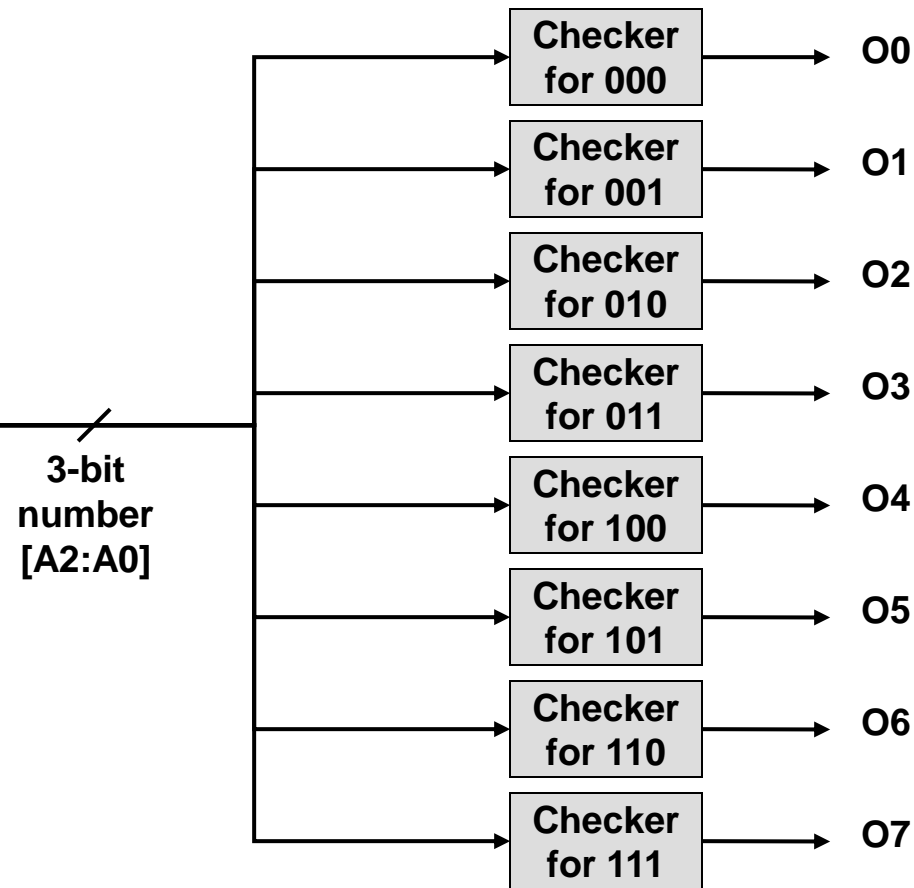

Vending Machine Example


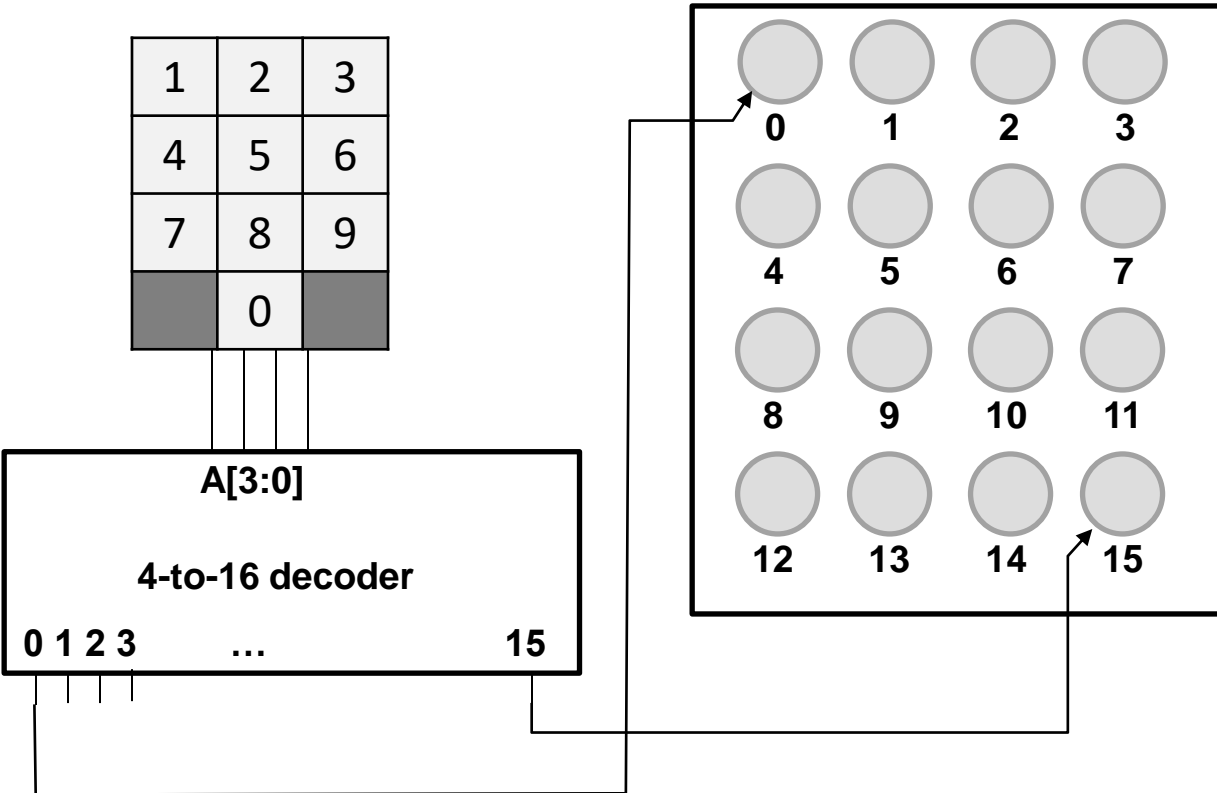
Assuming the keypad produces a 4-bit numeric output, add logic to produce the release signals for each of the 16 vending items.





Consider any problems with this design.

Enables

 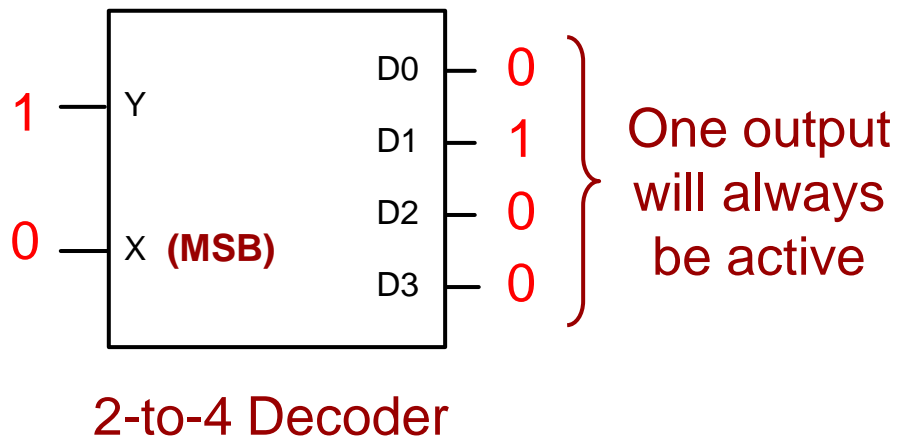- In a normal decoder, exactly one output is active at all times
- It may be undesirable to always have an active output
- We can add an extra input (called an enable) that can independently force all the outputs to their inactive values




Enables

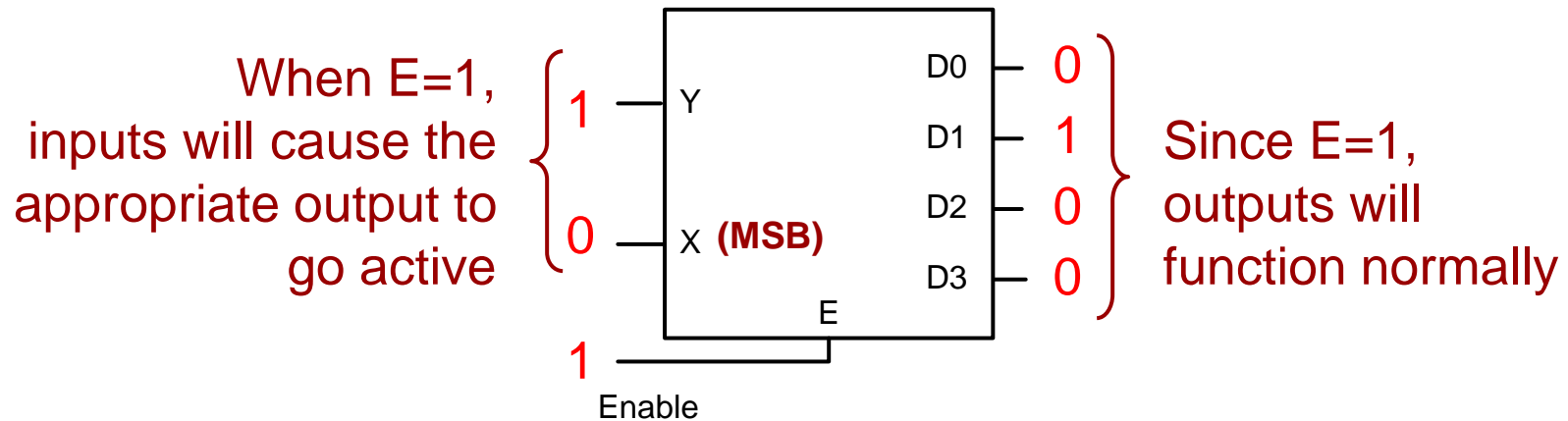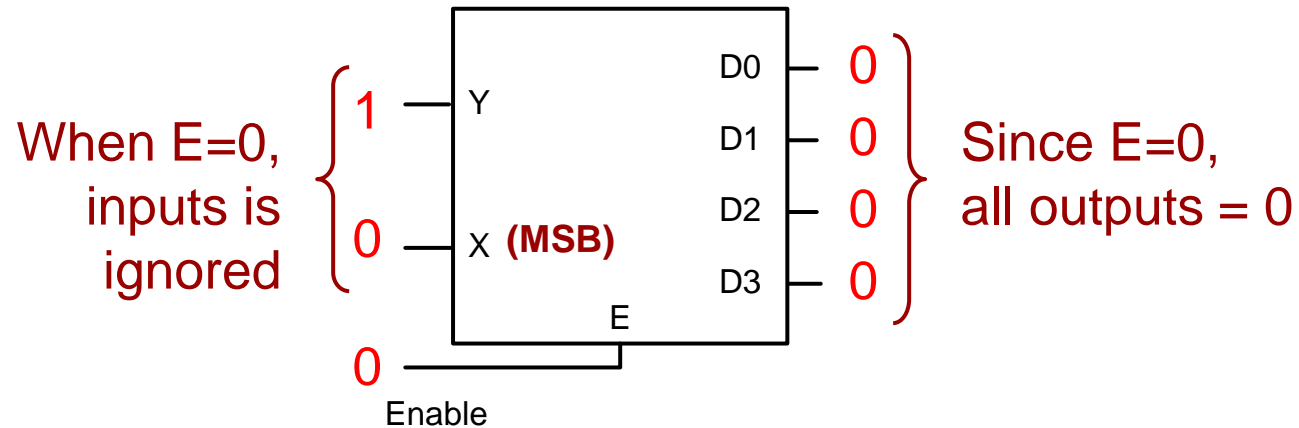

Implementing Enables

- Original 2-to-4 decoder


 


When E=0, force all outputs = 0

When E=1, outputs operate as they did originally


Another Application of Decoders: Memories

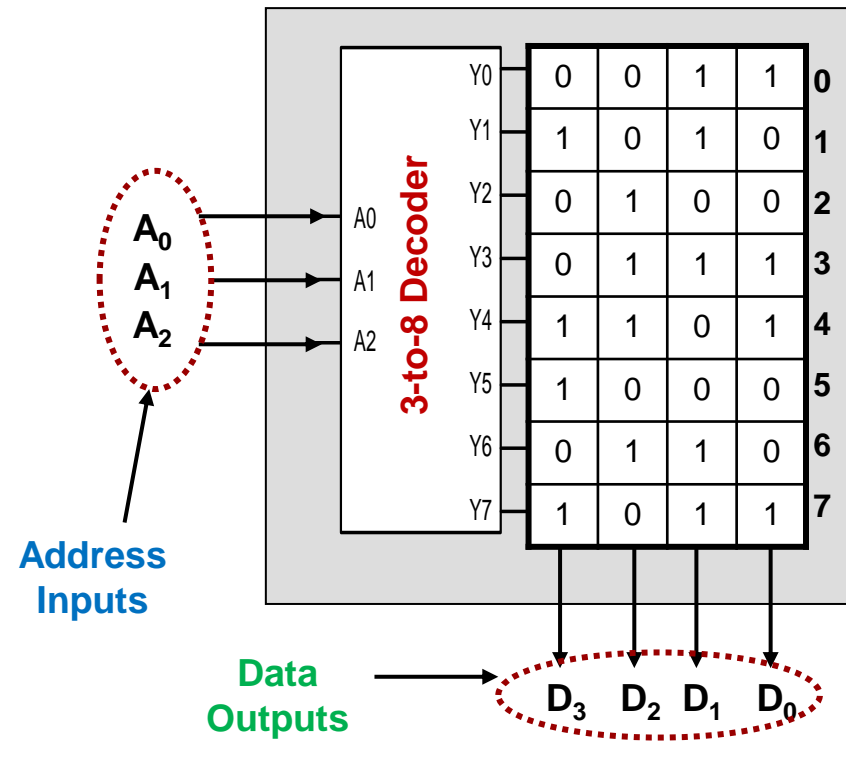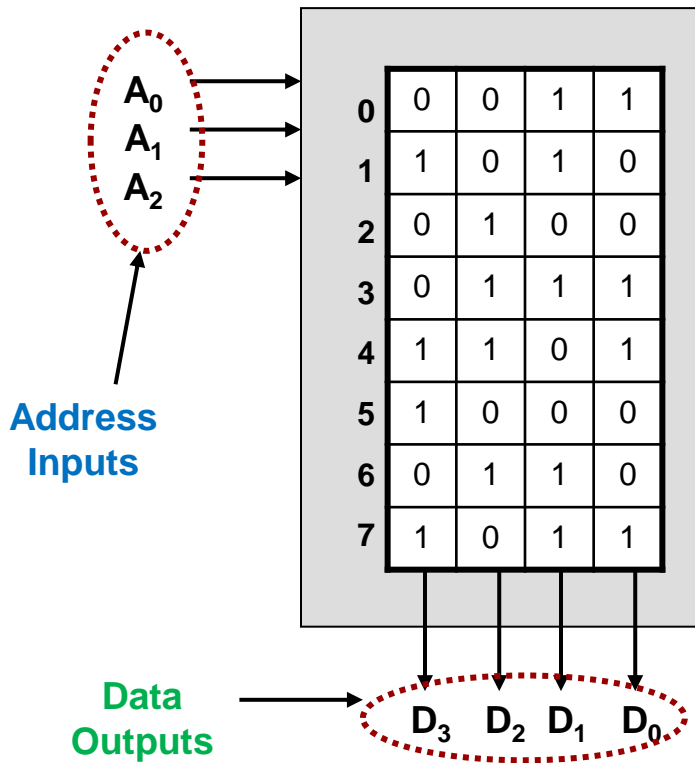- All memories (RAMs, ROMs) use decoders to select the desired data given an address (each location/byte corresponds to one address combination)
- If you have a 1 MB (2^{20} bytes) RAM, there is a 20-to- 2^{20} decoder present in that device



Building Large Decoders

 
- If you have 1 MB (2^{20} bytes) RAM, there is a 20-to- 2^{20} decoder present in that device
- How can we create such large decoders?
 - Through hierarchy (building-block methodology)..usually of linear chains or tree-based structures



Larger Decoder Exercise 1


- Build a 3-to-8 decoder from 1-to-2 decoders

1-to-2 Decoder Operation

 


E	A0	Y0	Y1
0	X	0	0
1	0	1	0
1	1	0	1

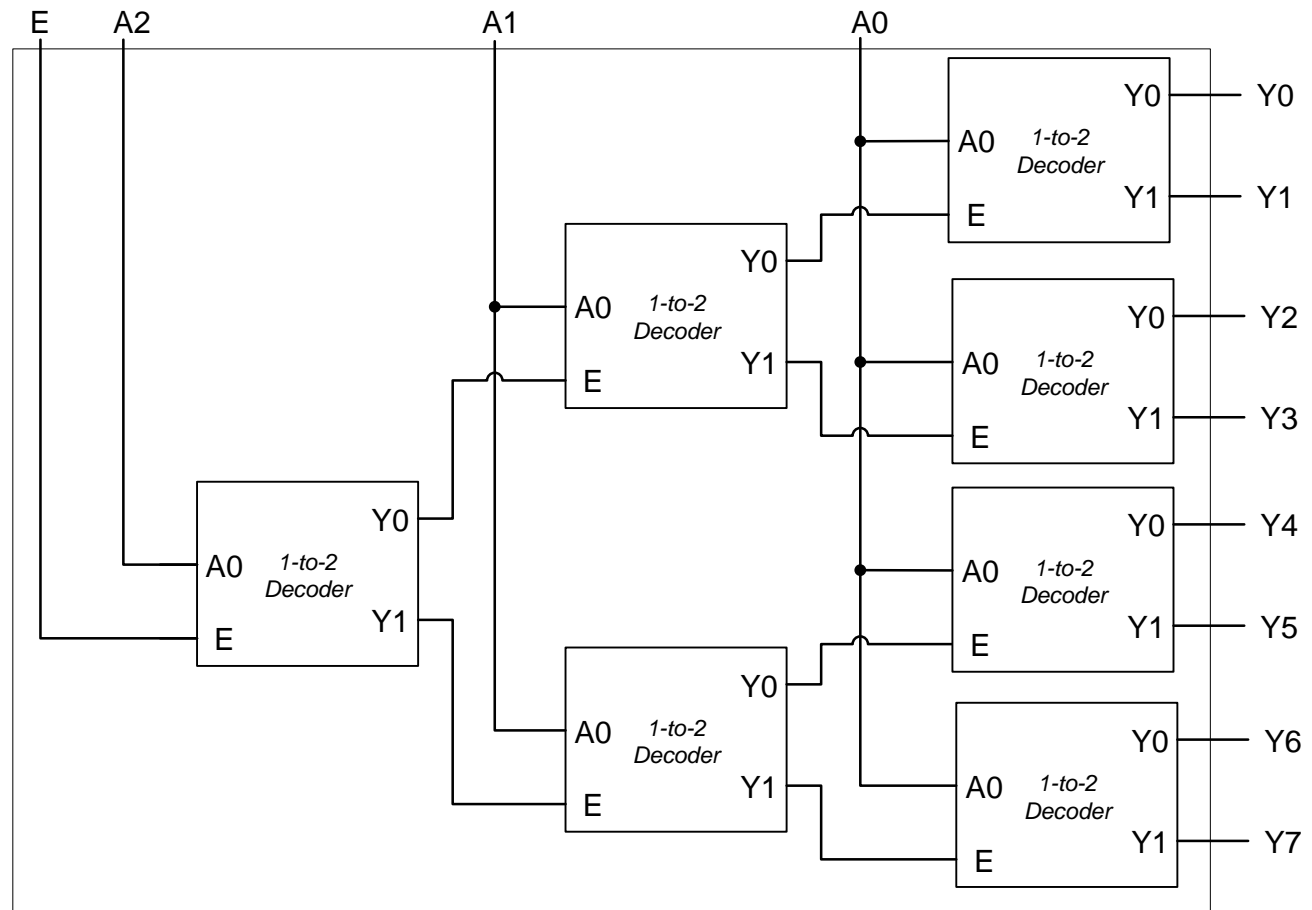X = not relevant
(same result for all possible values of A0)



Larger Decoder Exercise 1a

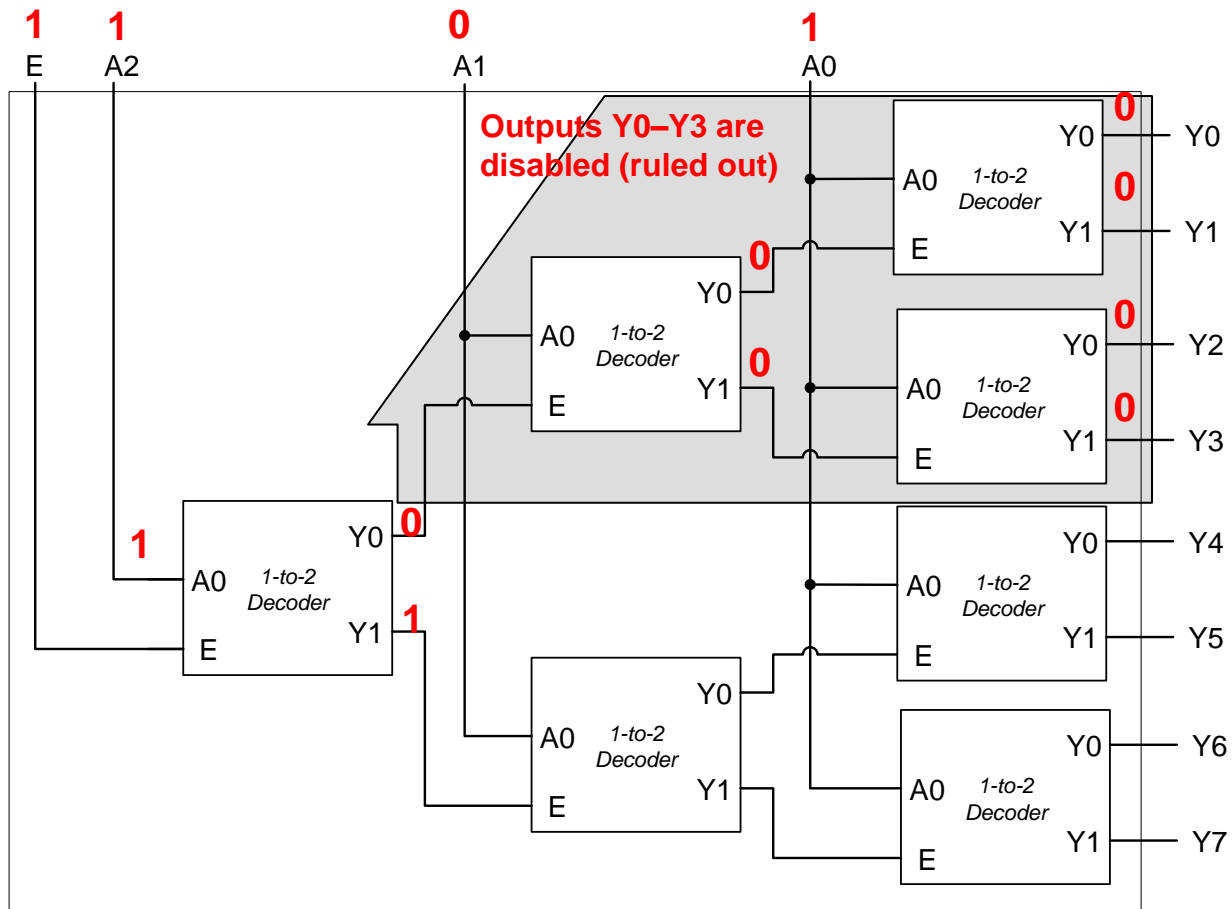


Outputs Y0–Y3 are disabled (ruled out)

A ₂	A ₁	A ₀	Active Output
0	0	0	Y ₀
0	0	1	Y ₁
0	1	0	Y ₂
0	1	1	Y ₃
1	0	0	Y ₄
	0	1	Y ₅
	1	0	Y ₆
	1	1	Y ₇

Decode the MSB...possible combos = 4-7


Larger Decoder Exercise 1b

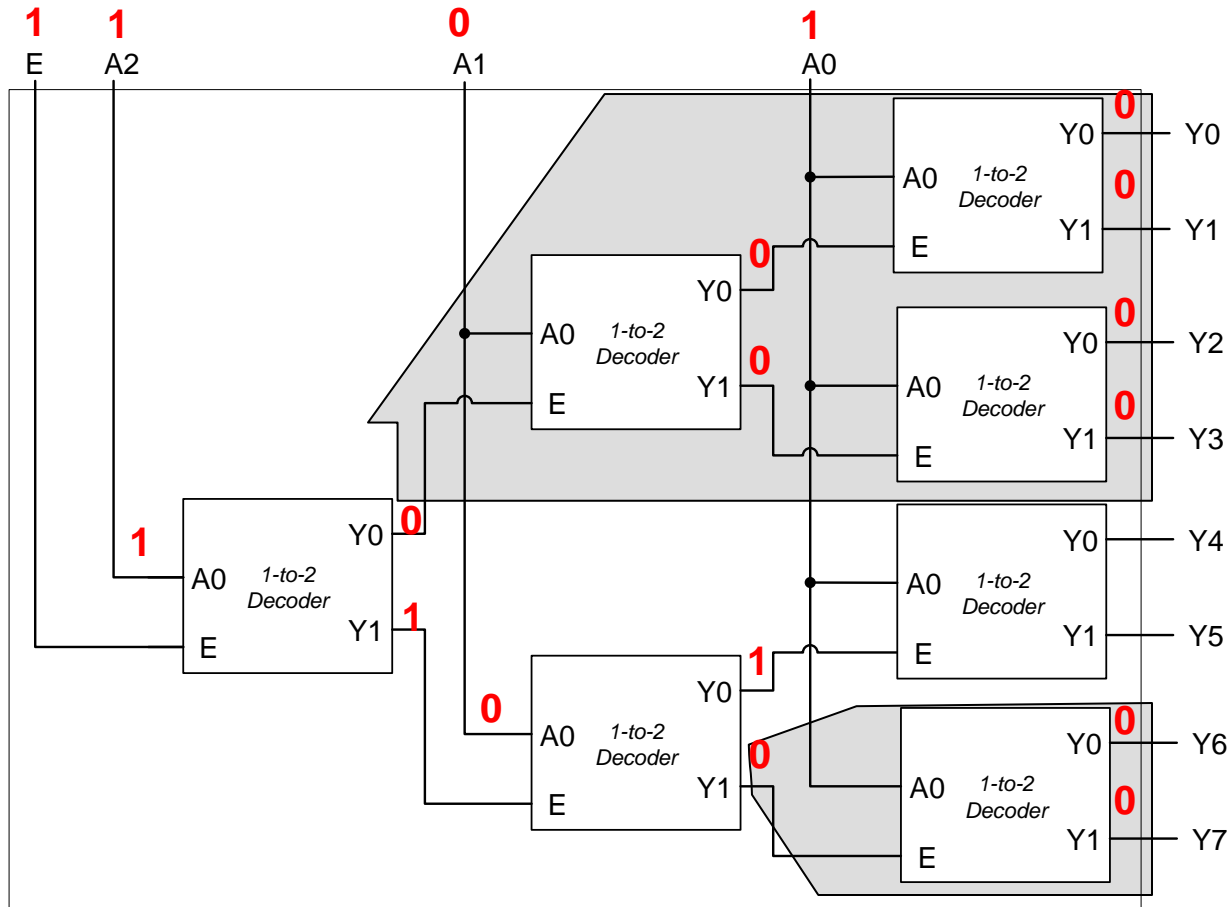

Decode the A_1 ... possible combos = 5-6

A_2	A_1	A_0	Active Output
0	0	0	Y_0
0	0	1	Y_1
0	1	0	Y_2
0	1	1	Y_3
1	0	0	Y_4
		1	Y_5
	1	0	Y_6
		1	Y_7

Larger Decoder Exercise 1c

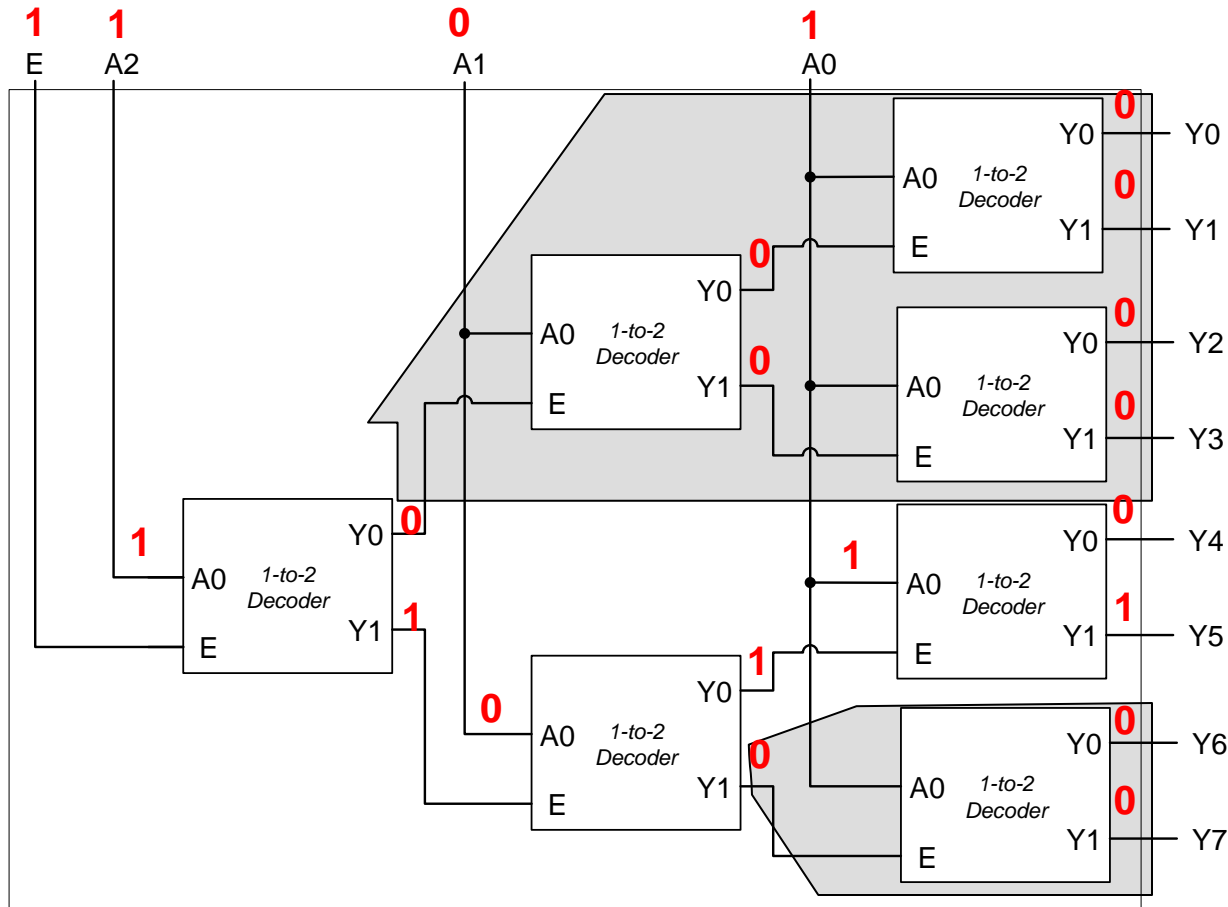

Decode the A_0 ...possible combo = 5


A_2	A_1	A_0	Active Output
0	0	0	Y_0
0	0	1	Y_1
0	1	0	Y_2
0	1	1	Y_3
1	0	0	Y_4
		1	Y_5
	1	0	Y_6
	1	1	Y_7

General Tree Decoder Approach

- Step 1: Outputs of one stage should connect to the enables of the next stage
- Step 2: All decoders in a stage (level) should decode the same bit(s)
 - Usually, the MSB is connected to the first stage and LSB to the last stage

Larger Decoder Exercise 2

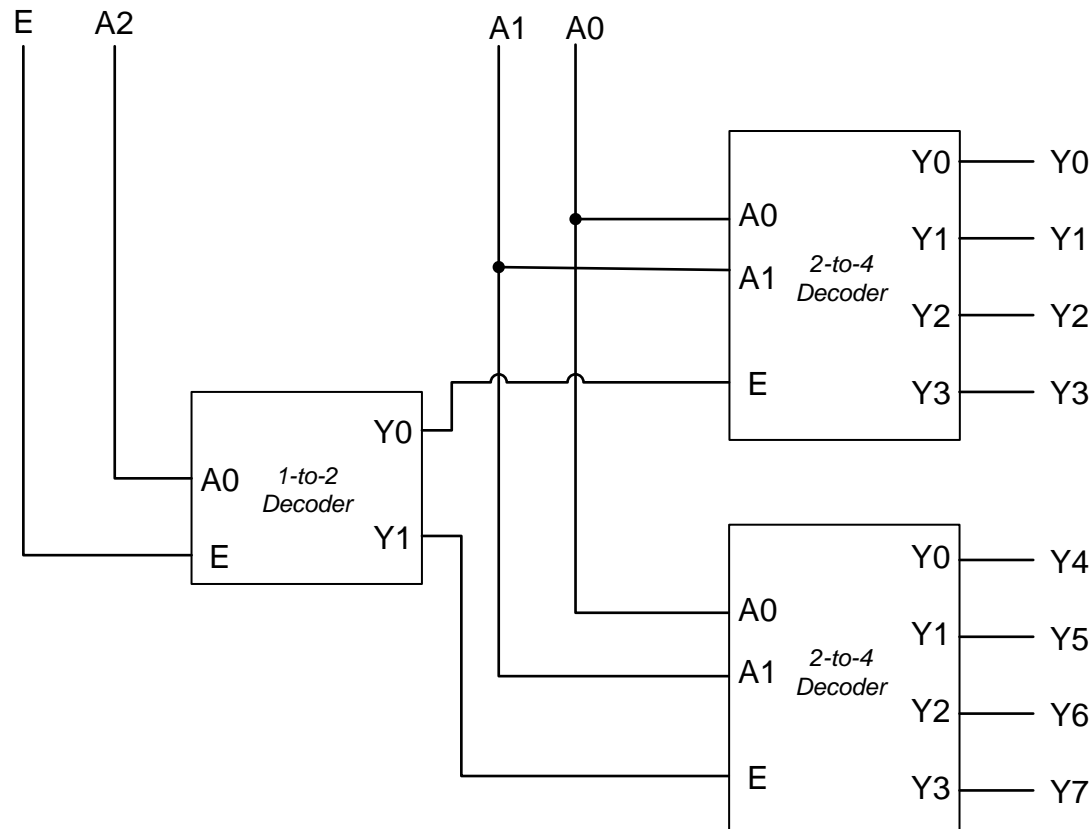- Different size decoders can be utilized
 - Build a 3-to-8 decoder using 1-to-2 and 2-to-4 decoders




The if..else of digital hardware

MULTIPLEXERS

Multiplexers

 
- Multiplexers are one of the most common digital circuits
- Anatomy: n data inputs, $\log_2 n$ select bits, 1 output
- A multiplexer (“mux” for short) selects one data input and passes it to the output



S_1	S_0	Y
0	0	i_0
0	1	i_1
1	0	i_2
1	1	i_3

Multiplexers

4-to-1 Mux

 

② Thus, input 2 = C is selected and passed to the output


① Select bits = $10_2 = 2_{10}$.

S_1	S_0	Y
0	0	i0
0	1	i1
1	0	i2
1	1	i3

As long as the select bits are $10_2 = 2$, whatever bit value appears on input 2 is copied to the output, same as if we had just wired input 2 directly to the output.

Multiplexers

4-to-1 Mux

 


2 Thus, input 0 = A is selected and passed to the output

1 Select bits = $00_2 = 0_{10}$.

S_1	S_0	Y
0	0	i0
0	1	i1
1	0	i2
1	1	i3

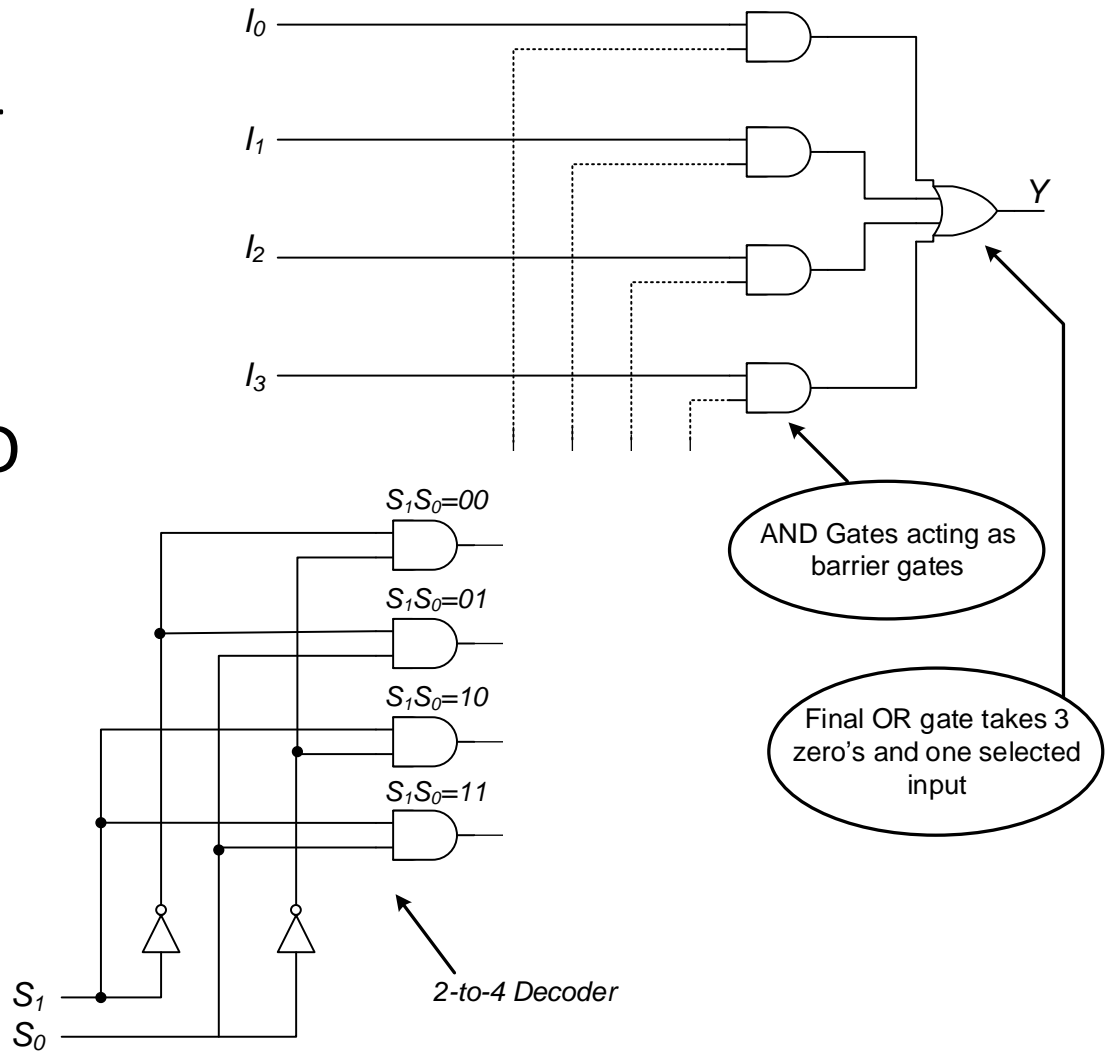Exercise: Build a 4-to-1 mux


- Complete the 4-to-1 mux to the right by drawing wires between the 2-to-4 decode and the AND gates



Building a Mux

- To build a mux
 - Decode the select bits and include the corresponding data input.
 - Finally OR all the first level outputs together.

$S_1 S_0 = 01_2$

 


S_1	S_0	Y
0	0	i_0
0	1	i_1
1	0	i_2
1	1	i_3

Building a Mux

- To build a mux
 - Decode the select bits and include the corresponding data input.
 - Finally OR all the first level outputs together.

$S_1 S_0 = 11_2$

 


S_1	S_0	Y
0	0	i_0
0	1	i_1
1	0	i_2
1	1	i_3

2-to-1 Multiplexers

- We can design and build muxes with any number of inputs (2-to-1, 5-to-1, 16-to-1, etc.)

2-to-1 Mux

 



② Thus, input 1 = B is selected and passed to the output

① Select bits = $1_2 = 1_{10}$.

S	Y
0	i0
1	i1


Building a 2-to-1 Mux

  - To build a mux
 - Decode the select bits and include the corresponding data input.
 - Finally OR all the first level outputs together.



Building Large Muxes

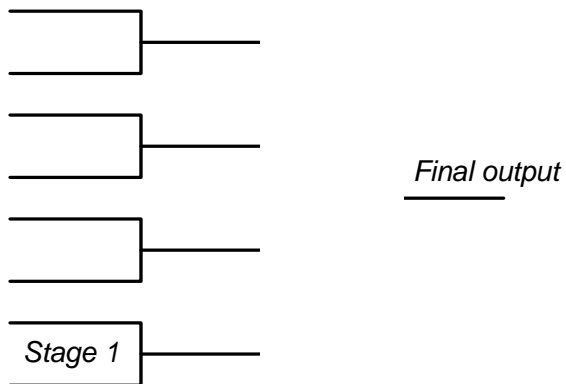
- When we build large muxes, the number of inputs to the gates grows too large to build them directly
- Instead, we will build larger muxes from smaller muxes
- Similar to a tournament of sports teams
 - Many teams enter and then are narrowed down to 1 winner
 - In each round winners play winners



Railroad Switch Station

Design an 8-to-1 mux with 2-to-1


Muxes

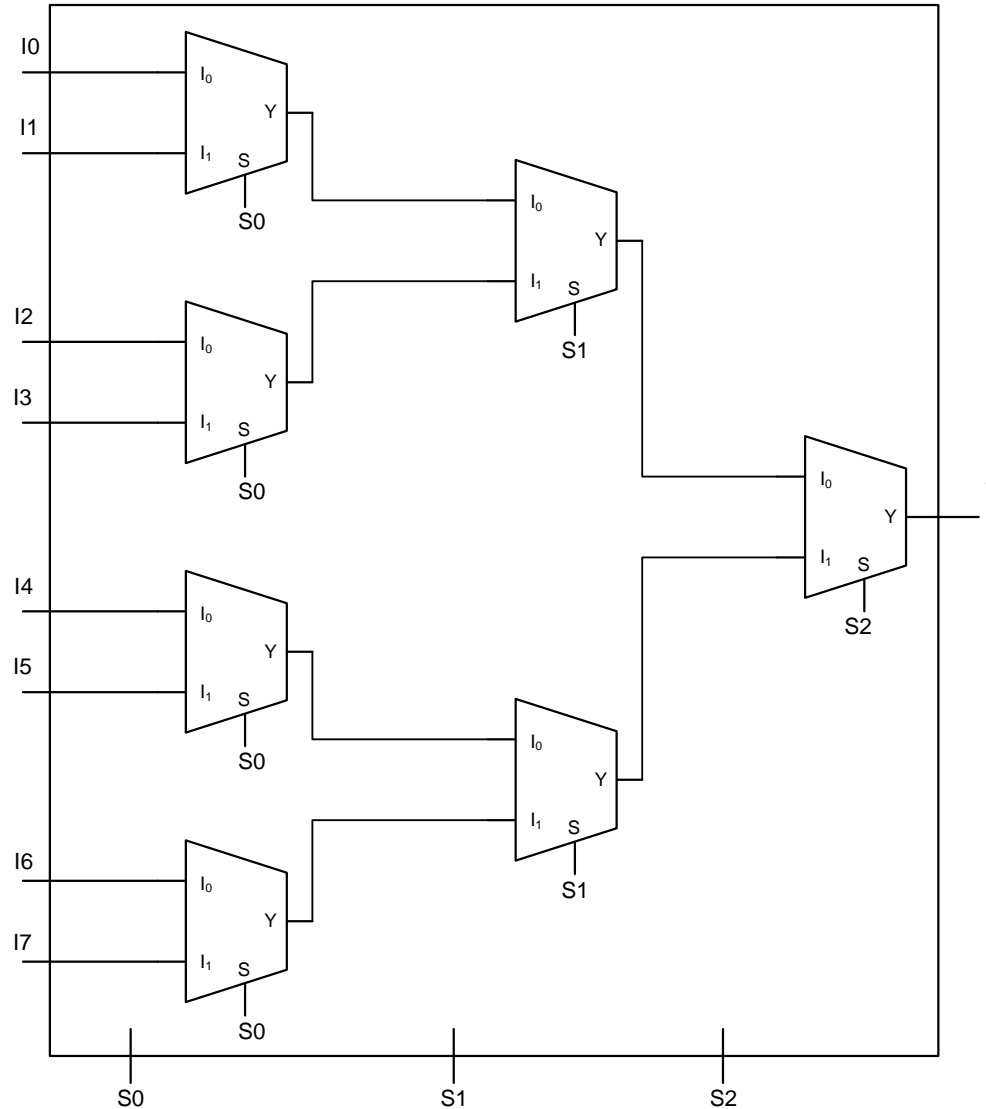

Cascading Muxes

- Use several small muxes to build large ones
- Rules
 1. Arrange the muxes in stages (based on necessary number of inputs in 1st stage)
 2. Outputs of one stage feed to inputs of the next until only 1 final output
 3. All muxes in a stage connect to the same group of select bits
 - Usually, LSB connects to first stage
 - MSB connect to last stage

Building a 4-to-1 Mux

 


Building a 4-to-1 Mux

S_1	S_0	Y
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3

Walk through an example:

$$S_1 S_0 = 01$$

 


Building a 4-to-1 Mux

S_1	S_0	Y
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3

Walk through an example:

$$S_1 S_0 = 01$$

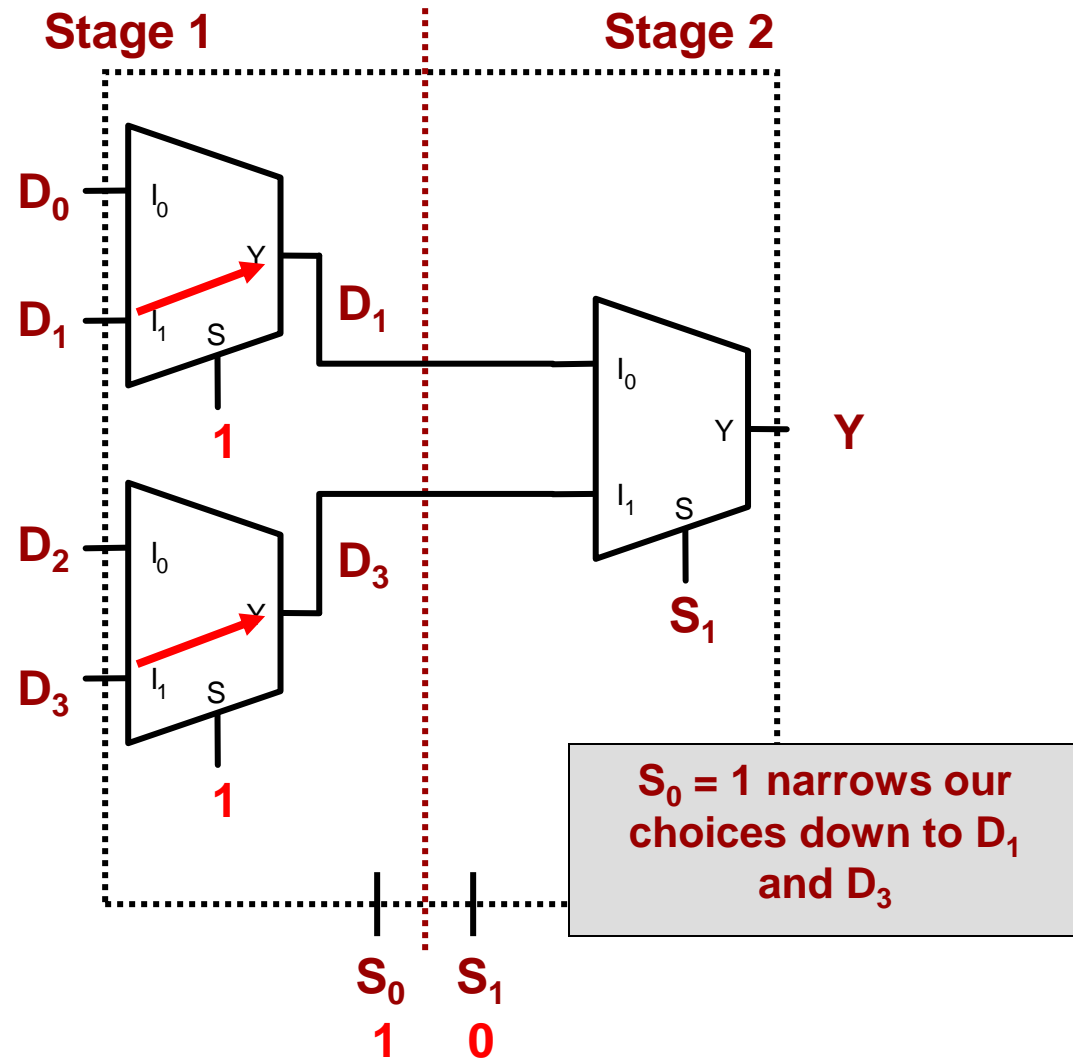


Building a 4-to-1 Mux

S_1	S_0	Y
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3

Walk through an example:

$S_1 S_0 = 01$

 

Device vs. System Labels

- When using hierarchy (i.e. building blocks) to design a circuit be sure to show both device and system labels
 - Device Labels: Signal names used inside the block
 - Placeholder names the **designer/manufacture of the block** uses to indicate which input/output is which to the outside user (Names may vary; read the manual)
 - System labels: Signal names used outside the block
 - Actual signals from the circuit being built
 - Can have the same name as the device label if such a signal name exists at the outside level


Analogy: **Formal** and **Actual** parameters in software function calls

- i_0 and i_1 are like device labels and indicate the names used inside a block.
- d_0 and d_1 are like system labels and represent the actual values to be used.

```
int div(int i0, int i1)
{ int t = i0/i1;
  return t; }
int main()
{
  int d0=10, d1=2;
  int s = div(d0,d1);
}
```



Device Labels:
Indicate which input/output is which inside the block.

 System Labels:
Actual signals from the circuit being built



  Exercise


- Sketch how you could build a 16-to-1 mux with 4-to-1 muxes? 8-to-1 and 2-to-1 muxes?



Exercise


- Create a 3-to-1 mux using 2-to-1 muxes
 - Inputs: I_0, I_1, I_2 and select bits S_1, S_0
 - Output: Y

S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2

 

Select-bit Ordering

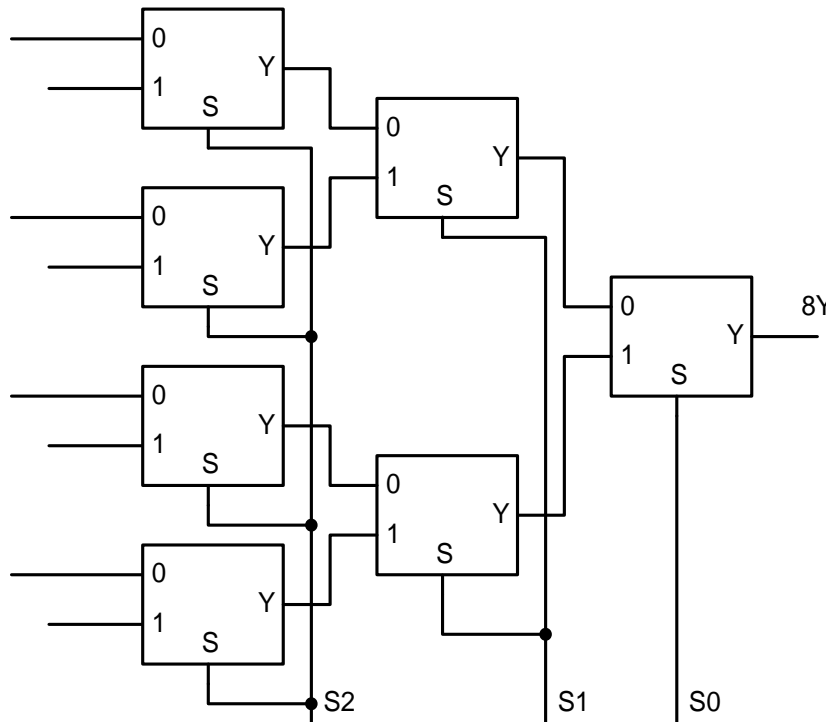- If we connect the select bits as shown to build an 8-to-1 mux, show how to label the inputs (i_0 - i_7) so that the correct input is passed based on the binary value of $S_2:S_0$




Selects			OUT
S_2	S_1	S_0	Y
0	0	0	i_0
1			i_4
0	1		i_2
1			i_6
0	0	1	i_1
1			i_5
0	1		i_3
1			i_7

Alternate Select Bit Ordering Example

- Given 6 inputs: **A-F**, design a **6-to-1** mux from 4- and 2-to-1 muxes that uses the following select bit combinations

S ₂	S ₁	S ₀	Y
0	0	0	A
0	1	0	B
0	1	1	C
1	0	0	D
1	1	0	E
1	1	1	F

S ₂	S ₁	S ₀	Y
0	0	0	A
0	1	0	B
0	1	1	C
1	0	0	D
1	1	0	E
1	1	1	F

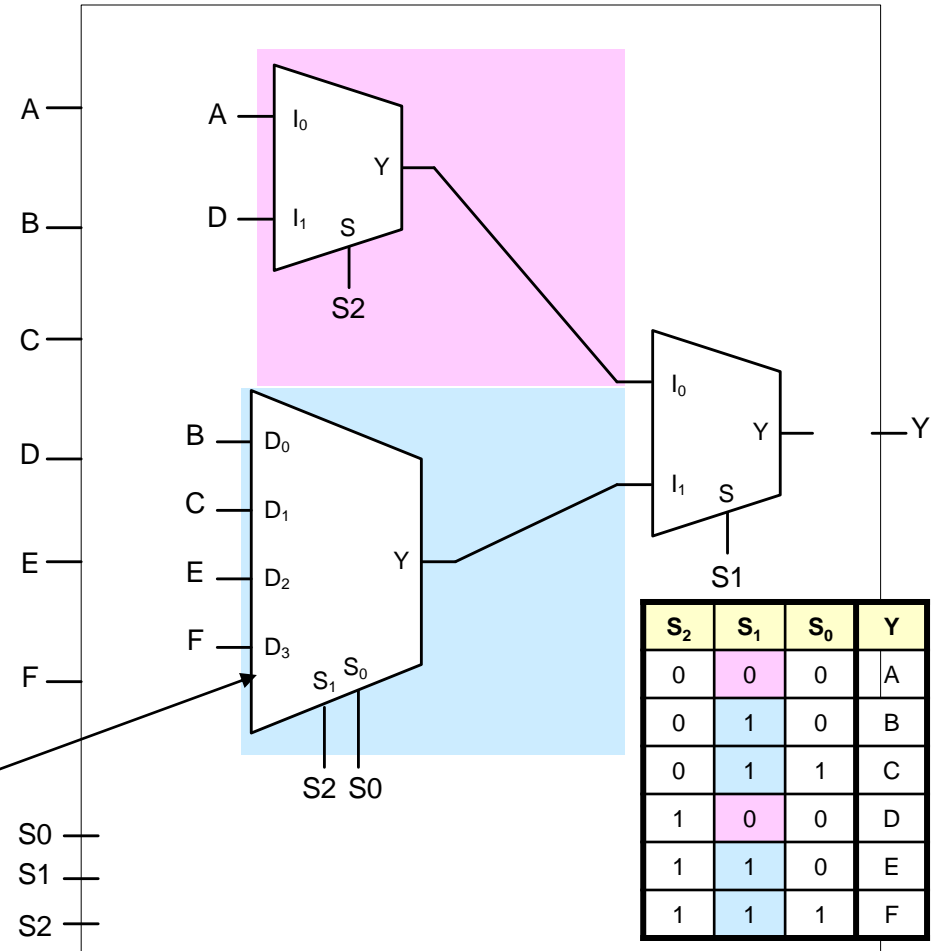

S ₂	S ₁	S ₀	Y
0	0	0	A
0	1	0	B
0	1	1	C
1	0	0	D
1	1	0	E
1	1	1	F

Tip 1: Whatever inputs you connect to a 4-to-1 mux, must correspond to 2 select bits that take on all combinations: 00, 01, 10, 11

Tip 2: For later stages, the select bit you connect must differentiate all potential options on 1 input from all the options on another (e.g. S₁ differentiates A,D from B,C,E,F)

Another way to multiplex

TRI-STATE GATES




Typical Logic Gate

- Gates can output two values: 0 & 1
 - Logic '1' ($V_{dd} = 3V$ or $5V$), or Logic '0' ($V_{ss} = GND$)
 - But they are ALWAYS outputting something!!!
- Analogy: a sink faucet
 - 2 possibilities: Hot ('1') or Cold ('0')
- In a real circuit, inputs cause *EITHER* a pathway from output to V_{DD} *OR* V_{SS}

Hot Water = Logic 1



Cold Water = Logic 0

 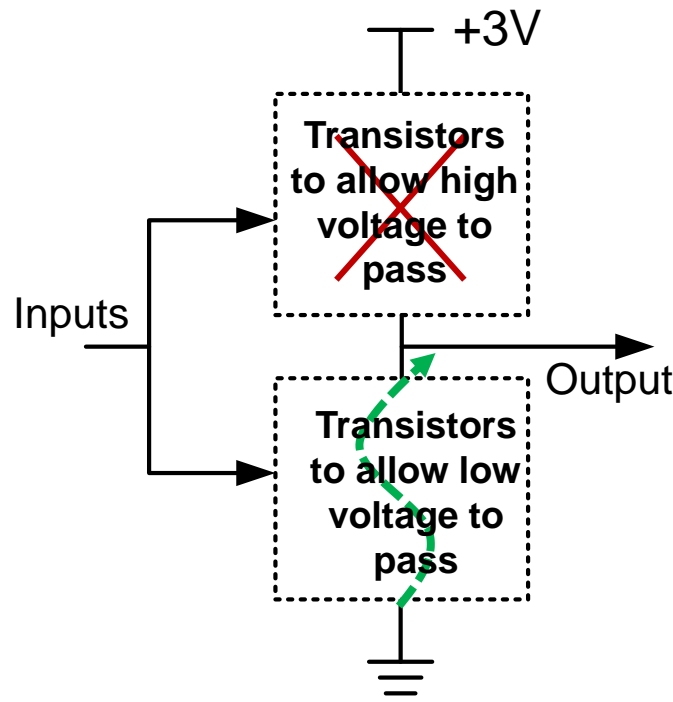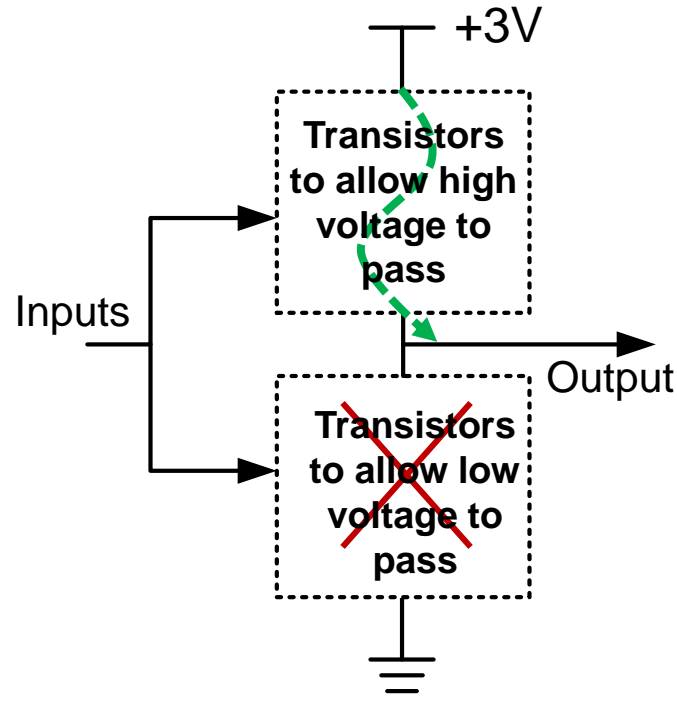(Strapped together so always one type of water coming out)



Output Connections

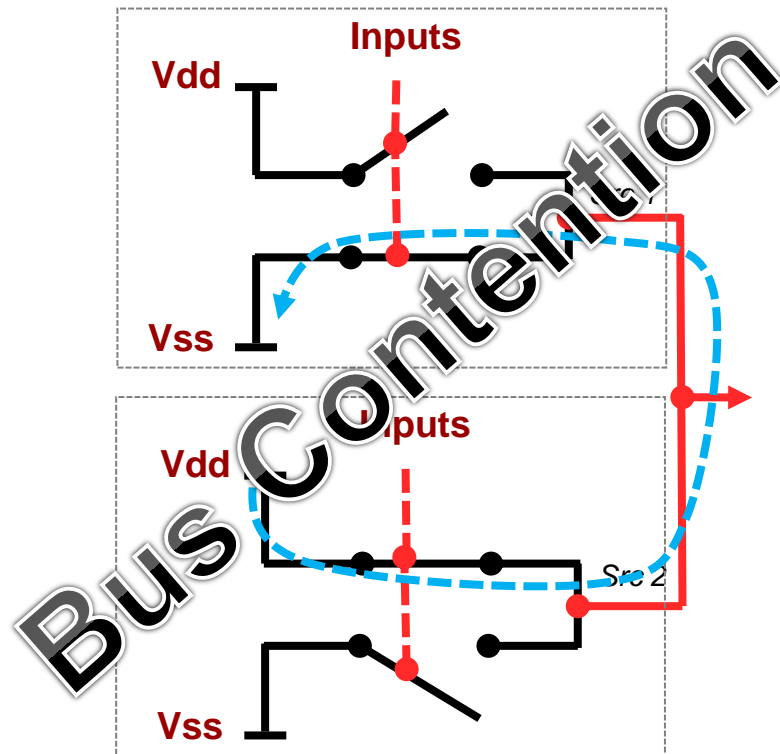 - Can we connect the output of two logic gates together?
- No! Possible short circuit (static, low-resistance pathway from Vdd to GND)
- We call this situation “bus contention”



Tri-State Buffers

- Normal digital gates can output two values: 0 & 1



1. Logic 0 = 0 volts
2. Logic 1 = 5 volts

- Tristate buffers can output a third value:

 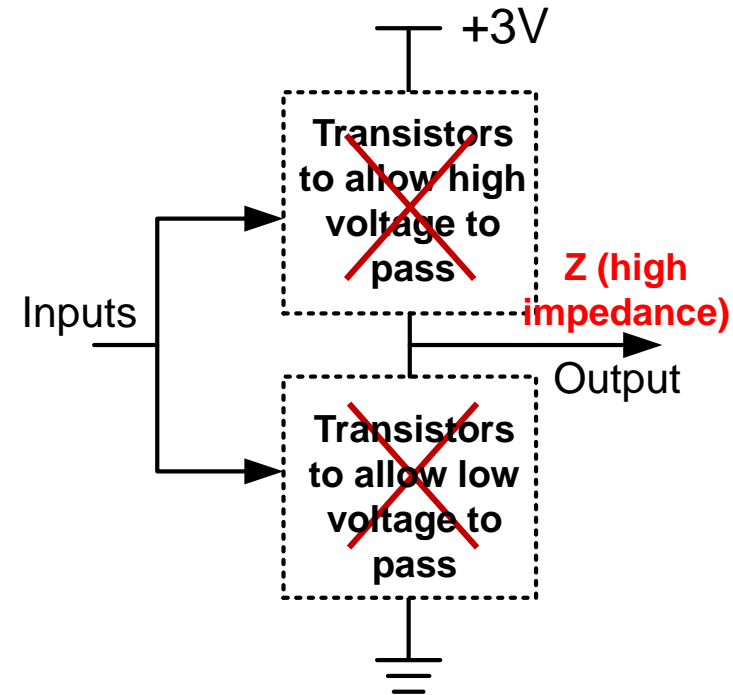3. Z = High-Impedance = "Floating"
(no connection to any voltage source...infinite resistance)

- Analogy: a sink faucet

- 3 possibilities:
 - 1.) Hot water,
 - 2.) Cold water,
 - 3.) NO water



Hot Water = Logic 1


Cold Water = Logic 0

NO Water = Z (High-Impedance)


Tri-State Buffers

- Tri-state buffers have an extra enable input
- When disabled, output is said to be at high impedance (a.k.a. Z)
 - High Impedance is equivalent to no connection (i.e. floating output) or an infinite resistance
 - It's like a brick wall between the output and any connection to source
- When enabled, normal buffer

Tri-State Buffer

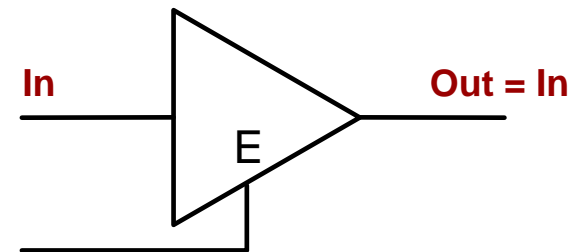

Enable=1

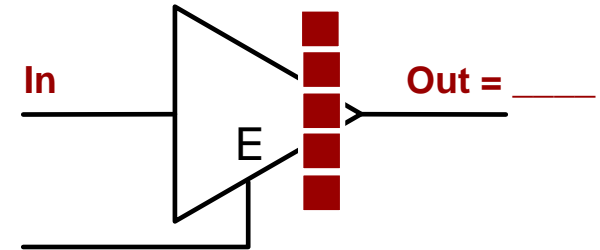


Enable=0

En	In	Out
0	-	Z
1	0	0
1	1	1


Tri-State Buffers

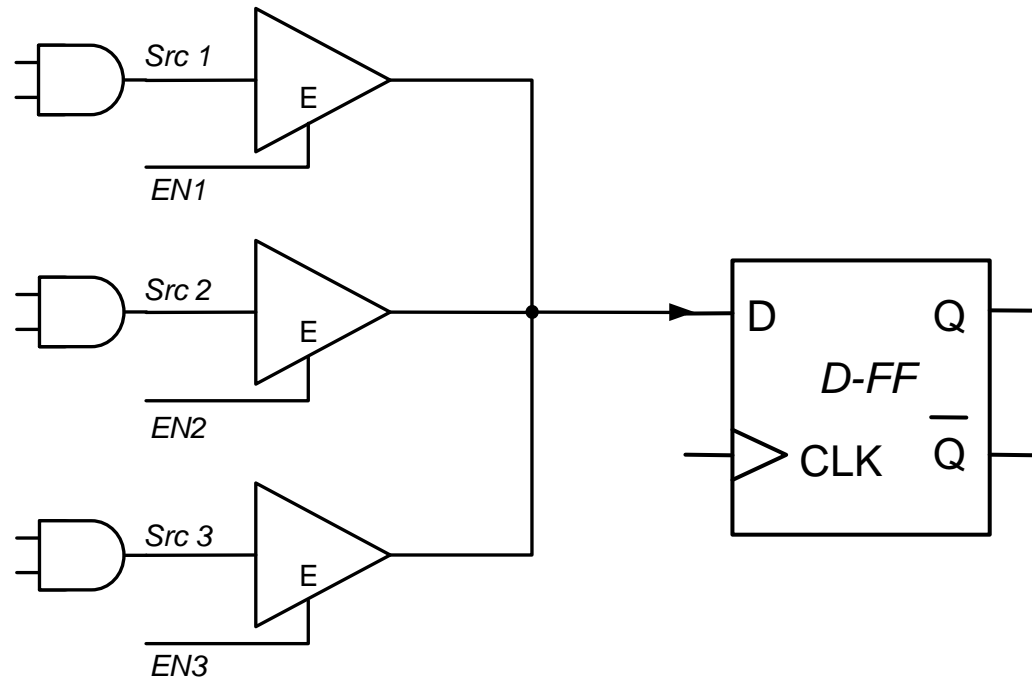- We use tri-state buffers to share one output amongst several sources
- Rule: Only 1 buffer enabled at a time







Tri-State Buffers

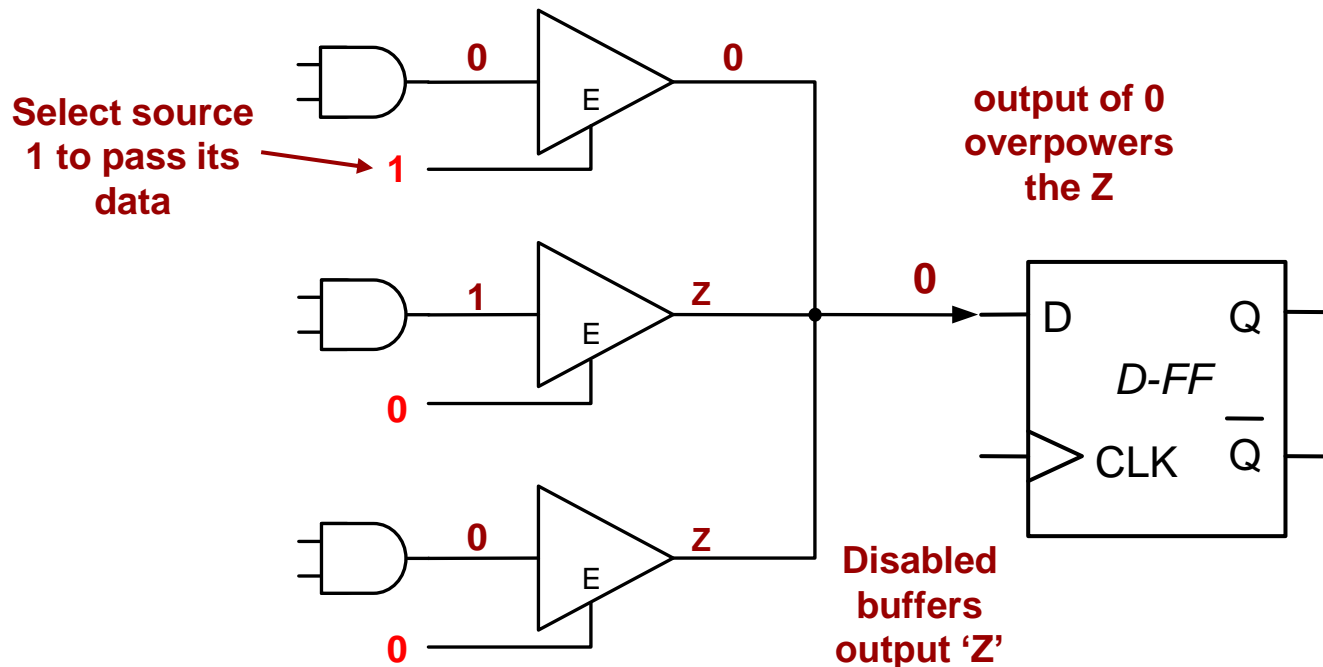- We use tri-state buffers to share one output amongst several sources
- Rule: Only 1 buffer enabled at a time
- When 1 buffer enabled, its output overpowers the Z's (no connection) from the other gates



Enable Polarity

 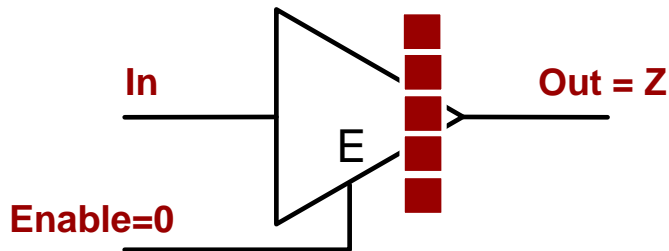  - Side note:** Some tri-states are design to pass the input (be enabled) when the enable is 0 (rather than 1)
 - A inversion bubble is shown at the enable input to indicate the "low" polarity needed to enable the tristate




En	In	Out
0	-	Z
1	0	0
1	1	1

En	In	Out
1	-	Z
0	0	0
0	1	1


Communication Connections

- Multiple entities need to communicate
- We could use
 - Point-to-point connections
 - A shared bus (set of wires)

Separate point to point connections

 


Shared Bus

 

Bidirectional Bus

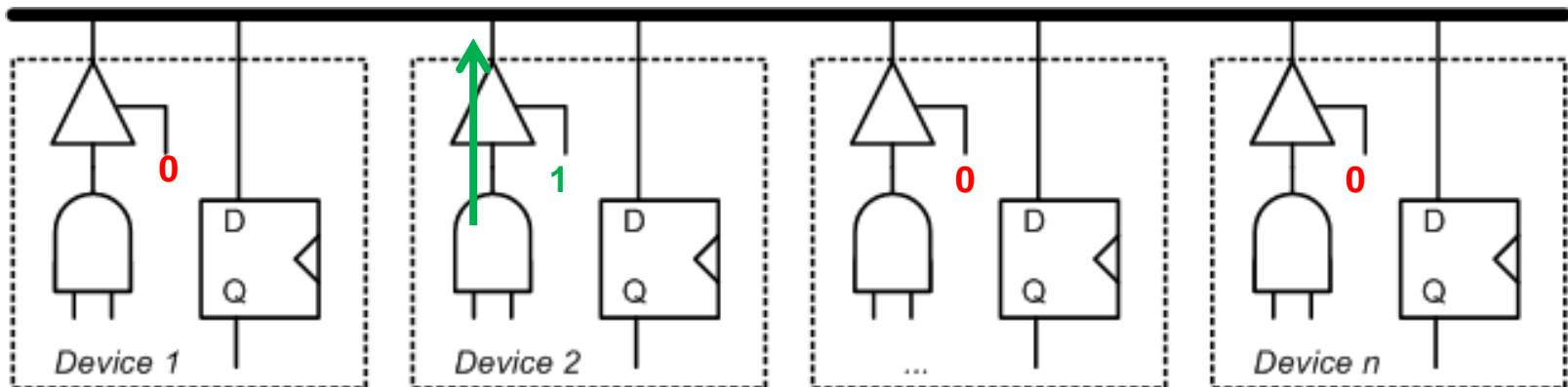- 1 transmitter (otherwise bus contention)
- N receivers
- Each device can send (though 1 at a time) or receive



Tri-State Gates

- Advantage: don't have to know in advance how many devices will be connected together
 - Tri-State gates give us the option of connecting together the outputs of many devices without requiring a circuit to multiplex many signals into one
- Just have to make sure only one is enabled (output active) at any one time.

