

# Unit 12

Adders & Arithmetic Circuits


# Learning Outcomes

- I understand what gates are used to design half and full adders
- I can build larger arithmetic circuits from smaller building blocks

# ADDERS
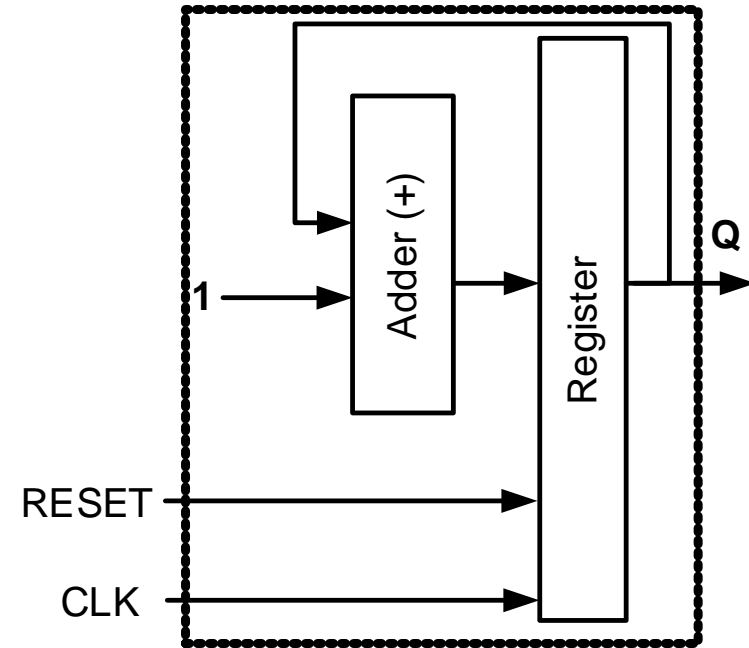
# Adder Intro

- Addition is one of the most common operations performed by computer systems
- We can use adders to build larger components like the \_\_\_\_\_ to the right
- Every clock cycle, the value Q (let's say 4-bits: Q[3:0]), \_\_\_\_\_ to the adder circuit which adds 1 to the value and the register captures that new value on the next clock edge
- The sequence on Q on each clock cycle would be: 0, \_\_\_\_\_...
- Could you design what's inside the adder block? How would you do it?



$$\begin{array}{r}
 0111 = \text{curr } Q \\
 + \quad 1 \\
 \hline
 1000 = \text{next } Q
 \end{array}$$

# Adder Intro

- What if we had to add \_\_\_\_\_  
 two 4-bit numbers,  $X[3:0]$  and  
 $Y[3:0]$ ? Do we have the  
 techniques to build such a  
 circuit directly?


$$\begin{array}{r}
 0110 = X \\
 + 0111 = Y \\
 \hline
 1101
 \end{array}$$

- \_\_\_\_\_  
 - \_\_\_\_\_  
 - \_\_\_\_\_
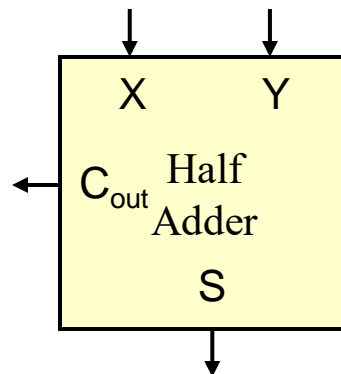
# Adder Intro

- **Idea:** Build a circuit that performs        column of addition and then use                                    of those circuits to perform the overall 4-bit addition
- Let's start by designing a circuit that adds 2-bits: X and Y that are in the same column of addition



$$\begin{array}{r}
 0110 = X \\
 + 0111 = Y \\
 \hline
 1101
 \end{array}$$



# Addition – Half Adders

- Addition is done in columns
  - Inputs are a bit from X and bit from Y, both from the same column
  - Outputs are the Sum Bit and Carry-Out ( $C_{out}$ )
- Design a Half-Adder (HA) circuit that takes in X and Y and outputs S and  $C_{out}$
- Use the truth table to find the gate implementation


X	Y	$C_{out}$	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

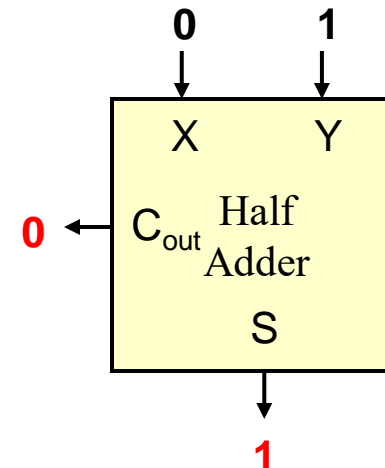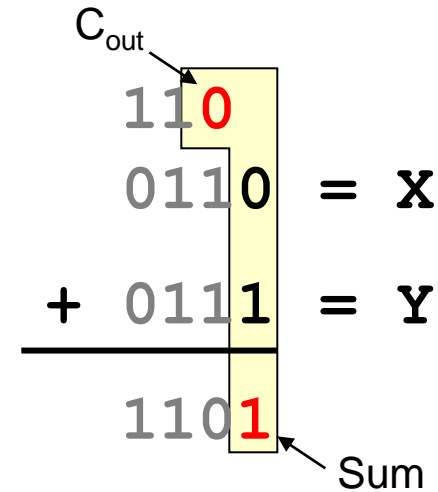
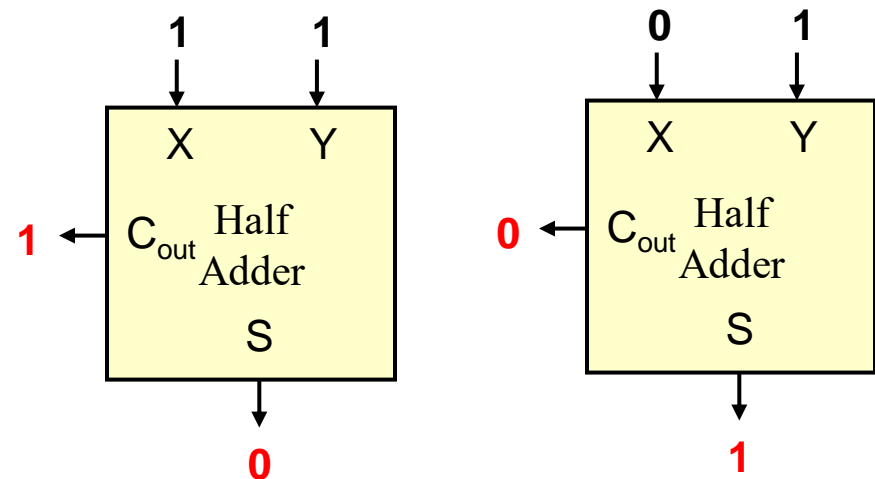
# Problem With Half Adders

- We'd like to use one adder circuit for each column of addition
- Problem:
  - No place for \_\_\_\_\_ of half adder to connect to the \_\_\_\_\_
- Solution
  - Redesign adder circuit to include an \_\_\_\_\_ input for the \_\_\_\_\_

$$\begin{array}{r}
 110 \\
 0110 = X \\
 + 0111 = Y \\
 \hline
 1101
 \end{array}$$







# Addition – Full Adders

- Add a Carry-In input( $C_{in}$ )
- New circuit is called a Full Adder (FA)

X	Y	$C_{in}$	$C_{out}$	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

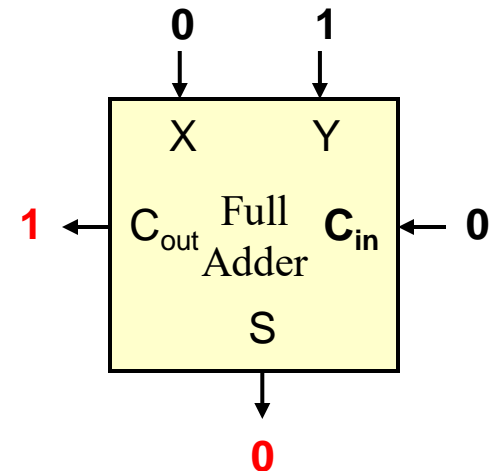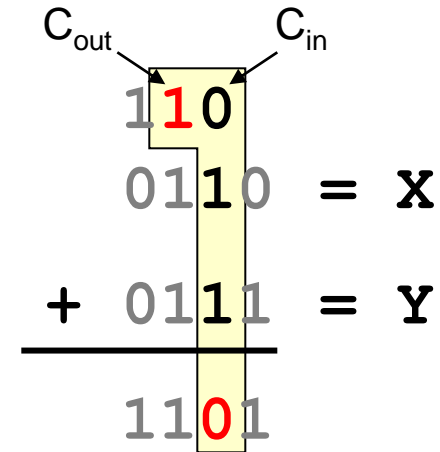

# Addition – Full Adders


- Find the minimal 2-level implementations for  $C_{out}$  and  $S$ ...

X	Y	$C_{in}$	$C_{out}$	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Recall a 2-input XOR can be written in SOP as  $F = x'y + xy'$
 
# XOR and XNOR Gates

- Recall a 2-input XOR can be written in SOP as  $F = x'y + xy'$
- A 2-input XNOR can be written in SOP as  $F = x'y' + xy$




True if an \_\_\_\_\_ # of inputs are true

X	Y	Z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Z \ XY	00	01	11	10
0	0 <sup>0</sup>	1 <sup>2</sup>	0 <sup>6</sup>	1 <sup>4</sup>
1	1 <sup>1</sup>	0 <sup>3</sup>	1 <sup>7</sup>	0 <sup>5</sup>

$$F = X \text{ xor } Y \text{ xor } Z$$

 

True if an \_\_\_\_\_ # of inputs are true

X	Y	Z	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0



Z \ XY	00	01	11	10
0	1 <sup>0</sup>	0 <sup>2</sup>	1 <sup>6</sup>	0 <sup>4</sup>
1	0 <sup>1</sup>	1 <sup>3</sup>	0 <sup>7</sup>	1 <sup>5</sup>

$$F = \overline{X \text{ xor } Y \text{ xor } Z}$$

A checkerboard K-map corresponds to either an XOR or XNOR
  
# Full Adder Logic


- $S =$  \_\_\_\_\_
  - Recall: XOR is defined as true when ODD number of inputs are true...exactly when the sum bit should be 1
- $C_{out} =$  \_\_\_\_\_
  - Carry when sum is 2 or more (i.e. when at least 2 inputs are 1)
  - Circuit is just checking all combinations of 2 inputs


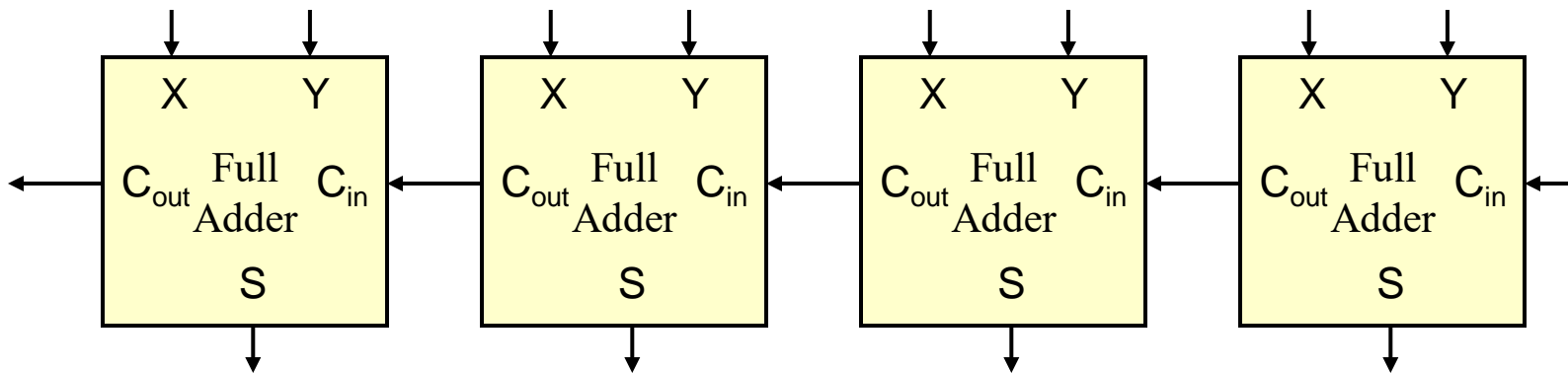
# Addition – Full Adders (1)

- Use 1 Full Adder for each column of addition


$$\begin{array}{r} 0110 \\ + 0111 \\ \hline \end{array}$$


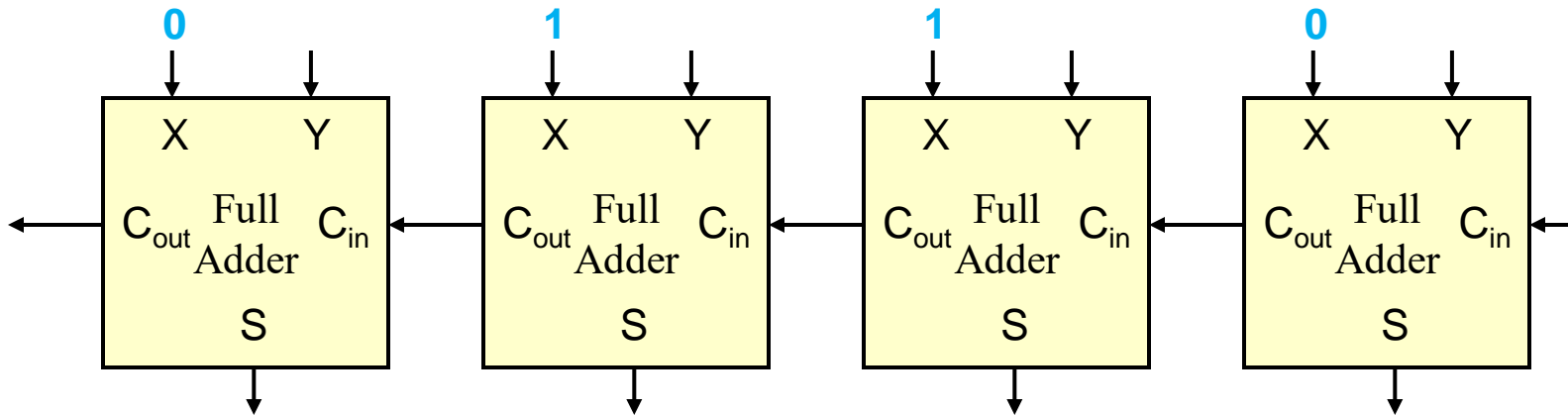
# Addition – Full Adders (2)

- Connect bits of top number to X inputs


$$\begin{array}{r}
 0110 \\
 + 0111 \\
 \hline
 \end{array}$$


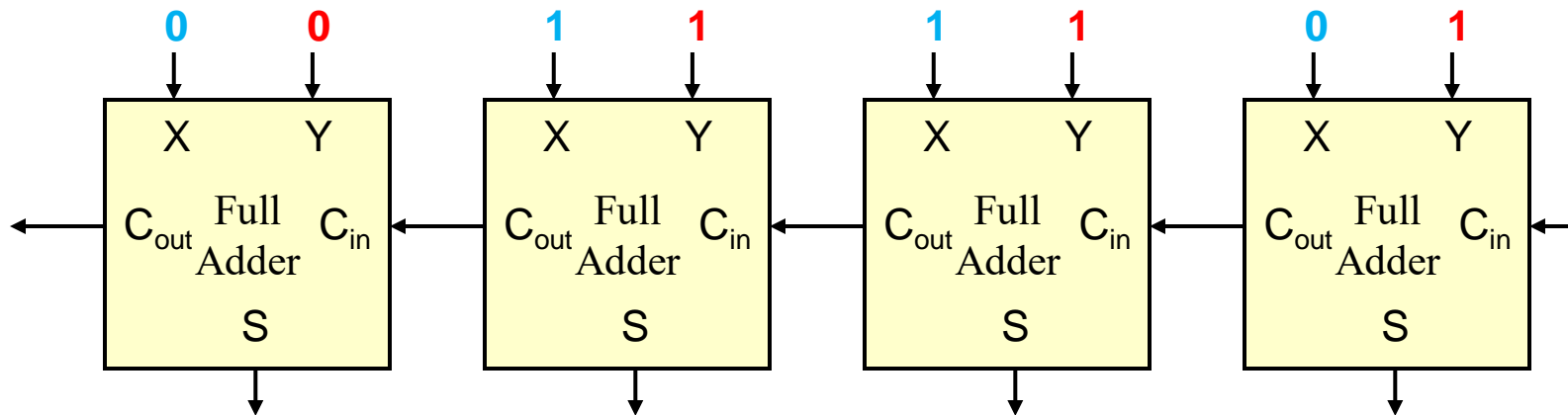
# Addition – Full Adders (3)

- Connect bits of bottom number to Y inputs


$$\begin{array}{r}
 0110 = X \\
 + 0111 = Y \\
 \hline
 \end{array}$$


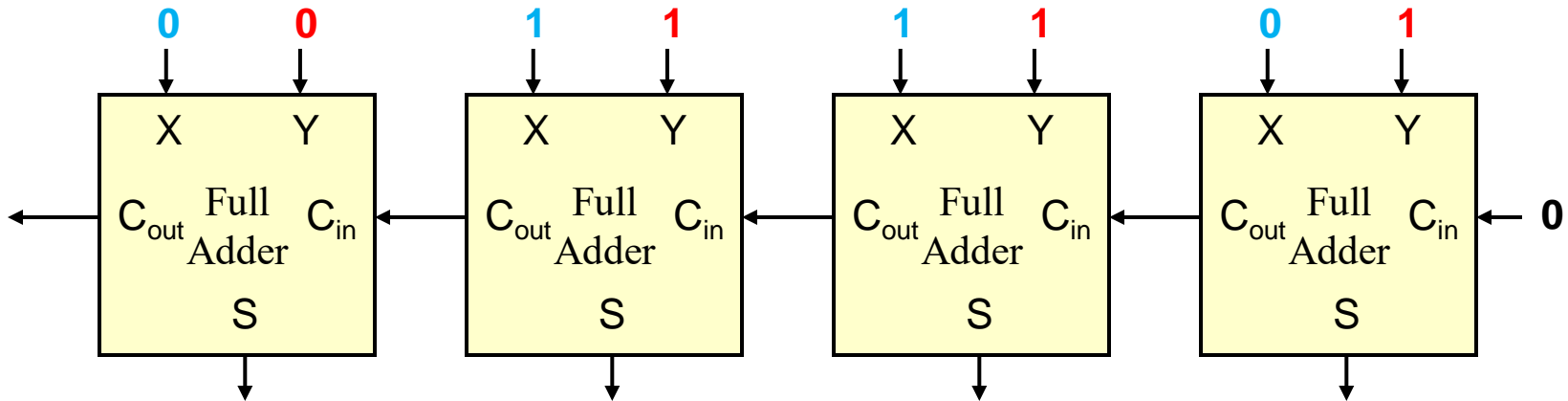
# Addition – Full Adders (4)

- Be sure to connect first  $C_{in}$  to 0

$$\begin{array}{r}
 0110 = X \\
 + 0111 = Y \\
 \hline
 \end{array}$$





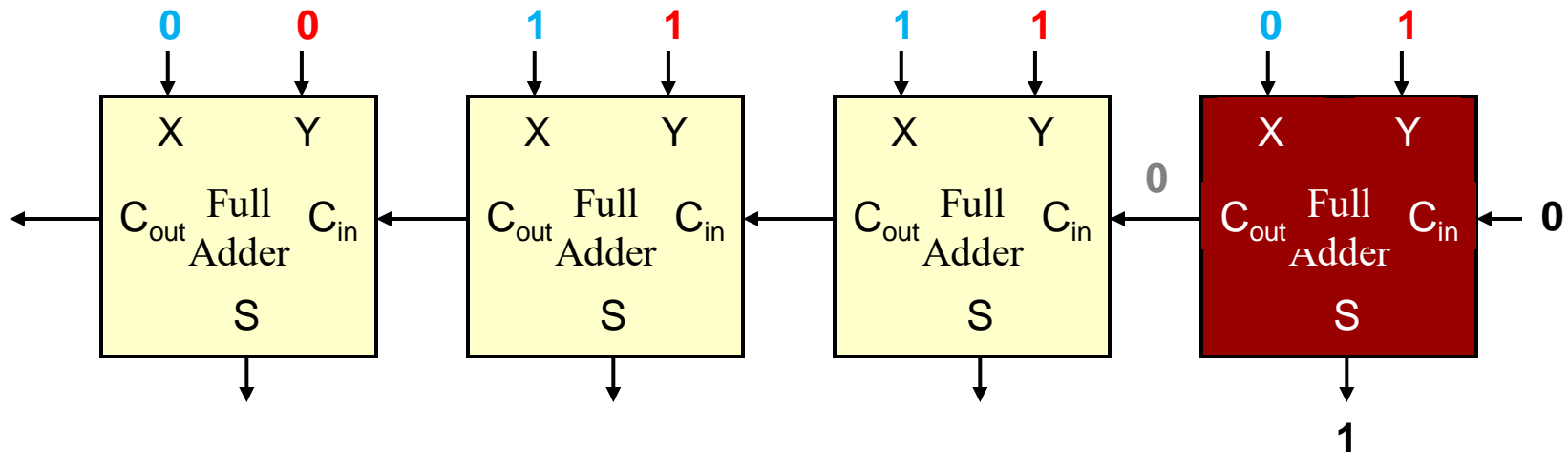
# Addition – Full Adders (5)

- Use 1 Full Adder for each column of addition


$$\begin{array}{r}
 00 \\
 0110 = X \\
 + 0111 = Y \\
 \hline
 1
 \end{array}$$


 
# Addition – Full Adders (6)

- Use 1 Full Adder for each column of addition


$$\begin{array}{r}
 100 \\
 0110 = X \\
 + 0111 = Y \\
 \hline
 01
 \end{array}$$


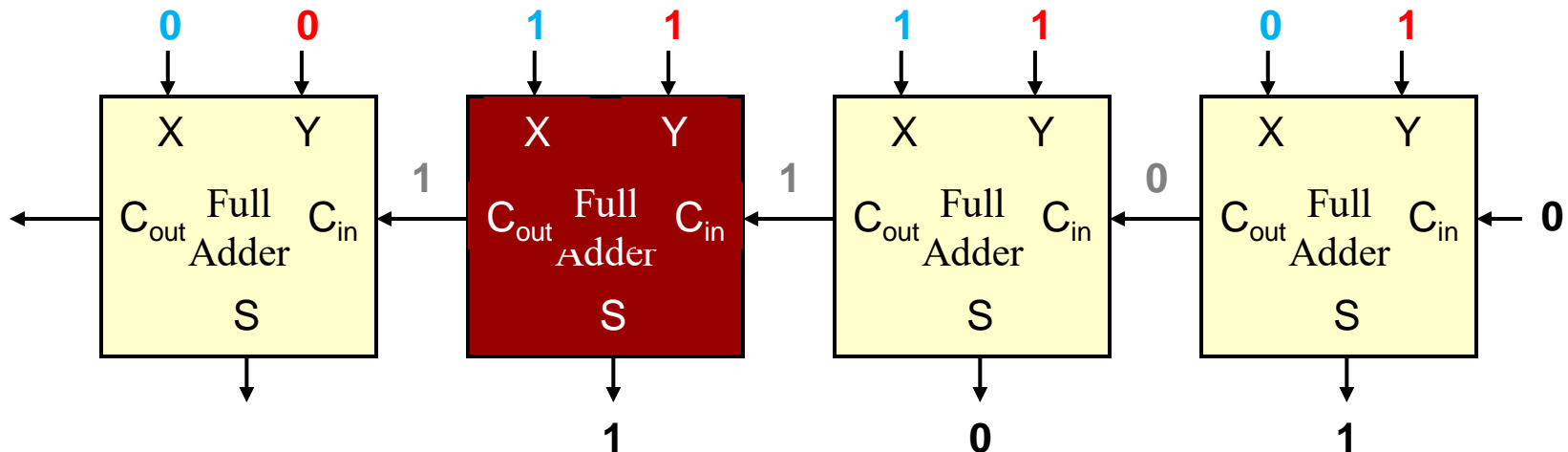
# Addition – Full Adders (7)

- Use 1 Full Adder for each column of addition


$$\begin{array}{r}
 1100 \\
 0110 = X \\
 + 0111 = Y \\
 \hline
 101
 \end{array}$$


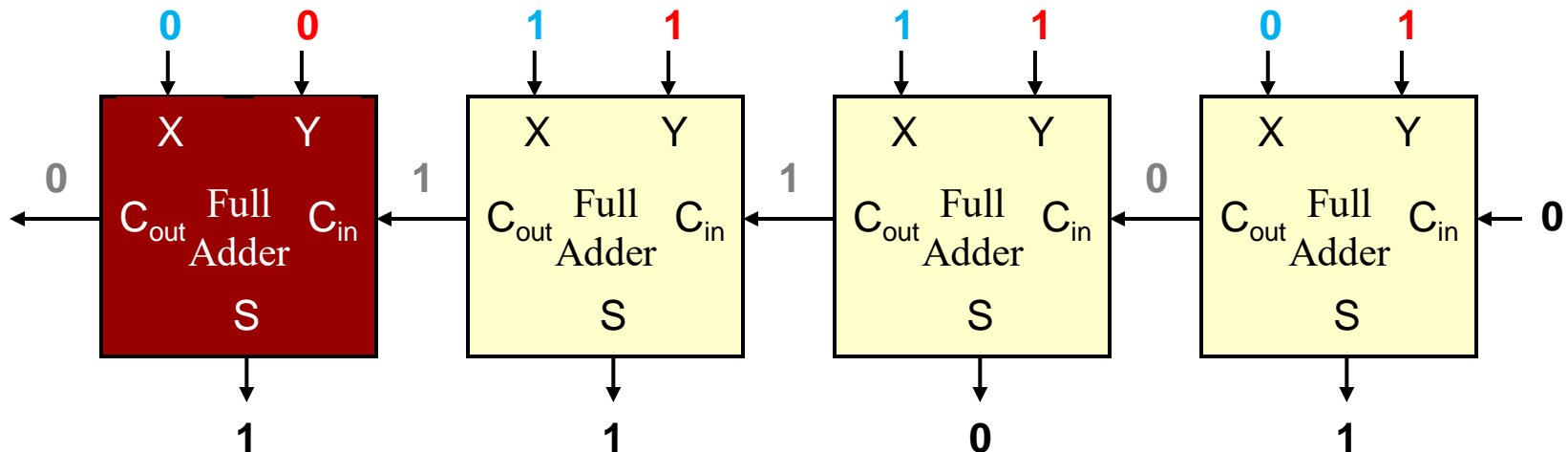
# Addition – Full Adders (8)

- Use 1 Full Adder for each column of addition

$$\begin{array}{r}
 01100 \\
 0110 = X \\
 + 0111 = Y \\
 \hline
 1101
 \end{array}$$




# Performing Subtraction

- To subtract

— \_\_\_\_\_  
— \_\_\_\_\_

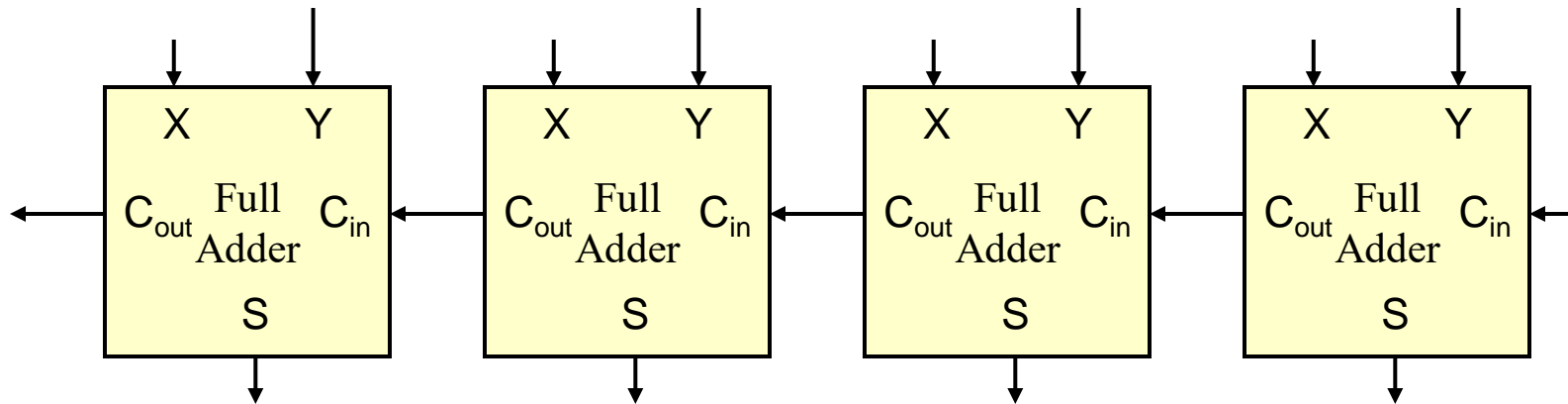
$$\begin{array}{r}
 0101 = X \\
 - 0011 = Y \\
 \hline
 0010
 \end{array}
 \Rightarrow \underline{\hspace{2cm}}$$


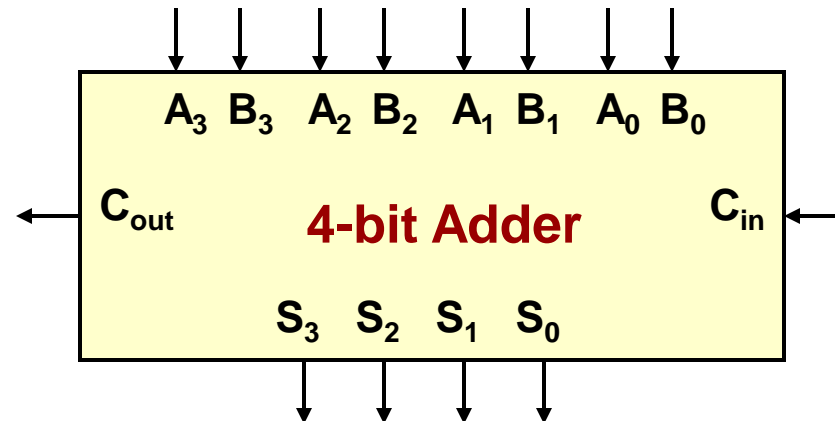
# 4-bit Adders

- We can create a component to perform 4-bit addition

$$\begin{array}{r} A_3 A_2 A_1 A_0 = A \\ + B_3 B_2 B_1 B_0 = B \\ \hline S_4 S_3 S_2 S_1 S_0 = S \end{array}$$



# Device vs. System Labels

- When using hierarchy (i.e. building blocks) to design a circuit be sure to show both device and system labels
  - Device Labels: Signal names used \_\_\_\_\_ the block
    - Placeholder names the **designer/manufacturer of the block** uses to indicate which input/output is which to the outside user (Names may vary; read the manual)
  - System labels: Signal names used \_\_\_\_\_ the block
    - \_\_\_\_\_ signals from the circuit being built and **given by the designer**
    - Can have the same name as the device label if such a signal name exists at the outside level


Analogy: **Formal** and **Actual** parameters

- a and b are like device labels and indicate the names used inside a block.
- x and y are like system labels and represent the actual values to be used.

```
int div(int a, int b)
{ int s = a/b;
  return s; }
int main()
{
  int x=10, y=2;
  int s = div(x,y);
}
```

**Device Labels:**  
Indicate which input/output is which inside the block.

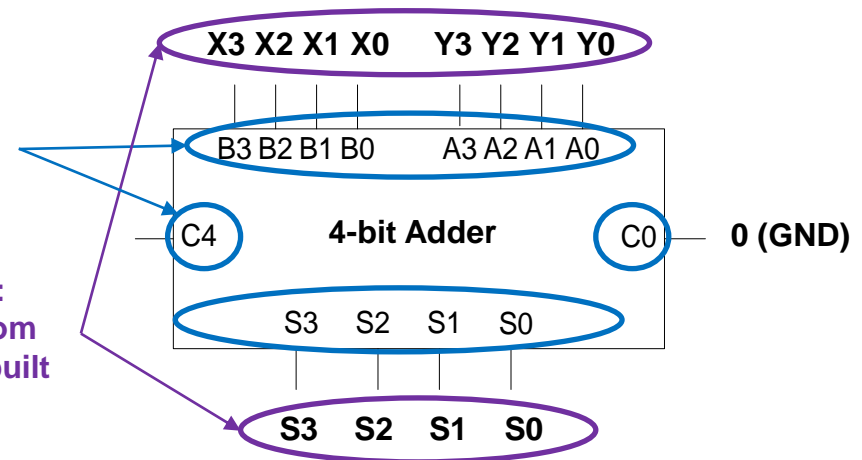**System Labels:**  
Actual signals from the circuit being built





# EXERCISES



  
# Building an 8-bit Adder

- Use (2) 4-bit adders to build an 8-bit adder to add  $X=X[7:0]$  and  $Y=Y[7:0]$  and produce a sum,  $S=S[7:0]$  and a carry-out,  $C_8$ .
  - Label the inputs and outputs and make appropriate connections




 
# Adding Many Bits

- You know that an FA adds  $X + Y + C_i$
- Use FA and/or HA components to add 4 individual bits:  
 $A + B + C + D$



  
# Adding 3 Numbers

- Add  $X[3:0] + Y[3:0] + Z[3:0]$  to produce  $F[?:0]$  using the adders shown plus any FA and HA components you need



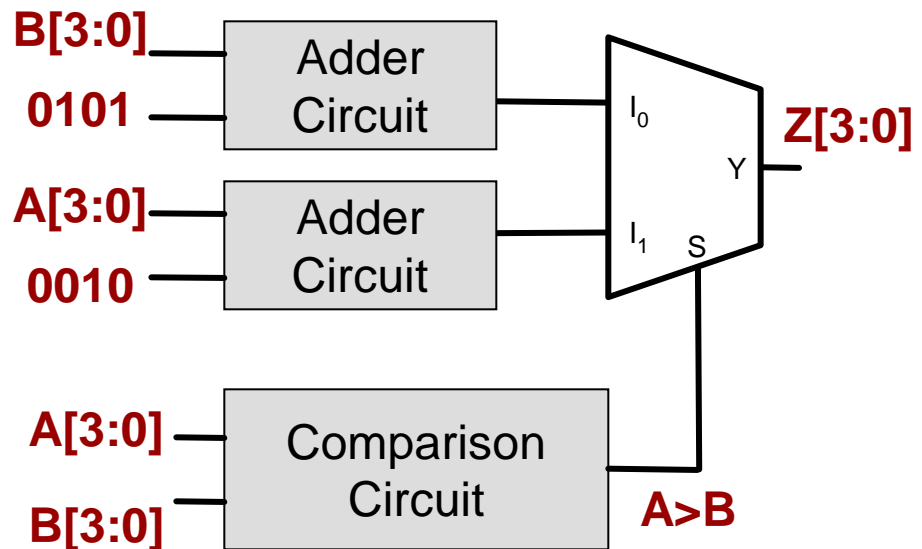
# Mapping Algorithms to HW

- Wherever an if..then..else statement is used usually requires a mux
  - if( $A[3:0] > B[3:0]$ )
    - $Z = A+2$
  - else
    - $Z = B+5$




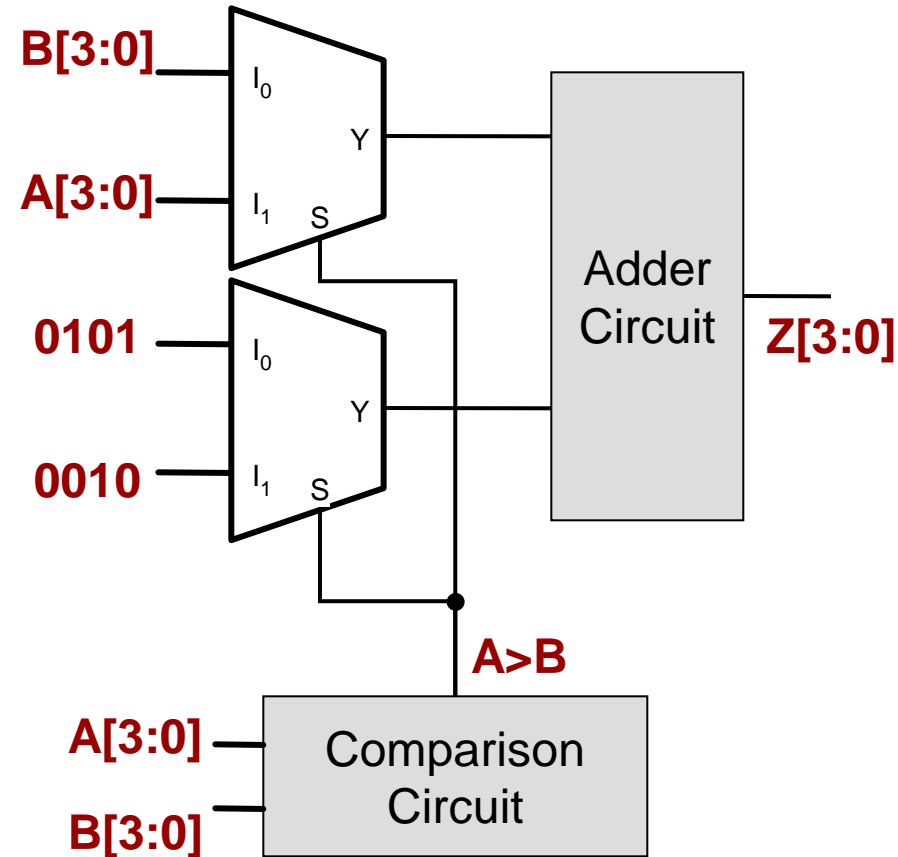
# Mapping Algorithms to HW

- Wherever an if..then..else statement is used usually requires a mux
  - if( $A[3:0] > B[3:0]$ )
    - $Z = A+2$
  - else
    - $Z = B+5$




 
 
# Adder / Subtractor

- If  $sub == 1$ 
  - $Z = X[3:0] - Y[3:0]$
- Else
  - $Z = X[3:0] + Y[3:0]$


  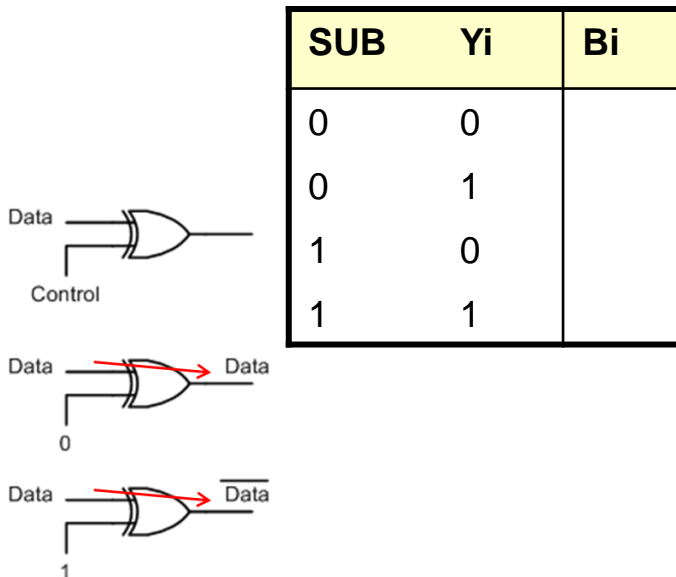
# Adder / Subtractor

- Go back and optimize the muxes by determining what logic function they are actually performing
- If  $sub == 1$ 
  - $Z = X[3:0] - Y[3:0]$
- Else
  - $Z = X[3:0] + Y[3:0]$




# Another Example

- Design a circuit that takes a 4-bit binary number,  $X$ , and two control signals,  $A5$  and  $M1$  and produces a 4-bit result,  $Z$ , such that:
- $Z = X + 5$ , when  $A5, M1 = 1, 0$
- $Z = X - 1$ , when  $A5, M1 = 0, 1$
- $Z = X$ , when  $A5, M1 = 0, 0$

4-bit Adder Input

A5	M1	B3	B2	B1	B0
0	0				
0	1				
1	0				
1	1	d	d	d	d

 



# MULTIPLIERS

# Unsigned Multiplication Review

- Same rules as decimal multiplication
- Multiply each bit of Q by M shifting as you go
- An m-bit \* n-bit mult. produces an m+n bit result (i.e. n-bit \* n-bit produces 2\*n bit result)
- Notice each partial product is a shifted copy of M or 0 (zero)

$$\begin{array}{r} 1010 \text{ M (Multiplicand)} \\ * 1011 \text{ Q (Multiplier)} \\ \hline \end{array}$$

# Unsigned Multiplication Review

- Same rules as decimal multiplication
- Multiply each bit of Q by M shifting as you go
- An m-bit \* n-bit mult. produces an m+n bit result (i.e. n-bit \* n-bit produces 2\*n bit result)
- Notice each partial product is a shifted copy of M or 0 (zero)

	1010	M (Multiplicand)
	* 1011	Q (Multiplier)
	<u>1010</u>	
	1010_	PP (Partial
	0000_	Products)
	<u>+ 1010</u>	
	<b>01101110</b>	P (Product)



# Combinational Multiplier

- Partial Product ( $PP_i$ ) Generation
  - Multiply  $Q[i] * M$ 
    - if  $Q[i]=0 \Rightarrow PP_i = 0$
    - if  $Q[i]=1 \Rightarrow PP_i = M$

	1010	M (Multiplicand)
	* 1011	Q (Multiplier)
	1010	
	1010_	PP (Partial
	0000_	Products)
	+ 1010	
	01101110	P (Product)
  
# Combinational Multiplier

- Partial Product ( $PP_i$ ) Generation
  - Multiply  $Q[i] * M$ 
    - if  $Q[i]=0 \Rightarrow PP_i = \underline{\hspace{2cm}}$
    - if  $Q[i]=1 \Rightarrow PP_i = \underline{\hspace{2cm}}$
  - gates can be used to generate each partial product




# Combinational Multiplier

- Partial Products must be added together
- Combinational multipliers require long propagation delay through the adders
  - propagation delay is proportional to the number of partial products (i.e. number of bits of input) and the width of each adder
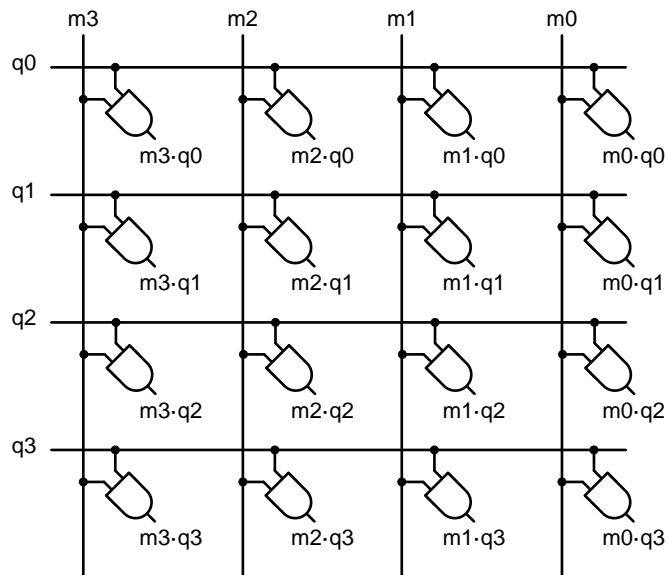
# Multiplication Overview


- Combinational: Array multiplier uses an array of adders
  - Can be as simple as N-1 ripple-carry adders for an NxN multiplication



**AND Gate Array produces partial product terms**

		m3	m2	m1	m0		
<b>x</b>		q3	q2	q1	q0		
		m3q0	m2q0	m1q0	m0q0		
		m3q1	m2q1	m1q1	m0q1	+	
		m3q2	m2q2	m1q2	m0q2	-	
	+	m3q3	m2q3	m1q3	m0q3	↓	↓
p7	p6	p5	p4	p3	p2	p1	p0

# Array Multiplier

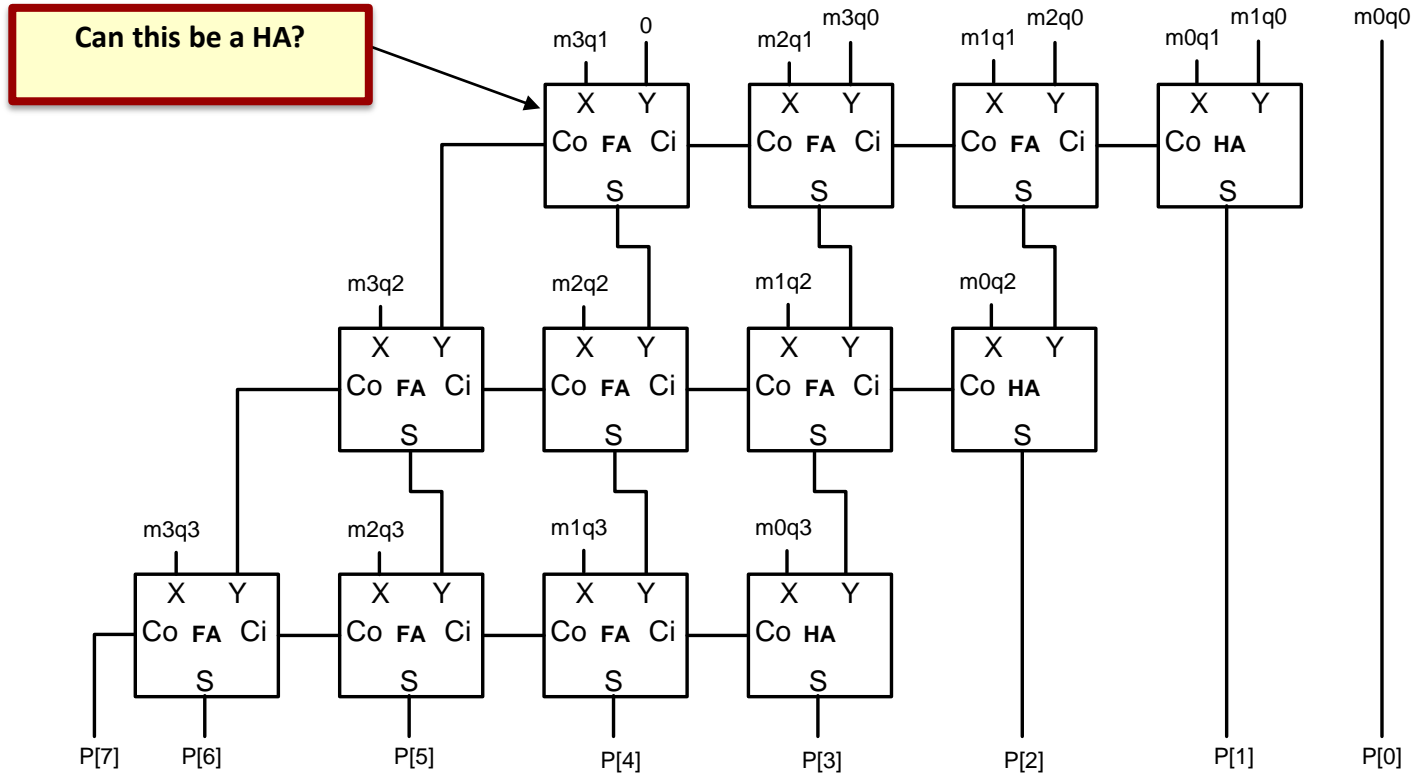

- Maximum n-bit \* n-bit delay is proportional to \_\_\_\_\_