

# Unit 16

Computer Organization  
Design of a Simple Processor

# INSTRUCTION SET OVERVIEW

# Instruction Set Overview

- The instruction set defines the \_\_\_\_\_ interface to the \_\_\_\_\_ and memory system
- Most processors define their own \_\_\_\_\_ instruction set unless they are trying to be compatible with some other vendor
  - Which means code compiled for one processor will \_\_\_\_\_ on another
- Instruction set is the \_\_\_\_\_ the HW processor can understand and the SW is composed with
  - Usually the compiler is the one that translates the high level software into the 1s and 0s (aka \_\_\_\_\_) that control the processor

# Components of the Instruction Set

- Instruction sets specify...
  - Maximum bit widths for \_\_\_\_\_ and \_\_\_\_\_
    - 8-, 16-, 32- or 64-bit
  - Which instructions are implemented
    - ADD, NEGate, SUB, MUL
  - How many \_\_\_\_\_ the processor provides to instructions
    - Usually 16 to 64
  - How each instruction is \_\_\_\_\_ binary (aka "machine code")

# Instruction Set Architecture (ISA)

- 2 instruction set approaches
  - \_\_\_\_\_ = \_\_\_\_\_ instruction set computer
    - Large, rich set of instructions (vocabulary)
    - Useful when programmers actually wrote \_\_\_\_\_
    - More work per instruction, slower clock cycle
  - \_\_\_\_\_ = \_\_\_\_\_ instruction set computer
    - Small, basic, but *sufficient* instruction set (vocabulary)
    - With maturation of \_\_\_\_\_, manual programming at assembly level is more rare
    - Less work per instruction, faster clock cycle
    - Usually a simple and small set of instructions with regular format facilitates building faster processors


# Kinds of Instructions

- Most assembly/machine instructions fall into one of **three** categories
- \_\_\_\_\_
  - Example: `ADD r1, r2, r3 // r1 = r2 + r3`
- \_\_\_\_\_ **(to and from memory)**
  - Example: `LOAD r1, addr // set register 1 to the value in mem. at addr`
- \_\_\_\_\_
  - Example: `JUMP addr // Go to instruction in mem. at addr`
- Notice that each instruction has predefined interpretation of the operands
  - `LOAD r1, addr // interprets 1st operand as a register number and 2nd as an address`
  - The interpretation of the meaning of the operand is part of the instruction set and known as "**addressing modes**"


# Operands

- Addressing modes refers to how an instruction specifies where the operands are
- Can be in a
  - \_\_\_\_\_ ,
  - \_\_\_\_\_ , or a
  - \_\_\_\_\_ that is part of the instruction itself (**aka. \_\_\_\_\_ value**)
- Most RISC processors: All data operands for arithmetic/logic instructions must be in a **register**
  - This allows the hardware to be simpler and faster


**ADD r1, r2, r3**

 

**LOAD r5, 0x1ac8**

 

**ADD r5, r3, immediate**

 

# DESIGN OF A SIMPLE INSTRUCTIONS SET AND PROCESSOR



# What Shall We Do?


- Let's design a simple processor to understand the entire flow from writing software to designing the hardware
  - This may not be the most advanced processor but the goal is to give you a fully working example from software to hardware

# The Instruction Set (1)

- To start we will define the instruction set
- Let's use \_\_\_-bit data values (i.e. all data operands will be \_\_\_-bits)
- Let's make this a simple calculator-like processor that can perform at least the following 3 operations:
  - \_\_\_\_\_
  - \_\_\_\_\_
  - \_\_\_\_\_
- Goal is to evaluate simple arithmetic expressions:  $(7+4-5)\&3$
- To keep the number of bits needed to code an instruction to a minimum, let's use an \_\_\_\_\_ architecture where the \_\_\_\_\_ register is always one \_\_\_\_\_
  - ADD 7 means: \_\_\_\_\_
  - SUB 5 means: \_\_\_\_\_
 
# The Instruction Set (2)

- Let's assume the output of this computer is just 4 LED's to display a 4-bit binary number
- We'll provide some additional instructions to help us perform the calculations:
  - \_\_\_\_\_
  - \_\_\_\_\_
  - \_\_\_\_\_
- That leaves us with 6 total instructions
  - How many bits do we need for the opcode of our instructions? \_\_\_\_\_
- If we want to store data/constants in our instructions (e.g. ADD 7, SUB 5) how many additional bits do we need in our instruction? \_\_\_\_\_
- Instructions need \_\_\_ opcode + \_\_\_ data bits = \_\_\_-bits
  - Let's round up to 8-bits for each instruction



**Output LEDs**  
(Display = 7 = 0111<sub>2</sub>)

7	6	5	4	3	2	1	0
Opcode (3-bits)			Unu sed	Constant (4-bits)			

**Chosen Instruction Format**

# Compilation

- Consider the following "high-level" code  
(7 - 4 + 6) & 3
- "Compile" it to an appropriate instruction sequence (i.e. assembly)
  - **Assembly** refers to the human readable syntax of each instruction

## Instruction Set Summary

- ADD k (ACC += k)
- SUB k (ACC -= k)
- AND k (ACC &= k)
- LOAD k (ACC = k)
- CLR (ACC = 0)
- OUT (OUT = ACC)


- Now we need to convert to binary...

# Defining the Machine Code

- **Machine code** refers to the \_\_\_\_\_ representation of each instruction.
- We first need to define the actual opcodes so we can translate the assembly you wrote on the previous slide into binary for the hardware to execute
- Before we do that, let's consider the hardware design as this will help us choose appropriate opcodes
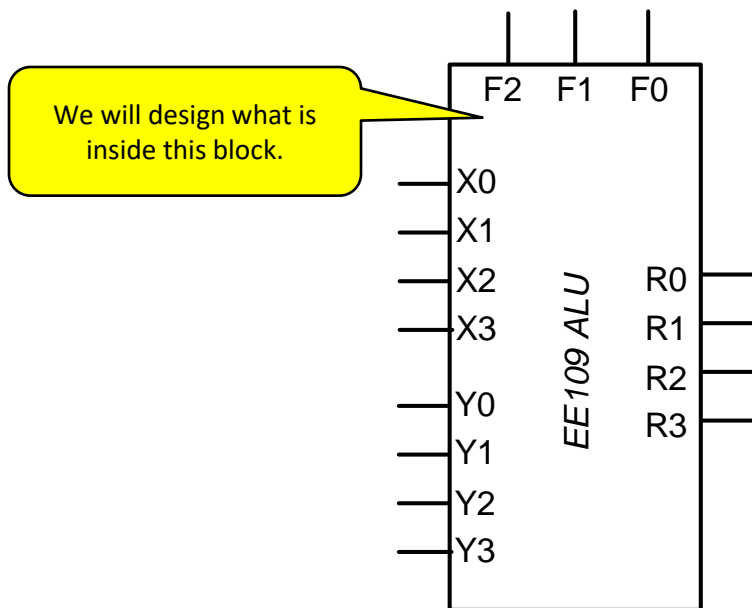
# Arithmetic and Logic Unit


- Let's use the ALU we designed in a previous unit...



We just made up these code assignments and the various operations. Remember, we definitely need to support ADD, SUB, AND, and CLR (R=0).

F[2:0]	Op./Result
000	R = X + Y
001	R = X - Y
010	R = X
011	R = Y - X
100	R = X & Y
101	Unused
110	R = 0
111	Unused

# Completed ALU

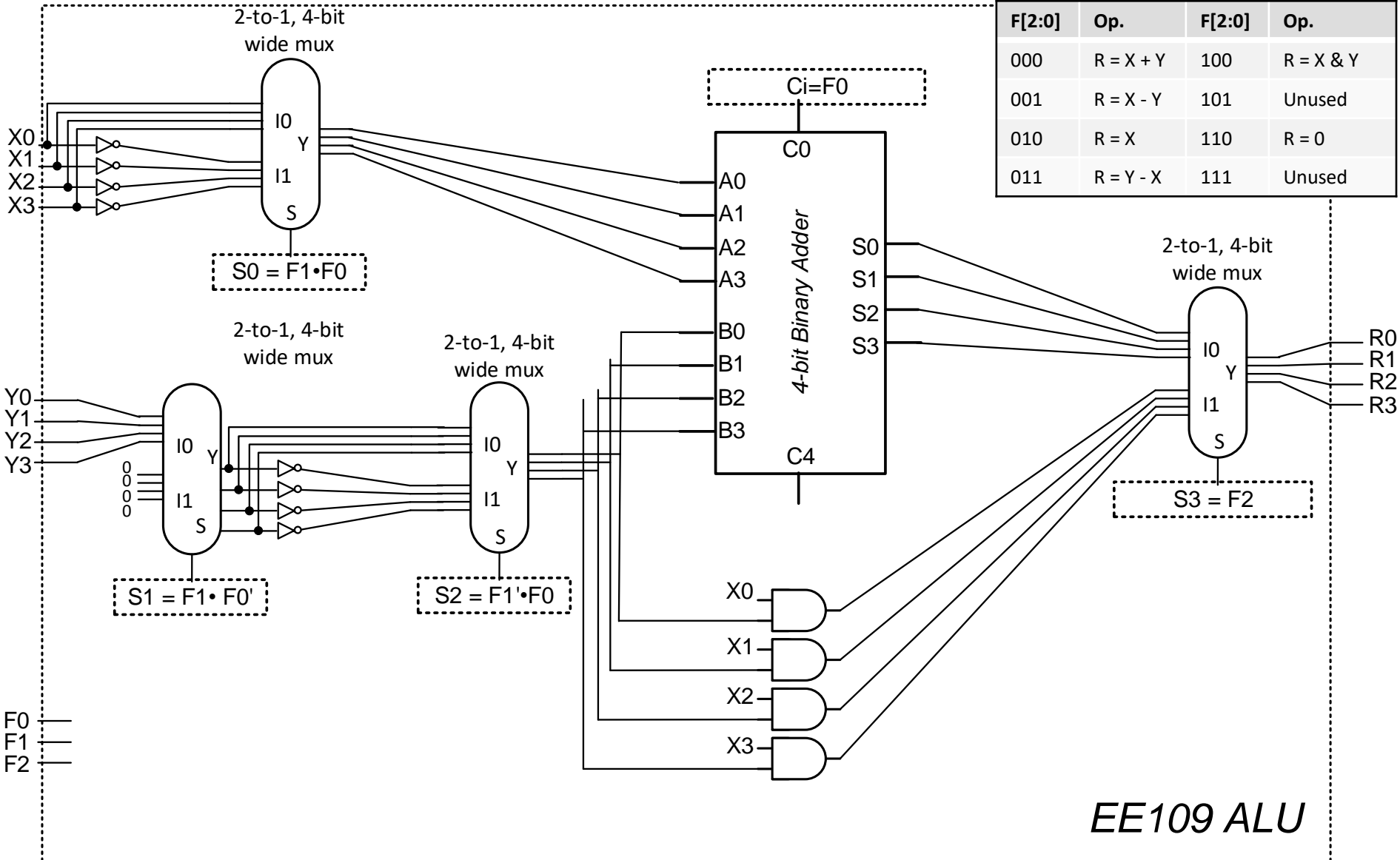

# Control Logic

R	FS[2:0]	S0	S1	S2	Ci	S3
X+Y	000	0	0	0	0	0
X-Y	001	0	0	1	1	0
X	010	0	1	0	0	0
Y-X	011	1	0	0	1	0
X & Y	100	0	0	0	d	1
unused	101	d	d	d	d	d
0	110	d	1	0	d	1
unused	111	d	d	d	d	d

		F0	
		0	1
F2F1	00		1
	01		
	11		d
	10		d

S2

		F0	
		0	1
F2F1	00		1
	01		1
	11	d	d
	10	d	d

Ci

- $S0 = F1 \bullet F0$
- $S1 = F1 \bullet F0'$
- $S2 = F1' \bullet F0$
- $Ci = F0$
- $S3 = F2$

		F0	
		0	1
F2F1	00		
	01		1
	11	d	d
	10		d

S0

		F0	
		0	1
F2F1	00		
	01	1	
	11	1	d
	10		d

S1

		F0	
		0	1
F2F1	00		
	01		
	11	1	d
	10	1	d


S3



# Defining the Machine Code Format

- Using the ALU design can you suggest opcodes for the various instructions?
  - The accumulator (ACC) will be connected to the result of the ALU
  - But should the ACC be connected to the X or Y input of the ALU?
    - Important: We achieve Load by passing `__` through the ALU to the ACC, so we need the constant to come in on X (so `_____` cannot)

<u>Instruction Set Summary</u>		
• ADD	k	(ACC += k)
• SUB	k	(ACC -= k)
• AND	k	(ACC &= k)
• LOAD	k	(ACC = k)
• CLR		(ACC = 0)
• OUT		(OUT = ACC)

 

F[2:0]	Op./Result
000	R = X + Y
001	R = X - Y
010	R = X
011	R = Y - X
100	R = X & Y
101	Unused
110	R = 0
111	Unused


Instruc.	OPCODE	Op./Result
	000	
	001	
	010	
	011	
	100	
	101	
	110	
	111	

# Assembler

- Now translate the assembly you found from a few slides back to machine code and show it as 2 hex digits per instruction
- The "high-level" code was  
(7 - 4 + 6) & 3
- "Compile" it to an appropriate instruction sequence (i.e. assembly)

- CLR = \_\_\_\_\_
- ADD 7 = \_\_\_\_\_
- SUB 4 = \_\_\_\_\_
- ADD 6 = \_\_\_\_\_
- AND 3 = \_\_\_\_\_


Instruc.	OPCODE	Op./Result
ADD	000	ACC = ACC + C
OUT	001	OUT = ACC
LOAD	010	ACC = C
SUB	011	ACC = ACC - C
AND	100	ACC = ACC & C
-	101	Unused
CLR	110	ACC = 0
-	111	Unused

 


**Chosen Instruction  
Format**
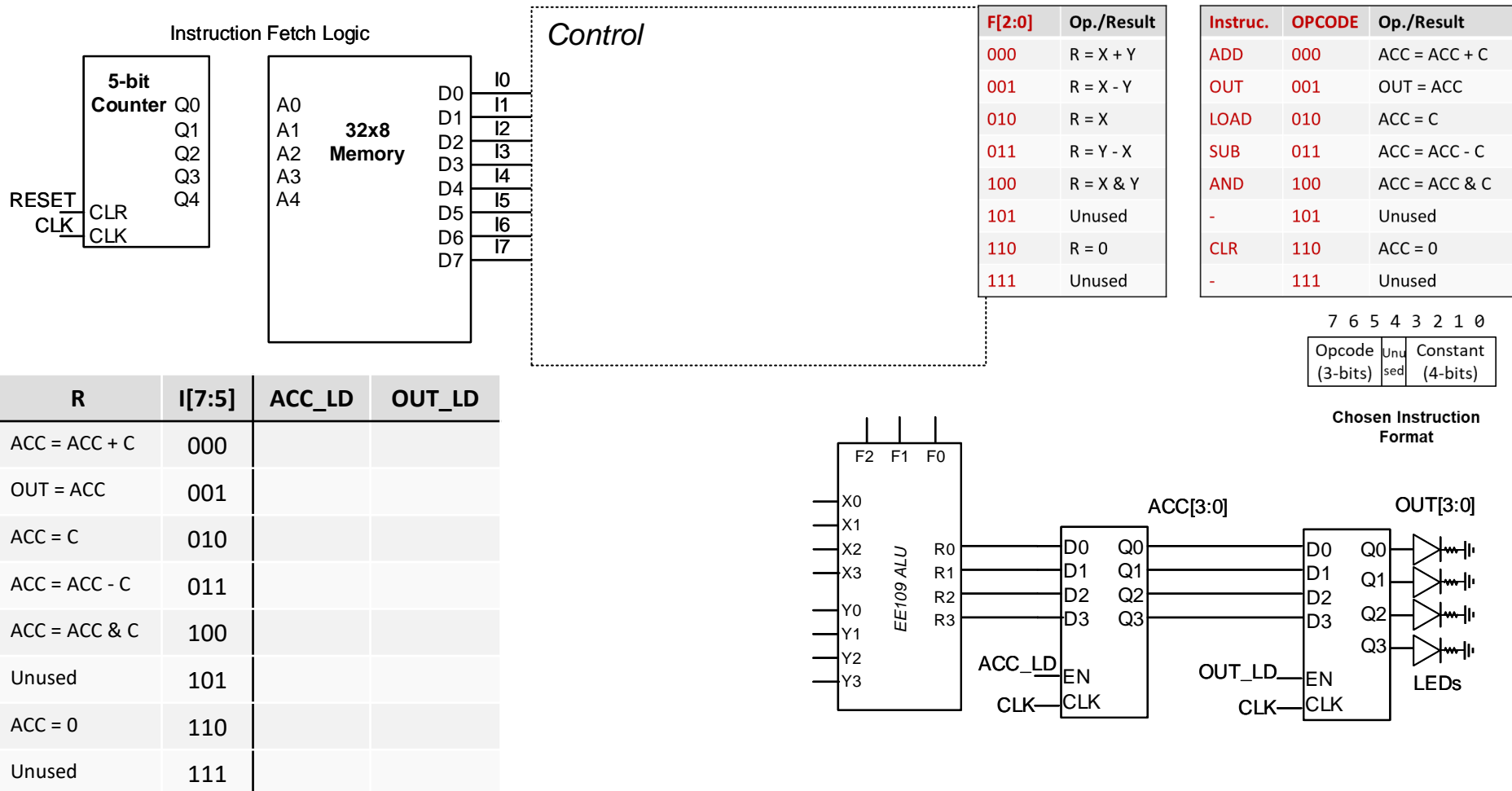
# Processor Datapath

- Now let's consider the processor data path



# Sample Execution of SUB 11

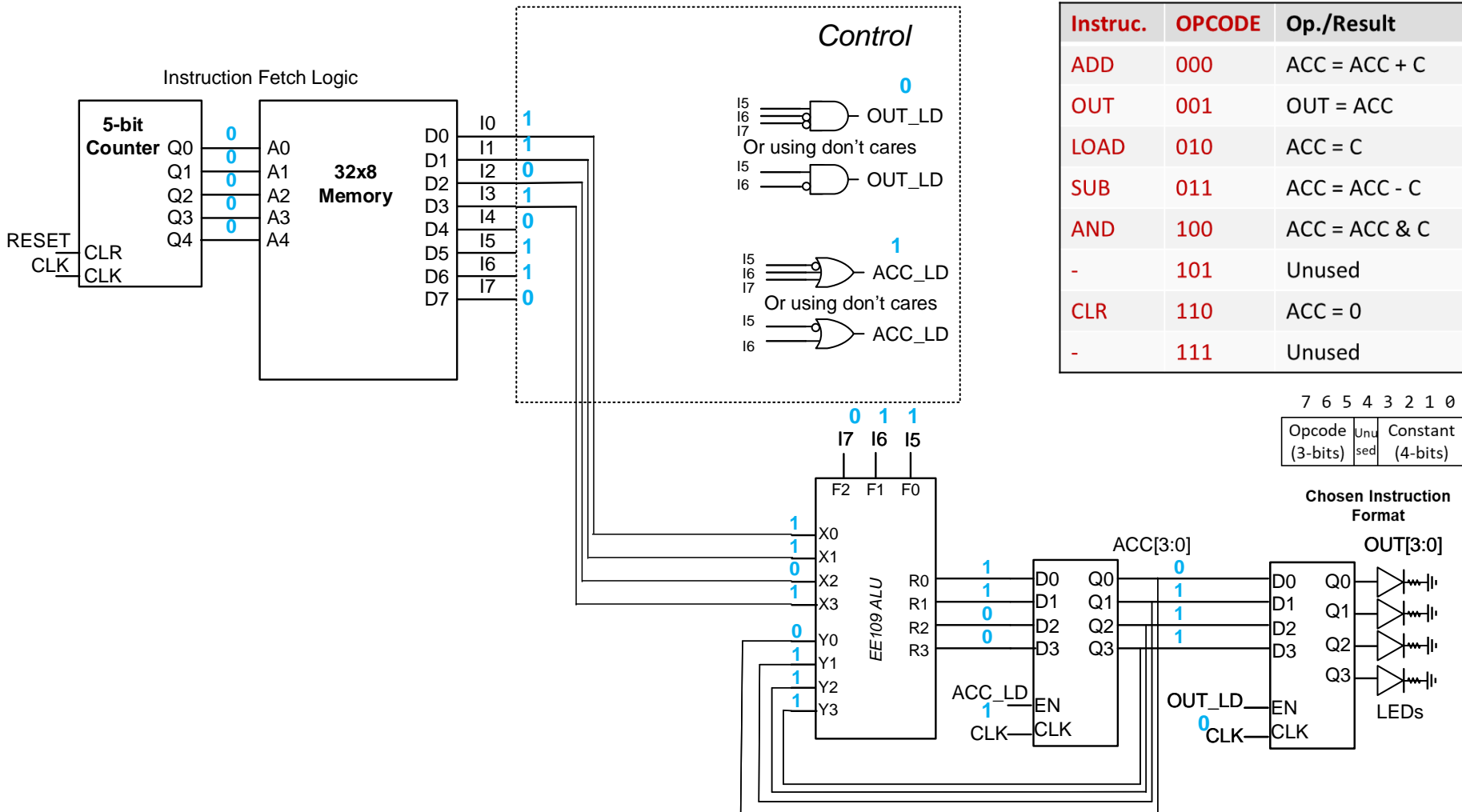


# A Problem

- Write assembly for:  
–  $((7 \ \& \ 3) + (6 \ \& \ 5))$

- ---
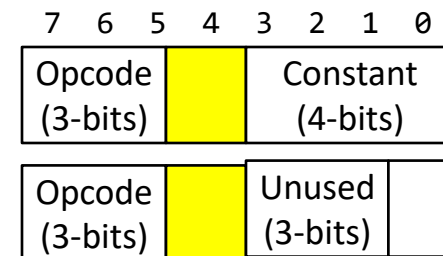
# A Solution

- Let's modify our processor as follows:
  - Add \_\_\_\_\_ for temporary storage: \_\_\_\_\_
    - Could add more but we'll keep it simple
  - A new instruction to save the \_\_\_\_\_ to a register:  
 SAVE Rx (\_\_\_\_\_)
  - Update ALU instructions to be able to specify a \_\_\_\_\_ rather than just a constant  
 ADD Rx (ACC = ACC + Rx)  
 SUB Rx (ACC = ACC - Rx)  
 AND Rx (ACC = ACC & Rx)  
 LOAD Rx (ACC = Rx)
  - Update the instruction format to use the leftover bit to indicate whether the operand is a constant or should come from a register




**New Instruction Format**

# Updated Assembly


- Write assembly for:
  - ( (7 & 3) + (6 & 5) )
- New assembly & machine code

Instruc.	OPCODE	Op./Result
ADD	000	ACC = ACC + C/R
OUT	001	OUT = ACC
LOAD	010	ACC = X
SUB	011	ACC = ACC - C/R
AND	100	ACC = ACC & C/R
-	101	Unused
CLR	110	ACC = 0
SAVE Rx	111	Rx = ACC

 

**New Instruction  
Format**

# Updated Processor Datapath

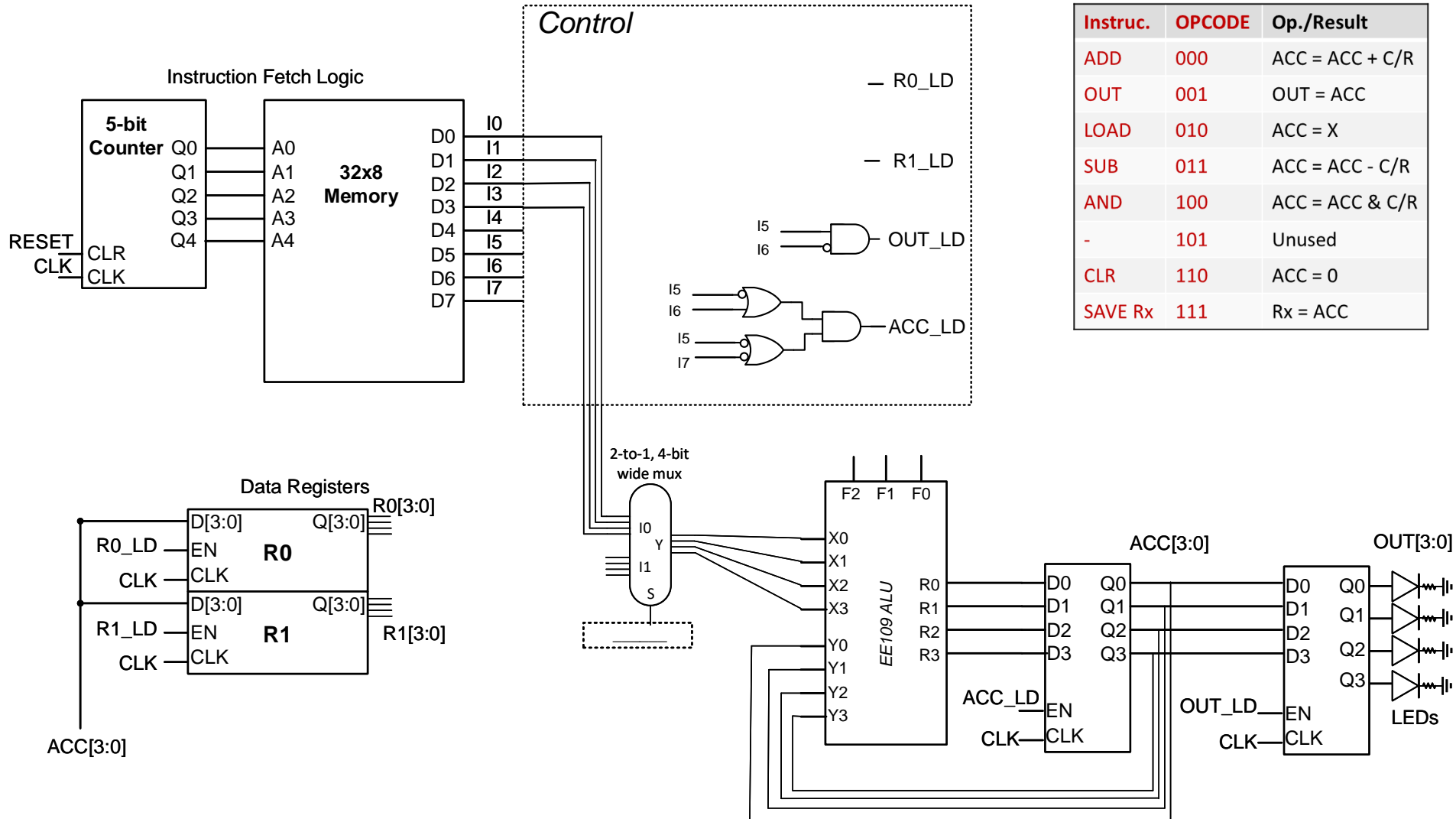


Instruc.	OPCODE	Op./Result
ADD	000	ACC = ACC + C/R
OUT	001	OUT = ACC
LOAD	010	ACC = X
SUB	011	ACC = ACC - C/R
AND	100	ACC = ACC & C/R
-	101	Unused
CLR	110	ACC = 0
SAVE Rx	111	Rx = ACC



# ADDING A JUMP/CONTROL


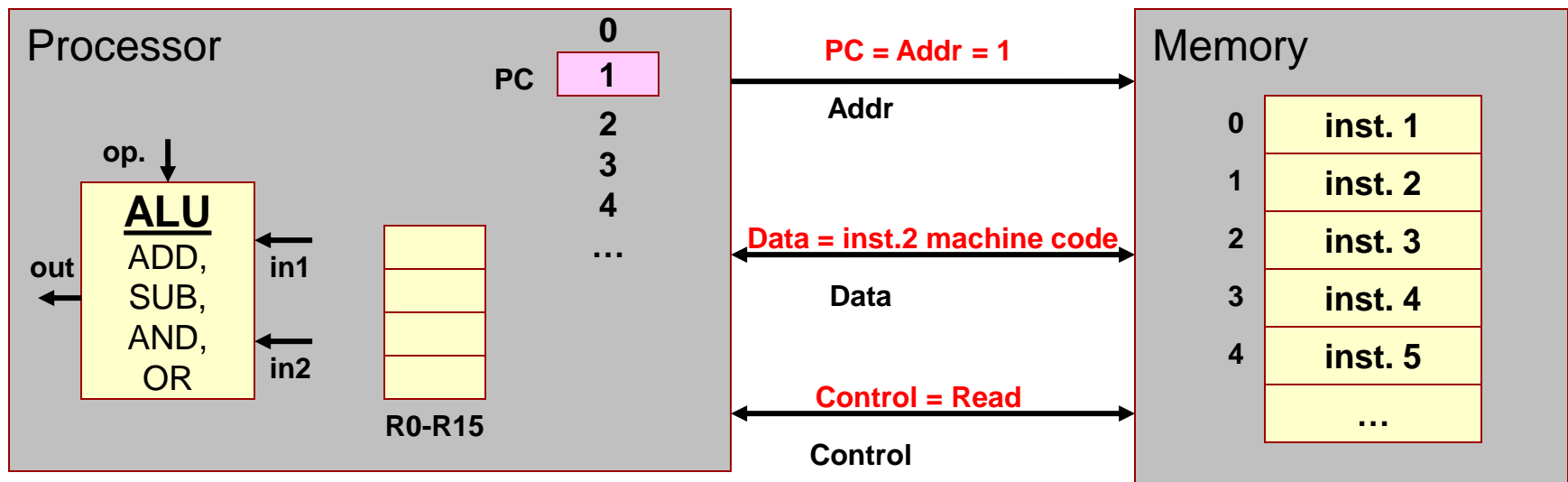
# Recall: PC and Sequential Execution

- By default, high level code and assembly instructions execute sequentially.
- The PC (Program Counter) stores the address of the instruction we will fetch next from memory
  - **Sequential** execution results because the PC simply counts (0,1,2,3,...)
  - But what if we want to skip forward or backward in our code?
  - We need branch instructions




 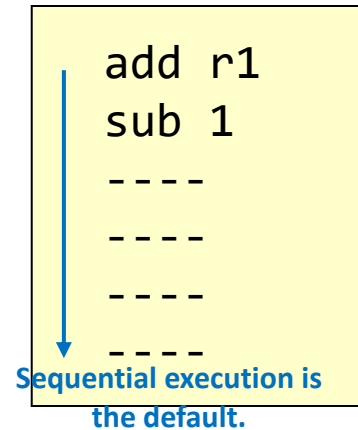
# Program Flow

- We need some way to implement conditionals (if statements) and loops (for / while), which require "jumping" to non-sequential instructions
- Sometimes jumping is conditional (only if a condition is true) and other time it is unconditional (always)
- In assembly, a **jump** (aka **branch**) instruction updates the PC (program counter) so that we fetch some new instruction
  - Let us add a **jeqz** instruction (jump if ACC is equal to zero)



 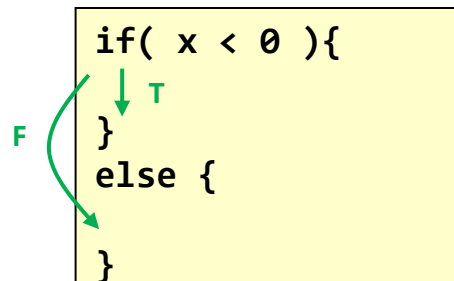Use special instructions to jump to non-sequential locations  
(backward = loop, forward = conditional)




# JEQZ

- We'll assign our one unused opcode for the new jump instruction, `jeqz`
  - We will use the lower 5 bits of the instruction for the new PC value
- Description: Jump to a new PC value IF the accumulator equals 0
 

```
if(ACC == 0)
    PC = _____ // jump
else
    PC = _____ // sequential
```
- Uses the result from the previous instruction (which is in the ACC) to compare to 0 (e.g. `SUB 1, JEQZ npc`)
- How can we achieve an unconditional jump (so that I jump for sure)

          
 JEQZ *npc*

Instruc.	OPCODE	Op./Result
ADD	000	ACC = ACC + C/R
OUT	001	OUT = ACC
LOAD	010	ACC = C/R
SUB	011	ACC = ACC - C/R
AND	100	ACC = ACC & C/R
JEQZ	101	If ACC=0, PC = NPC
CLR	110	ACC = 0
SAVE Rx	111	Rx = ACC

 


Machine code format for new JEQZ instruction
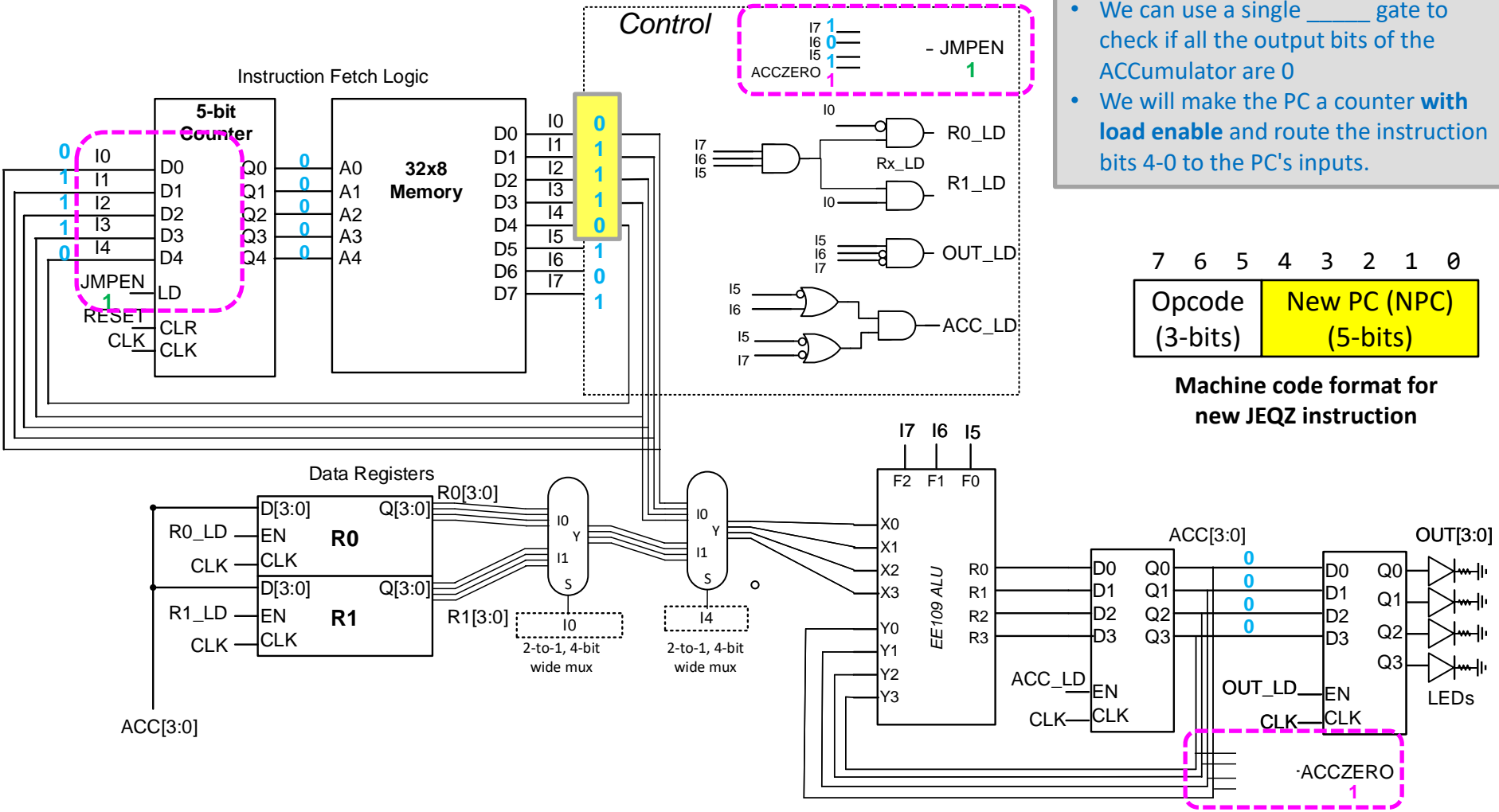
# Data & Control for JEQZ Instruction

Datapath updates

- We can use a single AND gate to check if all the output bits of the ACCumulator are 0
- We will make the PC a counter **with load enable** and route the instruction bits 4-0 to the PC's inputs.



# Example

- Examine the C code below, implementing a loop to sum the first n=5 integers. Complete the corresponding assembly
- Tips:
  - Allocate variables to specific registers (R0, R1)
  - A statement like `x += y` requires a 3-instruction sequence:
    - LOAD x** (to the ACC),
    - ADD y** (to the ACC),
    - SAVE x** (from ACC to x)

**C Code**

```

1 int s=0; // R0
2 int i; // R1
  for(i=5; i != 0; i--)
  {
4   s += i;
  }
7 print(s)
    
```

```

1 00: CLR
  01: SAVE R0
2 02: LOAD 5
  03: SAVE R1
  04: LOAD R1
3 05: JEQZ __
4 06: _____
  07: _____
  08: _____
5 09: _____
  0a: _____
  0b: _____
  0c: CLR
6 0d: JEQZ __
7 0e: LOAD R0
  0f: OUT
    
```

Corresponding Assembly

**OTHER INSTRUCTION SETS...**

# Historical Instruction Format Options

- Instruction sets limit the \_\_\_\_\_ used in an instruction due to...
  - To limit the complexity of the hardware
  - So that when an instruction is coded to binary it \_\_\_\_\_ in a certain # of bits
- Different instruction sets specify these differently
  - 3 operand instruction set (\_\_\_\_\_) -> (32-bit processors)
    - Usually all 3 operands in registers
    - Format: ADD DST, SRC1, SRC2 (DST = SRC1 + SRC2)
  - 2 operand instructions (\_\_\_\_\_)
    - Second operand doubles as source and destination
    - Format: ADD SRC1, S2/D (S2/D = SRC1 + S2/D)
  - 1 operand instructions (Low-End Embedded, Java Virtual Machine)
    - Implicit operand to every instruction usually known as the Accumulator (or ACC) register
    - Format: ADD SRC1 (ACC = ACC + SRC1)
  - 0 operand instructions / stack architecture
    - Push operands on a stack: PUSH X, PUSH Y
    - ALU operation: ADD (Implicitly adds top two items on stack: X + Y & replaces them with the sum)



# General Instruction Format Issues

- Consider the high-level code
  - $F = X + Y - Z$
  - $G = A + B$
- Simple embedded computers often use single operand format
  - Smaller data size (8-bit or 16-bit machines) means limited instruction size
- Modern, high performance processors (Intel, ARM) use 2- and 3-operand formats

Three-Operand	Two-Operand	Single-Operand	Stack Arch.
ADD F,X,Y SUB F,F,Z ADD G,A,B		LOAD A ADD B STORE G	PUSH Z PUSH Y SUB PUSH X ADD POP F
(+) More natural program style (+) Smaller instruction count			(+) Smaller size to encode each instruction

**MORE PRACTICE**

# More Practice (On Own Time)


- Write assembly for:
  - $((4 \& 14) + (5 \& 3) - (6 \& 11) + (8 \& 13))$
- Try to use as few instructions as you can

Instruc.	OPCODE	Op./Result
ADD	000	ACC = ACC + C/R
OUT	001	OUT = ACC
LOAD	010	ACC = X
SUB	011	ACC = ACC - C/R
AND	100	ACC = ACC & C/R
-	101	Unused
CLR	110	ACC = 0
SAVE Rx	111	Rx = ACC


	7	6	5	4	3	2	1	0
Opcode (3-bits)	C/R 0			Constant (4-bits)				
Opcode (3-bits)	C/R 1			Unused (3-bits)			Reg 0/1	

**New Instruction  
Format**

# ADD 7

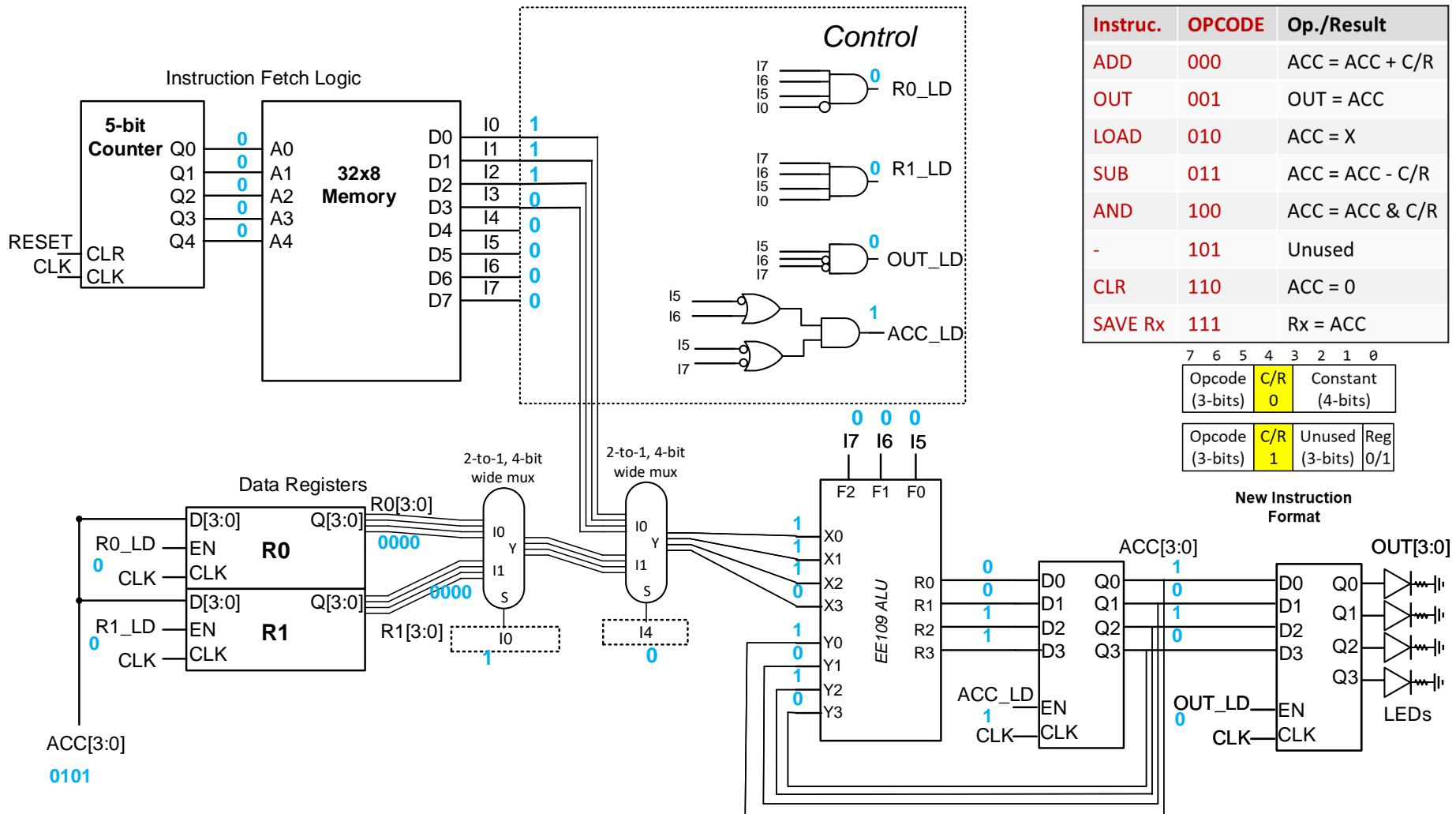


Instruc.	OPCODE	Op./Result
ADD	000	ACC = ACC + C/R
OUT	001	OUT = ACC
LOAD	010	ACC = X
SUB	011	ACC = ACC - C/R
AND	100	ACC = ACC & C/R
-	101	Unused
CLR	110	ACC = 0
SAVE Rx	111	Rx = ACC

 

New Instruction Format

# ADD R0

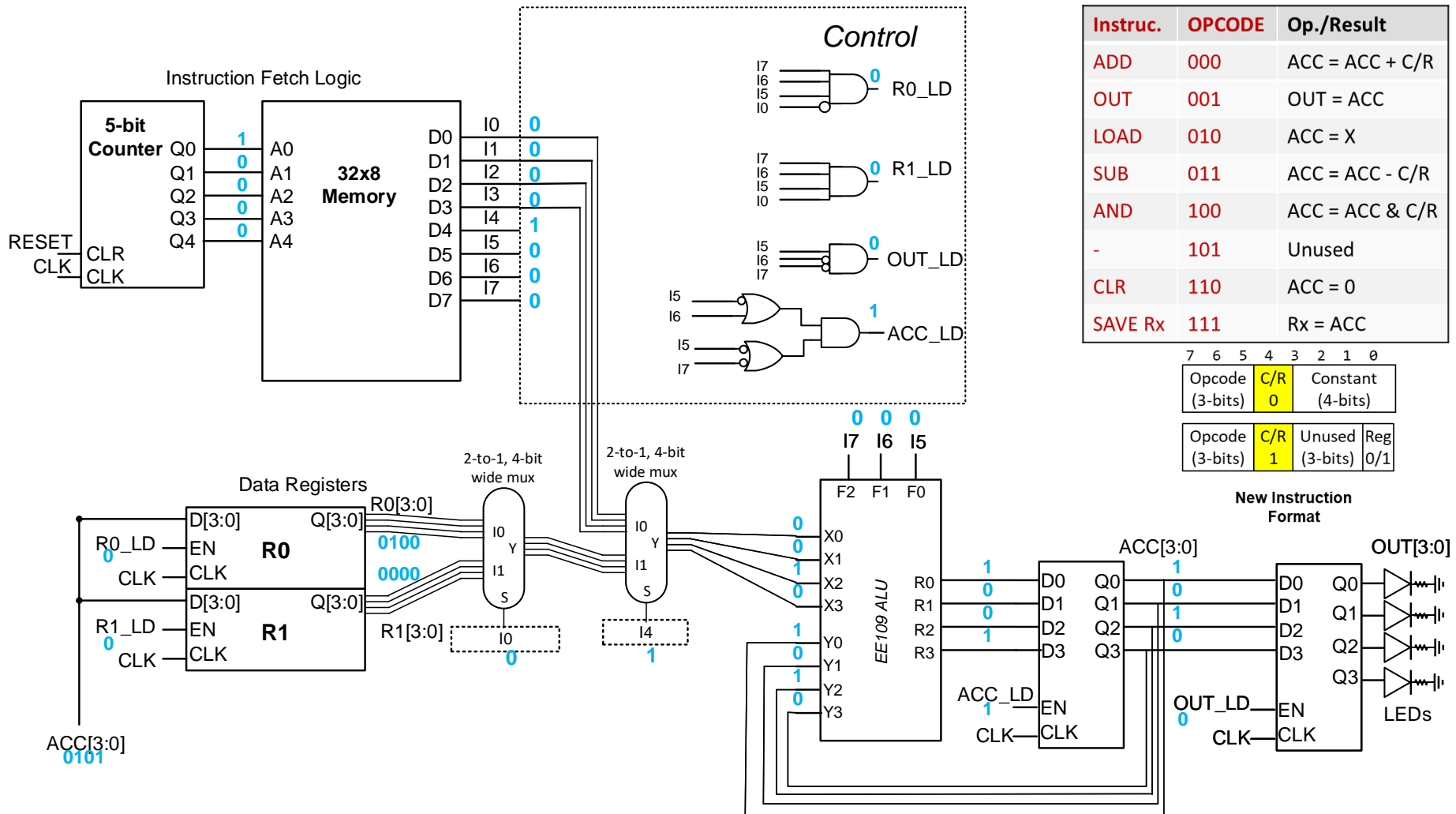


Instruc.	OPCODE	Op./Result
ADD	000	ACC = ACC + C/R
OUT	001	OUT = ACC
LOAD	010	ACC = X
SUB	011	ACC = ACC - C/R
AND	100	ACC = ACC & C/R
-	101	Unused
CLR	110	ACC = 0
SAVE Rx	111	Rx = ACC


7	6	5	4	3	2	1	0
Opcode (3-bits)			C/R (1-bit)	Constant (4-bits)			
Opcode (3-bits)			C/R (1-bit)	Unused (3-bits)	Reg (0/1)		

New Instruction Format

# SAVE R1

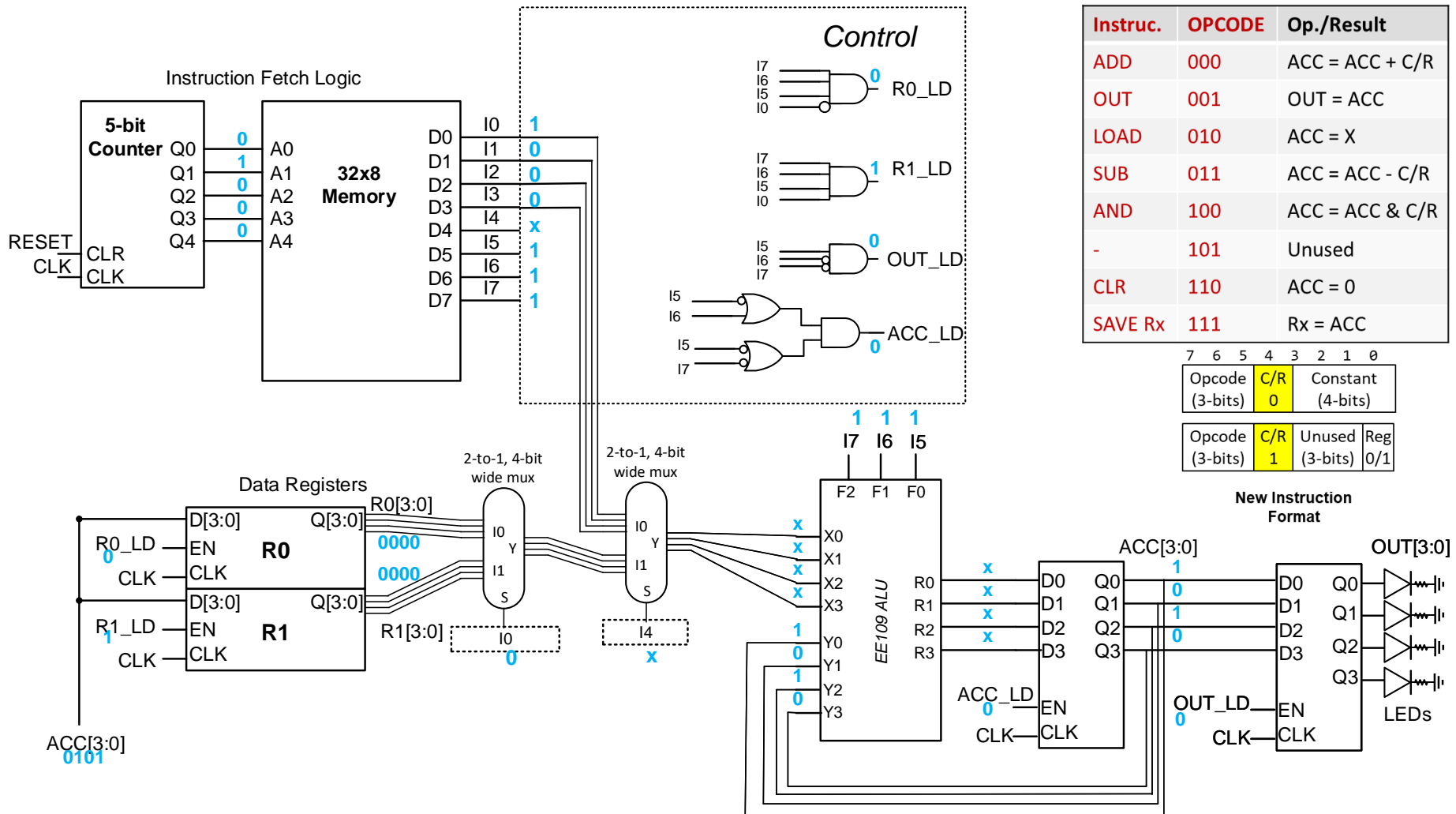

Instruc.	OPCODE	Op./Result
ADD	000	ACC = ACC + C/R
OUT	001	OUT = ACC
LOAD	010	ACC = X
SUB	011	ACC = ACC - C/R
AND	100	ACC = ACC & C/R
-	101	Unused
CLR	110	ACC = 0
SAVE Rx	111	Rx = ACC

 

New Instruction Format