

Unit 1

Circuit Basics

KVL, KCL, Ohm's Law



LED Outputs

Buttons/Switch Inputs


VOLTAGE AND CURRENT

Current and Voltage

- Charge is measured in units of Coulombs
- Current – Amount of charge flowing through a _____ in a certain _____
 - Measured in _____ = **Coulombs per second**
 - Current is usually denoted by the variable, **I**
- Voltage – Electric _____ energy
 - Analogous to mechanical potential energy (i.e. _____)
 - Must measure _____ points
 - Measured in **Volts (V)**
 - Common reference point: **Ground (GND) = 0V**
 - Often really connected to the ground


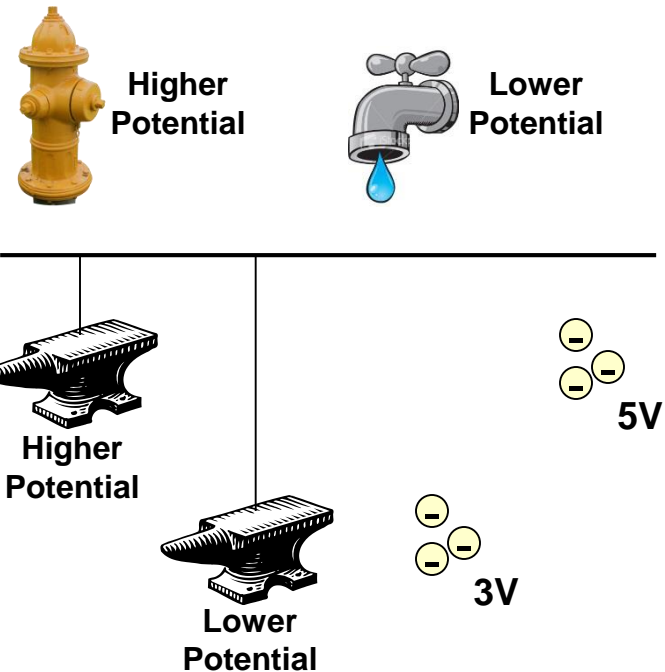
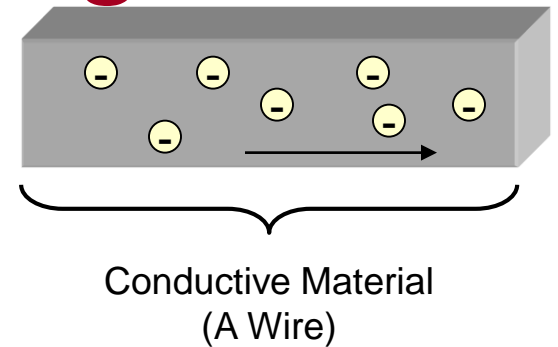


Current / Voltage Analogy

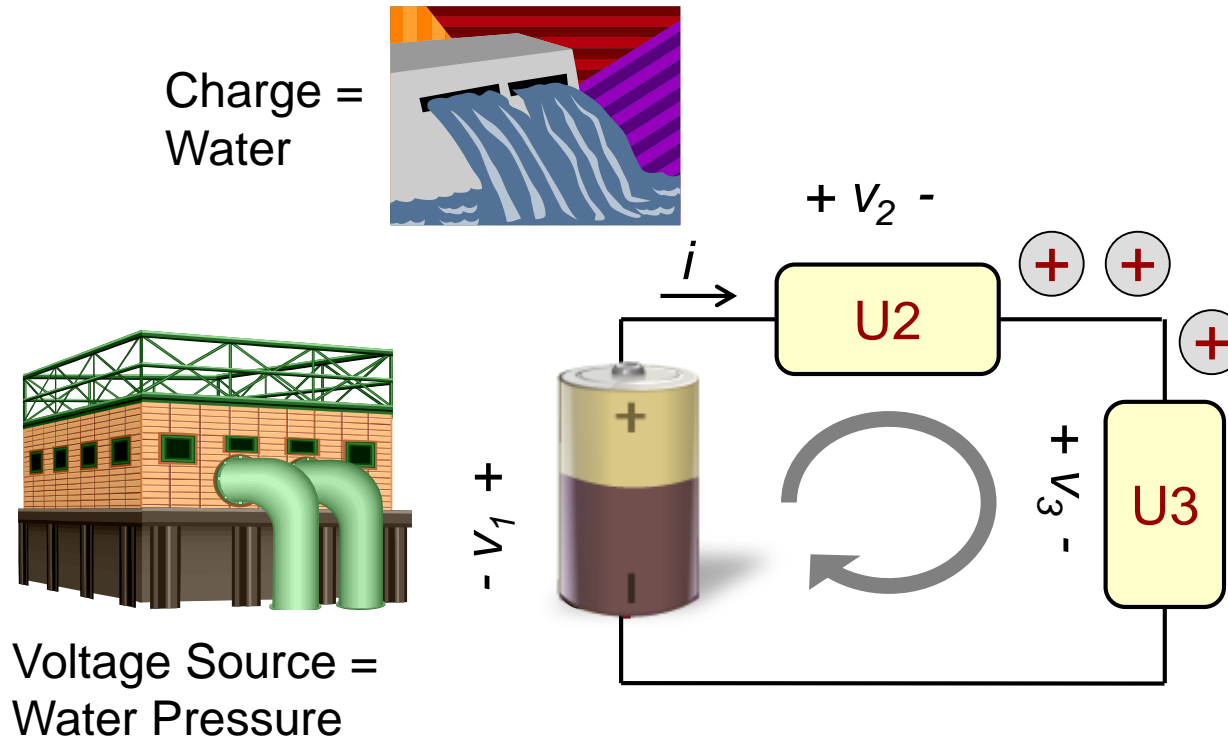


Meet The Components

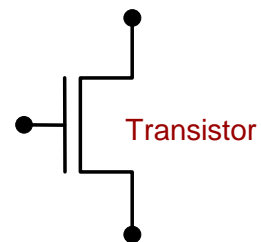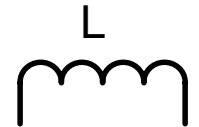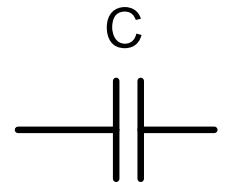- Most electronic circuits are modeled with the following components
- Resistor
 - Measures how well a material conducts electrons
- Capacitor & Inductor
 - Measures material's ability to store charge and energy
- Transistor
 - Basic amplification or switching technology



Kirchhoff's Laws

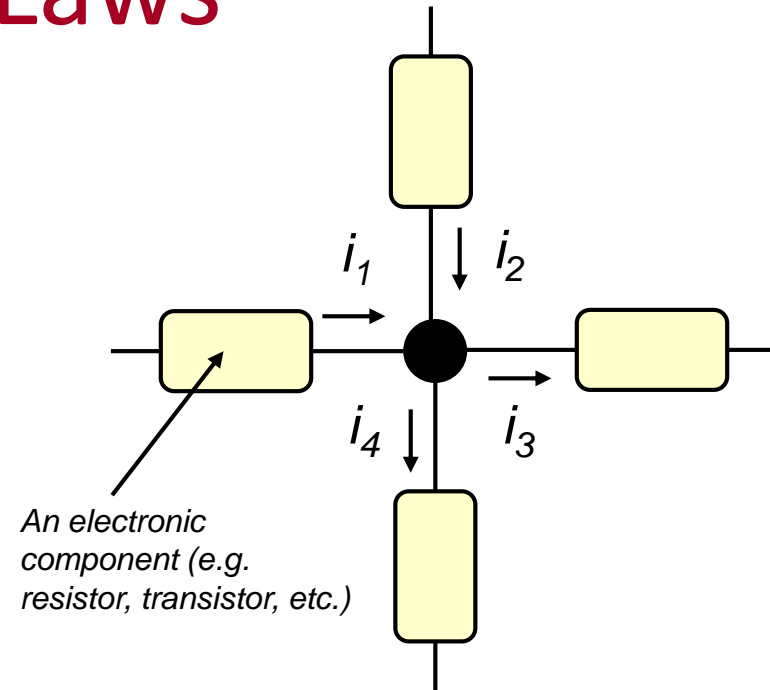
- Common sense rules that govern current and voltage
 - Kirchhoff's Current Law (KCL)
 - Kirchhoff's Voltage Law (KVL)
- Kirchhoff's Current Law (KCL)
 - The current flowing _____ a location (a.k.a. node) must equal the current flowing _____ of the location
 - ...or put another way...
 - The sum of current at any location must _____




KCL says _____

Kirchhoff's Current Law


- Reminder: KCL says _____
- Start by defining a _____ for each current
 - It does not matter what direction we choose
 - When we solve for one of the currents we may get a _____ current
 - "Negative" sign simply means the direction is _____ of our original indication
- In the examples to the right the top two examples the directions chosen are fine but physically in violation of KCL...
- ...but KCL helps us arrive at a consistent result since solving for one of the current values indicates...
 - The _____ of i_1 and i_2 are the same
 - They always flow in the _____ direction of each other (if one flows in the other flows out or vice versa)

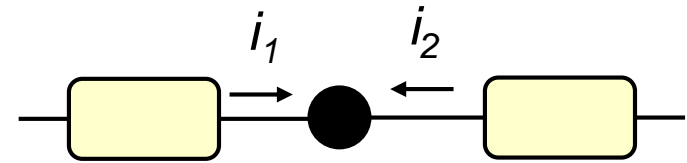


KCL says _____...implies _____

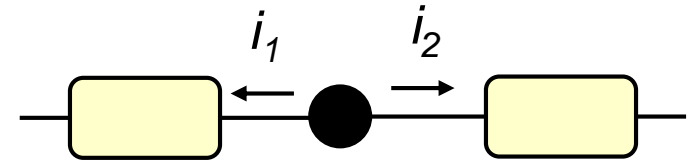

KCL says _____...implies _____

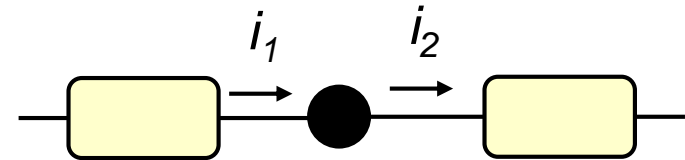


KCL says _____

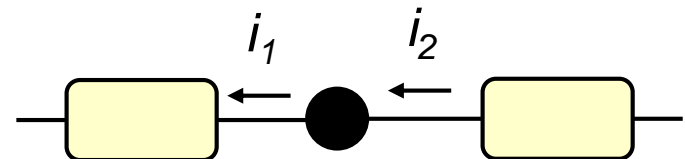

KCL says _____


Kirchhoff's Voltage Law

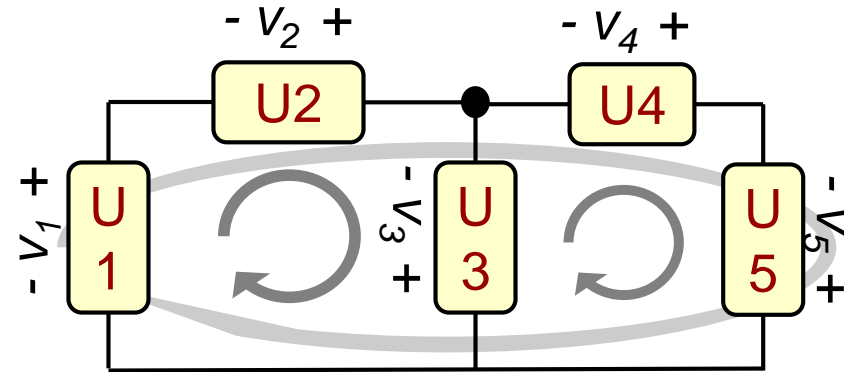- Kirchhoff's Voltage Law (KVL)
 - The sum of voltages around a _____ (i.e. walking around and returning to the _____) must equal 0
 - Define "polarity" of voltage and then be consistent as you go around the loop...obviously when you solve you may find a voltage to be negative which means you need to flip/reverse the polarity




KVL says:

KVL says:

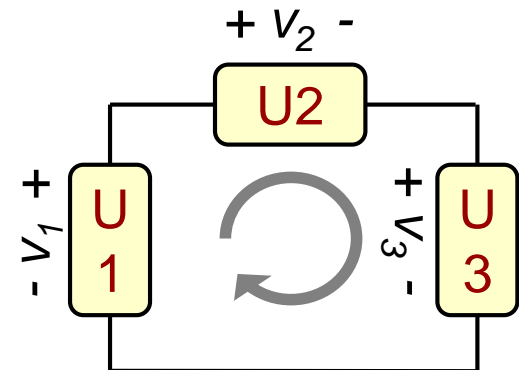

A Brief Summary

- KCL and KVL are _____ and _____
 no matter what kind of devices are used
 - The yellow boxes could be ANY electronic device: resistors, batteries, switches, transistors, etc...KVL and KCL will still apply
 - In a few minutes, we'll learn a law that only applies to resistors (or any device that can be modeled as a resistor)
- Some KVL or KCL equations may be _____
 - Writing the equation for loop {v1,v2,v3} and {v3,v4,v5} may be sufficient and writing {v1,v2,v4,v5} may not be necessary
 - But as a novice, feel free to _____
- Kirchoff's Laws apply to non time-varying circuits or circuits in the steady-state

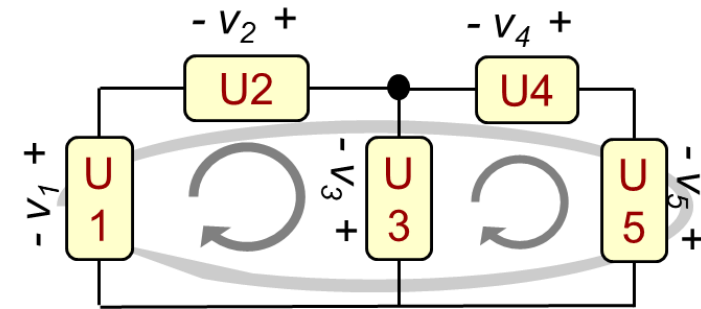

KVL says:


$$v_1 + v_2 + v_3 = 0$$

$$v_1 + v_2 + v_4 + v_5 = 0$$

$$-v_3 + v_4 + v_5 = 0$$

Nodes

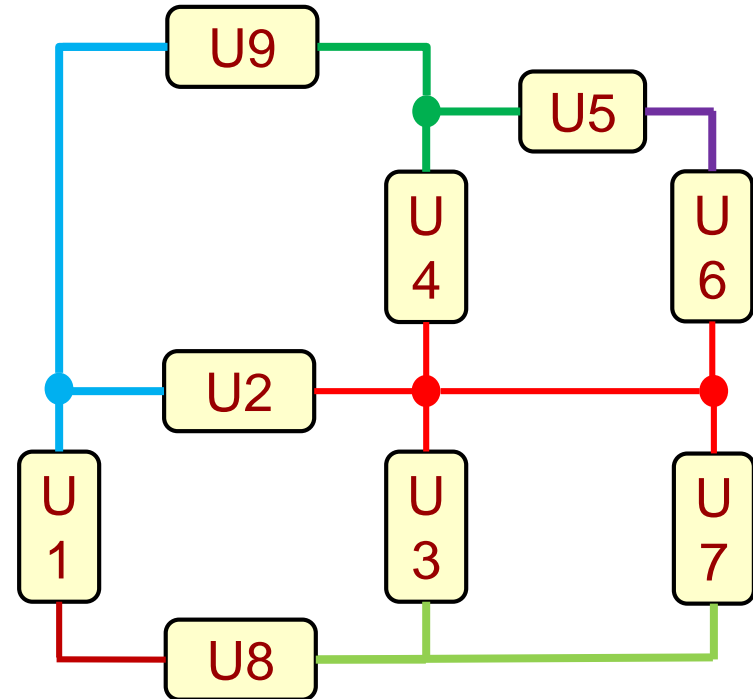
- **(Def.)** An electric node is the junction of _____ devices connected by wires
- _____ voltage at any point of the node
- How many nodes exist in the diagram to the right?



Practice KCL and KVL

- Use KCL to solve for i_3 , i_4 , and i_6
- Use KVL to solve for v_3 , v_8 , v_5

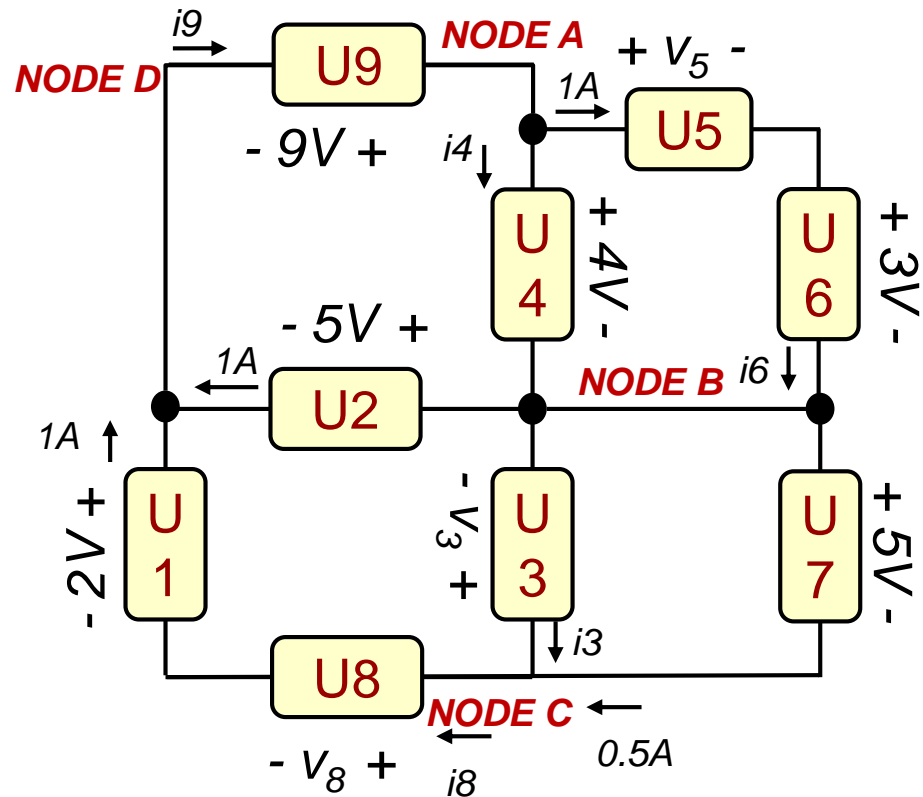Hint: Find a node or loop where there is only one unknown and that should cause a domino effect



Resistance and Ohms Law

- Measure of how hard it is for current to flow through the substance

- Resistance =

— How much _____ do you have to put to get a certain _____ to flow

- Measured in Ohms (Ω)

- Ohm's Law


— $I = \frac{V}{R}$ or $V = IR$

— $R = \frac{V}{I}$ => $I = \frac{V}{R}$



Large Resistance

Small Resistance


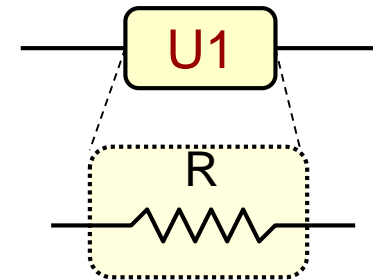


Schematic Symbol for a Resistor

Ohm's Law **ONLY** applies to resistors (or devices that can be modeled as a resistor such as switches and transistors)



Series & Parallel Resistance

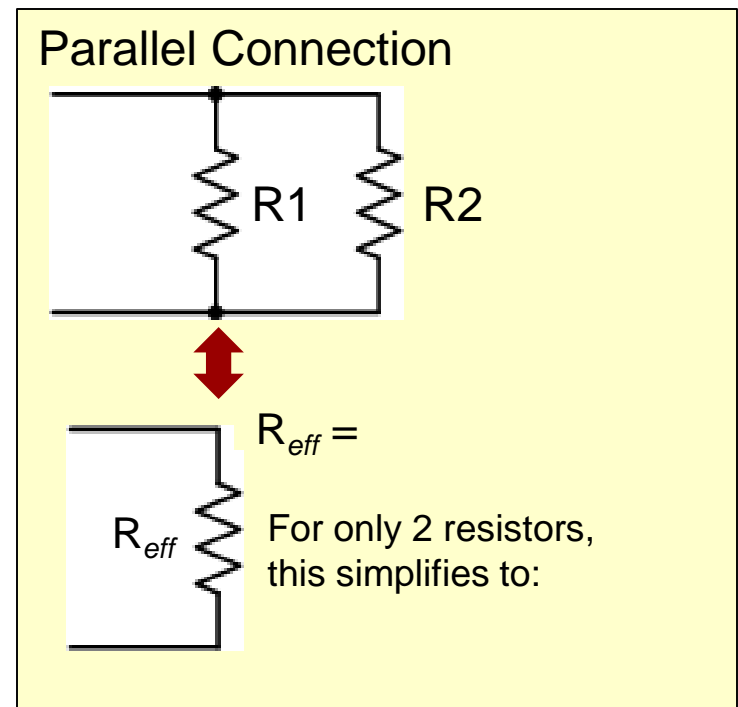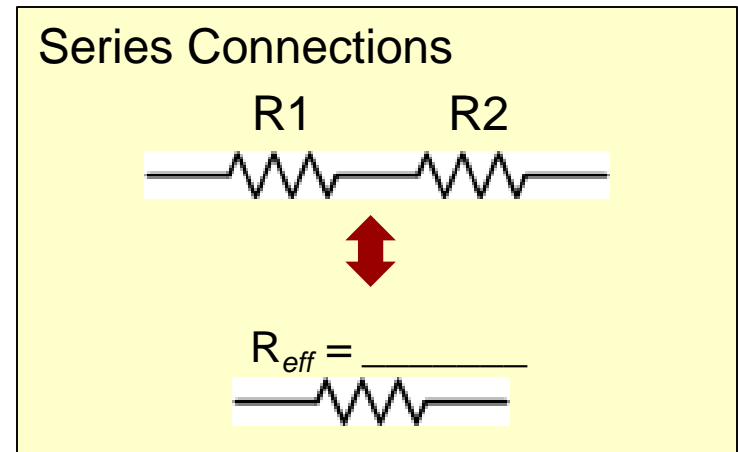- Series resistors = same current must pass through both
- Parallel resistors = each connects to the same two nodes (same voltage different applied to both)
- Series and parallel resistors can be combined to an equivalent resistor with value given as shown...





Solving Voltage & Current

- Given the circuit to the right, let...
 - $V_{dd} = +5V$, $R1 = 400$ ohms, $R2 = 600$ ohms
- Solve for the current through the circuit and voltages across each resistors (i.e. $V1$ and $V2$)
 - Since everything is in _____, KCL teaches us that the current through each component must be the _____, let's call it i
 - $i =$ _____
 - This alone lets us compute $V1$ and $V2$ since Ohm's law says
 - $V1 =$ _____ and $V2 =$ _____
 - $V1 =$ _____ and $V2 =$ _____
 - Though unneeded, KVL teaches us that
 - $V_{dd} - V1 - V2 = 0$ or that $V_{dd} = V1 + V2$

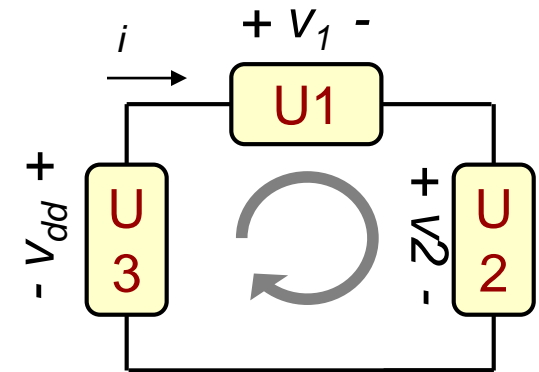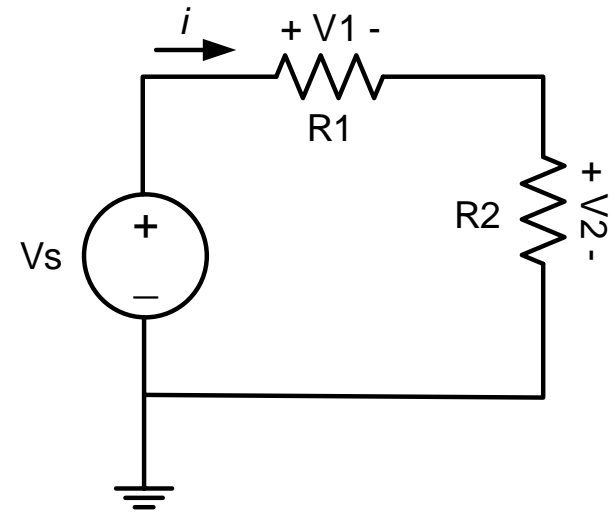


Voltage Supply Drawings

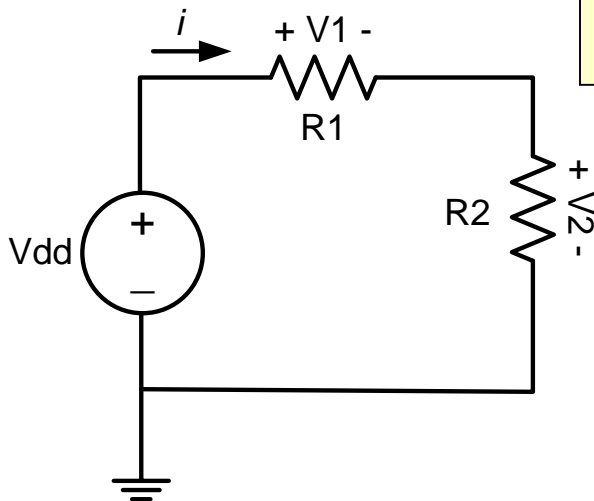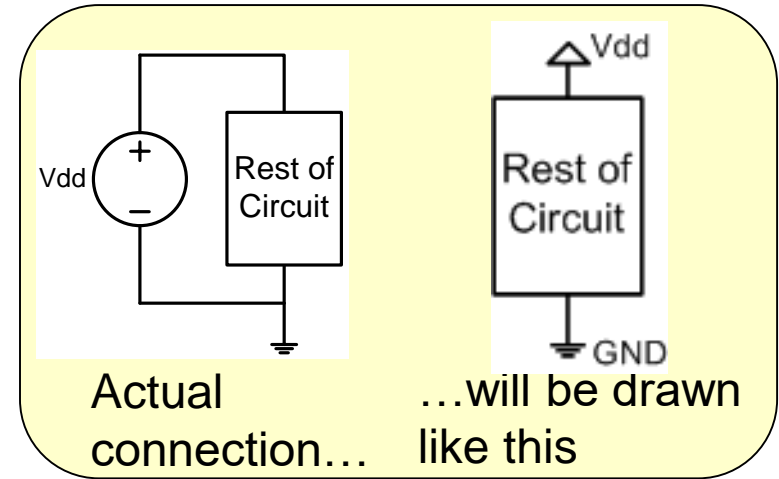- The voltage source (V_{dd}) in the left diagram (i.e. the circle connected to the "Rest of Circuit") is shown in an alternate representation in the right diagram (i.e. the triangle labeled " V_{dd} ")
- In the left diagram we can easily see a KVL loop available
- There is still a KVL loop available in the right diagram




Tip: V_{dd} is the name of the source voltage used for digital '1' signals. GND (0V) is often used for digital '0' signals.

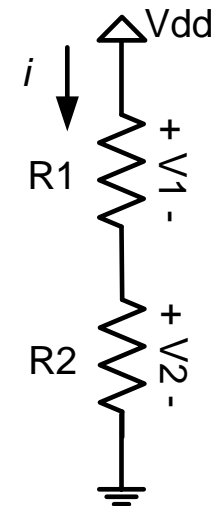Both are drawings of the same circuit (i.e. they are equivalent)



Shortcut: Voltage Dividers

- A shortcut application of KVL, KCL, and Ohm's law when two resistors are in series (**must be in series**)
- When two resistors **are in series** we can deduce an expression for the voltage across one of them
 - (1) $i = \text{___} / \text{_____}$; (2) $V1 = i * R1$; (3) $V2 = i * R2$
 - Substituting our expression for i into (2) and (3)
- The voltage across one of the resistors is proportional to the value of that resistor and the total series resistance
 - If you need 10 gallons of gas to drive 500 miles, how much gas you have you used up after driving 200 miles?
 - Gas = _____, Mileage = _____

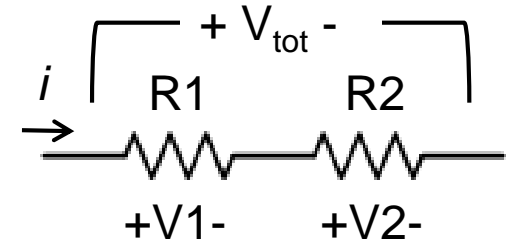


Voltage Divider Eqn: If two resistors $R1$ and $R2$ are in series then voltage across $R1$ is:

$$V1 = \text{_____}$$

Memorize this. We will use it often!


Solving Voltage & Current

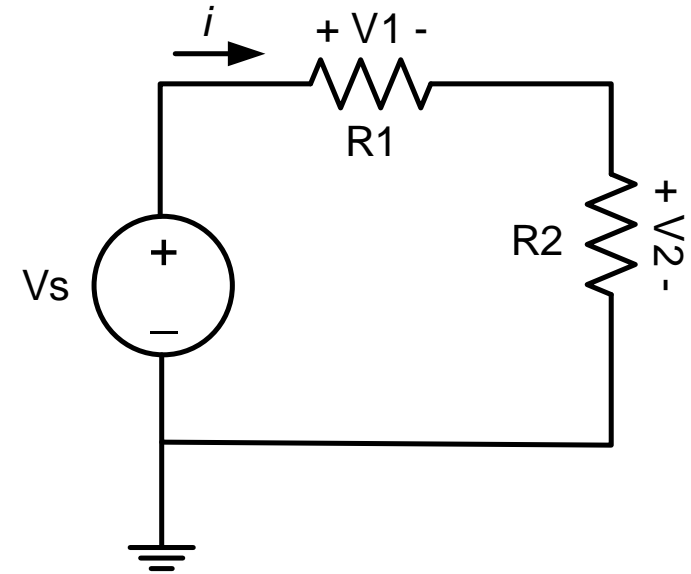- Reconsidering the circuit to the right with...
 - $V_{dd} = +5V$, $R1 = 400$ ohms, $R2 = 600$ ohms
- Solve for the current through the circuit and voltages across each resistors (i.e. $V1$ and $V2$)
 - We can use the voltage divider concept to immediately arrive at the value of $V2$
 - $V2 =$




Solving Voltage & Current

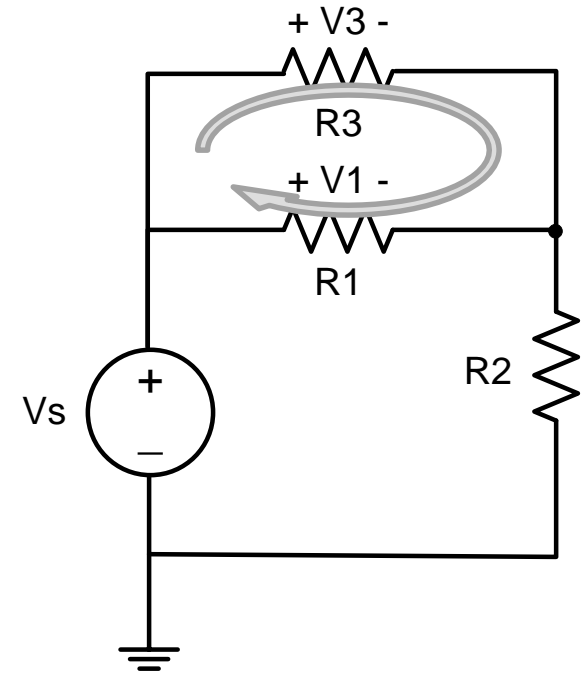- Consider the circuit on the right...
- What is the relationship between V_1 and V_3 ?
- Can you solve for the voltage V_1 (in terms of V_s , R_1 , R_2 , R_3)?
- Can you solve for the voltage V_2 (in terms of V_s , R_1 , R_2 , R_3)?




A Problem...

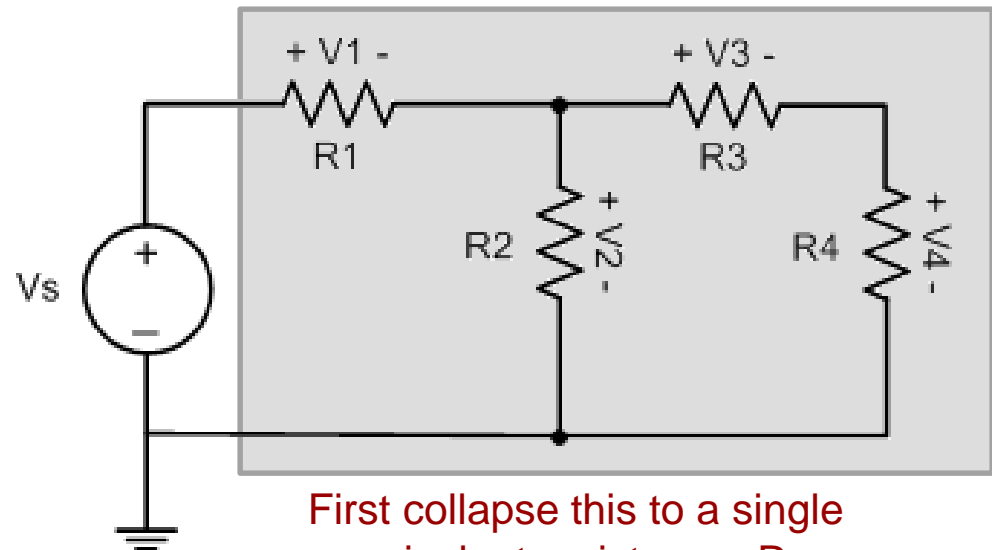- Given the following parameters...
 - $V_s=5V$, $R_1=4$, $R_2 = 12$, $R_3 = 2$ and $R_4 = 10$ ohms.
- Can we use the voltage divider concept to immediately solve the voltage across R_2 or do we need to first do some manipulation? What about R_4 ?
- First, find the total equivalent resistance (R_{eq}) seen by V_s and then solve for the voltage across each resistor



First collapse this to a single equivalent resistance, R_{eq}


...Continued (Blank Workspace)

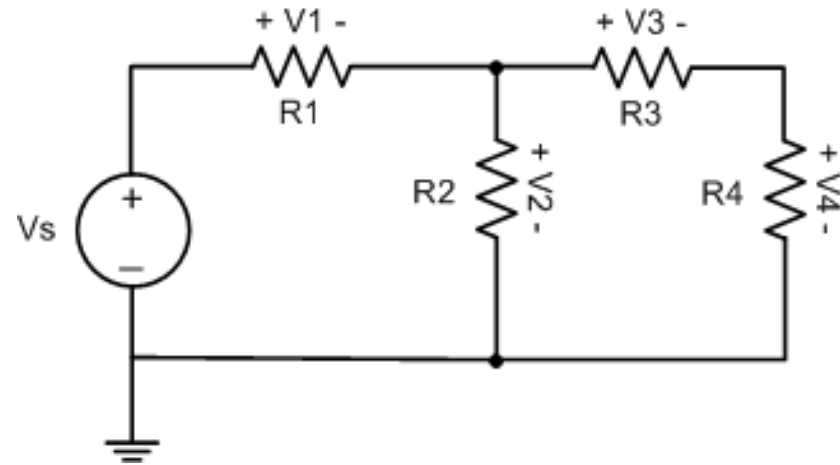

LEDS AS OUTPUTS AND SWITCHES/BUTTONS AS INPUTS

Generating Inputs & Measuring Outputs

- Where do inputs to a digital circuit originate?
 - Usually as _____ from another digital circuit (i.e. USB connecting to your laptop's main processing system)
 - For our class right now: A _____ controlled by a human (can be on or off)
- How will we know what voltage is coming out of a digital circuit?
 - Could use a voltmeter or oscilloscope (don't be afraid to use the equipment in our lab!)
 - _____ are commonly used to show the status of a digital output to a human

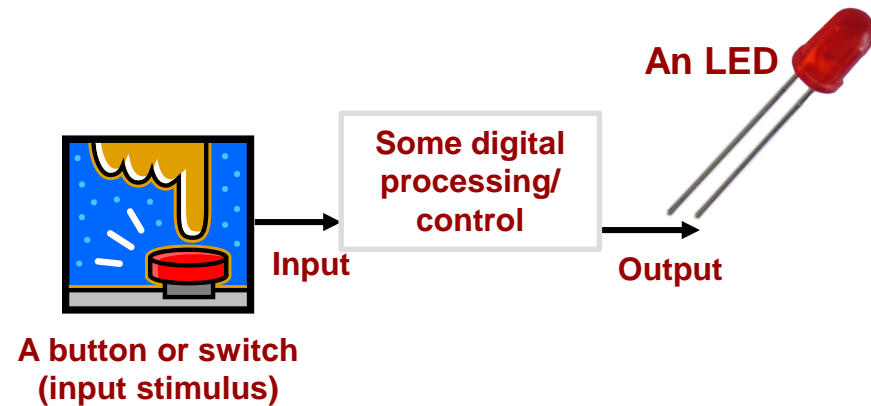


Each key on your keyboard is essentially a digital input generated by a push button (pressed or not pressed)

The status indicator on the Caps Lock button is simply an LED controlled by a digital output.


(Light-Emitting) Diodes

- The simplest output we can control is an LED (Light-emitting diode) which is like a tiny light bulb
- An LED glows ('on') when current _____ through it (i.e. when there is a voltage _____ across it)
- LEDs are polarized meaning they only work in one orientation (_____ leg must be at higher voltage)



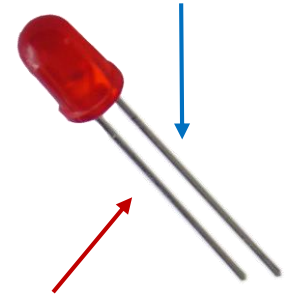
Longer leg connects to the side with the higher voltage



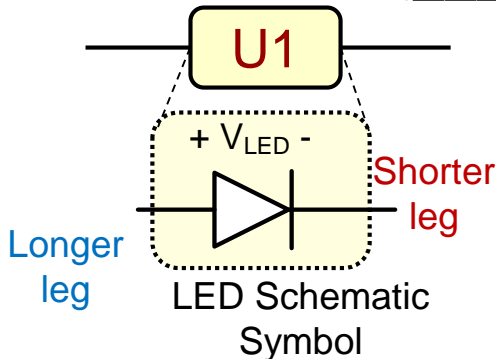Shorter leg connects to the side with the lower voltage



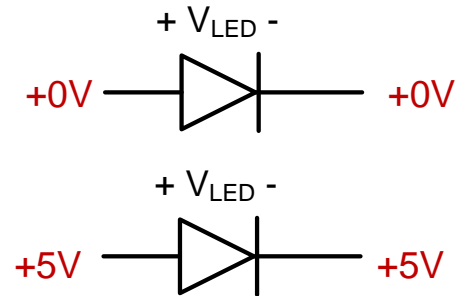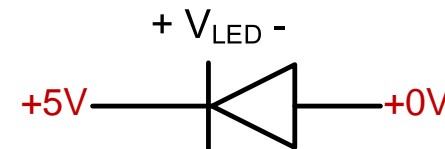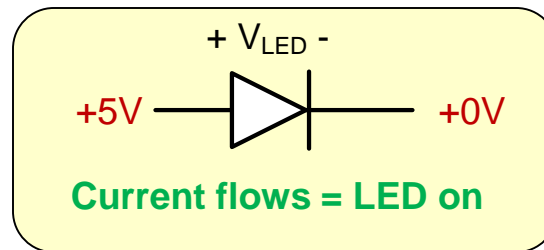http://www.custobots.com/sites/default/files/imagecache/product_full/products/Solarbotics-redLED.gif




No voltage differential = No Current flows = LED off



Main Point: To be 'on', there must be a voltage difference across the LED making current flow.

Need for Series Resistor with LEDs

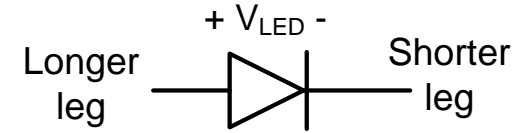- Problem:** LEDs may allow too much current to flow which may blow out the LED
- Solution:** Use a series resistor to limit current
 - Amount of current will determine _____ of LED
 - $R \uparrow$ then i ___ and thus LED brightness ___
 - $i = V1/R1 = (Vs - V_{LED}) / R1$
 - Usually $R1$ is a few hundred ohms (_____ ohms)




LED Schematic Symbol

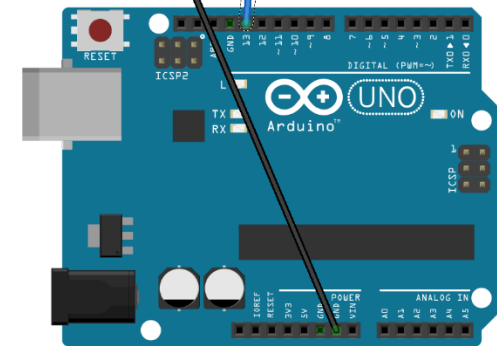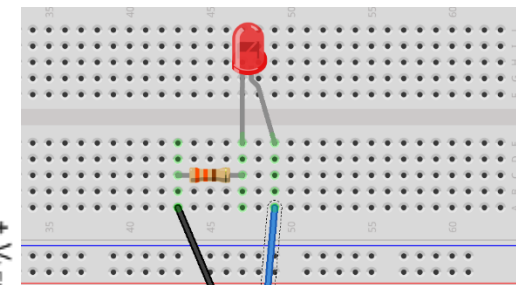


fritzing


Breadboard view

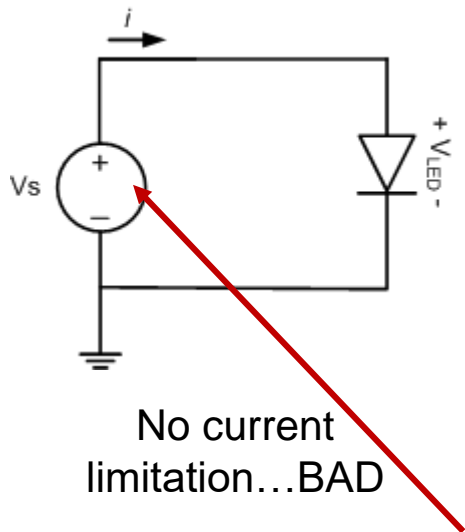

No current limitation...BAD

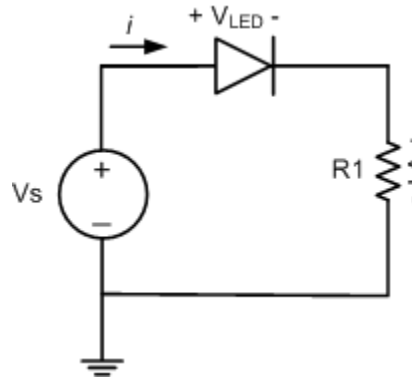

Choose resistor to limit current

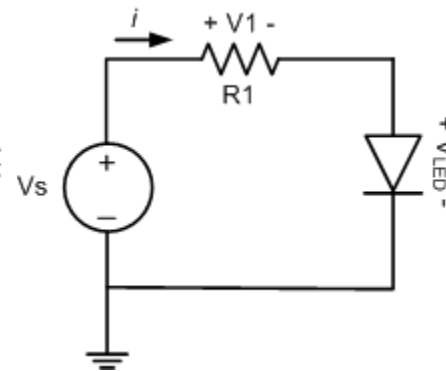

Doesn't matter where resistor is placed as long as it is in series

A digital (gate) output will usually serve as our voltage source that can be either '0' (0V) or '1' (5V)



Main Point: LED's should always be connected _____ with a current-limiting resistor

LED Connection Approaches

- When letting a digital output control an LED, the value (i.e. '0' = low or '1' = high voltage) that causes the LED to light up depends on how the circuit is wired
 - Note: Gates can often _____ (take in) more current than they can _____ (push out), so option 2 may be preferred...but let's not worry about this now...let's use option 1

This box represents a digital output (e.g. your Arduino) that can generate a high (1) or low (0) voltage.

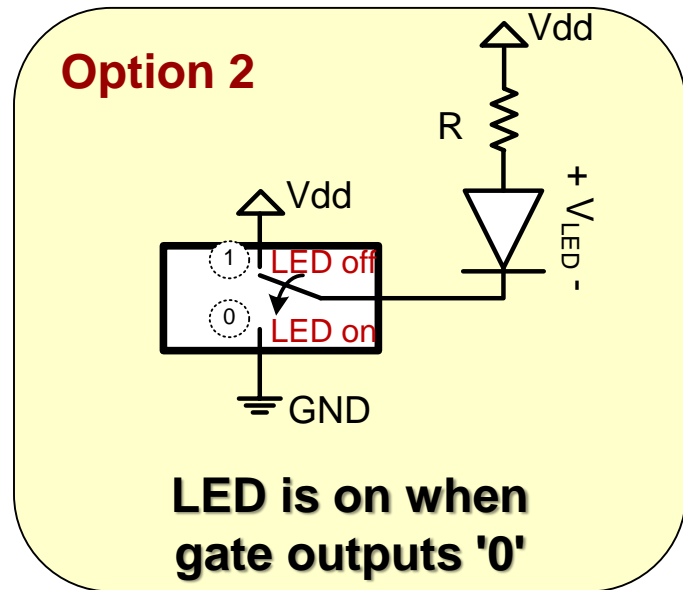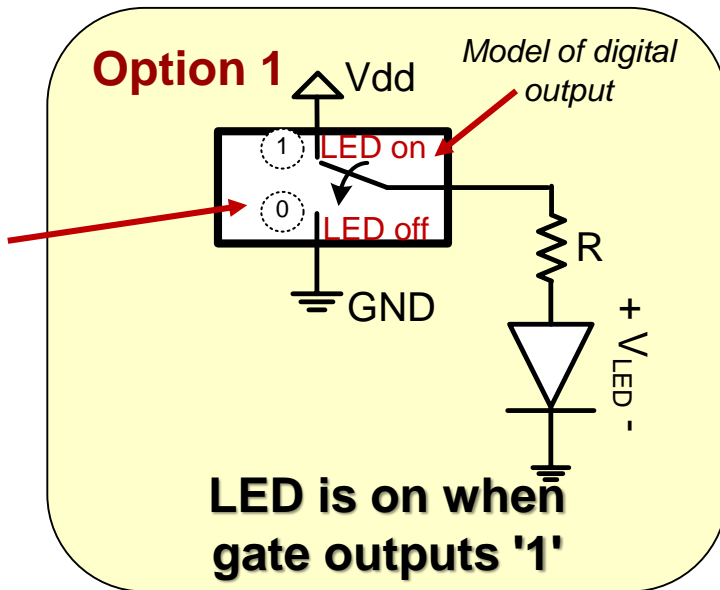What digital output value must be present for the LED to be on?



Main Point: LED's can light for either a logic '1' or '0' output...it depends on how they are wired.

Switch and PushButton Inputs

- Switches and pushbuttons can be in one of two configurations: _____ or _____
 - Switches can be opened or closed and then _____ in that position until changed
 - Pushbuttons are open by _____ and require you to push them to close the circuit (they then open when you release)
- Can be used as an input to digital device







Example pushbuttons



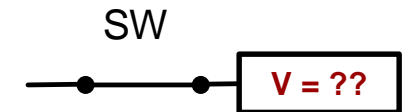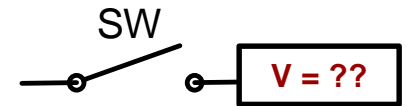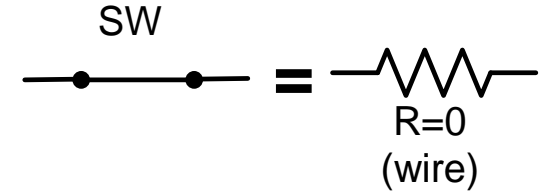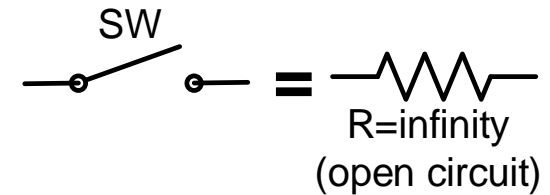Example switch


Switches and Pushbuttons

- Important Note 1: We can model a button or switch as a resistor of either 0 ohms or inf. (very large) ohms
 - When open a SW/PB looks like an _____ resistance (no current can flow)
 - When closed a SW/PB looks like a _____ ($R=0$) and no voltage drops across it
- **Question:** What voltage does an open or closed switch (pushbutton) generate?
- **Answer:** _____.
- Important Note 2:
 - SW or PBs don't produce digital 0's or 1's _____, they control what voltage (PWR/GND) is connected to your device




Connecting a Switch

- Switches only _____ the voltage going into a device, **they do not produce a voltage** (0V or 5V) by themselves
- Option 1: Attach one side to GND and the other side to the device
 - When the switch=open, nothing is connected to the device (a.k.a. "_____")
 - A floating input may sometimes appears as zero, and other times as a one.
 - We need the inputs to logic gates to be in either the 0 or 1 state...not floating
- Option 2:
 - When switch closed => _____ resistance connection from power to ground = _____ current flow...BAD!!! (This is known as a "**short circuit**").

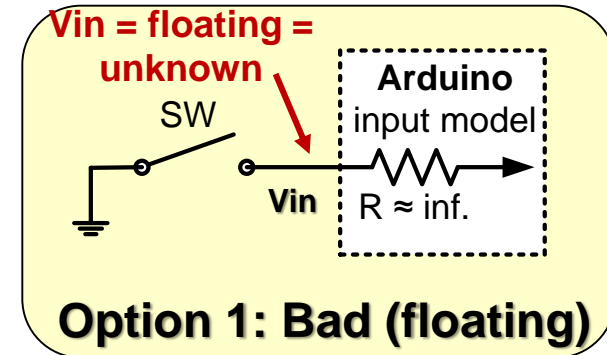

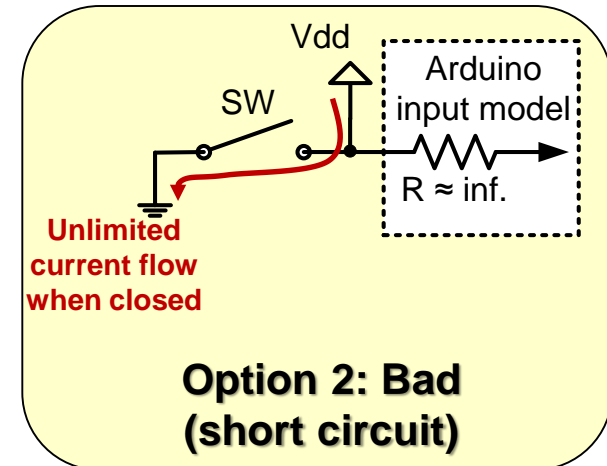Switch Closed = 0V (Logic 0) to input
 Switch Open = ??? (does not work)



Switch Open = Vdd=5V (Logic 1) to input
 Switch Closed = Short Circuit (does not work)


Preferred Wiring of Switches

- Solution: Put GND on the far side and a "pull-up" resistor at the input side
 - "Pull-up resistor" used to hold the input high unless something is forcing it to a zero
 - SW open => Arduino input looks like inf. Resistance in series with Rp. Thus _____ through Rp and thus no voltage drop across Rp...Vin = _____
 - SW closed => Direct wire from GND to input...input = _____...Also current flowing from Vdd to GND is limited by Rp preventing a short circuit.
 - Usually Rp is large (10k ohms) to limit current

Analogy:



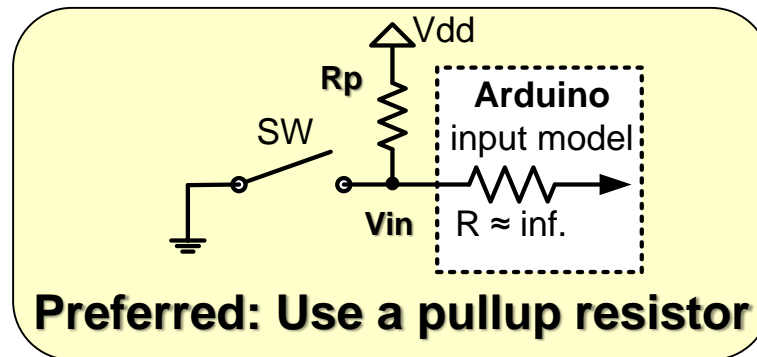This Photo by Unknown Author is licensed under [CC BY-SA](https://creativecommons.org/licenses/by-sa/4.0/)



To calculate Vin when switch is open:

$V_{in} = V_{dd} - V_{RP}$

$V_{in} = V_{dd} - \underline{\hspace{2cm}}$


$i_{RP} = \underline{\hspace{1cm}}$ since in _____ with _____
 resistance of Arduino input

Thus, $V_{in} = \underline{\hspace{2cm}}$


Main Point: Buttons & switches should have GND connected to one side & a pull-up resistor on the other

Power & Ground Connections

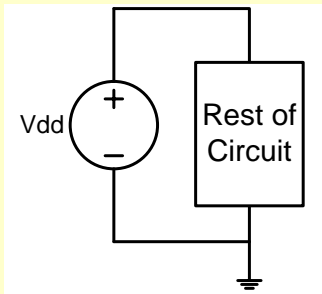
- Easy mistake when you're just learning to wire up circuits:
 - Wire the inputs & outputs but forget to connect power and ground
- All circuits and chips require a connection to a power source and ground
 - Digital circuits (aka "gates")
 - Switches
 - Buttons



Actual connection...

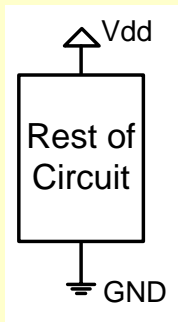

...will be drawn like this

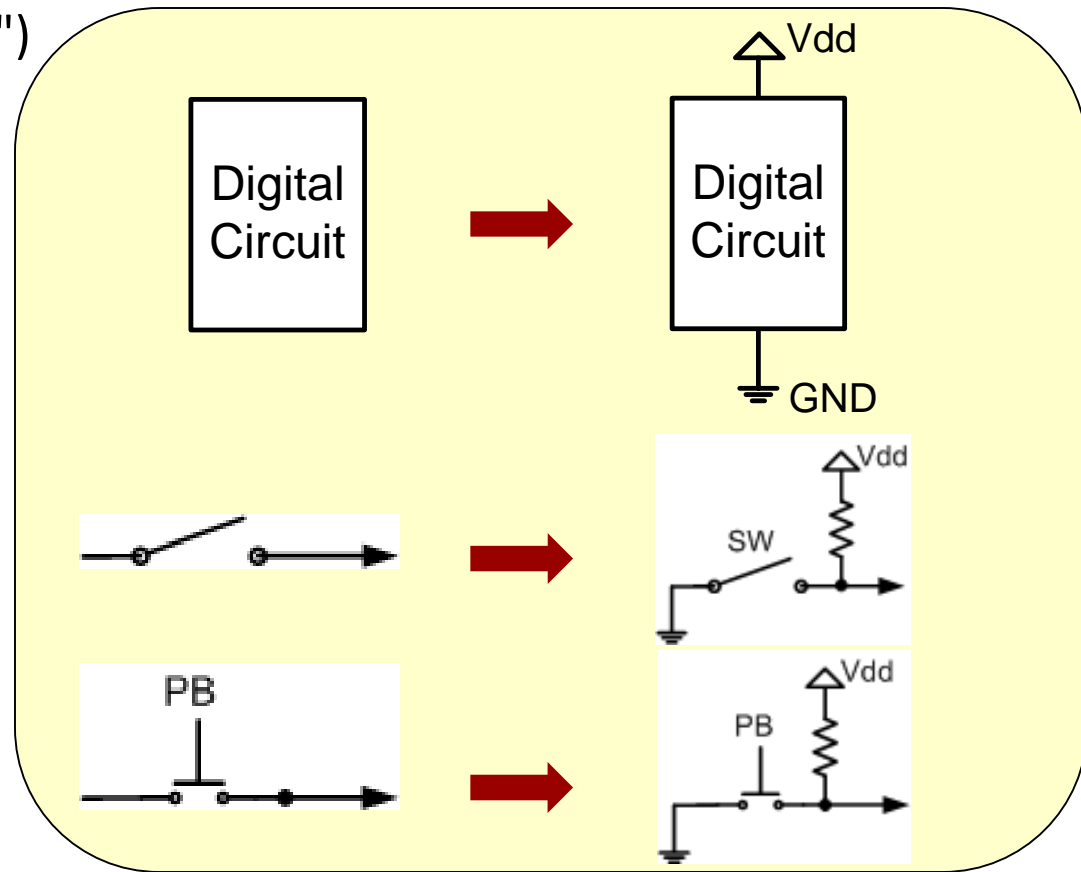

Summary

- KCL and KVL apply to **ALL** electronic devices
- Ohm's law applies **ONLY** to resistors and governs the relationship between the **current through** and the **voltage across** a resistor
- A resistor network can be collapsed to a **single equivalent resistance** by applying **series** and **parallel** transformations
- If two or more resistors are in series, the voltage across any of those resistors can be quickly found by applying the **voltage divider equation**
- LEDs are used as digital outputs and must be wired in the correct direction
- Switches can be modeled as a **small (0) resistance when closed** or **large (inf.) resistance when open**