

EE 109 Final Review

"Final" Jeopardy

Binary Brainteasers	1	2	3	4	5
Programming Picklers	1	2	3	4	5
Logic Functions Uncertainties	1	2	3	4	5
Combinational Conundrums	1	2	3	4	5
Sequential Stumpers	1	2	3	4	5
Computer Queries	1	2	3	4	5

"Final" Jeopardy

Binary Brainteasers	1	2	3	4	5
Programming Picklers	1	2	3	4	5
Logic Functions Uncertainties	1	2	3	4	5
Combinational Conundrums	1	2	3	4	5
Sequential Stumpers	1	2	3	4	5
Computer Queries	1	2	3	4	5
2022	1	2	3	4	5

DESIGN PROBLEMS

State Machine Example


- An old TV remote control and TV only supports 2-digit channels: 00-99. Normally, to change the channel we would have to hit two buttons: 38, first 3 then 8, and as soon as you hit the second button it should change the channel. However, for channels 2-9 the remote should allow you to just enter 1-digit and if another button is not pushed soon afterwards should cause the channel to be changed. Implement a state machine that can indicate when the channel should be changed. Have a single input PUSH and single output CHANGE. If you don't push the second button with in 2 clock periods of the first press it should just change the channel no matter what. Four states: 0PUSH, 1PUSH, WAIT, CHGCHAN.
- INPUTS: PUSH
- OUTPUTS: CHANGE

State Machine Example

	P=0	P=1	Change
0Push			
1Push			
Wait			
ChgChan			

Adder and Combinational Design

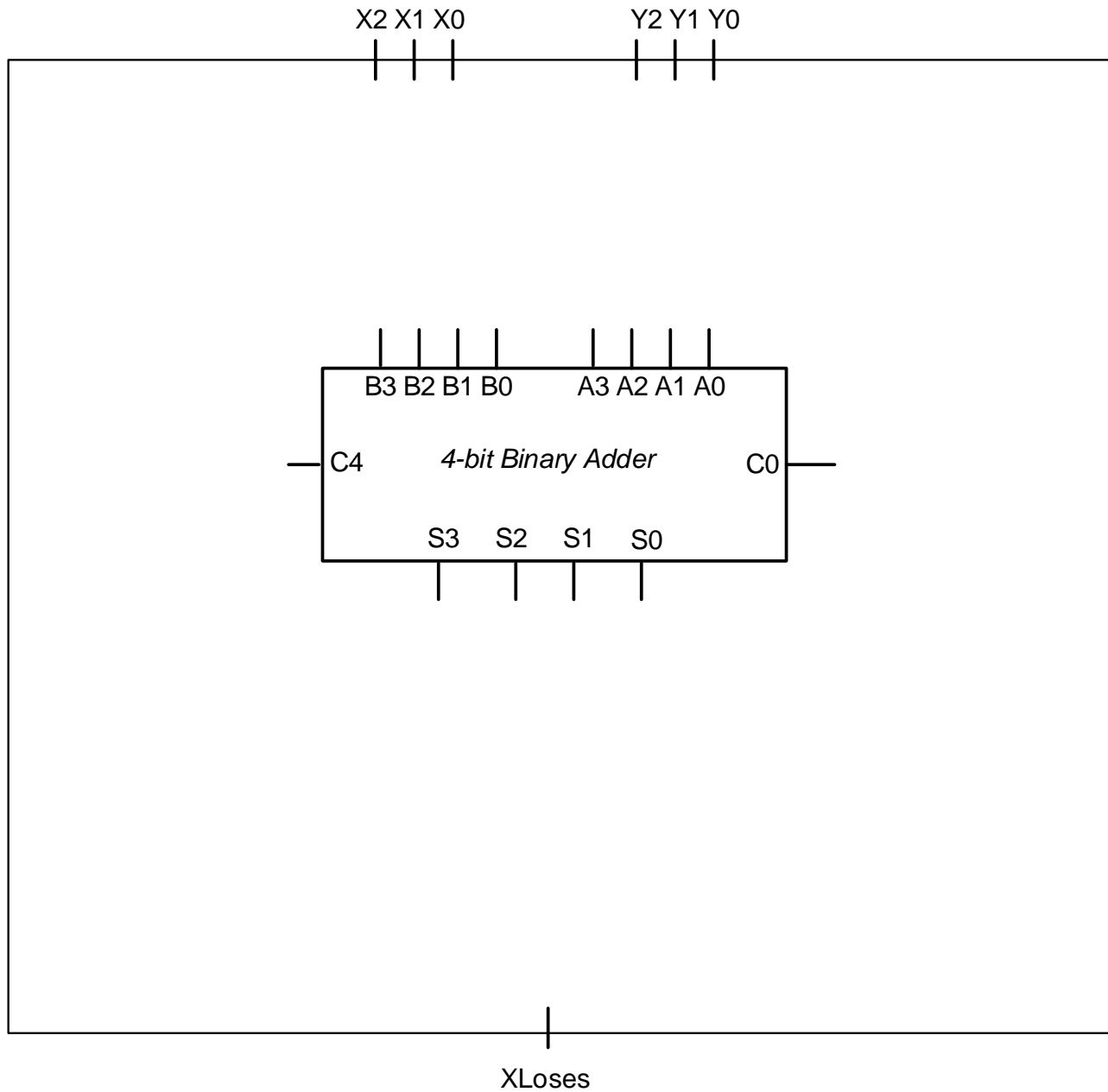- Suppose team X and team Y play a game where their scores range 0-7 decimal. Team X is much better than team Y so they give Y a handicap: to truly win, team X must score 5 points more than team Y. Design a circuit that will produce a signal: XLoses given the two 3-bit unsigned input numbers $X[2:0]$ and $Y[2:0]$ representing the scores of each team.



ISR

- Determine a prescalar, OCR0A value, and ISR for an 8-bit timer generate at 400Hz square wave for 3 seconds on PD1. Recall the Arduino runs at 16MHz and valid prescalars are: 1, 8, 64, 256, 1024 (choose the smallest prescalar that works).
 - OCR0A: _____
 - Prescalar: _____

ISR Code


```
ISR(TIMER0_COMPA_vect)
```

```
{
```




```
}
```

FPGA

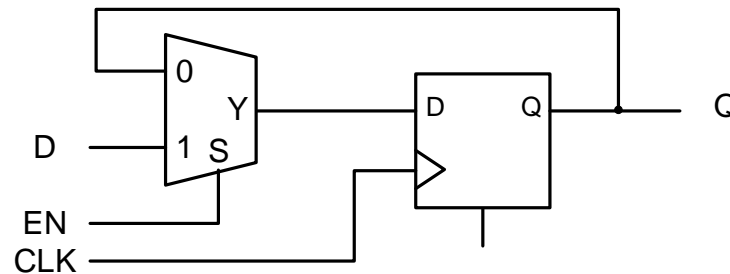- Show how to implement this flip-flop with load enable by determining the values to program into an FPGA's configurable logic block shown to the right.



A2 A1 A0

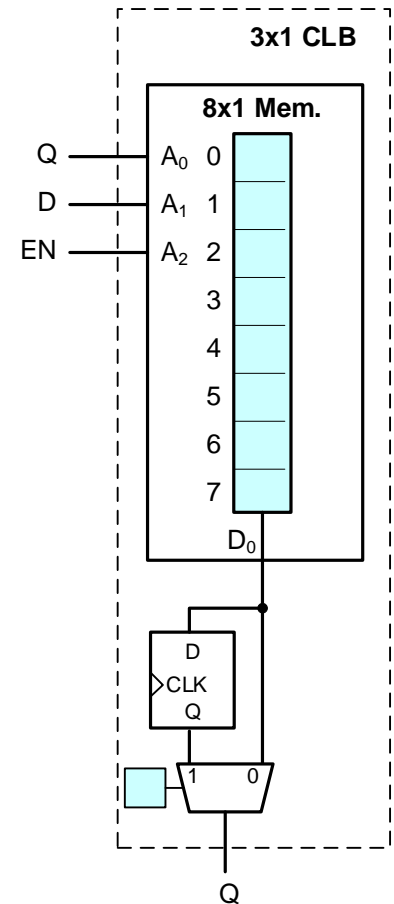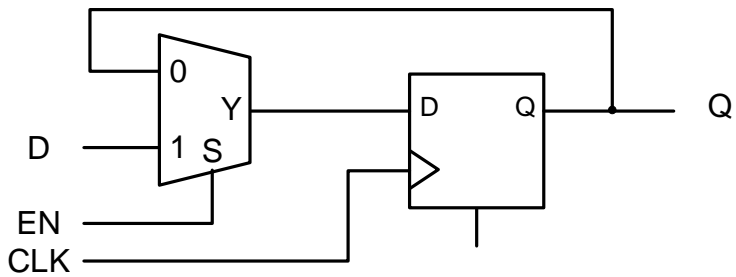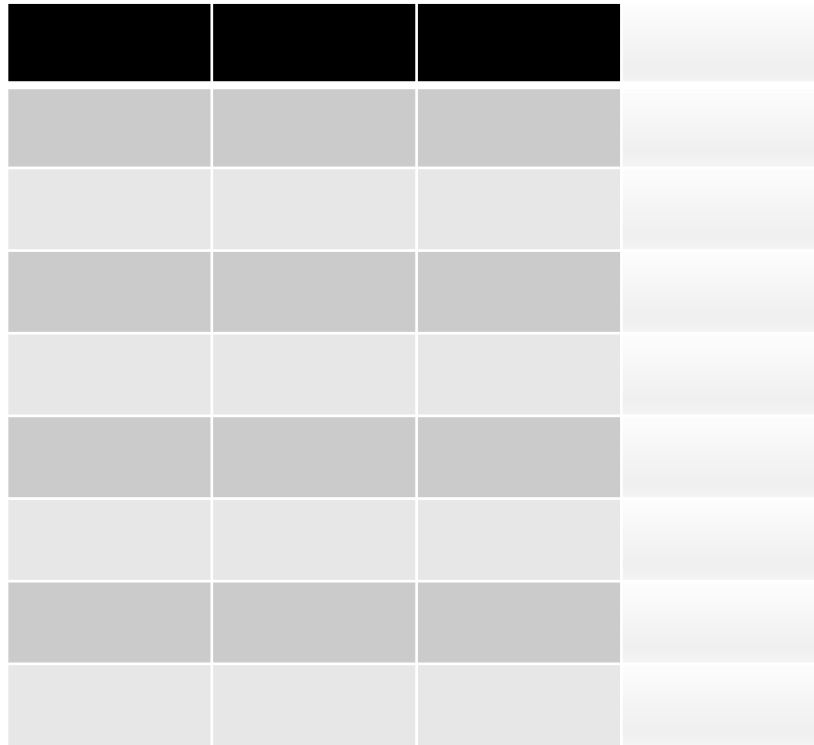

SOLUTIONS

State Machine Example

	P=0	P=1	Change
0Push	0Push	1Push	0
1Push	Wait	ChgChan	0
Wait	ChgChan	ChgChan	0
ChgChan	0Push	0Push	1

$$D0Push = Q0Push * \sim P + QChgChan$$

$$D1Push = Q0Push * P$$


$$Dwait = Q1Push * \sim P$$


$$DChgChan = Q1Push * P + Qwait$$

$$Change = QChange$$

Adder and Combinational Design

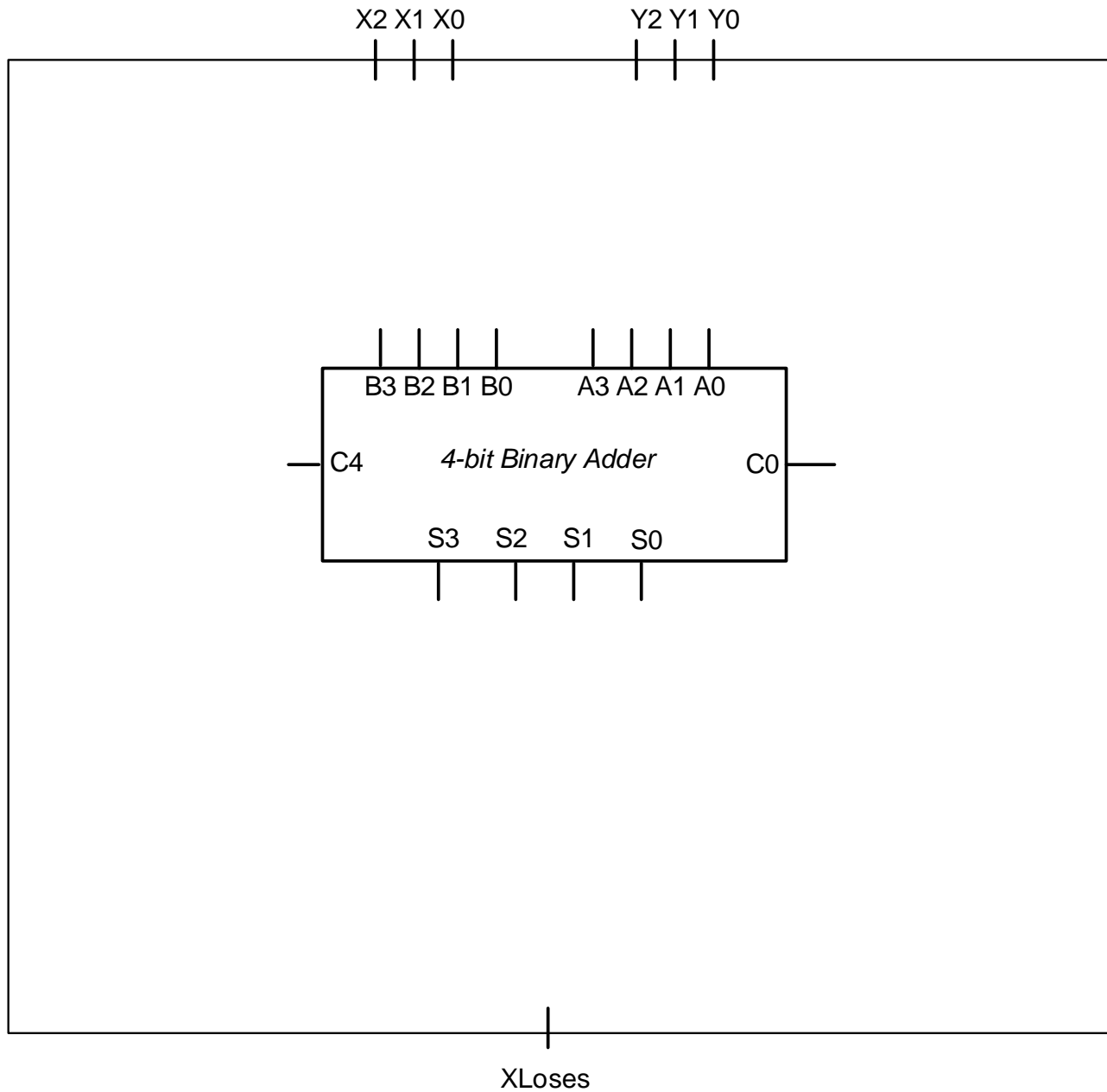- Suppose team X and team Y play a game where their scores range 0-7 decimal. Team X is much better than team Y so they give Y a handicap: to truly win, team X must score 5 points more than team Y. Design a circuit that will produce a signal: XLoses given the two 3-bit input numbers $X[2:0]$ and $Y[2:0]$ representing the scores of each team.




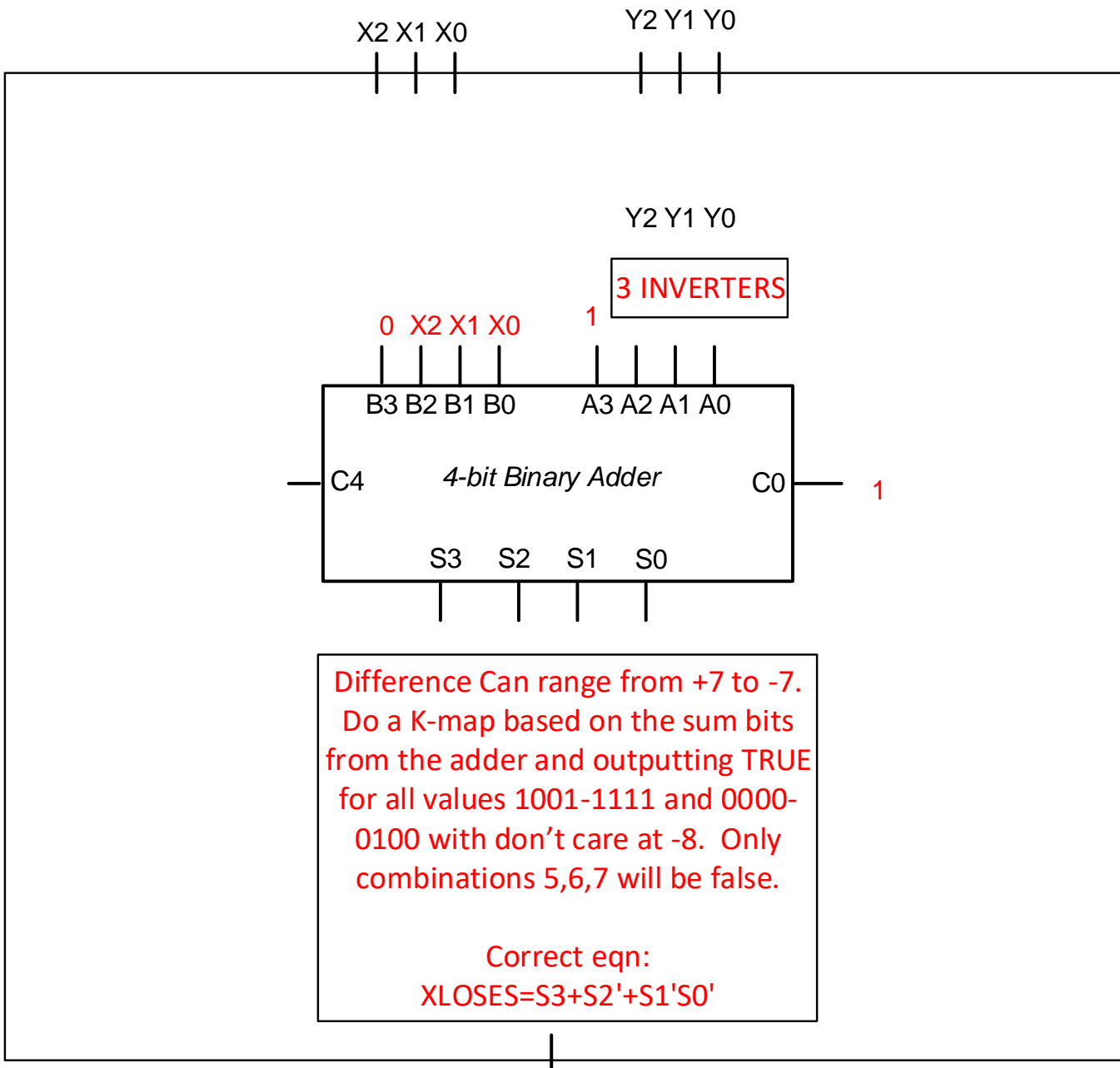

Difference Can range from +7 to -7.
 Do a K-map based on the sum bits
 from the adder and outputting TRUE
 for all values 1001-1111 and 0000-
 0100 with don't care at -8. Only
 combinations 5,6,7 will be false.

Correct eqn:
 $XLOSES = S3 + S2' + S1'S0'$

X-Y	S3S2S1S0	XLOSES
0	0111	1
1	0110	1
2	0101	1
3	0100	1
4	0100	1
5	0101	0
6	0110	0
7	0111	0
-8	1000	1
-7		1
-6		1
-5		1
-4		1
-3		1
-2		1
-1		1

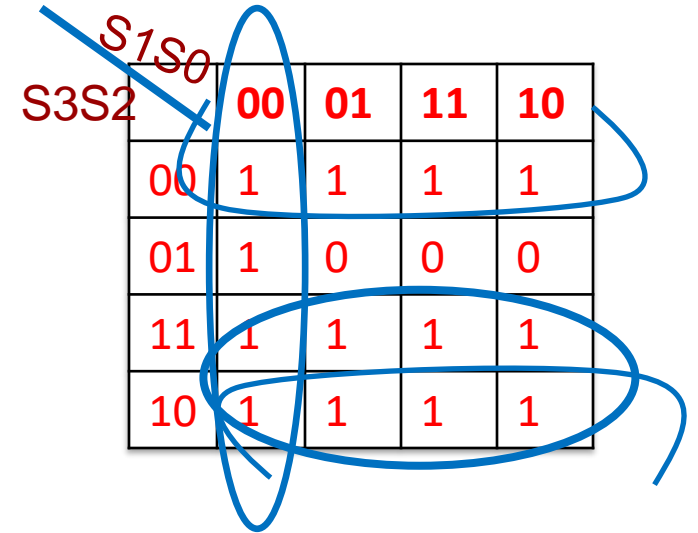

$$S_3 + S_2' + S_1'S_0'$$

ISR

- Determine a prescalar, OCR0A value, and ISR for an 8-bit timer generate at 400Hz square wave for 3 seconds on PD1. Recall the Arduino runs at 16MHz and valid prescalars are: 1, 8, 64, 256, 1024 (choose the smallest prescalar that works).

Timer/ISRs



- $400\text{Hz} = 1/400 \text{ second} = 2.5\text{ms}$
- So ISR at half that rate: 1.25ms
- 800 ISR/sec ; 2400 total ISRs for 3 secs
- $16\text{MHz clk} * 1.25\text{ms} = 20,000 \text{ clocks}$ but an 8-bit counter can hold 255 max
 - Prescalar of 64 $\Rightarrow 20000/64 = 312.5$
 - Prescalar of 256 $\Rightarrow 20000/256 = 78.125$
 - Prescalar of 1024 $\Rightarrow 20000/1024 = 19.53125$
- Choose prescalar of 256 and set OCR to 78

Solutions

```
int cnt=0;
ISR(TIMER0_COMPA_vect)
{
    if (cnt < 2400) {
        PORTD ^= (1<<1);
        cnt++;
    }
    else {
        cnt=0;
        // turn off prescalar - we wouldn't expect
        // you to know the exact bits.
    }
}
```

A2 A1 A0

En	D	Q	Q*
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

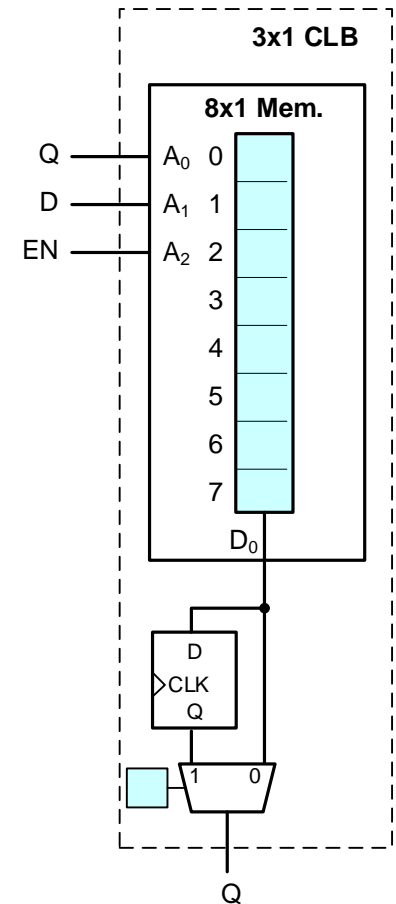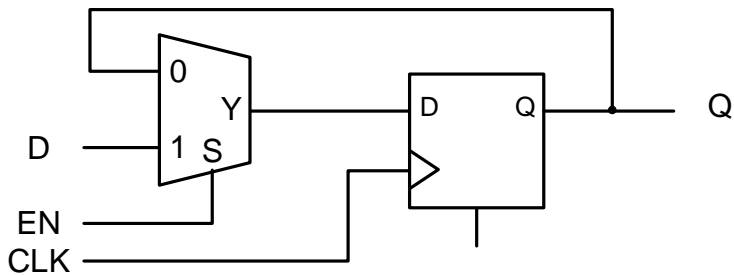

A2 A1 A0

En	D	Q	Q*
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

