

Unit 8

Minterm and Canonical Sums


2- and 3-Variable Boolean Algebra Theorems

DeMorgan's Theorem

Simplification using Boolean Algebra


Duality

 - As we progress in this unit, remember and look for the idea of duality at work
- Duality says: A new, true statement could be found from another by swapping:



$$X + 1 = 1$$

Original equation

 


Dual

CHECKERS / DECODERS


Gates

 - Gates can have more than 2 inputs but the operations stay the same
 - AND = output = 1 if ALL inputs are 1
 - Outputs 1 for only 1 input combination
 - OR = output = 1 if ANY input is 1
 - Outputs 0 for only 1 input combination



X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

3-input AND

 


X	Y	Z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

3-input OR


Checkers / Decoders

 - An AND gate only outputs '1' for 1 combination
 - That combination can be changed by adding inverters to the inputs
 - We can think of the AND gate as “checking” or “decoding” a specific combination and outputting a '1' when it matches.



X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

 Add inverters to
 create an AND gate
 decoding
 (checking for)
 combination 101




X	Y	Z	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

Add inverters to
 create an AND gate
 decoding
 (checking for)
 combination 000


Checkers / Decoders

 - Place inverters at the input of the AND gates such that
 - F produces '1' only for input combination $\{x,y,z\} = \{\underline{\quad}\}$
 - G produces '1' only for input combination $\{x,y,z\} = \{\underline{\quad}\}$



AND gate decoding
 (checking for)
 combination _____

X	Y	Z	F
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

 


AND gate decoding
 (checking for)
 combination _____

X	Y	Z	G
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	


Checkers / Decoders

 - An OR gate only outputs '0' for 1 combination
 - That combination can be changed by adding inverters to the inputs
 - We can think of the OR gate as “checking” or “decoding” a specific combination and outputting a '0' when it matches.



X	Y	Z	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

 Add inverters to
 create an OR gate
 decoding
 (checking for)
 combination 010



X	Y	Z	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

Add inverters to
 create an OR gate
 decoding
 (checking for)
 combination 110

Circuit Design and Analysis

- There are two basic tasks as a digital design engineer...
 - **Circuit Design/Synthesis:** Take a set of requirements or functional descriptions and arrive at a logic circuit
 - **Circuit Analysis:** Given a logic circuit, find or verify the logic function it implements


Design a circuit that finds the minimum valued 8-bit number in a set of 32 values in under 200 ns

Problem specification and requirements

Truth Tables

X	Y	C _{in}	C _{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Circuit Design

 

Boolean Algebra


Canonical Sums/Products

Karnaugh Maps

CAD tools



Circuit Analysis

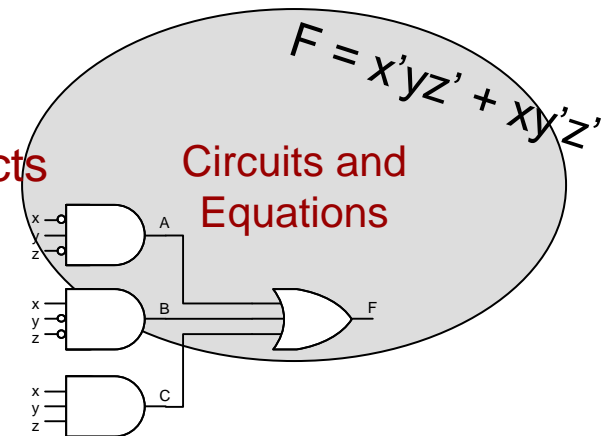

SYNTHESIZING LOGIC FUNCTIONS

The Problem


- The goal of this unit is to teach you how you can take **ANY** logic function expressed as a _____ and design a digital circuit to implement that logic function

How can I find a circuit that implements this truth table?




Primes between 0-7

X	Y	Z	P
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

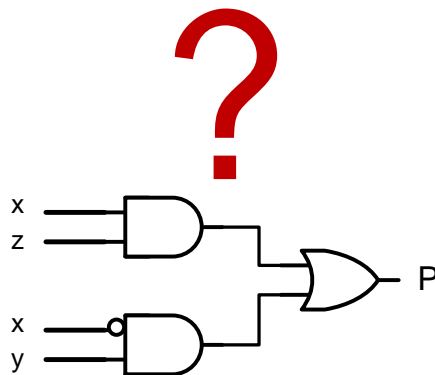

1's Count
(Addition) of Inputs

I3	I2	I1	C1	C0
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

Two Approaches: Minterms & Maxterms

- Because of duality, there are at least two ways to implement any circuit
- Using _____ gate checkers
(aka **product-or** "_____" **terms**)
 - Then combining their results with a single OR gate
- Using _____ gate checkers
(aka **sum-or** "_____" **terms**)
 - Then combining their results with a single AND gate

Using AND Gates (Minterms) to Implement Functions


- Given an any logic function, it can be implemented with the superposition of AND gate decoders/checkers

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Using AND Gates (Minterms) to Implement Functions

- Generate an **AND** gate checker ("minterm") for each combination *where the output of the logic function evaluates to 1 (i.e. $F=1$)*

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 


X	Y	Z	m2
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

Using AND Gates (Minterms) to Implement Functions

- Generate an **AND** gate checker ("minterm") for each combination *where the output of the logic function evaluates to 1* (i.e. $F=1$)

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 


X	Y	Z	m2	m4
0	0	0	0	0
0	0	1	0	0
0	1	0	1	0
0	1	1	0	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	0	0

Using AND Gates (Minterms) to Implement Functions

- Generate an **AND** gate checker ("minterm") for each combination *where the output of the logic function evaluates to 1* (i.e. $F=1$)

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 


X	Y	Z	m2	m4	m7
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	1	0	0
0	1	1	0	0	0
1	0	0	0	1	0
1	0	1	0	0	0
1	1	0	0	0	0
1	1	1	0	0	1

Using AND Gates (Minterms) to Implement Functions

- Then, OR together all outputs of the AND gate checkers to form the overall function output

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 


X	Y	Z	m2	m4	m7	F
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	1	0	0	1
0	1	1	0	0	0	0
1	0	0	0	1	0	1
1	0	1	0	0	0	0
1	1	0	0	0	0	0
1	1	1	0	0	1	1

Using AND Gates (Minterms) to Implement Functions

- Test it by plugging in combinations that should cause $F=1$
 - As long as one AND gate outputs 1, the output will be 1

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 


X	Y	Z	m2	m4	m7	F
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	1	0	0	1
0	1	1	0	0	0	0
1	0	0	0	1	0	1
1	0	1	0	0	0	0
1	1	0	0	0	0	0
1	1	1	0	0	1	1

$F(1,0,0) = 1$

Using AND Gates (Minterms) to Implement Functions

- Test it by plugging in combinations that should cause $F=1$
 - As long as one AND gate outputs 1, the output will be 1

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 


X	Y	Z	m2	m4	m7	F
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	1	0	0	1
0	1	1	0	0	0	0
1	0	0	0	1	0	1
1	0	1	0	0	0	0
1	1	0	0	0	0	0
1	1	1	0	0	1	1

$F(0,1,0) = 1$

Using AND Gates (Minterms) to Implement Functions

- Test it by plugging in combinations that should cause $F=0$
 - All AND gates output 0, thus the OR gate will output 0

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 


X	Y	Z	m2	m4	m7	F
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	1	0	0	1
0	1	1	0	0	0	0
1	0	0	0	1	0	1
1	0	1	0	0	0	0
1	1	0	0	0	0	0
1	1	1	0	0	1	1

$F(0,1,1) = 0$

Minterms

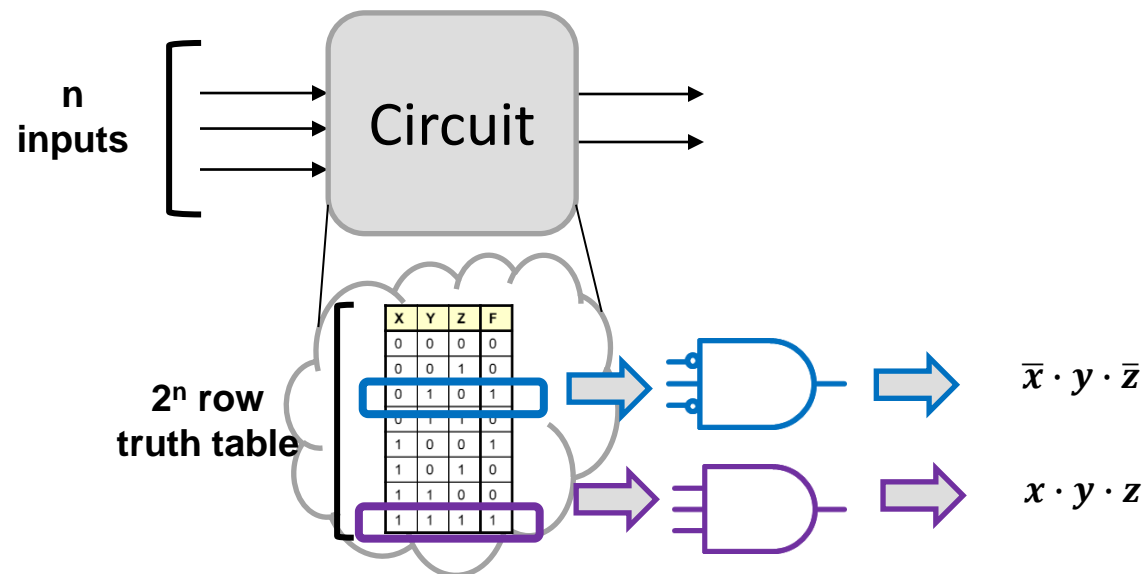- An n-input combinational function can be described with 2^n row truth table
- Each row in the truth table (input combination) has a **unique logic expression** (i.e. an AND gate) that only evaluates to '1' for that combination
 - This logic expression is known as a **minterm**



Applying Minterms to Synthesize a Function

- Each numbered **minterm** checks whether the inputs are equal to the corresponding combination. When the inputs are equal, the **minterm** will evaluate to 1 and thus the whole function will evaluate to **1**.

x	y	z	P
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

use...
 m_2
 m_3
 m_5
 m_7

$$\begin{aligned}
 P &= m_2 + m_3 + m_5 + m_7 \\
 &= x'yz' + x'yz + xy'z + xyz
 \end{aligned}$$

when $x,y,z = \{0,1,0\} = 2$ then


$$\begin{aligned}
 P &= \mathbf{0' \cdot 1 \cdot 0'} + \mathbf{0' \cdot 1 \cdot 0} + \mathbf{0 \cdot 1' \cdot 0} + \mathbf{0 \cdot 1 \cdot 0} \\
 &= \mathbf{1} + \mathbf{0} + \mathbf{0} + \mathbf{0} = \mathbf{1}
 \end{aligned}$$

when $x,y,z = \{1,0,1\} = 5$ then

$$\begin{aligned}
 P &= \mathbf{1' \cdot 0 \cdot 1'} + \mathbf{1' \cdot 0 \cdot 1} + \mathbf{1 \cdot 0' \cdot 1} + \mathbf{1 \cdot 0 \cdot 1} \\
 &= \mathbf{0} + \mathbf{0} + \mathbf{1} + \mathbf{0} = \mathbf{1}
 \end{aligned}$$

when $x,y,z = \{0,0,1\} = 1$ then
 
$$\begin{aligned}
 P &= \mathbf{0' \cdot 0 \cdot 1'} + \mathbf{0' \cdot 0 \cdot 1} + \mathbf{0 \cdot 0' \cdot 1} + \mathbf{0 \cdot 0 \cdot 1} \\
 &= \mathbf{0} + \mathbf{0} + \mathbf{0} + \mathbf{0} = \mathbf{0}
 \end{aligned}$$




Using OR-gate checkers

AN ALTERNATIVE


OR-Gate Checkers / Decoders

 - An OR gate only outputs '0' for a single combination
 - That combination can be changed by adding inverters to the inputs
 - We can think of the OR gate as “checking” or “decoding” a specific combination and outputting a '0' when it matches.



OR gate decoding
 (checking for)
 combination 010

X	Y	Z	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

 

OR gate decoding
 (checking for)
 combination 110

X	Y	Z	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

Using OR Checkers to Implement Functions


- Given an any logic function, it can be implemented with the superposition of OR-gate checkers/decoders (aka "sum or maxterms")

X	Y	Z	G
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Using OR Checkers to Implement Functions

- Generate an **OR** gate checker ("**maxterm**") for each combination *where the output of the logic function evaluates to 0* (i.e. $G=0$)

X	Y	Z	G
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1


 


X	Y	Z	M1
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Using OR Checkers to Implement Functions

- Generate an **OR** gate checker ("**maxterm**") for each combination *where the output of the logic function evaluates to 0* (i.e. $G=0$)

X	Y	Z	G
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1


 
 


X	Y	Z	M1	M4
0	0	0	1	1
0	0	1	0	1
0	1	0	1	1
0	1	1	1	1
1	0	0	1	0
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

Using OR Checkers to Implement Functions

- Generate an **OR** gate checker ("maxterm") for each combination *where the output of the logic function evaluates to 0* (i.e. $G=0$)

X	Y	Z	G
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

   


X	Y	Z	M1	M4	M6
0	0	0	1	1	1
0	0	1	0	1	1
0	1	0	1	1	1
0	1	1	1	1	1
1	0	0	1	0	1
1	0	1	1	1	1
1	1	0	1	1	0
1	1	1	1	1	1

Using OR Checkers to Implement Functions

- Then, AND together all outputs of the OR gate checkers to form the overall function output

X	Y	Z	G
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

 


X	Y	Z	M1	M4	M6	G
0	0	0	1	1	1	1
0	0	1	0	1	1	0
0	1	0	1	1	1	1
0	1	1	1	1	1	1
1	0	0	1	0	1	0
1	0	1	1	1	1	1
1	1	0	1	1	0	0
1	1	1	1	1	1	1

Using OR Checkers to Implement Functions

- Test it by plugging in combinations that should cause $G=0$
 - As long as one OR gate outputs 0, the output will be 0

X	Y	Z	G
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

 


X	Y	Z	M1	M4	M6	G
0	0	0	1	1	1	1
0	0	1	0	1	1	0
0	1	0	1	1	1	1
0	1	1	1	1	1	1
1	0	0	1	0	1	0
1	0	1	1	1	1	1
1	1	0	1	1	0	0
1	1	1	1	1	1	1

$F(0,0,1) = 0$

Using OR Checkers to Implement Functions

- Test it by plugging in combinations that should cause $G=0$
 - As long as one OR gate outputs 0, the output will be 0

X	Y	Z	G
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

 


X	Y	Z	M1	M4	M6	G
0	0	0	1	1	1	1
0	0	1	0	1	1	0
0	1	0	1	1	1	1
0	1	1	1	1	1	1
1	0	0	1	0	1	0
1	0	1	1	1	1	1
1	1	0	1	1	0	0
1	1	1	1	1	1	1

$F(1,1,0) = 0$

Using OR Checkers to Implement Functions

- Test it by plugging in combinations that should cause $G=1$
 - All OR gates output 1, thus the AND gate will output 1

X	Y	Z	G
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

 

X	Y	Z	M1	M4	M6	G
0	0	0	1	1	1	1
0	0	1	0	1	1	0
0	1	0	1	1	1	1
0	1	1	1	1	1	1
1	0	0	1	0	1	0
1	0	1	1	1	1	1
1	1	0	1	1	0	0
1	1	1	1	1	1	1

$F(1,0,1) = 1$

Applying Maxterms to Synthesize a Function

- Each output that should produce a '0' can be checked-for with an OR gate
 - We refer to that OR-gate checker as a Maxterm of the function (M_i) where i represents the decimal value of the binary combination being checked
- We then AND together the maxterms

x	y	z	P	use...
0	0	0	0	M_0
0	0	1	0	M_1
0	1	0	1	
0	1	1	1	
1	0	0	0	M_4
1	0	1	1	
1	1	0	0	M_6
1	1	1	1	

$$P = M_0 \cdot M_1 \cdot M_4 \cdot M_6$$

$$= (x+y+z) \cdot (x+y+z') \cdot (x'+y+z) \cdot (x'+y'+z)$$

when $x,y,z = \{0,0,1\} = 1$ then

$$P = (0+0+1) \cdot (0+0+1') \cdot (0'+0+1) \cdot (0'+0'+1)$$

$$= 1 \cdot 0 \cdot 1 \cdot 1 = 0$$

when $x,y,z = \{1,1,0\} = 6$ then


$$P = (1+1+0) \cdot (1+1+0') \cdot (1'+1+0) \cdot (1'+1'+0)$$

$$= 1 \cdot 1 \cdot 1 \cdot 0 = 0$$

when $x,y,z = \{1,1,1\} = 7$ then

$$P = (1+1+1) \cdot (1+1+1') \cdot (1'+1+1) \cdot (1'+1'+1)$$

$$= 1 \cdot 1 \cdot 1 \cdot 1 = 1$$

 

Defining Min-/Max-terms

- Below are the min-/max-terms for a function of 3-inputs: x,y,z
- Given a desired output, the designer could choose to include the appropriate set of min-/max-terms

Row #	Abbrev	Min-/Max-term Expression	Inputs			Min-/Max-term Outputs							
			x	y	z	m ₀ / M ₀	m ₁ / M ₁	m ₂ / M ₂	m ₃ / M ₃	m ₄ / M ₄	m ₅ / M ₅	m ₆ / M ₆	m ₇ / M ₇
0	m ₀ /M ₀	x'•y'•z' / x+y+z	0	0	0	1/0	0/1	0/1	0/1	0/1	0/1	0/1	0/1
1	m ₁ /M ₁	x'•y'•z / x+y+z'	0	0	1	0/1	1/0	0/1	0/1	0/1	0/1	0/1	0/1
2	m ₂ /M ₂	x'•y•z' / x+y'+z	0	1	0	0/1	0/1	1/0	0/1	0/1	0/1	0/1	0/1
3	m ₃ /M ₃	x'•y•z / x+y'+z'	0	1	1	0/1	0/1	0/1	1/0	0/1	0/1	0/1	0/1
4	m ₄ /M ₄	x•y'•z' / x'+y+z	1	0	0	0/1	0/1	0/1	0/1	1/0	0/1	0/1	0/1
5	m ₅ /M ₅	x•y'•z / x'+y+z'	1	0	1	0/1	0/1	0/1	0/1	0/1	1/0	0/1	0/1
6	m ₆ /M ₆	x•y•z' / x'+y'+z	1	1	0	0/1	0/1	0/1	0/1	0/1	0/1	1/0	0/1
7	m ₇ /M ₇	x•y•z / x'+y'+z'	1	1	1	0/1	0/1	0/1	0/1	0/1	0/1	0/1	1/0

Finding simplified equations and circuits

2- AND 3-VARIABLE THEOREMS

Why Boolean Algebra

- We can now convert *any truth table* into an equation and circuit by using **minterms or maxterms**
- But minterms/maxterms yield the _____ equation/circuit
- By starting with sum of minterm (product of maxterm) form and then using _____ to simplify, we can arrive and smaller (even minimal) circuits

2 & 3 Variable Theorems

T6	$X+Y = Y+X$	T6'	$X \cdot Y = Y \cdot X$	Commutativity
T7	$(X+Y)+Z = X+(Y+Z)$	T7'	$(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$	Associativity
T8	$XY+XZ = X(Y+Z)$	T8'	$(X+Y)(X+Z) = X+YZ$	Distribution & Factoring
T9	$X + XY = X$	T9'	$X(X+Y) = X$	Covering
T10	$XY + XY' = X$	T10'	$(X+Y)(X+Y') = X$	Combining
T11	$XY + X'Z + YZ =$ $XY + X'Z$	T11'	$(X+Y)(X'+Z)(Y+Z) =$ $(X+Y)(X'+Z)$	Consensus
DM	$(X+Y)' = X' \cdot Y'$	DM'	$(X \cdot Y)' = X' + Y'$	DeMorgan's

Proofs Through Other Theorems

- Prove T9: $X + XY = X$
- Prove T10: $XY + XY' = X$
- Prove T10': $(X+Y)(X+Y')=X$

T8	$XY+XZ = X(Y+Z)$	T8'	$(X+Y)(X+Z) = X+YZ$
T9	$X + XY = X$	T9'	$X(X+Y) = X$
T10	$XY + XY' = X$	T10'	$(X+Y)(X+Y') = X$
T11	$XY + X'Z + YZ =$ $XY + X'Z$	T11'	$(X+Y)(X'+Z)(Y+Z) =$ $(X+Y)(X'+Z)$

OR

Logic Synthesis

- Describe the function
 - Usually with a truth table
- Find the sum of minterm (or product of maxterm) expression
- Use Boolean Algebra (T8-T11) to find a simplified expression

Synthesize/Simplify Exercise 1

- Synthesize this function
 - First generate the canonical sum
 - Then use theorems to simplify

T8	$XY + XZ = X(Y + Z)$	T8'	$(X + Y)(X + Z) = X + YZ$
T9	$X + XY = X$	T9'	$X(X + Y) = X$
T10	$XY + XY' = X$	T10'	$(X + Y)(X + Y') = X$
T11	$XY + X'Z + YZ = XY + X'Z$	T11'	$(X + Y)(X' + Z)(Y + Z) = (X + Y)(X' + Z)$

- $P =$

Primes between 0-7

X	Y	Z	P
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Synthesize/Simplify Exercise 2a

- Synthesize each output separately
 - First generate the canonical prod.
 - Then use theorems to simplify

T8	$XY + XZ = X(Y + Z)$	T8'	$(X + Y)(X + Z) = X + YZ$
T9	$X + XY = X$	T9'	$X(X + Y) = X$
T10	$XY + XY' = X$	T10'	$(X + Y)(X + Y') = X$
T11	$XY + X'Z + YZ = XY + X'Z$	T11'	$(X + Y)(X' + Z)(Y + Z) = (X + Y)(X' + Z)$

• G1 =

• G0 =

A	B	C	G1	G0
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	0
1	0	0	1	1
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

Encode the highest input ID (ie. 3, 2, or 1) that is ON (=1)

Synthesize/Simplify Exercise 2b

- Synthesize each output separately
 - First generate the canonical sum
 - Then use theorems to simplify

T8	$XY + XZ = X(Y + Z)$	T8'	$(X + Y)(X + Z) = X + YZ$
T9	$X + XY = X$	T9'	$X(X + Y) = X$
T10	$XY + XY' = X$	T10'	$(X + Y)(X + Y') = X$
T11	$XY + X'Z + YZ = XY + X'Z$	T11'	$(X + Y)(X' + Z)(Y + Z) = (X + Y)(X' + Z)$

• $G1 = m2 + m3 + m4 + m5 + m6 + m7$

- $A'BC' + A'BC + AB'C' + AB'C + ABC' + ABC$
- [T3 ($A = A + A$) allows us to replicate m_6 and m_7 ($ABC' + ABC$)]
- $A'BC' + A'BC + ABC' + ABC + AB'C' + AB'C + ABC' + ABC$
- $B(A'C' + A'C + AC' + AC) + A(B'C' + B'C + BC' + BC)$ [T8]
- $B(A'(C'+C) + A(C'+C)) + A(B'(C+C') + B(C'+C))$ [T8/T5 or T10]
- $B(A'+A) + A(B'+B)$ [T8/T5] = **$B + A$** [Final Answer]

• $G0 = m1 + m4 + m5 + m6 + m7$

- $A'B'C + AB'C' + AB'C + ABC' + ABC$
- $A'B'C + AB'C + AB'C' + AB'C + ABC' + ABC$ [Use T3 to replicate m_5]
- $B'C(A' + A) + A(B'C' + B'C + BC' + BC)$ [T8]
- $B'C + A$ [T8/T5 or T10] = **$B'C + A$** [Final Answer]

A	B	C	G1	G0
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	0
1	0	0	1	1
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

Encode the highest input ID (ie. 3, 2, or 1) that is ON (=1)

Synthesize/Simplify Exercise 3 (Optional)

- Synthesize each output separately
 - First generate the canonical sum
 - Then use theorems to simplify

T8	$XY + XZ = X(Y + Z)$	T8'	$(X + Y)(X + Z) = X + YZ$
T9	$X + XY = X$	T9'	$X(X + Y) = X$
T10	$XY + XY' = X$	T10'	$(X + Y)(X + Y') = X$
T11	$XY + X'Z + YZ = XY + X'Z$	T11'	$(X + Y)(X' + Z)(Y + Z) = (X + Y)(X' + Z)$

C1 =

C0 = $m_1 + m_2 + m_4 + m_7$

- $A'B'C + A'BC' + AB'C' + ABC$ [Not much to factor that will cause simplification]
- $A'(B'C + BC') + A(B'C' + BC)$ [But write the truth tables of $B'C + BC'$ and $B'C' + BC$]
- $A'(B \oplus C) + A(B \oplus C)'$ [But if we let $W = B \oplus C$ then we have $A'W + AW'$...write its TT]
- **$A \oplus B \oplus C$ [Final Answer]**

1's Count of Inputs

A	B	C	C1	C0
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

How to make faster circuits...


DEFINITIONS, EXPRESSION FORMS, SPEED, AND DEMORGAN'S

Definitions


- **Literal:** A single bit _____ or its _____
 - **Good:** x , y' , SLEEPING'
 - **Bad:** $(x+y)$
- **Product Term:** A single literal by itself or an _____'ing (not _____'ing) of literals
 - **Good:** z , $x \cdot y$, AWAKE • LISTENING • THINKING
 - **BAD:** $(x \cdot y)'$, AWAKE • (LISTENING + THINKING)
 - The _____ we defined earlier are product terms where EACH input variable of a function is 1 literal in the product term
- **Sum Term:** A single literal by itself or an _____'ing (not _____'ing) of literals
 - **Good:** z , $x' + y$, CURIOUS + PERSISTENT
 - **BAD:** $(x + y)'$, TIRED • (BORED + SLEEPY)
 - The _____ we defined earlier are sum terms where EACH input variable of a function is 1 literal in the sum term

Expression/Circuit Forms

- **SOP (_____) Form:** An **SOP** expression is a logical sum (OR) of product terms
 - Correct Examples: $[x' \cdot y' \cdot z + w + a' \cdot b \cdot c]$, $[w + x' \cdot z \cdot y + y' \cdot z]$
 - Incorrect Examples: $[x' \cdot y \cdot z + w \cdot (a+b)]$, $[x \cdot y + (y' \cdot z)']$
- SOP equations yield **___-level circuits** with AND gates in the 1st level with an OR gate in the 2nd (aka _____ circuits)
- **POS (_____) Form:** A **POS** expression is a logical product (AND) of sum terms.
 - Correct Examples: $[(x+y'+z) \cdot (w'+z) \cdot (a)]$, $[z' \cdot (x+y) \cdot (w'+y)]$
 - Incorrect Examples: $[x' + y \cdot (x+w)]$, $[(x+y) \cdot (x+z)']$
- POS equations yield **___-level circuits** with OR gates in the 1st level with an AND gate in the 2nd (aka _____ circuits)
- 1 level circuits (i.e. a single gate) are generally BOTH SOP and POS

 

 SOP ⇔ AND-OR
 (Sum of products yields AND-OR circuits)



POS ⇔ OR-AND
 (Product of sums yields OR-AND circuits)


Check Yourself

Expression	SOP / POS / Both / Neither
$w \cdot x \cdot (y \cdot z)' + xy'z + w$	
$xy+xz+(w'yz)$	
$(w+y'+z)(w+x)$	
$(w+y)x(w'+z)$	
$wy + wy + xy'$	
$w+x+y$	

Factoring and Distributing (Size vs. Speed)

- Factoring decreases _____
- Distributing decreases _____
 
$$G = a \cdot (b + (c \cdot (d + \bar{e}f))) = \underline{\hspace{10em}}$$






DeMorgan's Theorem

- Inverting output of an AND gate = inverting the inputs of an OR gate
- Inverting output of an OR gate = inverting the inputs of an AND gate

A function's inverse is equivalent to inverting all the inputs and changing AND to OR and vice versa

A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

$$\overline{A \cdot B}$$

  
 


$$\overline{A} + \overline{B}$$

A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

$$\overline{A + B}$$

  


$$\overline{A} \cdot \overline{B}$$

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

Analogy: Turning a gate "_____ " (like your _____).

AND-OR / NAND-NAND

 
- Canonical Sums yield
 - AND-OR Implementation
 - _____
Implementation
- Recall inverting gates such as NAND gates may be "_____" or have desirable properties vs. typical AND/OR gates



||



OR-AND / NOR-NOR

 - Canonical Products yield
 - OR-AND Implementation
 - _____
Implementation
- Recall inverting gates such as NOR gates may be "faster" or have desirable properties vs. typical AND/OR gates




DeMorgan's Practice

  - Convert the circuits shown below to use only NAND or NOR gates?




DeMorgan's Theorem Example

 - Cancel as many bubbles as you can using DeMorgan's theorem.



 - Convert as many gates as possible to NOR gates. You are allowed to add additional inverters



DeMorgan's Theorem

- DeMorgan's let's us break large inversions (of whole expressions) into smaller inversions (of individual literals).
 - This is necessary to arrive at SOP or POS (which can only have inversions of literals)
- Recursively find the last (lowest precedence operation) and apply DeMorgan's theorem by flipping the operation and inverting the inputs

$$F = \overline{(\overline{X+Y}) + \overline{Z}} \cdot (Y+W)$$

Use DeMorgan's theorem to simplify "move" inversions (either to break-up "big bars" or join "small bars")

Generalized DeMorgan's Theorem

$$F'(X_1, \dots, X_n, +, \cdot) = F(X_1', \dots, X_n', \cdot, +)$$

To find F' , swap AND's and OR's and complement each literal. However, you must maintain the original order of operations.

Note: This parentheses doesn't matter (we are just OR'ing X' , Y , and the following subexpression)

$$F = (\overline{X} + Y) + \overline{Z} \cdot (Y + W)$$

$$F = \overline{X} + Y + (\overline{Z} \cdot (Y + W))$$

Fully parenthesized to show original order of ops.

$$\overline{F} = X \cdot \overline{Y} \cdot (Z + (\overline{Y} \cdot \overline{W}))$$

*AND's & OR's swapped
Each literal is inverted*

Additional Content

Not Tested

Canonical Sums and Products

LOGIC FUNCTION NOTATION

Canonical Sums and Products

- Truth tables require us to list all 2^n combinations of the n inputs
- A shorthand for a truth table is to describe the function using the canonical sum (sigma, Σ) or product (pi, Π) notation
- These forms of expressing a function have all the information in the truth table but can be written more compactly
 - Though still may require listing 2^n input values
- We'll often use these shorthand notations in assignments/exams

	X	Y	Z	F
m_0	0	0	0	0
m_1	0	0	1	0
m_2	0	1	0	1
m_3	0	1	1	1
m_4	1	0	0	0
m_5	1	0	1	1
m_6	1	1	0	0
m_7	1	1	1	1



$$F = \underline{\hspace{10em}}$$

Canonical Sums

- Given a T.T., use the minterms where F=1 and SUM them together
 - (Σ = SUM or OR of all the minterms)

	X	Y	Z	F
m_0	0	0	0	0
m_1	0	0	1	0
m_2	0	1	0	1
m_3	0	1	1	1
m_4	1	0	0	0
m_5	1	0	1	1
m_6	1	1	0	0
m_7	1	1	1	1



$$F = m_2 + m_3 + m_5 + m_7$$

$$= (X'YZ') + (X'YZ) + (XY'Z) + (XYZ)$$



Canonical Sum:

$$F = \Sigma_{xyz} (2, 3, 5, 7)$$

List the variables in the _____ they would appear in the truth table and that you'd use to find the decimal values

List the minterms where F is 1, and just list their decimal number equivalent

Canonical Products

- Given a T.T., AND together all the maxterms where $F = 0$

	X	Y	Z	F
M_0	0	0	0	0
M_1	0	0	1	0
M_2	0	1	0	1
M_3	0	1	1	1
M_4	1	0	0	0
M_5	1	0	1	1
M_6	1	1	0	0
M_7	1	1	1	1

$$\begin{aligned}
 F &= M_0 \cdot M_1 \cdot M_4 \cdot M_6 \\
 &= (X+Y+Z) \cdot (X+Y+Z') \cdot \\
 &\quad (X'+Y+Z) \cdot (X'+Y'+Z)
 \end{aligned}$$

Canonical Product:

$$F = \Pi_{xyz}(0, 1, 4, 6)$$

List the variables in the order they would appear in the truth table and that you'd use to find the decimal values

List the maxterms where F is 0, and just list their decimal number equivalent

Canonical Sums & Products

- **Canonical Sum:** An SOP expression where all the product terms are minterms (i.e. have each literal in each product term)
- **Canonical Product:** A POS expression where all the sum terms are maxterms (i.e. each literal in each sum term)

Canonical Sum:

$$F = \sum_{xyz} (2, 3, 5, 7)$$

$$F = m_2 + m_3 + m_5 + m_7$$

$$= (X'YZ') + (X'YZ) + (XY'Z) + (XYZ)$$

Canonical Product:

$$F = \prod_{xyz} (0, 1, 4, 6)$$

$$F = M_0 \cdot M_1 \cdot M_4 \cdot M_6 =$$

$$(X+Y+Z) \cdot (X+Y+Z') \cdot (X'+Y+Z) \cdot (X'+Y'+Z)$$

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Definitions

- Minterm:** A **product** term where all the input variables of a function appear as exactly one literal

$f(x,y,z)$	Yes (m_i) / No	$g(w,x,y,z)$	Yes (m_i) / No
$x \cdot y$			Yes, m_4
$x' \cdot y \cdot z'$		$w \cdot x' \cdot z'$	No
$x + y' \cdot z'$		$w \cdot x' \cdot y \cdot z$	Yes, m_{11}
$(x \cdot y' \cdot z)'$			Yes, m_6

- Maxterm:** A **sum** term where each input variable of a function appears as exactly one literal

$f(a,b,c)$	Yes (M_i) / No	$g(v,w,x,y,z)$	Yes (M_i) / No
$a + b' + c$			Yes, M_{12}
$a + b'$		$v + z$	No
$a' \cdot (b' + c)$		$v' + w + x + y' + z'$	Yes, M_{19}
$(a' + b + c)'$			