

Unit 8b

Minterm and Canonical Sums

2- and 3-Variable Boolean Algebra Theorems

DeMorgan's Theorem

Simplification using Boolean Algebra

Logic Circuit Design and Analysis

- There are two basic tasks as a digital design engineer...
 - Circuit Design/_____**: Take a set of requirements or functional descriptions and arrive at a logic circuit
 - Circuit Analysis**: Given a logic circuit, find or verify the logic function it implements

Design a circuit that finds the minimum valued 8-bit number in a set of 32 values in under 200 ns

X1	X0	Y1	Y0	S2	S1	S0
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	1	1
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	1	0	0
1	0	0	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	1	0	0
1	0	1	1	1	0	1
1	1	0	0	0	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	1
1	1	1	1	1	1	0

Problem
specification and
requirements

Truth Tables

Circuit Design


Boolean Algebra

Canonical Sums/Products

Karnaugh Maps

CAD tools


Circuit Analysis

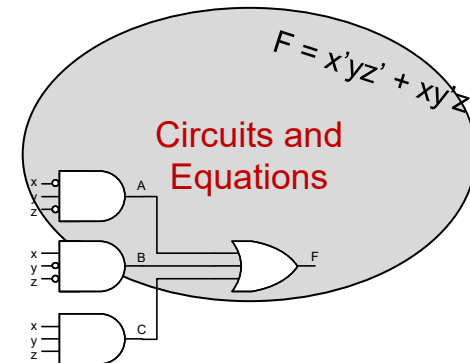


DERIVING TRUTH TABLES

Putting Combinational Logic in Context

 - Recall that **combinational logic**...
 - Refers to logic circuits where the output is function of only the _____-**time** inputs
 - Can **ALWAYS** be described using a _____ then converted to a circuit
 - Can implement common **arithmetic, logic, comparison, and data selection operators** typically used by **software**.





Typical Software Operators

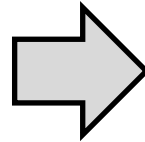

S	X	Y	Z
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1


Truth Table

  

Logic Circuit

Seeing Truth Tables

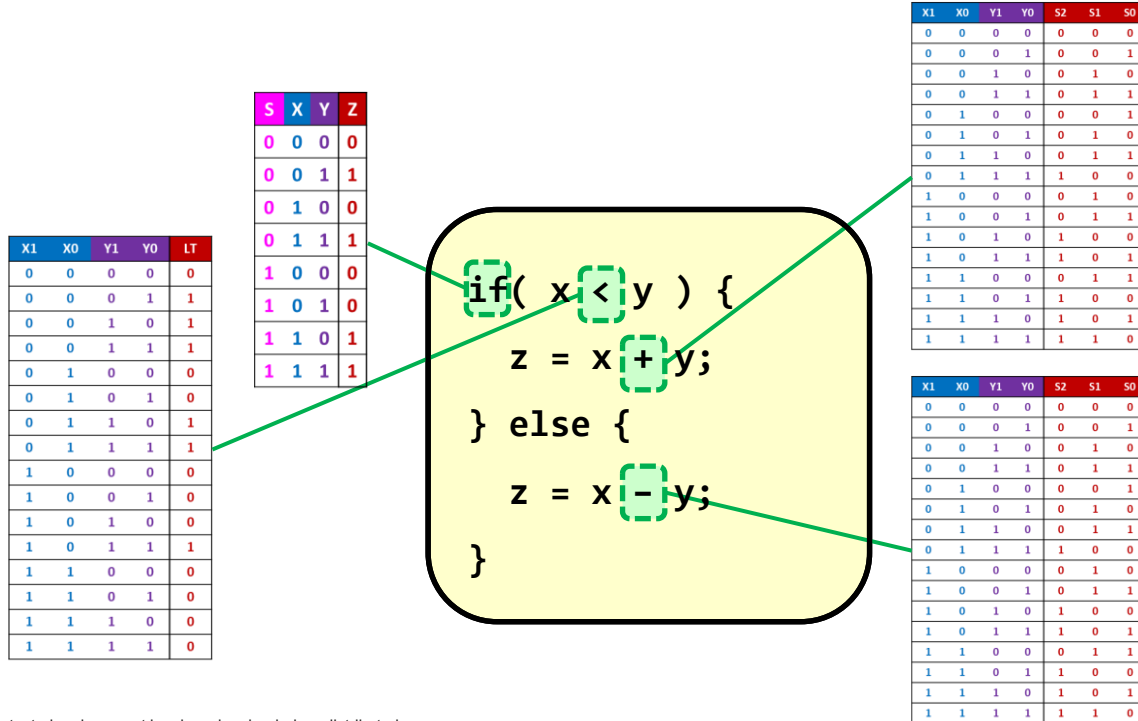
- Important skill:** Describe an operation or problem statement with a truth table.



Combinational Logic Design Steps


- **Important skill:** Describe an operation or problem statement with a truth table.
- Steps:
 - Identify the inputs and how many bits each requires [2-bit unsigned input range: _____ decimal]
 - Determine how many output bits are needed by considering the numeric range of all possible outputs [Min. Sum = _____, Max. Sum = _____. Thus, ____-bit output]
 - Write a truth table with all 2^n combinations of the n input bits and come up with the desired output on your own [____ total inputs => ____ combinations]
 - Convert each output to a logic circuit using one of the synthesis methods we will teach you in the next two units. [Focus of the next 2 units.]

 Task
Build an addition operation for 2-bit unsigned binary numbers: $X_1X_0 + Y_1Y_0$




X1	X0	Y1	Y0	S2	S1	S0
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	1	1
.	.	.	.	.	.	.
1	1	0	1	1	0	0
1	1	1	0	1	0	1
1	1	1	1	1	1	0

Addition

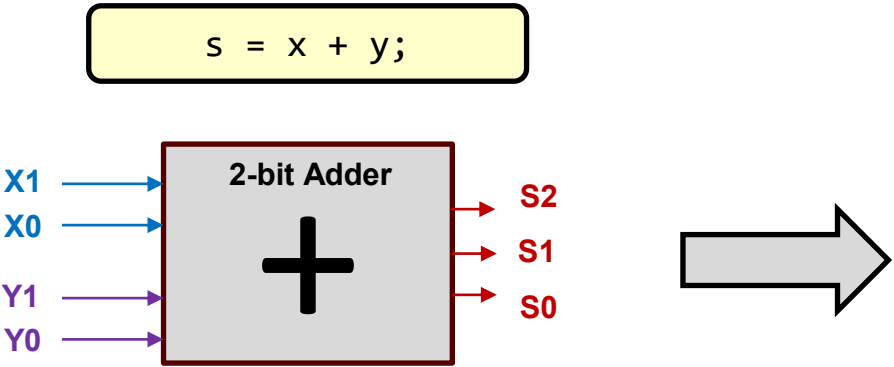

X1	X0	Y1	Y0	S2	S1	S0	Descrip
0	0	0	0	0	0	0	0+0=0
0	0	0	1	0	0	1	0+1=1
0	0	1	0	0	1	0	0+2=2
0	0	1	1	0	1	1	0+3=3
0	1	0	0	0	0	1	1+0=1
0	1	0	1	0	1	0	1+1=2
0	1	1	0	0	1	1	1+2=3
0	1	1	1	1	0	0	1+3=4
1	0	0	0				2+0=2
1	0	0	1				2+1=3
1	0	1	0				2+2=4
1	0	1	1				2+3=5
1	1	0	0				3+0=3
1	1	0	1				3+1=4
1	1	1	0				3+2=5
1	1	1	1				3+3=6

Comparison


 


X1	X0	Y1	Y0	LT	Descrip
0	0	0	0	0	0<0=F
0	0	0	1	1	0<1=T
0	0	1	0	1	0<2=T
0	0	1	1	1	0<3=T
0	1	0	0	0	1<0=F
0	1	0	1	0	1<1=F
0	1	1	0	1	1<2=T
0	1	1	1	1	1<3=T
1	0	0	0	0	2<0=F
1	0	0	1	0	2<1=F
1	0	1	0	0	2<2=F
1	0	1	1	1	2<3=T
1	1	0	0	0	3<0=F
1	1	0	1	0	3<1=F
1	1	1	0	0	3<2=F
1	1	1	1	0	3<3=F

If..Else (Ternary) Operator (aka "Mux")

```
z = (s==1) ? x : y;
```

 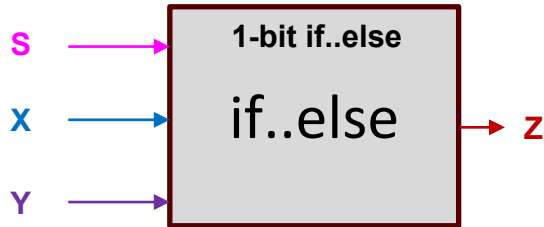
```
// if(s==1) { z=x; }  
// else    { z=y; }
```



S	X	Y	Z
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Coder / Decoder

 - Example:** Imagine we want to code (or "encrypt") 3-bit numbers and then decrypt/decode on the other side.




X2	X1	X0	C3	C2	C1	C0
0	0	0	1	0	1	1
0	0	1	0	1	1	0
0	1	0	1	0	1	0
0	1	1	1	1	0	1
1	0	0	0	1	1	1
1	0	1	0	0	0	1
1	1	0	1	1	1	1
1	1	1	0	1	0	1

C3	C2	C1	C0	X2	X1	X0
0	0	0	0	-	-	-
0	0	0	1			
0	0	1	0	-	-	-
0	0	1	1	-	-	-
0	1	0	0	-	-	-
0	1	0	1			
0	1	1	0			
0	1	1	1			
1	0	0	0	-	-	-
1	0	0	1	-	-	-
1	0	1	0	0	1	0
1	0	1	1	0	0	0
1	1	0	0	-	-	-
1	1	0	1	0	1	1
1	1	1	0	-	-	-
1	1	1	1	1	1	0

Scaling to Larger Input Sizes

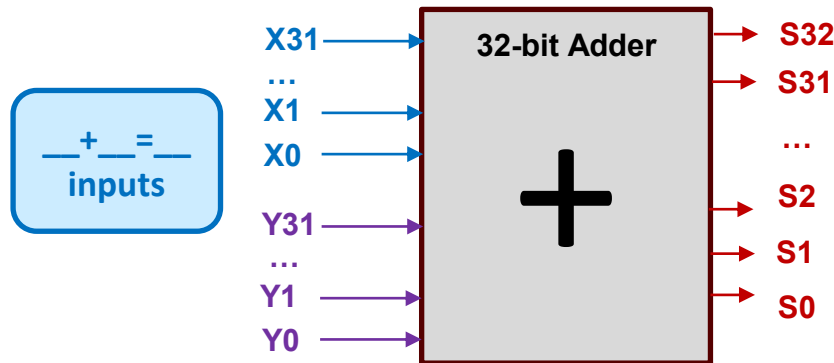
- Typical hardware systems process much larger inputs (32- or 64-bit inputs).
How would this process scale?
 - How many rows would a truth table for a 32-bit addition circuit require? _____
 - Clearly, that's not going to scale well for either human or computer-aided algorithms



X31	...	...	Y0	S32	...	S0
0			0	0		0
0			1	0		1
0			0	0		0
0			1	0		1
0			0	0		1
0			1			0
0						1
0						0
1				0		0
1			1	0		1
1			0	1		0
1			1	1		1
1			0	0		1
1			1	1		0
1			0	1		1
1			1	1		0


Dealing with Large Input Circuits [1]

 - So how do we deal with large-input designs?




Dealing with Large Input Circuits [2]

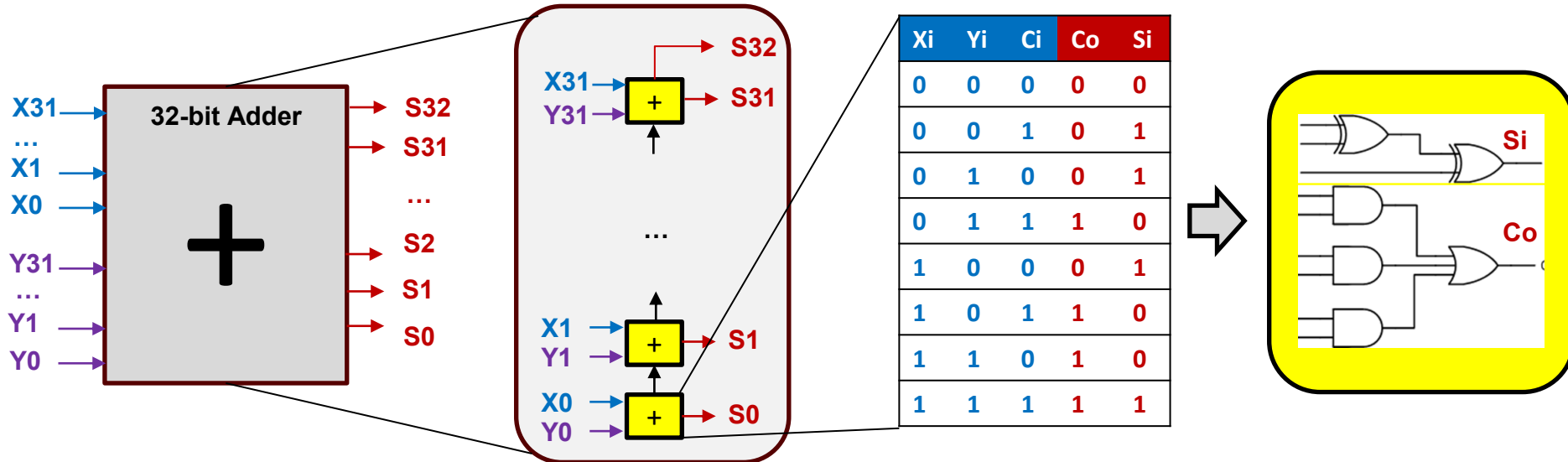- By decomposing the large circuits into **smaller, regularly structured blocks** where we CAN use truth tables and synthesis methods to find arrive at a circuit, we can simply connect these small blocks in a regular way to build the larger structure (like _____)!



Dealing with Large Input Circuits [3]

 - By decomposing the large circuits into **smaller, regularly structured blocks** where we CAN use truth tables and synthesis methods to find arrive at a circuit, we can simply connect these small blocks in a regular way to build the larger structure (like Legos)!




Synthesis: Truth Tables => Circuits

- So, now that we see how operations can be expressed as truth tables...
- ...**how do we convert (aka "synthesize") those tables to logic circuits?**
- Let's use the following 2 examples for our discussion
 - 3-bit Prime Checker: Ad-hoc (irregular) design
 - Full Adder: Regular building block for larger adders

3-bit Prime Number Checker

 - Given a 3-bit, unsigned number check if it is prime (output 1) or not (output 0).




Primes between 0-7


X2	X1	X0	P
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	



 How can I find a circuit that implements this truth table?



3-input Sum (aka Full Adder)

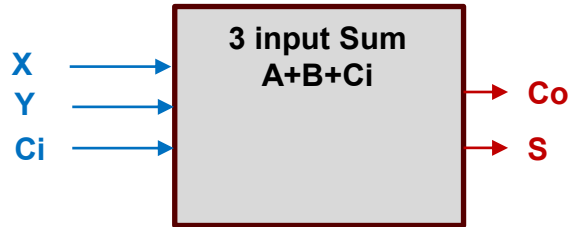


3 input Sum

X	Y	Ci	Co	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1



 How can I find a circuit that implements this truth table?



Ad-hoc vs. Regular Design Approach

- For **smaller** circuits or where there is **no regular pattern**, we use an ad-hoc approach of simply describing it with a truth table and trying to synthesize it using the methods we will teach you in the next two units.
 - Example: Prime number checker
- For **larger** circuits where there is a **discernable, regular pattern** we can decompose it into smaller blocks, design those smaller circuits using the techniques we will teach but then build the larger structure from these smaller blocks.
 - Example: Larger arithmetic of data selection circuits

The beginning of synthesis...

CHECKERS / DECODERS

Duality


- As we progress in this unit, remember and look for the idea of duality at work
- Duality says: A new, true statement could be found from another by swapping:

- $\underline{\hspace{1cm}} \Leftrightarrow \underline{\hspace{1cm}}$
- $\underline{\hspace{1cm}} \Leftrightarrow \underline{\hspace{1cm}}$

$$\begin{array}{ccc}
 X + 1 = 1 & \Rightarrow & X \cdot 0 = 0 \\
 \text{Original} & & \text{Dual} \\
 \text{equation} & &
 \end{array}$$


Gates

 - Gates can have more than 2 inputs but the operations stay the same
 - AND = output = 1 if ALL inputs are 1
 - Outputs 1 for only 1 input combination
 - OR = output = 1 if ANY input is 1
 - Outputs 0 for only 1 input combination



X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

3-input AND

 


X	Y	Z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

3-input OR


Checkers / Decoders

 - An AND gate only outputs '1' for 1 combination
 - That combination can be changed by adding inverters to the inputs
 - We can think of the AND gate as “checking” or “decoding” a specific combination and outputting a '1' when it matches.



Add inverters to
create an AND
gate decoding
(checking for)
combination 101

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

 


Add inverters to
create an AND
gate decoding
(checking for)
combination 000

X	Y	Z	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0


Checkers / Decoders

 - Place inverters at the input of the AND gates such that
 - F produces '1' only for input combination $\{x,y,z\} = \{010\}$
 - G produces '1' only for input combination $\{x,y,z\} = \{110\}$



AND gate
decoding
(checking for)
combination 010

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

 


AND gate
decoding
(checking for)
combination 110

X	Y	Z	G
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0


Checkers / Decoders

 - An OR gate only outputs '0' for 1 combination
 - That combination can be changed by adding inverters to the inputs
 - We can think of the OR gate as “checking” or “decoding” a specific combination and outputting a '0' when it matches.



OR gate decoding
(checking for)
combination 010

X	Y	Z	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

 

OR gate decoding
(checking for)
combination 110

X	Y	Z	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

SYNTHESIZING LOGIC FUNCTIONS

Two Approaches: Minterms & Maxterms

- Because of duality, there are at least two ways to implement any circuit
- Using _____ gate checkers
(aka **product- or "____-" terms**)
 - Then combining their results with a single OR gate
- Using _____ gate checkers
(aka **sum- or "____-" terms**)
 - Then combining their results with a single AND gate

Using AND Gates (Minterms) to Implement Functions

- Given an any logic function, it can be implemented with the superposition of AND gate decoders/checkers


X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

**An arbitrary truth table
(could be any truth table)**

Using AND Gates (Minterms) to Implement Functions

- Generate an **AND** gate checker ("minterm") for each combination *where the output of the logic function evaluates to 1 (i.e. $F=1$)*

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 


X	Y	Z	m2
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

Using AND Gates (Minterms) to Implement Functions

- Generate an **AND** gate checker ("minterm") for each combination *where the output of the logic function evaluates to 1* (i.e. $F=1$)

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

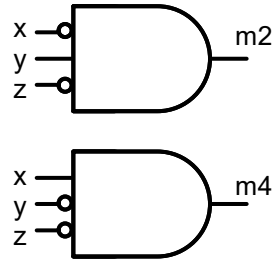


X	Y	Z	m2	m4
0	0	0	0	0
0	0	1	0	0
0	1	0	1	0
0	1	1	0	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	0	0

Using AND Gates (Minterms) to Implement Functions

- Generate an **AND** gate checker ("minterm") for each combination *where the output of the logic function evaluates to 1 (i.e. $F=1$)*

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 


X	Y	Z	m2	m4	m7
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	1	0	0
0	1	1	0	0	0
1	0	0	0	1	0
1	0	1	0	0	0
1	1	0	0	0	0
1	1	1	0	0	1

Using AND Gates (Minterms) to Implement Functions

- Then, OR together all outputs of the AND gate checkers to form the overall function output

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

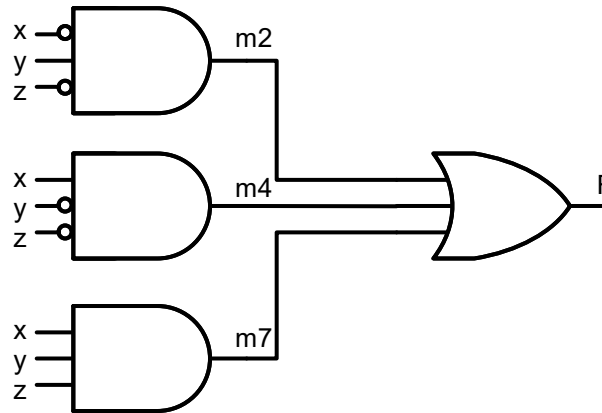


X	Y	Z	m2	m4	m7	F
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	1	0	0	1
0	1	1	0	0	0	0
1	0	0	0	1	0	1
1	0	1	0	0	0	0
1	1	0	0	0	0	0
1	1	1	0	0	1	1

Using AND Gates (Minterms) to Implement Functions

- Test it by plugging in combinations that should cause $F=1$
 - As long as one AND gate outputs 1, the output will be 1

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 


X	Y	Z	m2	m4	m7	F
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	1	0	0	1
0	1	1	0	0	0	0
1	0	0	0	1	0	1
1	0	1	0	0	0	0
1	1	0	0	0	0	0
1	1	1	0	0	1	1

$$F(1,0,0) = 1$$

Using AND Gates (Minterms) to Implement Functions

- Test it by plugging in combinations that should cause $F=1$
 - As long as one AND gate outputs 1, the output will be 1

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 


X	Y	Z	m2	m4	m7	F
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	1	0	0	1
0	1	1	0	0	0	0
1	0	0	0	1	0	1
1	0	1	0	0	0	0
1	1	0	0	0	0	0
1	1	1	0	0	1	1

$$F(0,1,0) = 1$$

Using AND Gates (Minterms) to Implement Functions

- Test it by plugging in combinations that should cause $F=0$
 - All AND gates output 0, thus the OR gate will output 0

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 


X	Y	Z	m2	m4	m7	F
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	1	0	0	1
0	1	1	0	0	0	0
1	0	0	0	1	0	1
1	0	1	0	0	0	0
1	1	0	0	0	0	0
1	1	1	0	0	1	1

$$F(0,1,1) = 0$$

Minterms

 - An n-input combinational function can be described with 2^n row truth table
- Each row in the truth table (input combination) has a **unique logic expression** (i.e. an AND gate) that only evaluates to '1' for that combination
 - This logic expression is known as a **minterm**



Applying Minterms to Synthesize a Function

- Each numbered **minterm** checks whether the inputs are equal to the corresponding combination. When the inputs are equal, the **minterm** will evaluate to 1 and thus the whole function will evaluate to 1.

Primes between 0-7

X	Y	Z	P
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Use...

m2

m3

m5

m7

$$P = m_2 + m_3 + m_5 + m_7$$

$$= x'yz' + x'yz + xy'z + xyz$$

when $x,y,z = \{0,1,0\} = 2$ then

$$P = 0' \cdot 1 \cdot 0' + 0' \cdot 1 \cdot 0 + 0 \cdot 1' \cdot 0 + 0 \cdot 1 \cdot 0$$

$$= 1 + 0 + 0 + 0 = 1$$

when $x,y,z = \{1,0,1\} = 5$ then


$$P = 1' \cdot 0 \cdot 1' + 1' \cdot 0 \cdot 1 + 1 \cdot 0' \cdot 1 + 1 \cdot 0 \cdot 1$$

$$= 0 + 0 + 1 + 0 = 1$$

when $x,y,z = \{0,0,1\} = 1$ then

$$P = 0' \cdot 0 \cdot 1' + 0' \cdot 0 \cdot 1 + 0 \cdot 0' \cdot 1 + 0 \cdot 0 \cdot 1$$

$$= 0 + 0 + 0 + 0 = 0$$

 


Using OR-gate checkers

AN ALTERNATIVE


OR-Gate Checkers / Decoders

 - An OR gate only outputs '0' for a single combination
 - That combination can be changed by adding inverters to the inputs
 - We can think of the OR gate as “checking” or “decoding” a specific combination and outputting a '0' when it matches.



OR gate decoding
(checking for)
combination 010

X	Y	Z	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

 

OR gate decoding
(checking for)
combination 110

X	Y	Z	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

Using OR Checkers to Implement Functions

- Given an any logic function, it can be implemented with the superposition of OR-gate checkers/decoders (aka "sum- or max-terms")

X	Y	Z	G
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Using OR Checkers to Implement Functions

- Generate an **OR** gate checker ("maxterm") for each combination *where the output of the logic function evaluates to 0* (i.e. $G=0$)

X	Y	Z	G
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1




X	Y	Z	M1
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Using OR Checkers to Implement Functions

- Generate an **OR** gate checker ("maxterm") for each combination *where the output of the logic function evaluates to 0* (i.e. $G=0$)

X	Y	Z	G
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

 


X	Y	Z	M1	M4
0	0	0	1	1
0	0	1	0	1
0	1	0	1	1
0	1	1	1	1
1	0	0	1	0
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

Using OR Checkers to Implement Functions

- Generate an **OR** gate checker ("maxterm") for each combination *where the output of the logic function evaluates to 0* (i.e. $G=0$)

X	Y	Z	G
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

 


X	Y	Z	M1	M4	M6
0	0	0	1	1	1
0	0	1	0	1	1
0	1	0	1	1	1
0	1	1	1	1	1
1	0	0	1	0	1
1	0	1	1	1	1
1	1	0	1	1	0
1	1	1	1	1	1

Using OR Checkers to Implement Functions

- Then, AND together all outputs of the OR gate checkers to form the overall function output

X	Y	Z	G
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

 


X	Y	Z	M1	M4	M6	G
0	0	0	1	1	1	1
0	0	1	0	1	1	0
0	1	0	1	1	1	1
0	1	1	1	1	1	1
1	0	0	1	0	1	0
1	0	1	1	1	1	1
1	1	0	1	1	0	0
1	1	1	1	1	1	1

Using OR Checkers to Implement Functions

- Test it by plugging in combinations that should cause $G=0$
 - As long as one OR gate outputs 0, the output will be 0

X	Y	Z	G
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

 


$$F(0,0,1) = 0$$

X	Y	Z	M1	M4	M6	G
0	0	0	1	1	1	1
0	0	1	0	1	1	0
0	1	0	1	1	1	1
0	1	1	1	1	1	1
1	0	0	1	0	1	0
1	0	1	1	1	1	1
1	1	0	1	1	0	0
1	1	1	1	1	1	1

Using OR Checkers to Implement Functions

- Test it by plugging in combinations that should cause $G=0$
 - As long as one OR gate outputs 0, the output will be 0

X	Y	Z	G
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

 


$$F(1,1,0) = 0$$

X	Y	Z	M1	M4	M6	G
0	0	0	1	1	1	1
0	0	1	0	1	1	0
0	1	0	1	1	1	1
0	1	1	1	1	1	1
1	0	0	1	0	1	0
1	0	1	1	1	1	1
1	1	0	1	1	0	0
1	1	1	1	1	1	1

Using OR Checkers to Implement Functions

- Test it by plugging in combinations that should cause $G=1$
 - All OR gates output 1, thus the AND gate will output 1

X	Y	Z	G
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

 

$$F(1,0,1) = 1$$

X	Y	Z	M1	M4	M6	G
0	0	0	1	1	1	1
0	0	1	0	1	1	0
0	1	0	1	1	1	1
0	1	1	1	1	1	1
1	0	0	1	0	1	0
1	0	1	1	1	1	1
1	1	0	1	1	0	0
1	1	1	1	1	1	1

Applying Maxterms to Synthesize a Function

- Each output that should produce a '0' can be checked-for with an OR gate
 - We refer to that OR-gate checker as a Maxterm of the function (M_i) where i represents the decimal value of the binary combination being checked
- We then AND together the maxterms

Primes between 0-7

X	Y	Z	P
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Use...

M0

M1

M4

M6

$$P = M_0 \cdot M_1 \cdot M_4 \cdot M_6$$

$$= (x+y+z) \cdot (x+y+z') \cdot (x'+y+z) \cdot (x'+y'+z)$$

when $x,y,z = \{0,0,1\} = 1$ then

$$P = (0+0+1) \cdot (0+0+1') \cdot (0'+0+1) \cdot (0'+0'+1)$$

$$= 1 \cdot 0 \cdot 1 \cdot 1 = 0$$

when $x,y,z = \{1,1,0\} = 6$ then


$$P = (1+1+0) \cdot (1+1+0') \cdot (1'+1+0) \cdot (1'+1'+0)$$

$$= 1 \cdot 1 \cdot 1 \cdot 0 = 0$$

when $x,y,z = \{1,1,1\} = 7$ then

$$P = (1+1+1) \cdot (1+1+1') \cdot (1'+1+1) \cdot (1'+1'+1)$$

$$= 1 \cdot 1 \cdot 1 \cdot 1 = 1$$

 

Defining Min-/Max-terms

- Below are the min-/max-terms for a function of 3-inputs: x,y,z
- Given a desired output, the designer could choose to include the appropriate set of min-/max-terms

Row #	Abbrev	Min-/Max-term Expression	Inputs			Min-/Max-term Outputs							
			x	y	z	m ₀ /M ₀	m ₁ /M ₁	m ₂ /M ₂	m ₃ /M ₃	m ₄ /M ₄	m ₅ /M ₅	m ₆ /M ₆	m ₇ /M ₇
0	m ₀ /M ₀	x'•y'•z' / x+y+z	0	0	0	1/0	0/1	0/1	0/1	0/1	0/1	0/1	0/1
1	m ₁ /M ₁	x'•y'•z / x+y+z'	0	0	1	0/1	1/0	0/1	0/1	0/1	0/1	0/1	0/1
2	m ₂ /M ₂	x'•y•z' / x+y'+z	0	1	0	0/1	0/1	1/0	0/1	0/1	0/1	0/1	0/1
3	m ₃ /M ₃	x'•y•z / x+y'+z'	0	1	1	0/1	0/1	0/1	1/0	0/1	0/1	0/1	0/1
4	m ₄ /M ₄	x•y'•z' / x'+y+z	1	0	0	0/1	0/1	0/1	0/1	1/0	0/1	0/1	0/1
5	m ₅ /M ₅	x•y'•z / x'+y+z'	1	0	1	0/1	0/1	0/1	0/1	0/1	1/0	0/1	0/1
6	m ₆ /M ₆	x•y•z' / x'+y'+z	1	1	0	0/1	0/1	0/1	0/1	0/1	0/1	1/0	0/1
7	m ₇ /M ₇	x•y•z / x'+y'+z'	1	1	1	0/1	0/1	0/1	0/1	0/1	0/1	0/1	1/0

Finding simplified equations and circuits

2- AND 3-VARIABLE THEOREMS

Why Boolean Algebra

- We can now convert *any truth table* into an equation and circuit by using **minterms or maxterms**
- But minterms/maxterms yield the _____ equation/circuit
- By starting with sum of minterm (product of maxterm) form and then using _____ **algebra** to simplify, we can arrive and smaller (even minimal) circuits

2 & 3 Variable Theorems

T6	$X+Y = Y+X$	T6'	$X \cdot Y = Y \cdot X$	Commutativity
T7	$(X+Y)+Z = X+(Y+Z)$	T7'	$(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$	Associativity
T8	$XY+XZ = X(Y+Z)$	T8'	$(X+Y)(X+Z) = X+YZ$	Distribution & Factoring
T9	$X + XY = X$	T9'	$X(X+Y) = X$	Covering
T10	$XY + XY' = X$	T10'	$(X+Y)(X+Y') = X$	Combining
T11	$XY + X'Z + YZ =$ $XY + X'Z$	T11'	$(X+Y)(X'+Z)(Y+Z) =$ $(X+Y)(X'+Z)$	Consensus
DM	$(X+Y)' = X' \cdot Y'$	DM'	$(X \cdot Y)' = X' + Y'$	DeMorgan's

Proofs Through Other Theorems

- Prove T9: $X + XY = X$

- Prove T10: $XY + XY' = X$

- Prove T10': $(X+Y)(X+Y')=X$

T8	$XY + XZ = X(Y + Z)$	T8'	$(X + Y)(X + Z) = X + YZ$
T9	$X + XY = X$	T9'	$X(X + Y) = X$
T10	$XY + XY' = X$	T10'	$(X + Y)(X + Y') = X$
T11	$XY + X'Z + YZ =$ $XY + X'Z$	T11'	$(X + Y)(X' + Z)(Y + Z) =$ $(X + Y)(X' + Z)$

OR

Logic Synthesis

- Describe the function
 - Usually with a truth table
- Find the sum of minterm (or product of maxterm) expression
- Use Boolean Algebra (T8-T11) to find a simplified expression

Synthesize/Simplify Exercise 1

- Synthesize this function
 - First generate the canonical sum
 - Then use theorems to simplify

T8	$AB+AC = A(B+C)$	T8'	$(A+B)(A+C) = A+BC$	Distribution & Factoring
T9	$A + AB = A$	T9'	$A(A+B) = A$	Covering
T10	$AB + AB' = A$	T10'	$(A+B)(A+B') = A$	Combining
T11	$AB + A'C + BC = AB + A'C$	T11'	$(A+B)(A'+C)(B+C) = (A+B)(A'+C)$	Consensus

- $P =$

Primes between 0-7	X	Y	Z	P	
	0	0	0	0	
	0	0	1	0	Use...
	0	1	0	1	m2
	0	1	1	1	m3
	1	0	0	0	
	1	0	1	1	m5
	1	1	0	0	
	1	1	1	1	m7

Synthesize/Simplify Exercise 2a

- Synthesize each output separately
 - First generate the canonical prod.
 - Then use theorems to simplify

T8	$XY + XZ = X(Y + Z)$	T8'	$(X + Y)(X + Z) = X + YZ$	Distribution & Factoring
T9	$X + XY = X$	T9'	$X(X + Y) = X$	Covering
T10	$XY + XY' = X$	T10'	$(X + Y)(X + Y') = X$	Combining
T11	$XY + X'Z + YZ = XY + X'Z$	T11'	$(X + Y)(X' + Z)(Y + Z) = (X + Y)(X' + Z)$	Consensus

• $G1 =$

• $G0 =$

A	B	C	G1	G0
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	0
1	0	0	1	1
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

Encode the highest input ID
(ie. 3, 2, or 1) that is ON (=1)

Synthesize/Simplify Exercise 2b

- Synthesize each output separately

- First generate the canonical sum
- Then use theorems to simplify

T8	$XY + XZ = X(Y + Z)$	T8'	$(X + Y)(X + Z) = X + YZ$	Distribution & Factoring
T9	$X + XY = X$	T9'	$X(X + Y) = X$	Covering
T10	$XY + XY' = X$	T10'	$(X + Y)(X + Y') = X$	Combining
T11	$XY + X'Z + YZ = XY + X'Z$	T11'	$(X + Y)(X' + Z)(Y + Z) = (X + Y)(X' + Z)$	Consensus

- $G1 = m2 + m3 + m4 + m5 + m6 + m7$
 - $A'BC' + A'BC + AB'C' + AB'C + ABC' + ABC$
 - [T3 ($A = A + A$) allows us to replicate m_6 and m_7 ($ABC' + ABC$)]
 - $A'BC' + A'BC + ABC' + ABC + AB'C' + AB'C + ABC' + ABC$
 - $B(A'C' + A'C + AC' + AC) + A(B'C' + B'C + BC' + BC)$ [T8]
 - $B(A'(C' + C) + A(C' + C)) + A(B'(C' + C) + B(C' + C))$ [T8/T5 or T10]
 - $B(A' + A) + A(B' + B)$ [T8/T5] = $B + A$ [Final Answer]
- $G0 = m1 + m4 + m5 + m6 + m7$
 - $A'B'C + AB'C' + AB'C + ABC' + ABC$
 - $A'B'C + AB'C + AB'C' + AB'C + ABC' + ABC$ [Use T3 to replicate m_5]
 - $B'C(A' + A) + A(B'C' + B'C + BC' + BC)$ [T8]
 - $B'C + A$ [T8/T5 or T10] = $B'C + A$ [Final Answer]

A	B	C	G1	G0
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	0
1	0	0	1	1
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1

Encode the highest input ID
(ie. 3, 2, or 1) that is ON (=1)

Synthesize/Simplify Exercise 3 (Optional)

- Synthesize each output separately

- First generate the canonical sum
- Then use theorems to simplify

T8	$AB+AC = A(B+C)$	T8'	$(A+B)(A+C) = A+BC$	Distribution & Factoring
T9	$A + AB = A$	T9'	$A(A+B) = A$	Covering
T10	$AB + AB' = A$	T10'	$(A+B)(A+B') = A$	Combining
T11	$AB + A'C + BC = AB + A'C$	T11'	$(A+B)(A'+C)(B+C) = (A+B)(A'+C)$	Consensus

- $Co = m3 + m5 + m6 + m7$
 - $X'YCi + XY'Ci + XYCi' + XYCi$
 - [Replicate m_7 twice so we can simplify the others: $m3 + m7 + m5 + m7 + m6 + m7$]
 - $X'BCi + XYCi + XY'Ci + XYCi + XYCi' + XYCi$
 - $YCi(X'+X) + XCi(Y'+Y) + XY(Ci'+Ci) = YCi + XCi + XY$ [Final Answer]
- $S = m1 + m2 + m4 + m7$
 - $X'Y'Ci + X'YCi' + XY'Ci' + XYCi$ [Not much to factor that will cause simplification]
 - $X'(Y'Ci + YCi') + X(Y'Ci' + YCi)$ [But write the truth tables of $Y'Ci+YCi'$ and $Y'Ci'+YCi$]
 - $X'(Y\oplus Ci) + X(Y\oplus Ci)'$ [But if we let $W=Y\oplus Ci$ then we have $X'W + XW'$...write its TT]
 - $X \oplus Y \oplus Ci$ [Final Answer]

3-bit Sum (Full Adder)

X	Y	Ci	Co	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

How to make faster circuits...

DEFINITIONS, EXPRESSION FORMS, SPEED, AND DEMORGAN'S

Definitions

- **Literal:** A single bit variable or its inverse
 - **Good:** x , y' , SLEEPING'
 - **Bad:** $(x+y)$
- **Product Term:** A single literal by itself or an _____'ing (not _____'ing) of literals
 - **Good:** z , $x \cdot y$, AWAKE • LISTENING • THINKING
 - **BAD:** $(x \cdot y)'$, AWAKE • (LISTENING + THINKING)
 - The minterms we defined earlier are product terms where EACH input variable of a function is 1 literal in the product term
- **Sum Term:** A single literal by itself or an _____'ing (not _____'ing) of literals
 - **Good:** z , $x' + y$, CURIOUS + PERSISTENT
 - **BAD:** $(x + y)'$, TIRED • (BORED + SLEEPY)
 - The maxterms we defined earlier are sum terms where EACH input variable of a function is 1 literal in the sum term

Expression/Circuit Forms

- **SOP (Sum of Products) Form:** An **SOP** expression is a logical sum (OR) of product terms

- Correct Examples: $[x' \cdot y' \cdot z + w + a' \cdot b \cdot c]$, $[w + x' \cdot z \cdot y + y' \cdot z]$
- Incorrect Examples: $[x' \cdot y \cdot z + w \cdot (a+b)]$, $[x \cdot y + (y' \cdot z)']$


- SOP equations yield **2-level circuits** with AND gates in the 1st level with an OR gate in the 2nd (aka _____ circuits)

- **POS (Product of Sums) Form:** A **POS** expression is a logical product (AND) of sum terms.


- Correct Examples: $[(x+y'+z) \cdot (w'+z) \cdot (a)]$, $[z' \cdot (x+y) \cdot (w'+y)]$
- Incorrect Examples: $[x' + y \cdot (x+w)]$, $[(x+y) \cdot (x+z)']$

- POS equations yield **2-level circuits** with OR gates in the 1st level with an AND gate in the 2nd (aka _____ circuits)

 - 1 level circuits (i.e. a _____ gate) are generally BOTH SOP and POS



 SOP $\Leftrightarrow$ _____
(Sum of products yields
AND-OR circuits)



POS $\Leftrightarrow$ _____
(Product of sums yields
OR-AND circuits)



Check Yourself

Expression	SOP / POS / Both / Neither
$w \cdot x \cdot (y \cdot z)' + xy'z + w$	
$xy + xz + (w'y)z$	
$(w + y' + z)(w + x)$	
$(w + y)x(w' + z)$	
$wy + wy + xy'$	
$w + x + y$	

Factoring and Distributing (Size vs. Speed)

- Factoring decreases size
- Distributing decreases levels of logic (delay)
  
$$G = a \cdot (b + (c \cdot (d + \bar{e}f))) = \underline{\hspace{10cm}}$$






DeMorgan's Theorem

- Inverting output of an AND gate = inverting the inputs of an OR gate
- Inverting output of an OR gate = inverting the inputs of an AND gate

A function's inverse is equivalent to inverting all the inputs and changing AND to OR and vice versa

A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

$$\overline{A \cdot B}$$

   


$$\overline{A} + \overline{B}$$

A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

$$\overline{A + B}$$

 


$$\overline{A} \cdot \overline{B}$$

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0


Analogy: Turning a gate "_____ " (like your _____).

AND-OR / NAND-NAND

 - Canonical Sums yield
 - AND-OR Implementation
 - _____ - _____ Implementation
- Recall inverting gates such as NAND gates may be "faster" or have desirable properties vs. typical AND/OR gates





||

 

||







OR-AND / NOR-NOR

 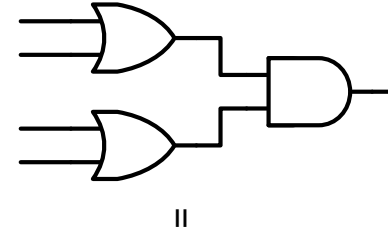- Canonical Products yield
 - OR-AND Implementation
 - NOR-NOR Implementation
- Recall inverting gates such as NOR gates may be "faster" or have desirable properties vs. typical AND/OR gates





DeMorgan's Practice

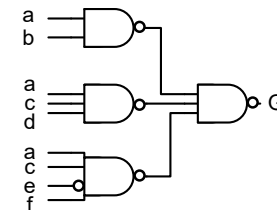     - Convert the circuits shown below to use only NAND or NOR gates?





DeMorgan's Theorem Example

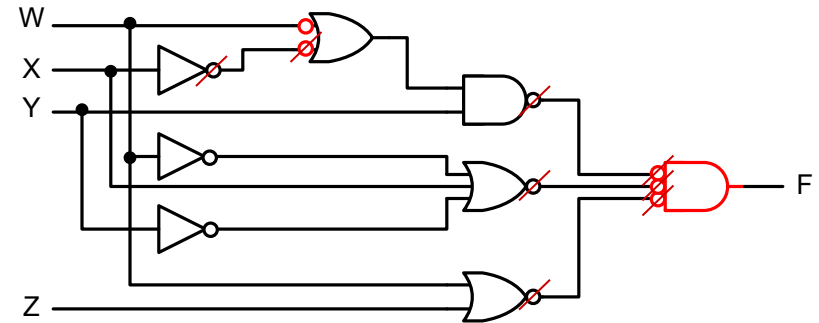 - Cancel as many bubbles as you can using DeMorgan's theorem.



  - Convert as many gates as possible to NOR gates. You are allowed to add additional inverters



DeMorgan's Theorem

- DeMorgan's let's us break large inversions (of whole expressions) into smaller inversions (of individual literals).
 - This is necessary to arrive at SOP or POS (which can only have inversions of literals)
- Recursively find the last (lowest precedence operation) and apply DeMorgan's theorem by flipping the operation and inverting the inputs

$$F = \overline{(\overline{X} + Y)} + \overline{Z} \cdot (Y + W)$$

Use DeMorgan's theorem to simplify "move" inversions (either to break-up "big bars" or join "small bars")

Generalized DeMorgan's Theorem

$$F'(X_1, \dots, X_n, +, \cdot) = F(X_1', \dots, X_n', \cdot, +)$$

To find F' , swap AND's and OR's and complement each literal. However, you must maintain the original order of operations.

Note: This parentheses doesn't matter (we are just OR'ing X' , Y , and the following subexpression)

$$F = (\overline{X+Y}) + \overline{Z} \cdot (Y+W)$$

$$\overline{F} = \overline{(\overline{X+Y}) + \overline{Z} \cdot (Y+W)}$$

$$F = (\overline{X+Y}) + \overline{Z} \cdot (Y+W)$$

$$\overline{F} = \overline{\overline{X+Y} + (\overline{Z} \cdot (Y+W))}$$

Fully parenthesized to show original order of ops.

$$\overline{F} = X \cdot \overline{Y} \cdot (Z + (\overline{Y} \cdot \overline{W}))$$

*AND's & OR's swapped
Each literal is inverted*



Additional Content

Not Tested

Canonical Sums and Products

LOGIC FUNCTION NOTATION

Canonical Sums and Products

- Truth tables require us to list all 2^n combinations of the n inputs
- A shorthand for a truth table is to describe the function using the canonical sum (sigma, Σ) or product (pi, Π) notation
- These forms of expressing a function have all the information in the truth table but can be written more compactly
 - Though still may require listing 2^n input values
- We'll often use these shorthand notations in assignments/exams

	X	Y	Z	F
m_0	0	0	0	0
m_1	0	0	1	0
m_2	0	1	0	1
m_3	0	1	1	1
m_4	1	0	0	0
m_5	1	0	1	1
m_6	1	1	0	0
m_7	1	1	1	1



$$F = \Sigma_{xyz} (2, 3, 5, 7)$$

Canonical Sums

- Given a T.T., use the minterms where $F=1$ and SUM them together
 - (Σ = SUM or OR of all the minterms)

	X	Y	Z	F
m_0	0	0	0	0
m_1	0	0	1	0
m_2	0	1	0	1
m_3	0	1	1	1
m_4	1	0	0	0
m_5	1	0	1	1
m_6	1	1	0	0
m_7	1	1	1	1



$$F = m_2 + m_3 + m_5 + m_7$$

$$= (X'YZ') + (X'YZ) + (XY'Z) + (XYZ)$$



Canonical Sum:

$$F = \Sigma_{xyz}(2, 3, 5, 7)$$

List the variables in the order they would appear in the truth table and that you'd use to find the decimal values

List the minterms where F is 1, and just list their decimal number equivalent

Canonical Products

- Given a T.T., AND together all the maxterms where $F = 0$

	X	Y	Z	F
M_0	0	0	0	0
M_1	0	0	1	0
M_2	0	1	0	1
M_3	0	1	1	1
M_4	1	0	0	0
M_5	1	0	1	1
M_6	1	1	0	0
M_7	1	1	1	1



$$\begin{aligned}
 F &= M_0 \bullet M_1 \bullet M_4 \bullet M_6 \\
 &= (X+Y+Z) \bullet (X+Y+Z') \bullet \\
 &\quad (X'+Y+Z) \bullet (X'+Y'+Z)
 \end{aligned}$$



Canonical Product:

$$F = \Pi_{xyz}(0, 1, 4, 6)$$

List the variables in the order they would appear in the truth table and that you'd use to find the decimal values

List the maxterms where F is 0, and just list their decimal number equivalent

Canonical Sums & Products

- **Canonical Sum:** An SOP expression where all the product terms are minterms (i.e. have each literal in each product term)
- **Canonical Product:** A POS expression where all the sum terms are maxterms (i.e. each literal in each sum term)

Canonical Sum:

$$F = \sum_{xyz} (2, 3, 5, 7)$$

$$F = m_2 + m_3 + m_5 + m_7 \\ = (X'YZ') + (X'YZ) + (XY'Z) + (XYZ)$$

Canonical Product:

$$F = \prod_{xyz} (0, 1, 4, 6)$$

$$F = M_0 \cdot M_1 \cdot M_4 \cdot M_6 = \\ (X+Y+Z) \cdot (X+Y+Z') \cdot (X'+Y+Z) \cdot (X'+Y'+Z)$$

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Definitions

- **Minterm:** A **product** term where all the input variables of a function appear as exactly one literal

$f(x,y,z)$	Yes (m_i) / No	$g(w,x,y,z)$	Yes (m_i) / No
$x \cdot y$	No	$w' \cdot x \cdot y' \cdot z'$	Yes, m_4
$x' \cdot y \cdot z'$	Yes, m_2	$w \cdot x' \cdot z'$	No
$x + y' \cdot z'$	No (not prod. term)	$w \cdot x' \cdot y \cdot z$	Yes, m_{11}
$(x \cdot y' \cdot z)'$	No (not prod. term)	$w' \cdot x \cdot y \cdot z'$	Yes, m_6

- **Maxterm:** A **sum** term where each input variable of a function appears as exactly one literal

$f(a,b,c)$	Yes (M_i) / No	$g(v,w,x,y,z)$	Yes (M_i) / No
$a + b' + c$	Yes, M_2	$v + w' + x' + y + z$	Yes, M_{12}
$a + b'$	No	$v + z$	No
$a' \cdot (b' + c)$	No (not sum term)	$v' + w + x + y' + z'$	Yes, M_{19}
$(a' + b + c)'$	No (not sum term)		


BACKUP

Key: Truth tables

- **Important skill:** Describe an operation or problem statement with a truth table.
- Steps:
 - Identify the inputs and how many bits each requires
 - Determine how many output bits are needed by considering the numeric range of all possible outputs
 - Write a truth table with all 2^n combinations of the n input bits and come up with the desired input on your own
 - Convert each output to a logic circuit using one of the synthesis methods we will teach you in the next two units.

 Task

Build an addition operation for 2-bit unsigned binary numbers: $X_1X_0 + Y_1Y_0$




X_1	X_0	Y_1	Y_0	S_2	S_1	S_0	Descrip
0	0	0	0	0	0	0	$0+0=0$
0	0	0	1	0	0	1	$0+1=1$
0	0	1	0	0	1	0	$0+2=2$
0	0	1	1	0	1	1	$0+3=3$
0	1	0	0	0	0	1	$1+0=1$
0	1	0	1	0	1	0	$1+1=2$
0	1	1	0	0	1	1	$1+2=3$
0	1	1	1	1	0	0	$1+3=4$
1	0	0	0	0	1	0	$2+0=2$
1	0	0	1	0	1	1	$2+1=3$
1	0	1	0	1	0	0	$2+2=4$
1	0	1	1	1	0	1	$2+3=5$
1	1	0	0	0	1	1	$3+0=3$
1	1	0	1	1	0	0	$3+1=4$
1	1	1	0	1	0	1	$3+2=5$
1	1	1	1	1	1	0	$3+3=6$

Key: Truth tables

- **Important skill:** Describe an operation or problem statement with a truth table.
- Steps:
 - Identify the inputs and how many bits each requires
 - Determine how many output bits are needed by considering the numeric range of all possible outputs
 - Write a truth table with all 2^n combinations of the n input bits and come up with the desired input on your own
 - Convert each output to a logic circuit using one of the synthesis methods we will teach you in the next two units.

 Task

Build an addition operation for 2-bit unsigned binary numbers: $X_1X_0 + Y_1Y_0$



X1	X0	Y1	Y0	S2	S1	S0
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	1	1
.	.	.	.	.	.	.
1	1	0	1	1	0	0
1	1	1	0	1	0	1
1	1	1	1	1	1	0

S	X	Y	Z
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

X	Y	F
0	0	1
0	1	0
1	0	1
1	1	1

The Problem


- The goal of this unit is to teach you how you can take **ANY** logic function expressed as a truth table and design a digital circuit to implement that logic function

How can I find a circuit that implements this truth table?




Primes between 0-7

X	Y	Z	P
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1


 


1's Count (Addition) of Inputs

I3	I2	I1	C1	C0
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 


Addition

  

X31	...	...	Y0	S32	...	S0
0			0	0		0
0			1	0		1
0			0	0		0
0			1	0		1
0			0	0		1
0			1	0		0
0			0	0		1
0			1	1		0
1			0	0		0
1			1	0		1
1			0	1		0
1			1	1		1
1			0	0		1
1			1	1		0
1			0	1		1
1			1	1		0

Comparison

```
bool lt = x < y;
```

 





X31	...	...	Y0	LT
0			0	
0			1	
0			0	
0			1	
0			0	
0			1	
0			0	
0			1	
1			0	
1			1	
1			0	
1			1	
1			0	
1			1	
1			0	
1			1	

If..Else (Ternary) Operator (aka "Mux")

```
z = (s==1) ? x : y;
```

```
// if(s==1) { z=x; }  
// else     { z=y; }
```

S	X	Y	Z
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

   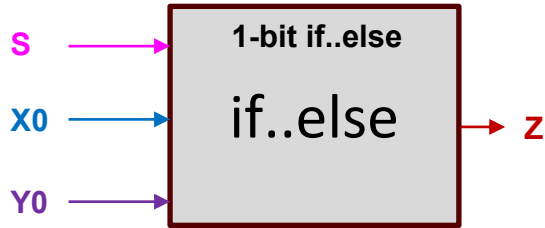

?

T8	$XY + XZ = X(Y + Z)$	T8'	$(X + Y)(X + Z) = X + YZ$	Distribution & Factoring
T9	$X + XY = X$	T9'	$X(X + Y) = X$	Covering
T10	$XY + XY' = X$	T10'	$(X + Y)(X + Y') = X$	Combining
T11	$XY + X'Z + YZ =$ $XY + X'Z$	T11'	$(X + Y)(X' + Z)(Y + Z) =$ $(X + Y)(X' + Z)$	Consensus

T8	$AB + AC = A(B + C)$	T8'	$(A + B)(A + C) = A + BC$	Distribution & Factoring
T9	$A + AB = A$	T9'	$A(A + B) = A$	Covering
T10	$AB + AB' = A$	T10'	$(A + B)(A + B') = A$	Combining
T11	$AB + A'C + BC \equiv$	T11'	$(A + B)(A' + C)(B + C) \equiv$	Consensus