


State Machine Design

An old TV remote control and TV only supports 2-digit channels: 00-99. Normally, to change the channel we would have to hit two buttons: 38, first 3 then 8, and as soon as you hit the second button it should change the channel. However, for channels 0-9 the remote should allow you to just enter 1-digit and if another button is not pushed soon afterwards should cause the channel to be changed. Implement a state machine that can indicate when the channel should be changed. After it is changed, restart waiting for a push.

Have a single input PUSH and single output CHANGE. If you get the 1st push but then don't get the second push within 2 cycles, just change the channel no matter what. Use four states: 0PUSH, 1PUSH, WAIT, CHGCHAN.

Adder and Combinational Design

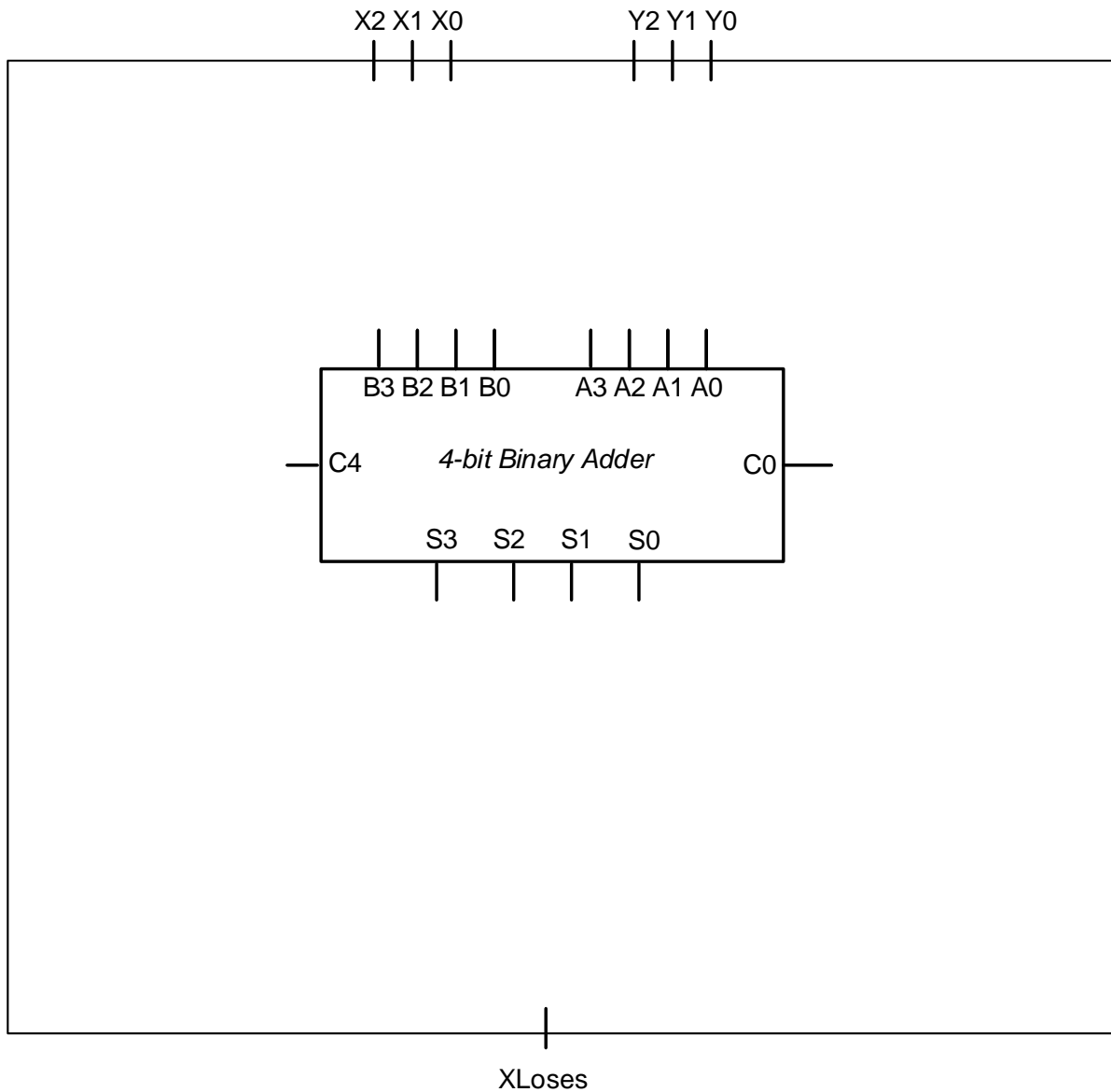Suppose team X and team Y play a game where their scores range 0-7 decimal. Team X is much better than team Y so they give Y a handicap: to truly win, team X must score 5 points more than team Y. Design a circuit that will produce a signal: XLoses given the two 3-bit input numbers X[2:0] and Y[2:0] representing the scores of each team.



Determine a prescaler, OCR0A value, and ISR for an 8-bit timer generate at 400Hz square wave for 3 seconds on PD1. Recall the Arduino runs at 16MHz and valid prescalars are: 1, 8, 64, 256, 1024 (choose the smallest prescaler that works).

```
ISR(TIMERO0_COMPA_vect)
{
```

}

Show how to implement this flip-flop with load enable by determining the values to program into an FPGA's configurable logic block shown to the right.

